



Lecture 14

-- Laplace Transform in Circuit Analysis



V-I relations of R,L,C

$R: V(t) = RI(t)$
 $\downarrow \mathcal{L}$
 $\mathcal{L} \rightarrow \mathcal{L}$
 $V(s) = R \cdot I(s)$

• R

$U_R(s) = \underline{R} I_R(s)$

• C

$$V(s) = \frac{1}{sC} I(s) + \frac{V_0}{s}$$

$$I(s) = sCV(s) - CV_0$$

• L

$$I(s) = \frac{1}{sL} V(s) + \frac{I_0}{s}$$

$$V(s) = sLI(s) - LI_0$$

$C: \begin{array}{c} \downarrow i(t) + \\ \text{---} \\ \text{---} C V_c(t) \\ \downarrow \end{array}$
 $\underline{i(t) = C \cdot \frac{dV_c(t)}{dt}}$

$\underline{I(s) = \mathcal{F}\left[C \cdot \frac{dV_c(t)}{dt}\right] = C \mathcal{F}\left[\frac{dV_c(t)}{dt}\right]}$

$\underline{= C \cdot [s \cdot V_c(s) - V_c(0)]}$

$I(s) = C \cdot s \cdot V(s) - C V_0 \quad \textcircled{1}$

$V(s) = \frac{1}{Cs} [I(s) + C V_0] = \frac{1}{Cs} \cdot I(s) + \frac{V_0}{s} \quad \textcircled{2}$

Notes

$(1) \quad V_c(t) = \underline{V_0} + \frac{1}{C} \int_0^\infty i_c dt$



$\underline{V(s) = \frac{V_0}{s} + \frac{1}{C} \cdot \frac{I(s)}{s}}$

$(2) \quad S\text{-domain: } \underline{\text{No diff. Equation}}$

(3) Pictorial illustration:



$$I(s) = C \cdot s \cdot V(s) - C V_0$$

①

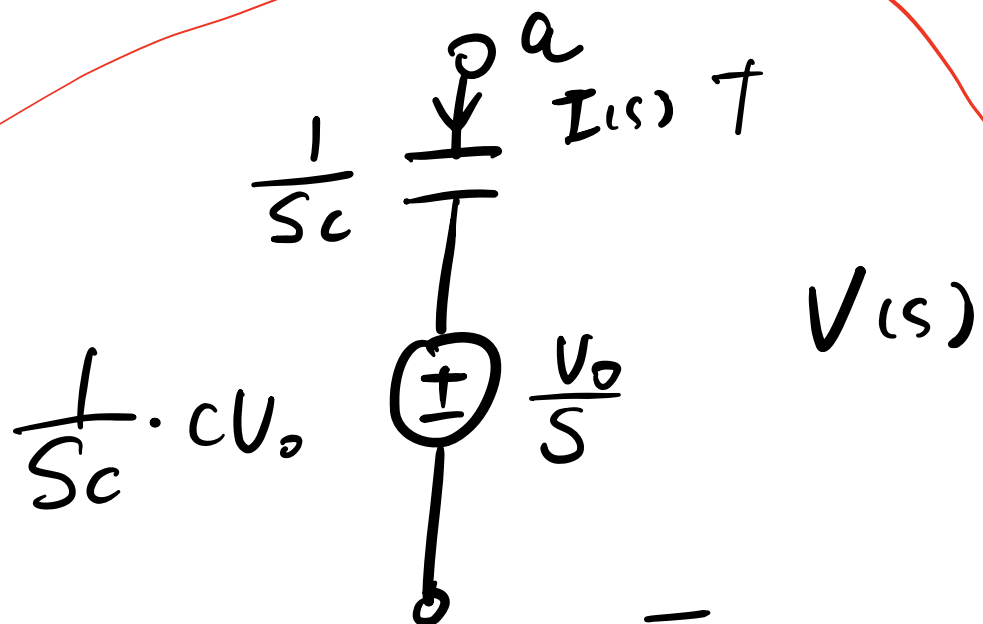
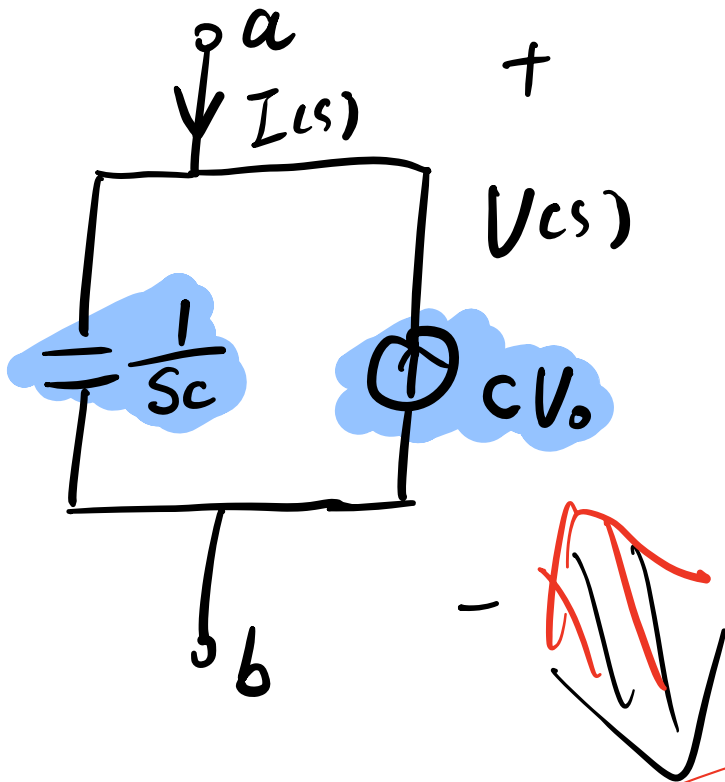


$$V(s) = I(s) \cdot \frac{1}{sC} + \frac{V_0}{s}$$


T.D. Phasor D.

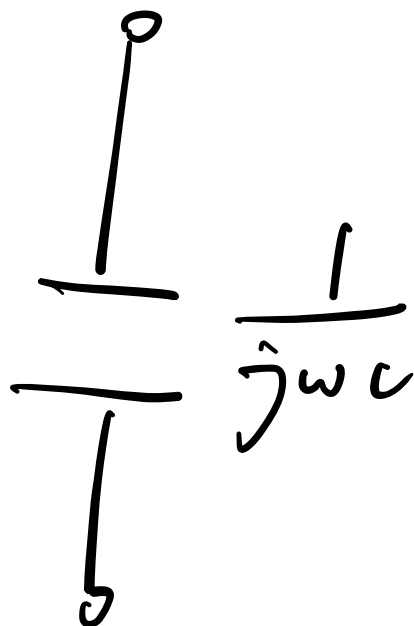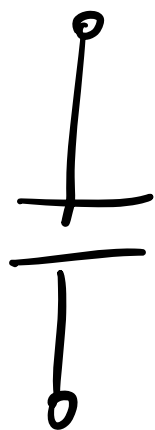

S.D.

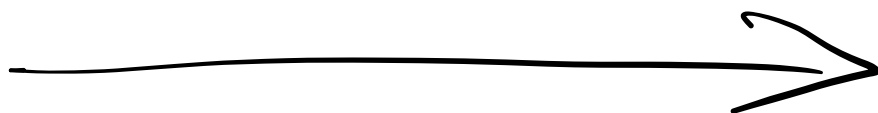
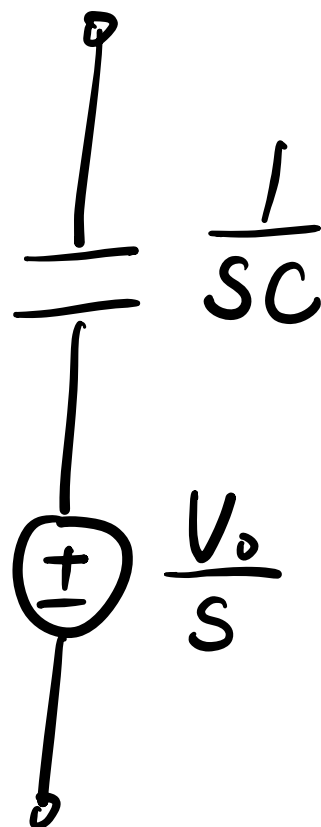


$$f(-t) = V_0$$

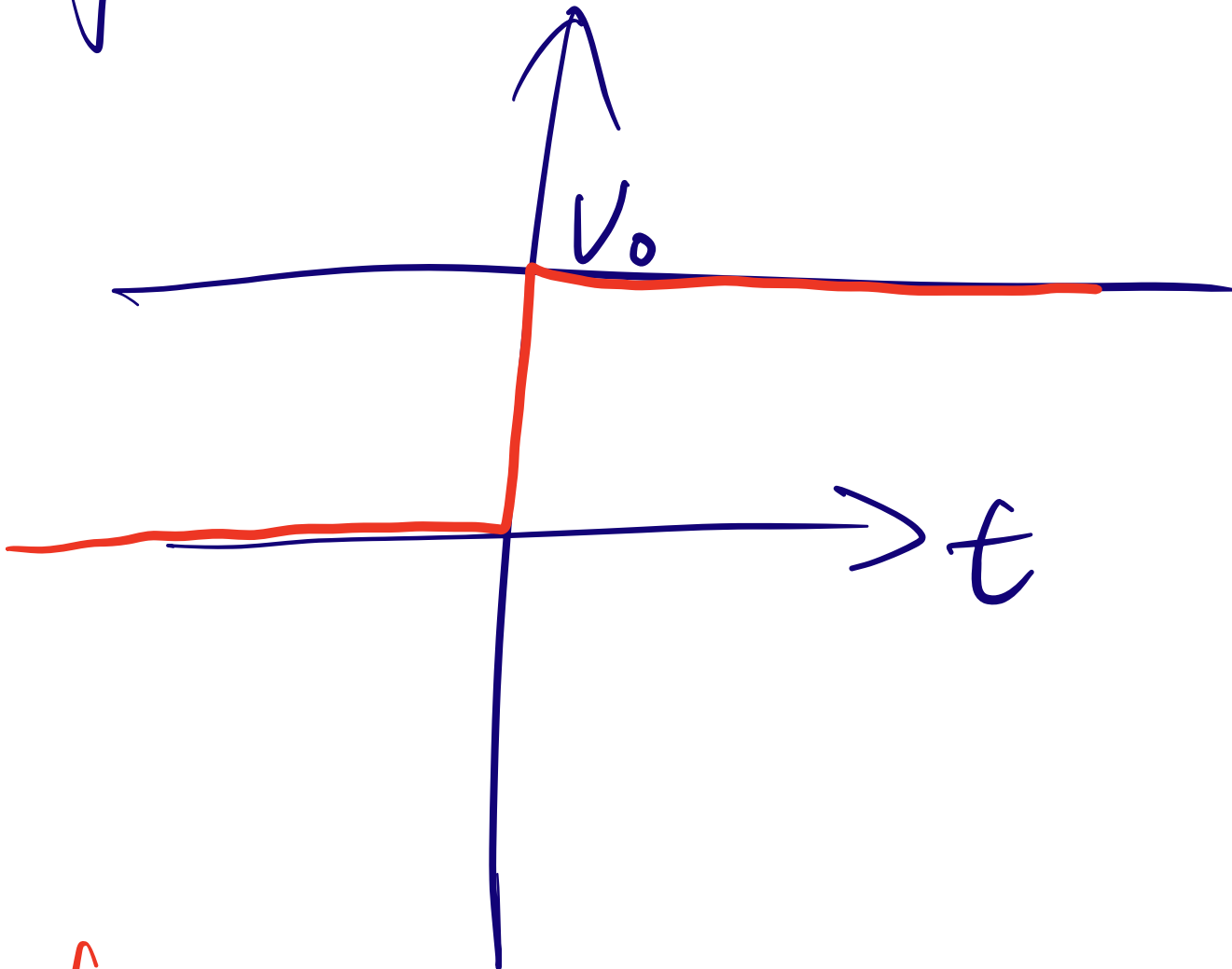


$$f(t) = V_0 \cdot u(t)$$


T.D.

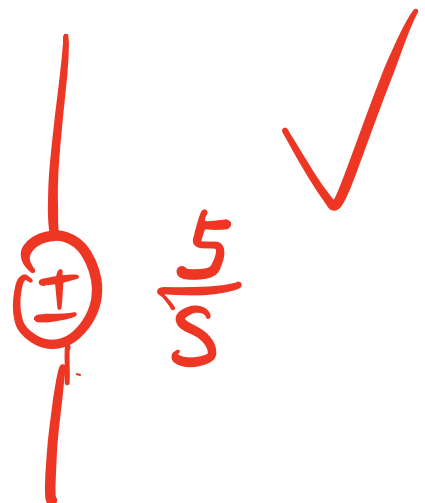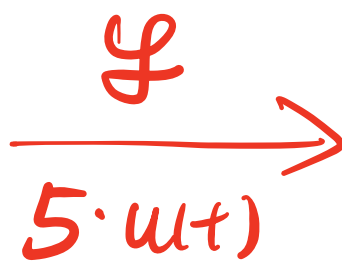

T. D.

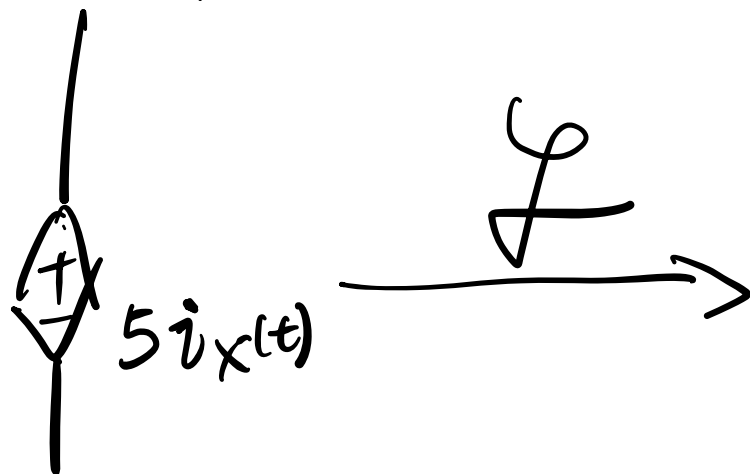


S. domain

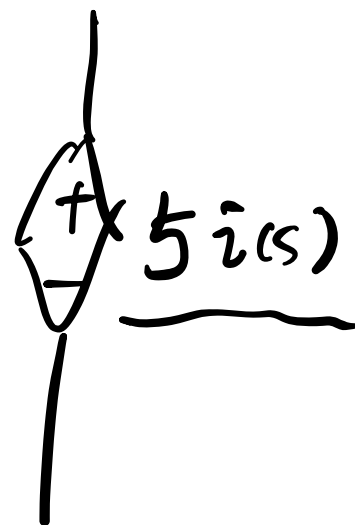

S-domain circuit models for a capacitor


s-Domain Circuit Models

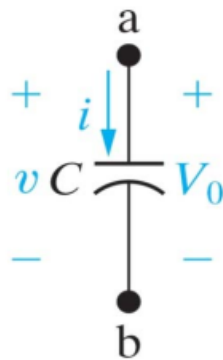


$$i(t) = C \frac{dv(t)}{dt}$$


For a capacitor
(with initial conditions)

$$\Rightarrow I(s) = sCV(s) - CV_0$$

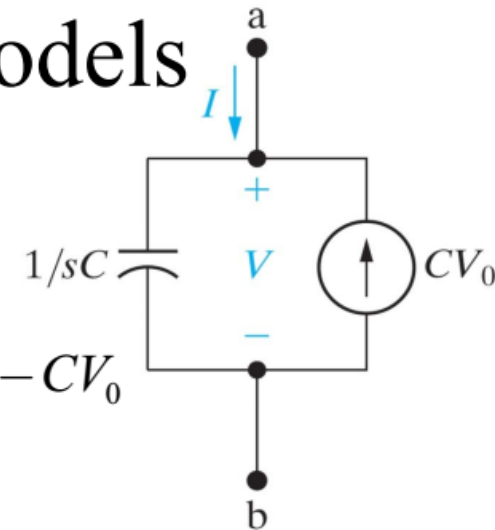
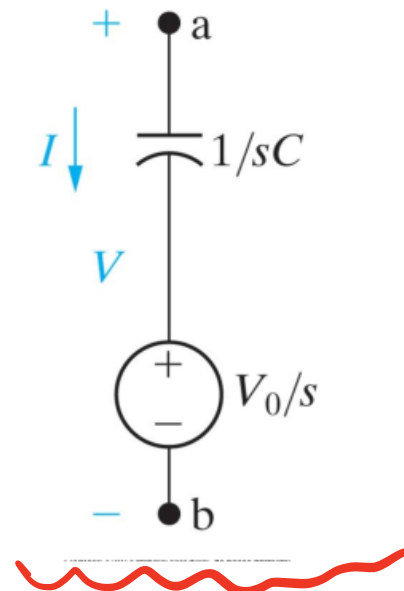
$$V(s) = \frac{1}{sC} I(s) + \frac{V_0}{s}$$



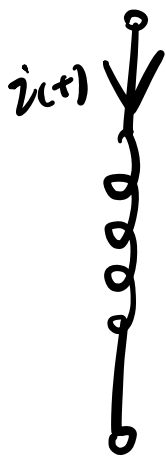


$$V(t) = L \frac{di(t)}{dt}$$

$$V(s) = L [s I(s) - i(0_-)]$$

$$= L s I(s) - L I_0 \quad (3)$$

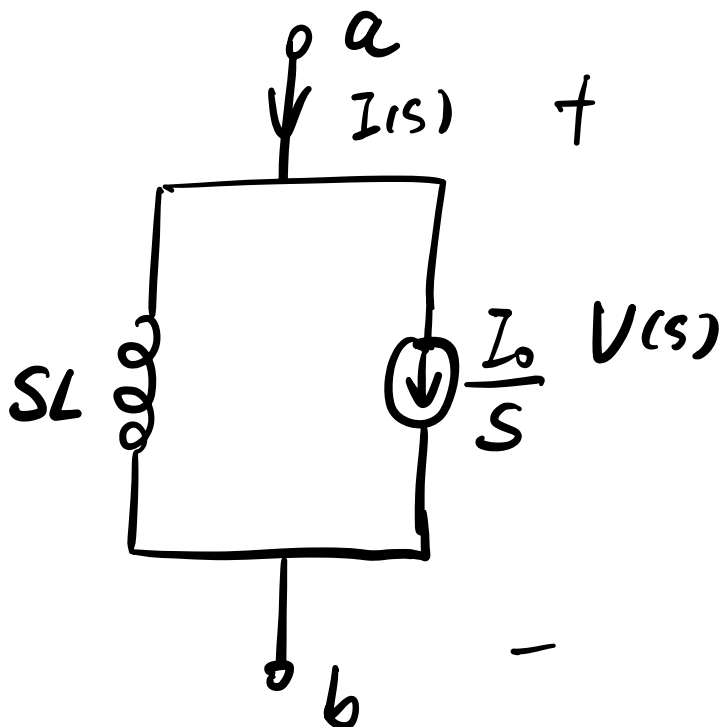
$$I(s) = \frac{1}{Ls} V(s) + \frac{I_0}{s} \quad (4)$$





S-domain circuit models for an inductor

s-Domain Circuit Models

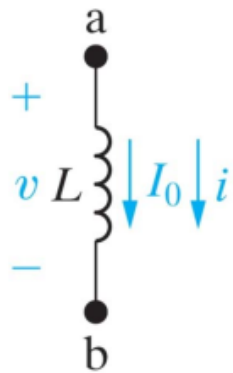


$$v(t) = L \frac{di(t)}{dt}$$


For an inductor
(with initial conditions)



$$V(s) = sLI(s) - LI_0$$

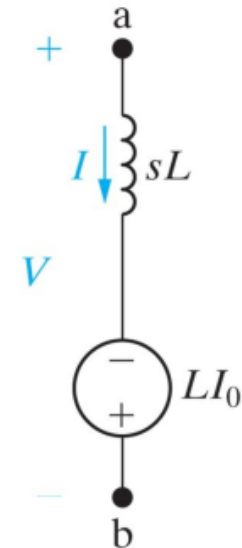
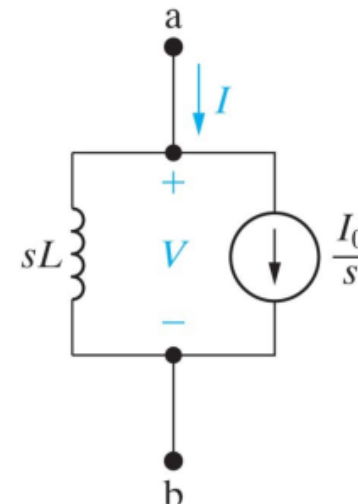
$$I(s) = \frac{1}{sL} V(s) + \frac{I_0}{s}$$



T.D.




Phasor D.



$j\omega L$









$j\omega \rightarrow S$

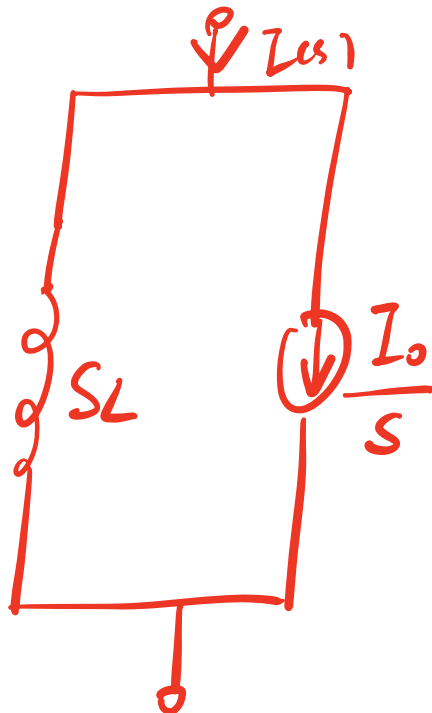



Time domain

s-domain

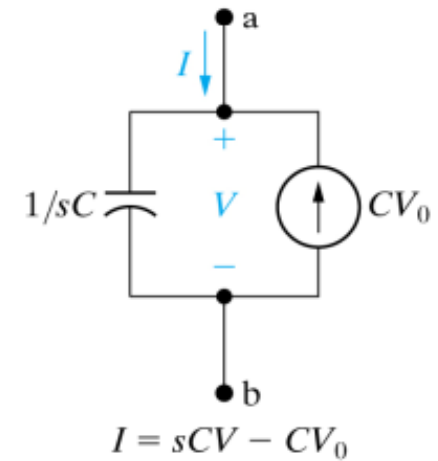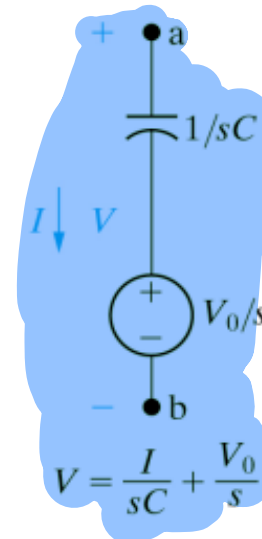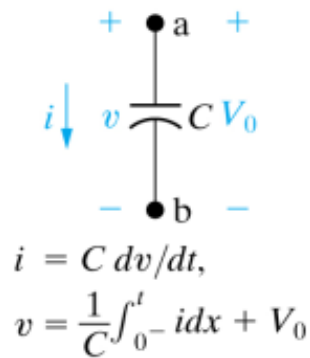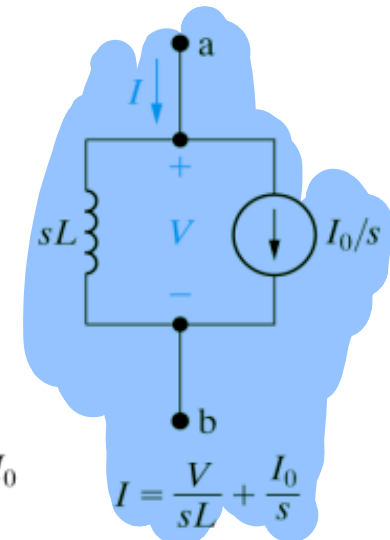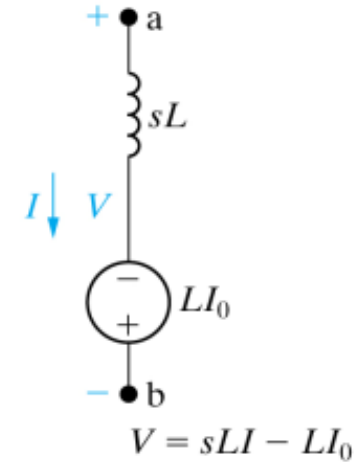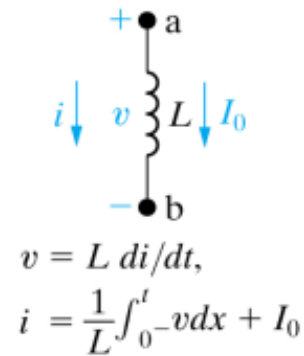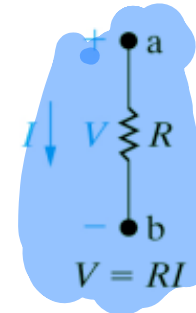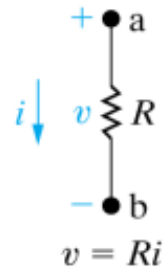



D.C. sources and Dependent Sources

- The models for dependent sources are easy to develop, drawing from the simple fact that if the Laplace transform of $f(t)$ is $F(s)$, then the Laplace transform of $af(t)$ is $aF(s)$ — the linearity property.

$$\mathcal{L}[av(t)] = aV(s)$$

$$\mathcal{L}[ai(t)] = aI(s)$$




Steps in Applying the Laplace transform

- Transform the circuit from the time domain to the Laplace (s) domain, including initial conditions.
--The elegance of using the Laplace transform in circuit analysis lies in (1) transforming the differential equation into an *algebraic* equation; and (2) automatic inclusion of initial conditions in the transformation process, thus providing a complete (**transient and steady-state**) solution.
- Solve the circuit using nodal analysis, mesh analysis, source transformation, superposition, or any other analysis technique with which we are familiar.
- Take the inverse transform of the solution and thus obtain the solution in the time domain.



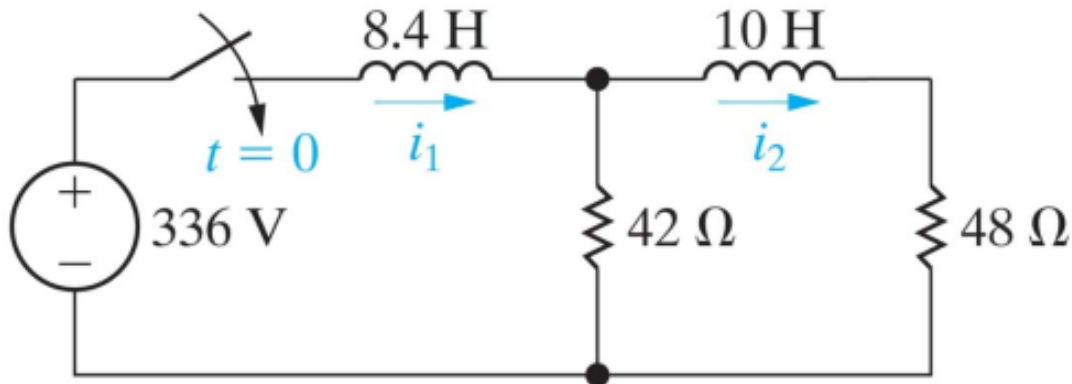Example 1


Assuming no initial energy storage, find $i_1(t)$ and $i_2(t)$ for $t > 0$.



\hookrightarrow S-domain circuit:

$$f(t) = 336 \text{ V}$$
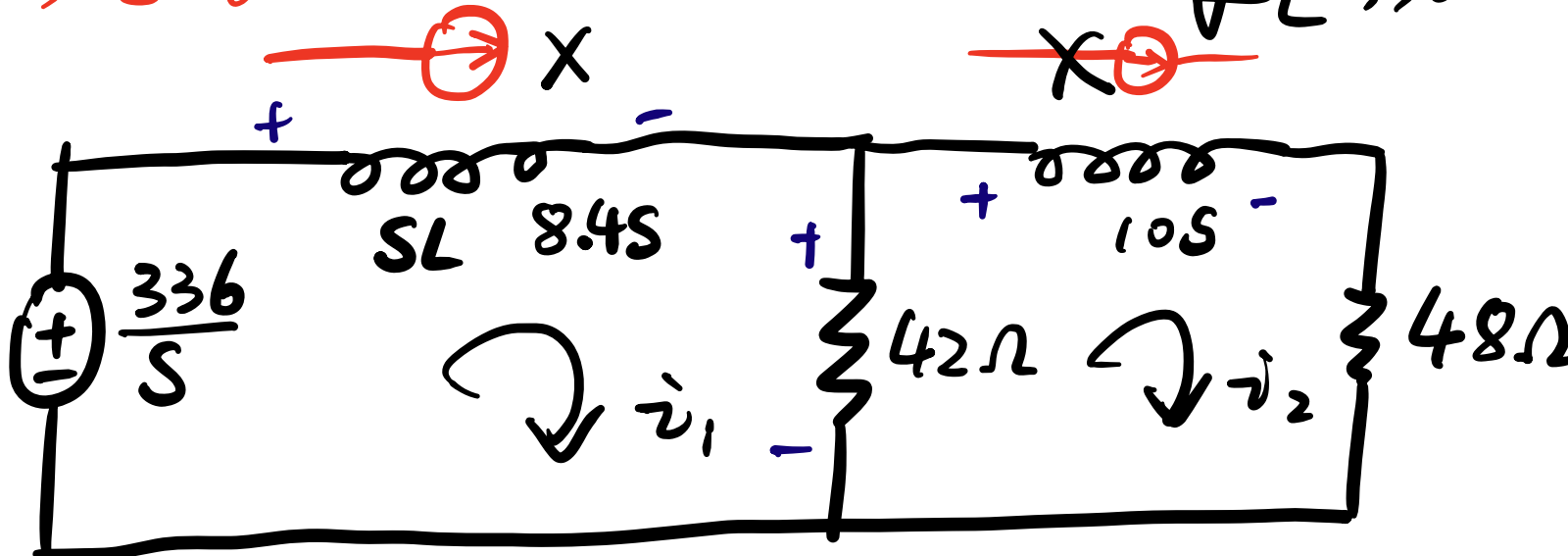
$$\hookrightarrow \mathcal{F}[336 \cdot u(t)]$$





Mesh:

$$\frac{336}{s} = 8.4s \cdot \dot{v}_1 + 42(\dot{v}_1 - \dot{v}_2) \quad \textcircled{1}$$

$$42(\dot{v}_1 - \dot{v}_2) = 10s \cdot (\dot{v}_2) + 48\dot{v}_2 \quad \textcircled{2}$$


$$\text{由 } \textcircled{2} \quad \dot{v}_1 = \frac{90 + 10s}{42} \cdot \dot{v}_2$$

$$\Rightarrow \dot{v}_2 = \frac{168}{s^3 + 14s^2 + 24s} = \frac{168}{s(s+2)(s+12)}$$

$$= \frac{k_1^7}{s} + \frac{k_2^{-8.4}}{s+2} + \frac{k_3^{1.4}}{s+12}$$

$$\mathcal{L}^{-1} \quad \dot{i}_2(t) = [7 - 8.4e^{-2t} + 1.4e^{-12t}]u(t)$$
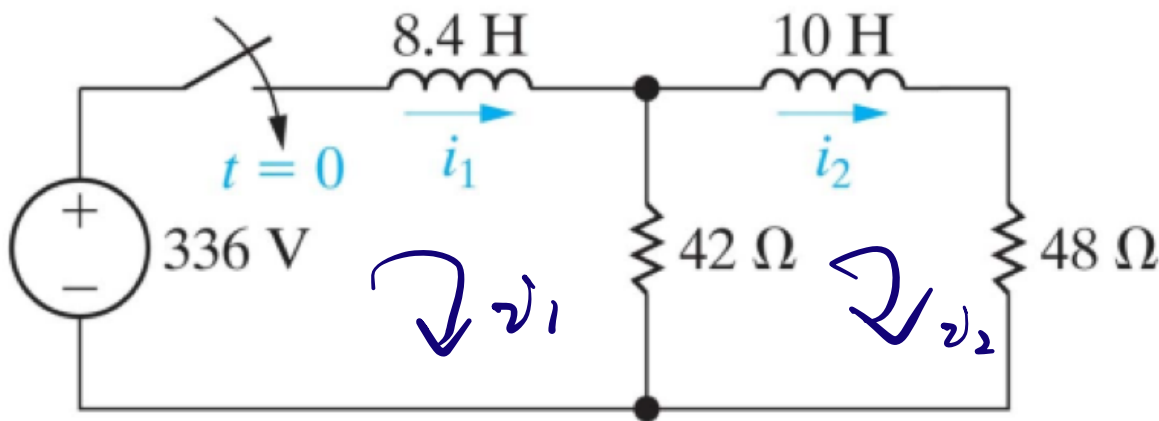
$$\dot{v}_1 = (15 - 14e^{-2t} - e^{-12t})u(t)$$



$$336 = 8.4 \frac{d\dot{v}_1}{dt} + 42(v_1 - v_2)$$

$$42(v_1 - v_2) = 10 \frac{d\dot{v}_2}{dt} + 48v_2$$

①
②

$$\rightarrow \ddot{v}_2 + 14\dot{v}_2 + 24v_2 = 168$$

$$s^2 + 14s + 24 = 0$$

$$(S+2)(S+12)=0$$
