




Outline

- Linearity property
- Superposition
- Thevenin's theorem
- Source transformation
- Norton's theorem
- Power transfer



Example

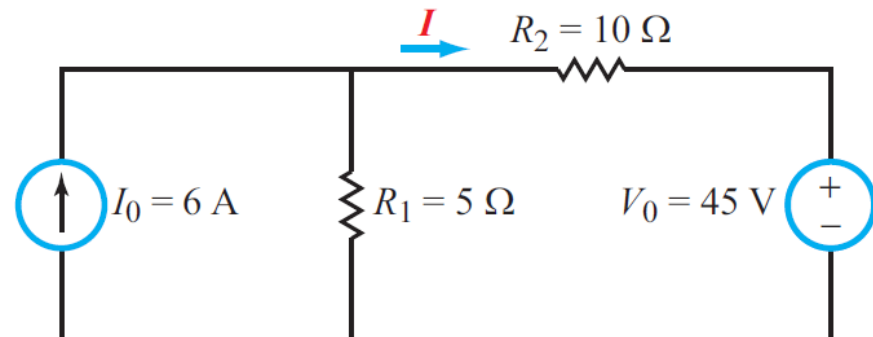- Q1: If $R_2 = 1\Omega$, $I = ?$
- Q2: What if $R_2 = 5\Omega$, $I = ?$
- ??







Thevenin's Theorem – Motivation

- In many circuits, it is quite common that only one element (called *the load*) is variable while others are fixed.
 - An example is the household outlet: different appliances may be plugged into the outlet, each presenting a different resistance.
 - Ordinarily one has to **re-analyze** the circuit upon changing load.
 - This complexity can be simplified by **circuit theorem** (e.g. Thevenin's theorem), which provides a technique to **replace the fixed part of the circuit with an equivalent circuit**.


Thevenin's Theorem (1880s, Leon Thevenin, French)

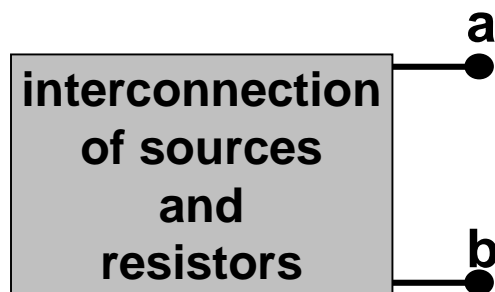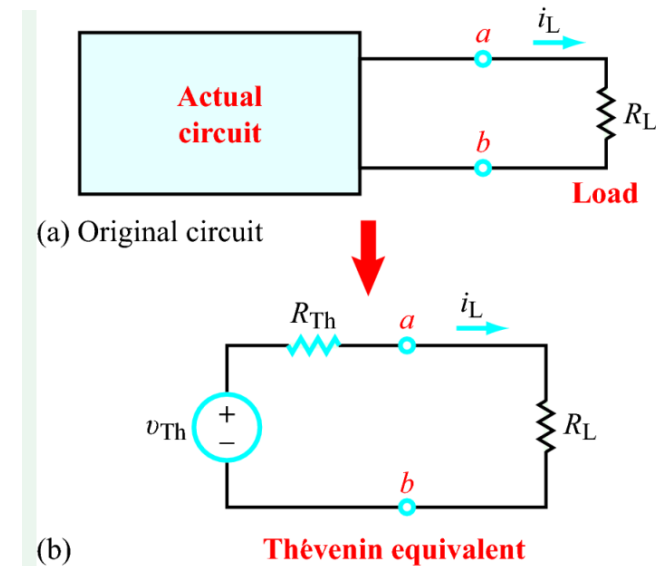
- Thevenin's theorem states that a two terminal circuit (including resistors, linear dependent sources, and independent sources.) may be replaced with a voltage source in series with a resistor:



≡

Thévenin equivalent circuit

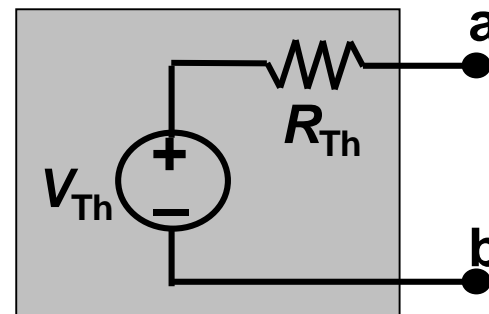


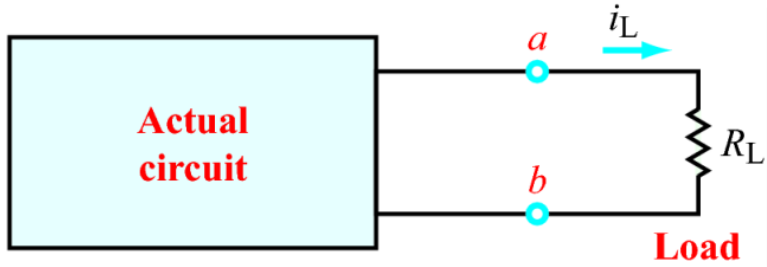



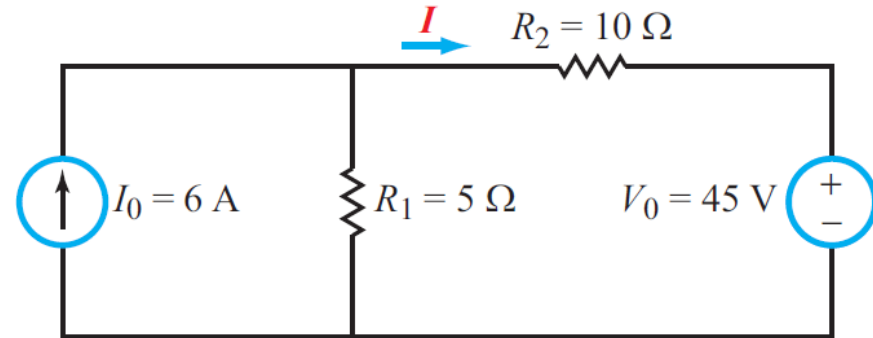Example


- Use Thévenin Equivalent Circuits
- Q1: If $R_2 = 1\Omega$, $I = ?$
- Q2: What if $R_2 = 5\Omega$, $I = ?$



How Do We Find Thévenin Equivalent Circuits?


Method 1: Equivalent Resistance

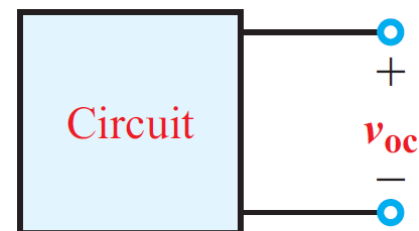1. Analyze circuit to find v_{oc}
2. **Deactivate** all **independent** sources by replacing voltage sources with short circuits and current sources with open circuits.
3. Simplify circuit to find equivalent resistance.



(a) $v_{Th} = v_{oc}$

Equivalent-Resistance Method

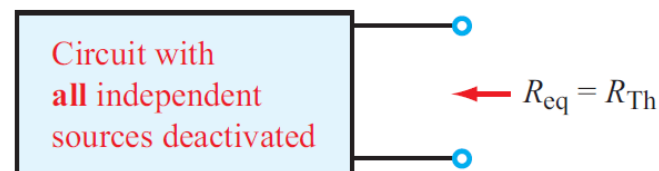



Note: This method **does not** apply to circuits that contain **dependent** sources.




Example

Thévenin Equivalent Circuit

(Circuit has no dependent sources)

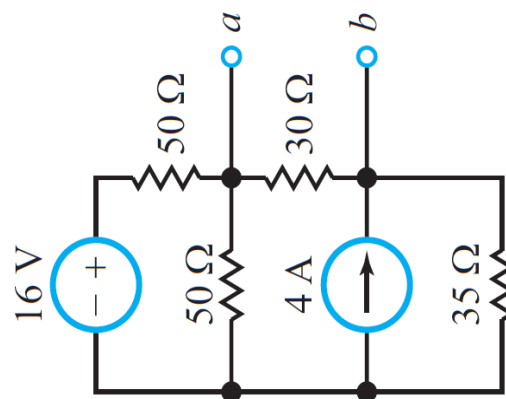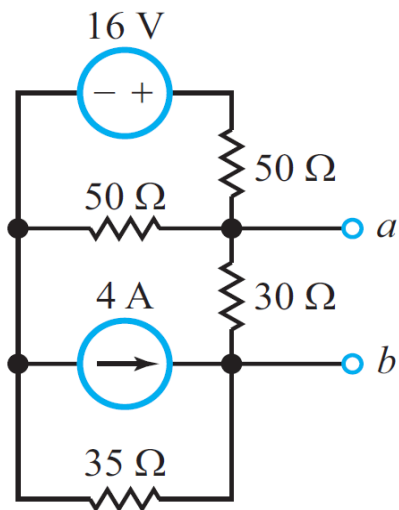

How Do We Find Thévenin Equivalent Circuits ?

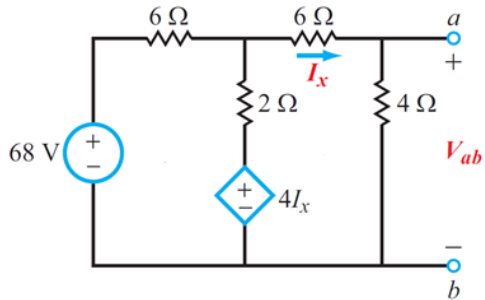

Method 2: Open/short circuit



1. Analyze circuit to find v_{oc}
2. Analyze circuit to find i_{sc}

$$v_{Th} = v_{oc}$$

$$R_{Th} = \frac{v_{oc}}{i_{sc}}$$


Note: This method is applicable to **any linear circuit**, whether or not it contains dependent sources.

Open-Circuit / Short-Circuit Method

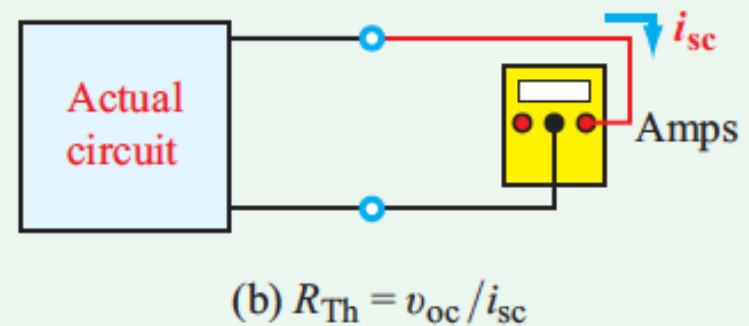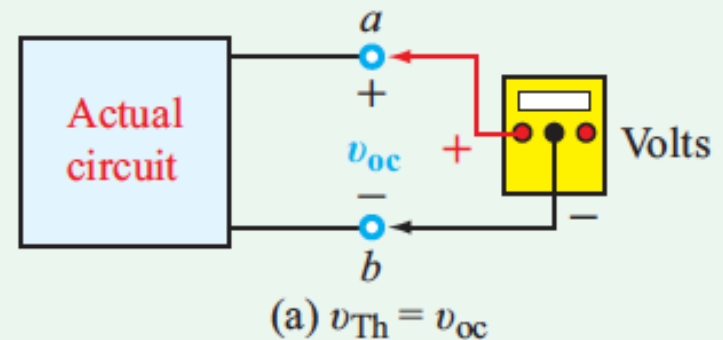




Example

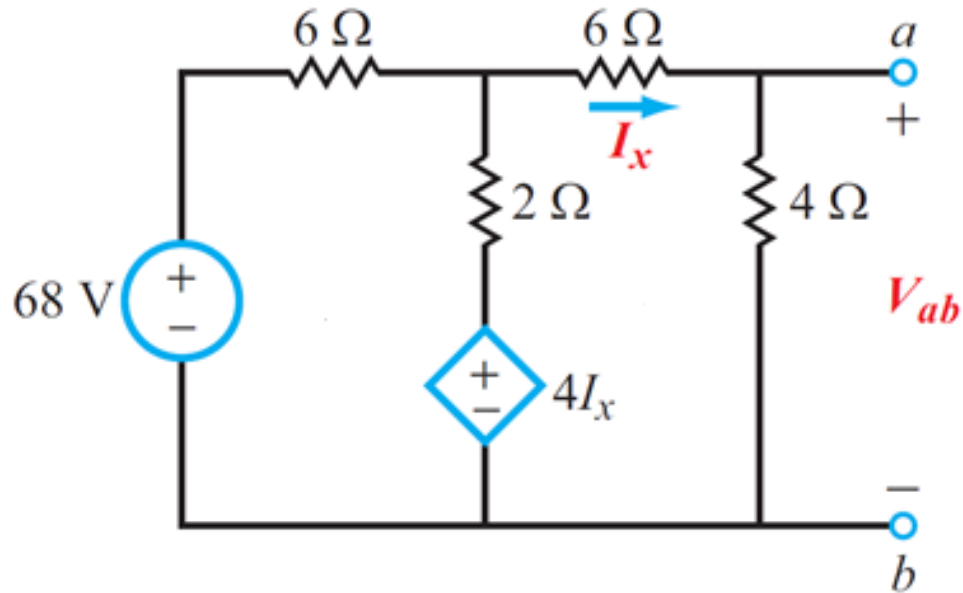



Practice

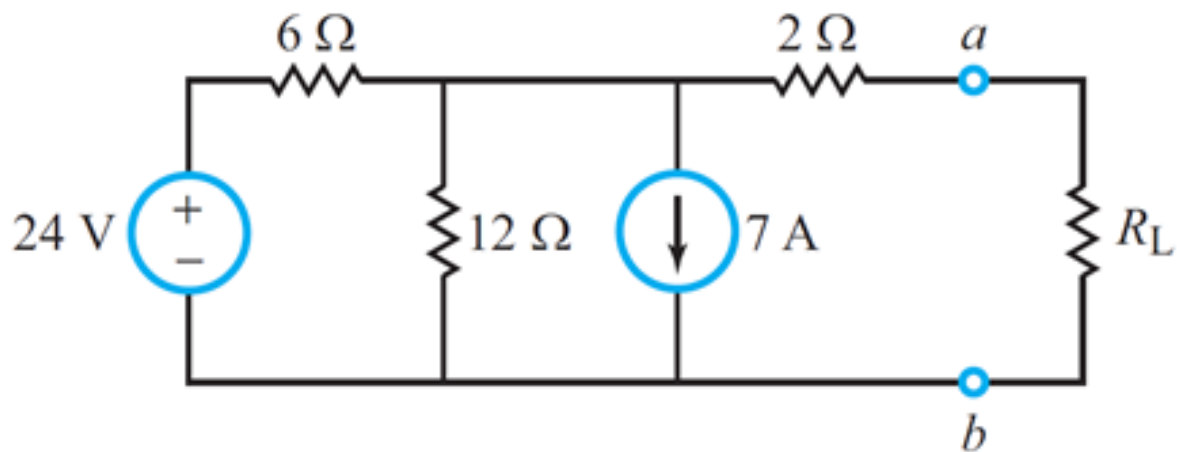


How Do We Find Thévenin Equivalent Circuits?

Method 3:

Step 1. **Again** $v_{Th} = v_{oc}$



Step 2. **External-Source Method**

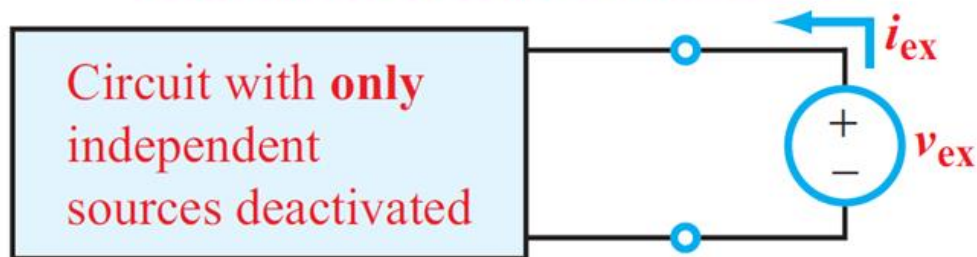

If a circuit contains both dependent and independent sources, R_{Th} can be determined by (a) deactivating independent sources (only), (b) adding an external source v_{ex} , and then (c) solving the circuit to determine i_{ex} . The solution is $R_{Th} = v_{ex}/i_{ex}$.





Example

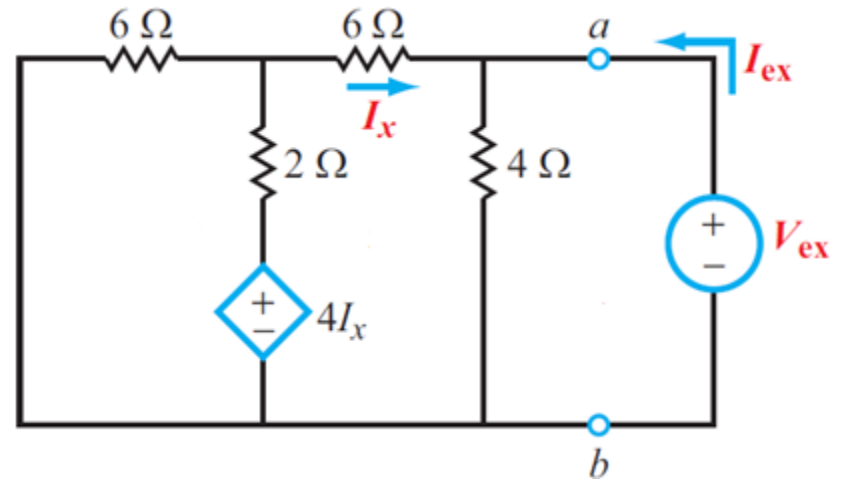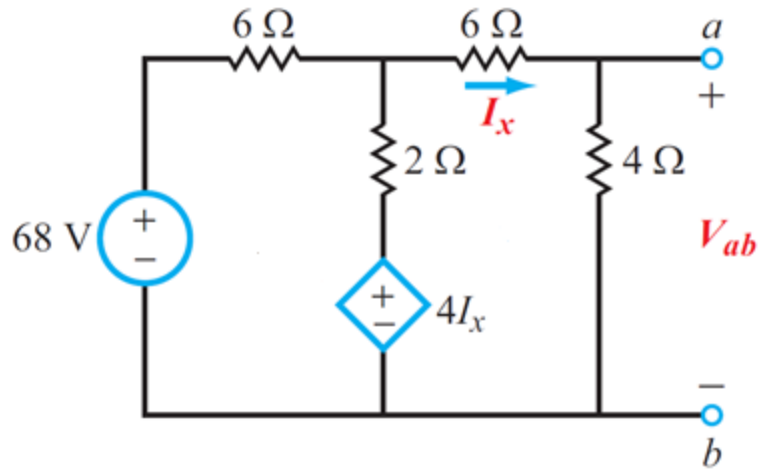



Example

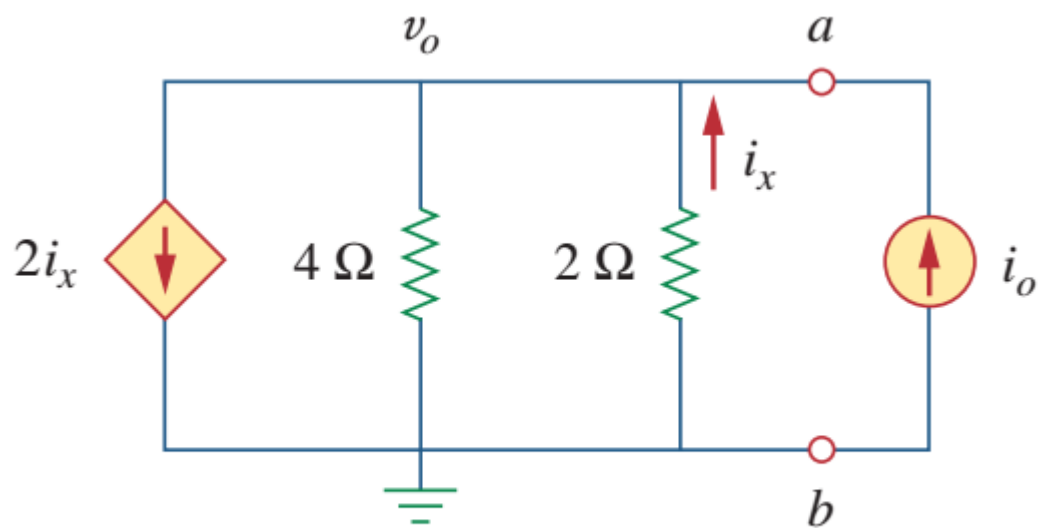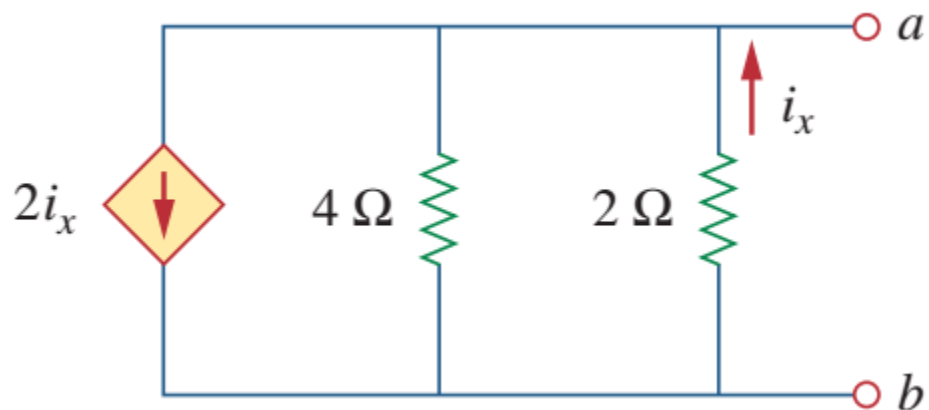

(b)