

## **Homework 8**


Due date: 11.59 am, Jan. 15th, 2023

Turn in your hard-copy hand-writing homework to Room 324 #3 SIST

Rules:

- Work on your own. Discussion is permissible, but extremely similar submissions will be judged as plagiarism.
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.

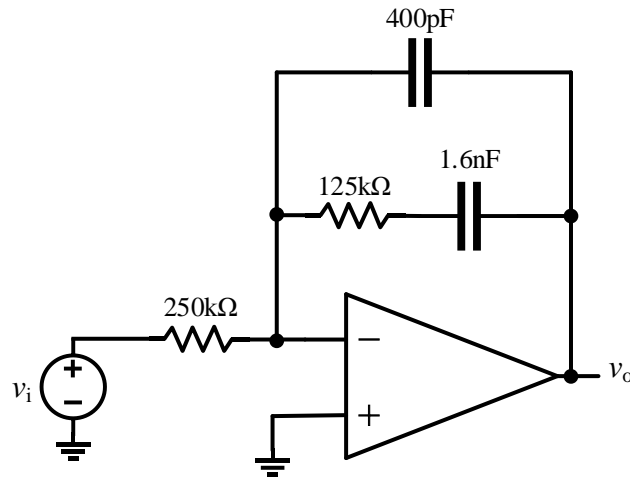
1. Please find the transfer function  $v_o/v_i$ .



$$\frac{V_i}{250k} + \frac{V_o}{s \cdot 400p} + \frac{V_o}{125k + \frac{1}{s \cdot 1.6n}} = 0 \quad 10$$


$$H(s) = \frac{V_o}{V_i} = -10000 \cdot \frac{s + 5000}{s(s + 25000)} \quad 5$$

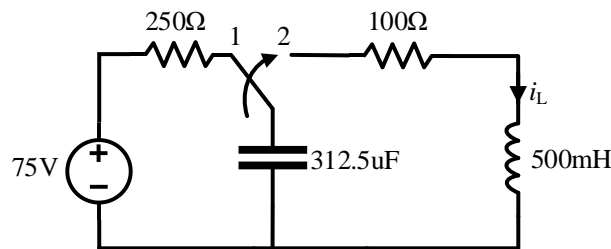2. For the following circuit, the switch had been at node 1 for a long time before  $t=0s$ . When  $t=0s$ , the switch was turned to node 2 immediately. If no initial energy was stored for the inductor, please use **Laplace domain method** to find  $i_L(t)$  for  $t>0s$



2.  $V_c(0^-) = 75V$ ,  $i_L(0^-) = 0$ ,  $V_c(0^+) = V_c(0^-) = 75$ ,  $i_L(0^+) = i_L(0^-) = 0 \quad (15)$

when  $t>0$ :

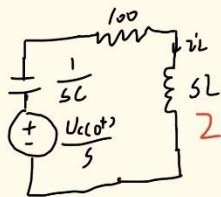

$$\frac{1}{sC} + sL + 100 \quad i_L = \frac{V_c(0^+)}{s} \quad 4$$

$$\therefore i_L(s) = \frac{75s}{(s^2LC + 100sC + 1)s} = \frac{75}{s^2LC + 100sC + 1} \quad 2$$


$$= \frac{75}{(0.00625s + 1)(0.025s + 1)}$$

$$= 25 \left( \frac{4}{0.025s + 1} - \frac{1}{0.00625s + 1} \right)$$

$$= 25 \left( \frac{160}{s + 40} - \frac{160}{s + 160} \right) \quad 2$$

$$\therefore i_L(t) = 1.25 (e^{-40t} - e^{-160t}), t > 0 \quad 3$$

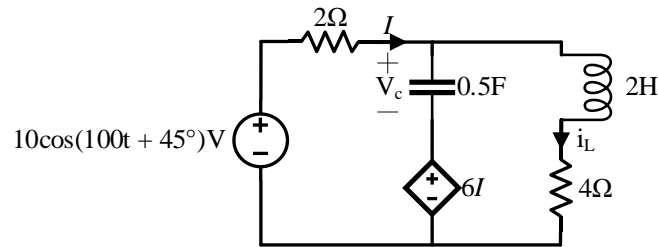3. Given no initial energy was stored for the energy storage elements, find steady-state response  $v_c$  by **Laplace domain method** and **phasor domain method**.



3. ①  $\dot{V} = 10 \angle 45^\circ$  1

2

$$\begin{cases} \dot{V}_c + 6I + 2I = 10 \angle 45^\circ & 2 \\ (I - \dot{V}_c j50)(j200 + 4) + 2I = 10 \angle 45^\circ & 2 \end{cases}$$

$$\dot{V}_c = 0.018 - 0.017j \approx 0.025 \angle -45^\circ$$

$$\therefore V_c(t) = 0.025 \cos(100t - 45^\circ)$$


---

②

2

$$\begin{cases} V_c(s) + 6I + 2I = V(s) & 2 \\ (I - V_c(s)sc)(sL + 4) + 2I = V(s) & 2 \end{cases}$$

$$H(s) = \frac{V_c(s)}{V(s)} = \frac{s-1}{4s^2 + 9s + 3}$$

$$V_c(s) = H(s)V(s) = 10e^{j0.45s} \cdot \frac{s(s-1)}{(s^2+100^2)(4s^2+9s+3)}$$

$$V_c(s) = 10e^{j0.45s} \cdot \frac{s(s-1)}{(s^2+100^2)(4s^2+9s+3)}$$


$$= \left( \frac{-4 \times (129997s + 29991)}{1600570009 \times (4s^2 + 9s + 3)} + \frac{129997s + 399880000}{1600570009 \times (s^2 + 100^2)} \right) 10e^{j0.45s}$$

steady-state response  $V_c(s) = \left( \frac{8.12 \times 10^{-5}s}{s^2 + 100^2} + \frac{2.50 \times 10^{-3} \times 100}{s^2 + 100^2} \right) 10e^{j0.45s}$

$$= 8.12 \times 10^{-4} \cos(100t + 45^\circ) + 2.5 \times 10^{-2} \sin(100t + 45^\circ)$$

$$\approx 0.025 \cos(100t - 45^\circ)$$

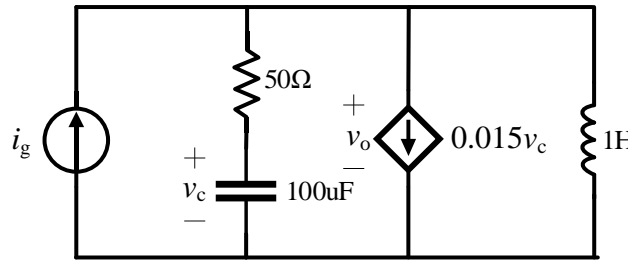4. When  $t=0$ , the current through the inductor is 5mA and no initial energy is stored for the capacitor. If  $i_g=20u(t)$ mA, find  $v_o(t)$  for  $t>0$  by **Laplace domain method**.




4.

$i_g(s) = \frac{0.02}{s}$  (2) (15)  
 $i_L(0^+) = i_L(0^-) = 5\text{mA}$  (1)  
 $v_o(s) = V_C(s) + 50sC V_C(s)$  (2)  
 $V_C(s)sC + \frac{V_C(s)}{sL} + 0.015 V_C(s) + \frac{0.005}{s} = \frac{0.02}{s}$  (2)  
 $V_C(s) = \frac{7.5 \times 10^{-5}s + 0.015}{0.0001s^2 + 0.02s + 1} = \frac{0.75}{s + 100} + \frac{75}{(s + 100)^2}$  (2)  
 $\therefore v_o(t) = 0.75 e^{-100t} + 75 t e^{-100t}, t > 0$  (1)


来自华为笔记

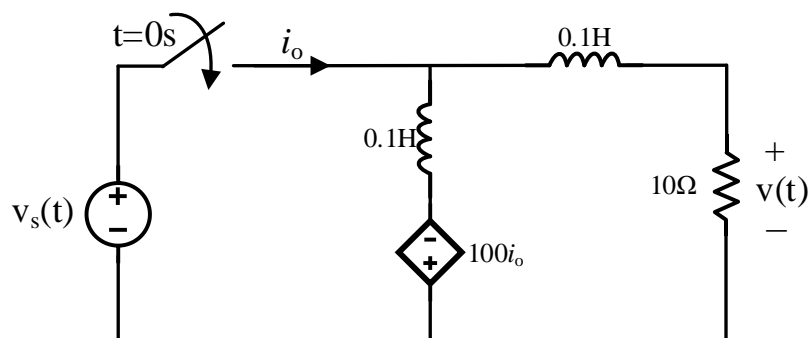5. For the following circuit,  $v_s(t)=10\cos(200t)$  V, and the switch closed immediately at  $t=0$ s. There is no energy stored for the inductors before  $t=0$ s. Please

- Use **phasor method** to find the **steady-state** for the voltage of  $v(t)$ .
- Use **Laplace domain method** to find **complete response** of  $v(t)$  for  $t>0$  and compare the results from (a).




5. (a)  $\dot{V}_s = 10 \angle 0^\circ$ ,  $\omega = 200$  |

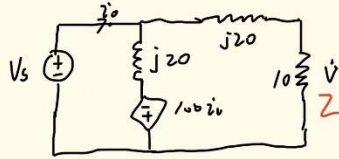

$$\frac{\dot{V}}{10} (10 + j20) = \dot{V}_s \quad 2$$

$$\therefore \dot{V} = \frac{10}{1+j2} = 2-4j = 4.47 \angle -63.4^\circ \quad 1$$
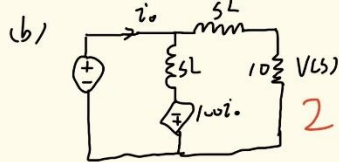
$$\therefore V(t) = 4.47 \cos(200t - 63.4^\circ), t > 0 \quad 1$$



$$\left\{ \begin{aligned} \frac{V(s)}{10} (5L + 10) &= V_s(s) \quad 2 \\ V_s(s) &= \frac{10s}{s^2 + 200^2} \quad 1 \end{aligned} \right.$$


$$\therefore V(s) = \frac{100s}{s^2 + 200^2} \cdot \frac{10}{s + 100} = \frac{2(s + 400)}{s^2 + 200^2} - \frac{2}{s + 100} \quad 2$$

$$\therefore V(t) = 2(0.5 \cos(200t) + 4 \sin(200t)) - 2e^{-100t}$$


$$= 4.47 \cos(200t - 63.4^\circ) - 2e^{-100t}, t > 0 \quad 1$$

来自华为笔记

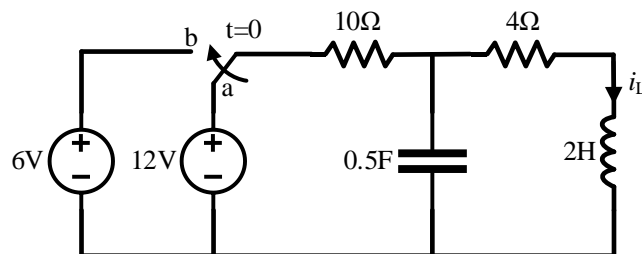6. For the following circuit, the switch had been at node **a** for a long time before  $t=0$ s. When  $t=0$ s, the switch was turned to node **b** immediately. Please use (a) **Laplace domain method** and (b) **time domain method** to find  $i_L(t)$  for  $t > 0$ s.


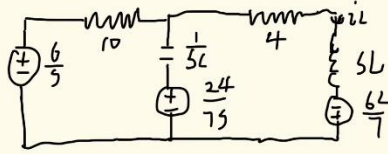
$$6.(a) \quad V_c(0^-) = V_c(0^+) = \frac{12}{10+4} \times 4 = \frac{24}{7} \text{ V} \quad i_L(0^-) = i_L(0^+) = \frac{12}{10+4} = \frac{6}{7} \text{ A} \quad (20)$$



$$\begin{cases} i_L(s)(5s+4) - \frac{6}{7} = V_c(s) + \frac{24}{7s} \\ [V_c(s)5s + i_L(s)] \cdot 10 + V_c(s) + \frac{24}{7s} = \frac{6}{s} \end{cases} \quad 2$$

$$\therefore \tilde{v}_L(s) = \frac{30s^2 + 66s + 21}{35s^3 + 77s^2 + 49s} \quad 2$$

$$= 0.43 \frac{s+1.1}{(s+1.1)^2 + 0.44^2} + 1.06 \frac{0.44}{(s+1.1)^2 + 0.44^2} + \frac{0.43}{s} \quad 2$$

$$\therefore i_L(t) = e^{-1.1t} [0.43 \cos 0.44t + 1.06 \sin 0.44t] + 0.43, \quad t \geq 0 \quad |$$

来自华为笔记

$$(b) \quad \begin{cases} C \frac{dv_c}{dt} + v_c \cdot 10 + 4i_L + L \frac{di_L}{dt} = 6 \\ v_c = 4i_L + L \frac{di_L}{dt} \end{cases} \quad 2$$

$$\Rightarrow 10 \frac{di_L^2}{dt^2} + 22 \frac{di_L}{dt} + 14i_L = 6 \quad |$$

$$x_1 = -1.1 - 0.44j, \quad x_2 = -1.1 + 0.44j \quad |$$

齐次解:

$$\tilde{i}_L(t) = e^{-1.1t} (C_1 \cos 0.44t + C_2 \sin 0.44t) \quad |$$

$$\text{特解: } \tilde{i}_L(t) = 0.43$$

$$\therefore i_L(t) = e^{-1.1t} (C_1 \cos 0.44t + C_2 \sin 0.44t) + 0.43 \quad |$$

$$\text{代入} \quad \begin{cases} i_L(0^+) = \frac{6}{7} \\ v_c(0^+) = \frac{24}{7} \end{cases} \Rightarrow \begin{cases} C_1 + 0.43 = \frac{6}{7} \\ (C_1 + 0.43) \times 4 + 2(-1.1C_1 + 0.44C_2) = \frac{24}{7} \end{cases}$$

$$\therefore \begin{cases} C_1 = 0.43 \\ C_2 = 1.06 \end{cases} \quad 2 \quad \therefore i_L(t) \text{ 同上}$$

来自华为笔记