



# Lecture 2

# Basic Laws & Circuit Analysis




# Outline

- *Concepts*: Branches, Nodes, and Loops
- *Basic Laws*
  - Ohm's Law
  - Kirchhoff's Laws -- KCL, KVL
- *Circuit Analysis*
  - Nodal Analysis
  - Mesh Analysis

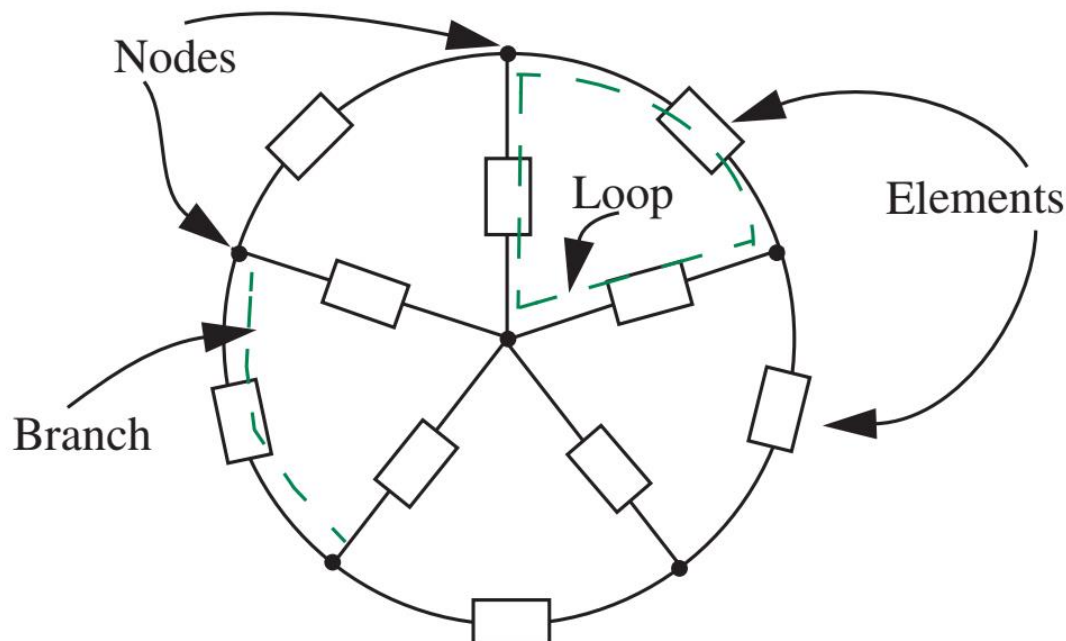
# Concepts: Branch, Node, and Loop

- **Branch**: represents a single element;
- **Node**: a point of connection between two or more branches;
- **Loop**: **any** closed path in a circuit.





## Example

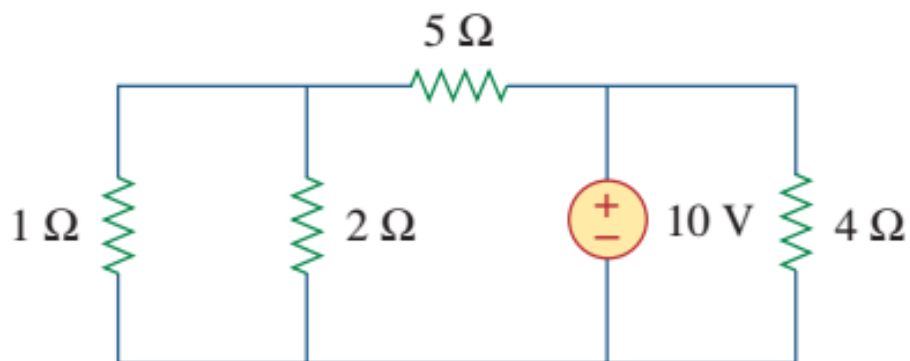

- $b$  – number of branches
- $n$  – number of nodes
- $l$  – number of loops



# Outline

- *Concepts*: Branches, Nodes, and Loops
- *Basic Laws*
  - Ohm's Law
  - Kirchhoff's Laws -- KCL, KVL
- *Circuit Analysis*
  - Nodal Analysis
  - Mesh Analysis

# Ohm's Law

Circuit symbol: 


- The current flowing in the resistor is proportional to the voltage across the resistor:

$$V = I * R$$

(Ohm's Law)

- Conductance** is the reciprocal of resistance

$$G = \frac{1}{R} = \frac{I}{V}$$

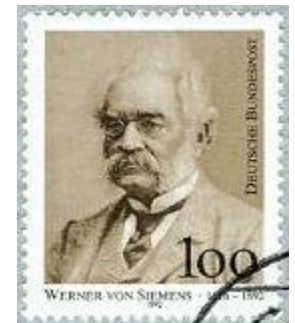


Werner von Siemens  
1816-1892

# Kirchhoff's Laws

- Kirchhoff's Current Law (KCL):

- The algebraic sum of all the **currents entering** any **node** in a circuit equals zero.
- Why?

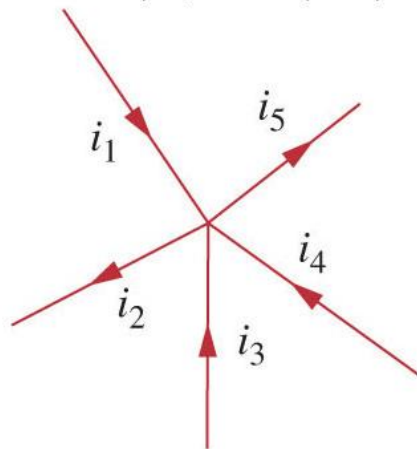
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



Gustav Robert Kirchhoff  
1824-1887

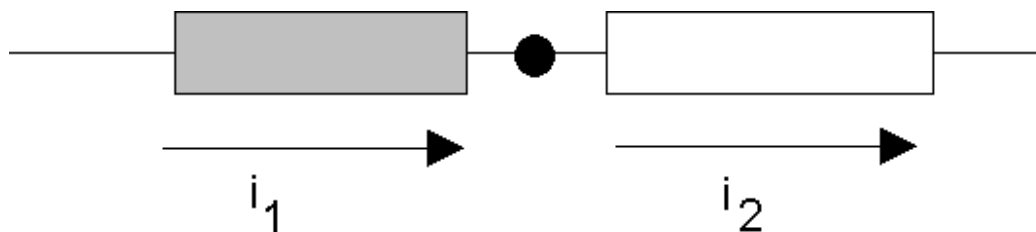
# KCL

- KCL tells us that **all of the elements that are connected *in series* carry the same current.**



Current entering node = Current leaving node

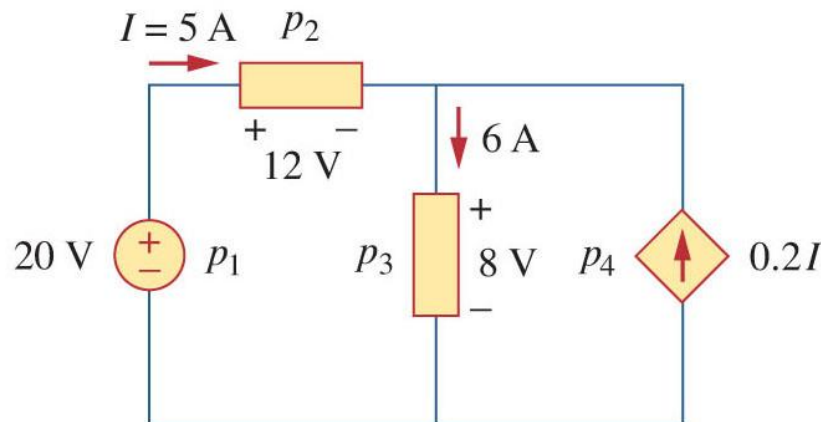Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display





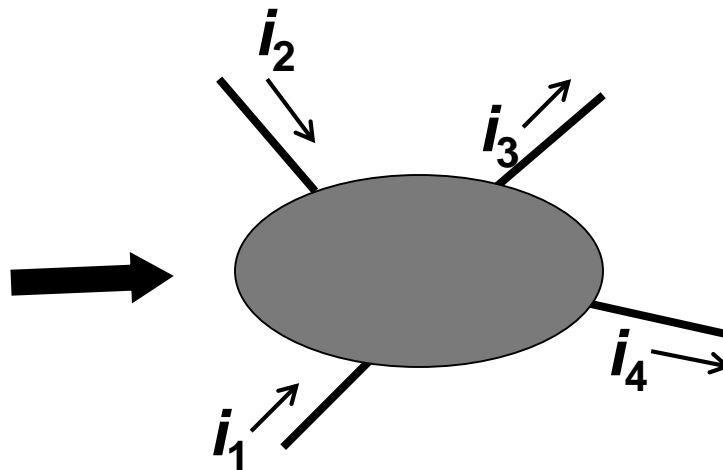
# Generalization of KCL



- The sum of currents entering/leaving a **closed surface** is zero.
  - Circuit branches can be inside this surface, *i.e.* the surface can enclose more than one node!

This could be a big chunk of a circuit, *e.g.* a “black box”






# Generalized KCL Examples

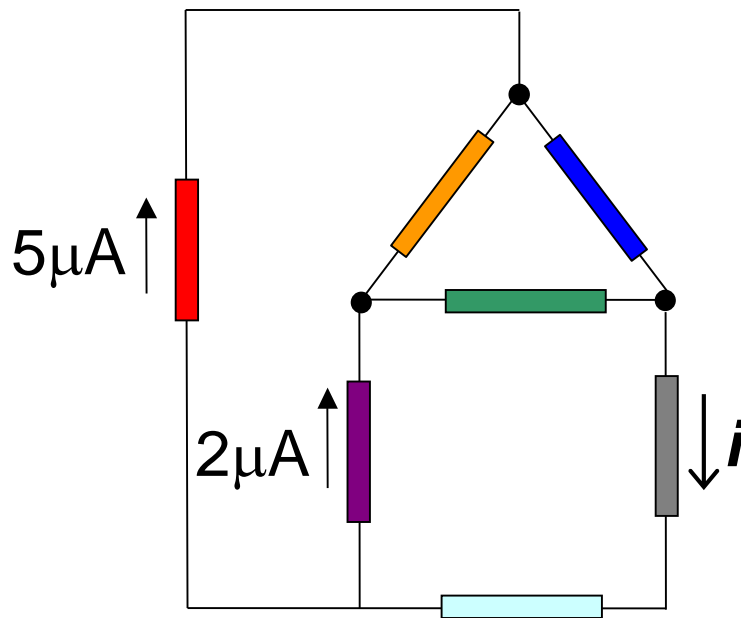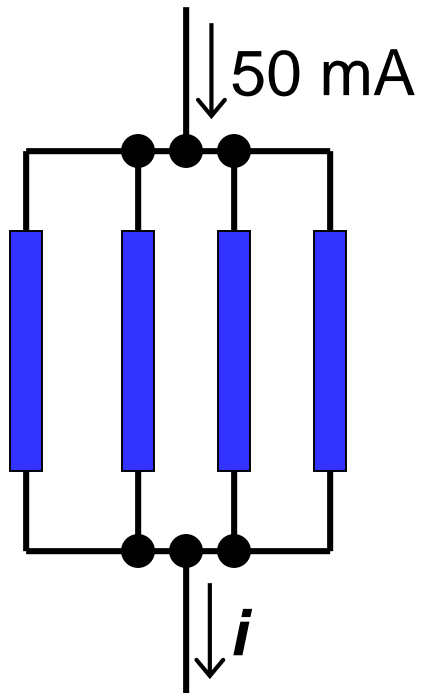


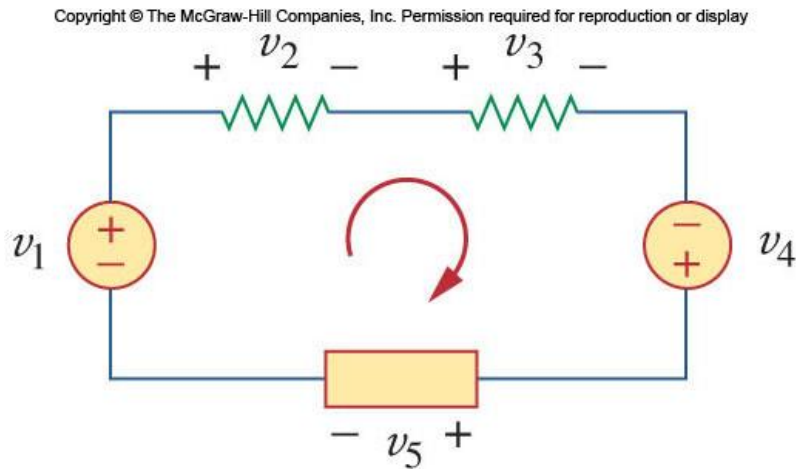
# Kirchhoff's Voltage Law (KVL)


- The algebraic sum of all the **voltages** around any **loop** in a circuit equals zero.
- Why?




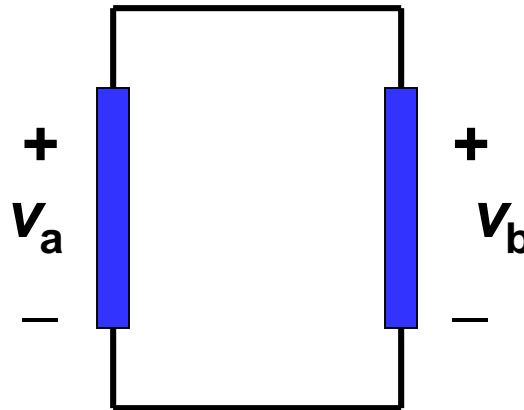
# KVL


- KVL tells us that **any set of elements which are connected at both ends carry the same voltage.**
- We say these elements are connected **in parallel.**





# KVL Example

Three closed paths:

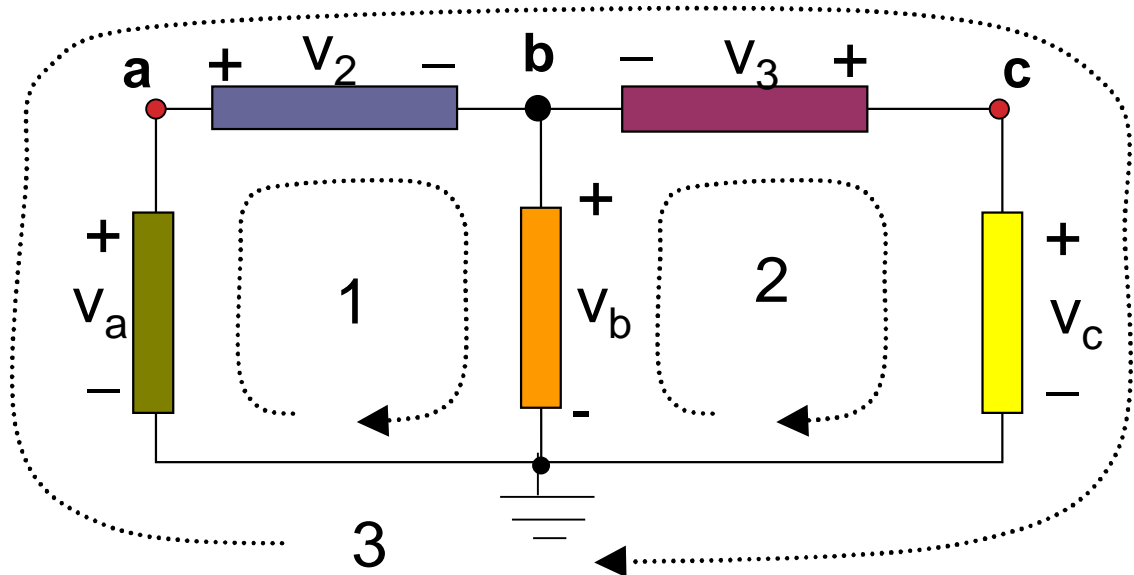


Path 1:

Path 2:


Path 3:



# Series Resistors

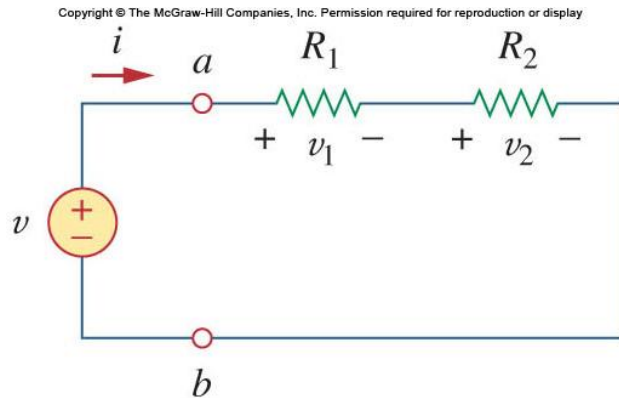


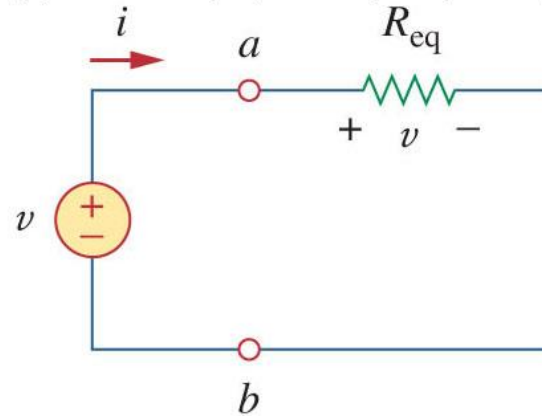
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display




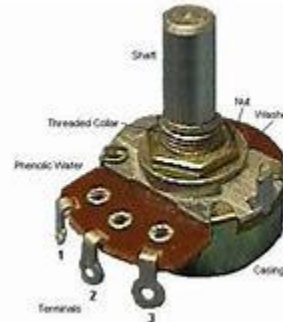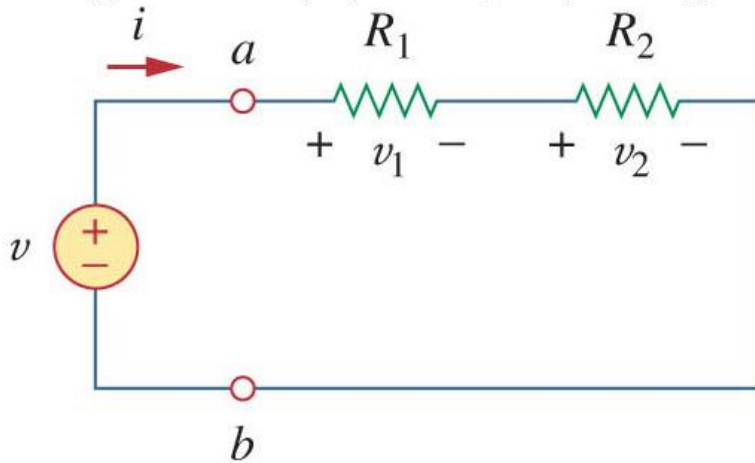
# Voltage Division

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display




Three-terminal rheostat



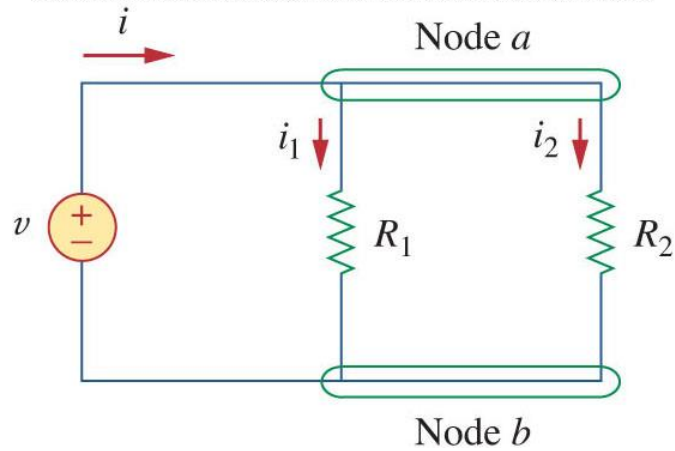
# Parallel Resistors

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



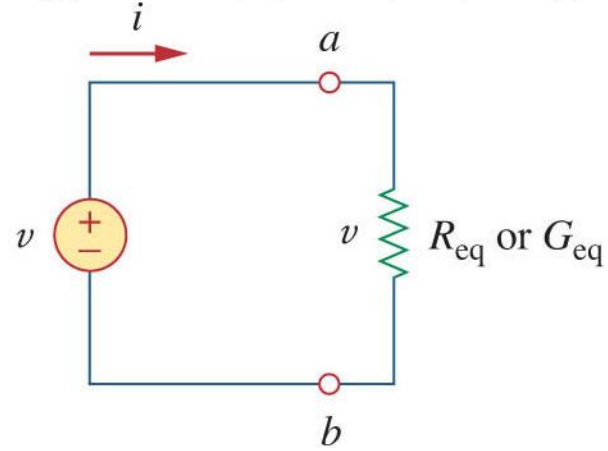Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display







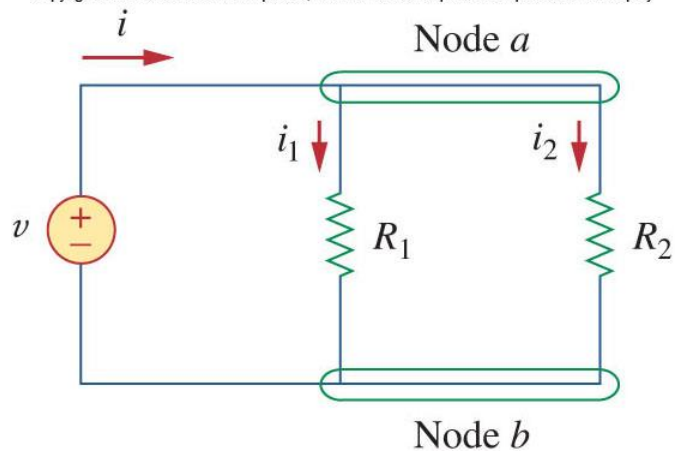
# Current Division

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display






# Summary-1

- KCL and KVL


$$\sum_{n=1}^N i_n = 0$$

$$\sum_{m=1}^M v_m = 0$$

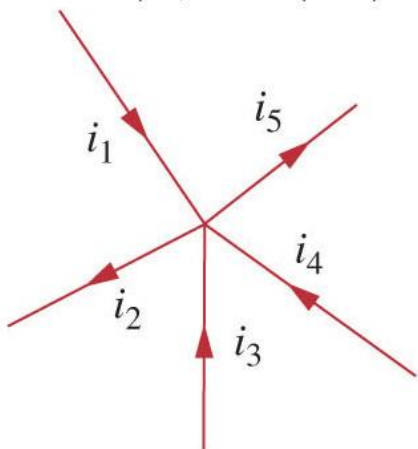Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display







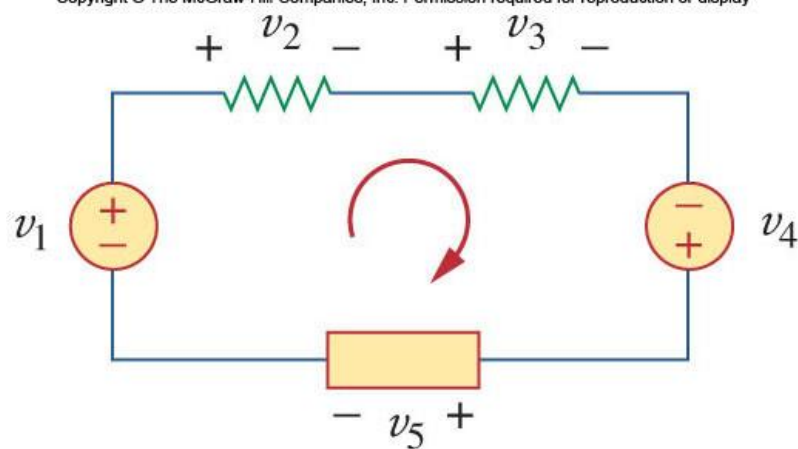Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display






## Summary-2

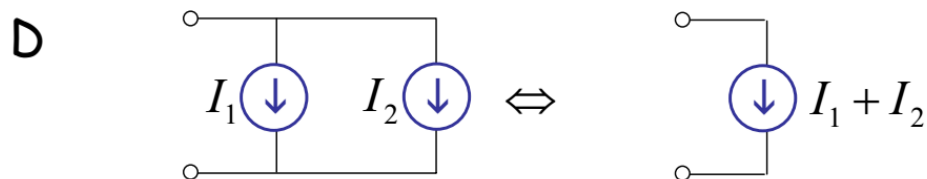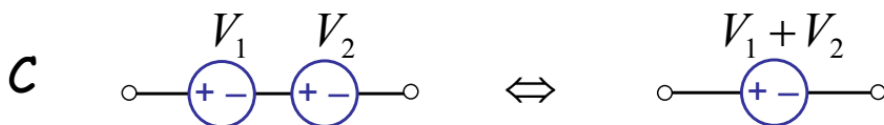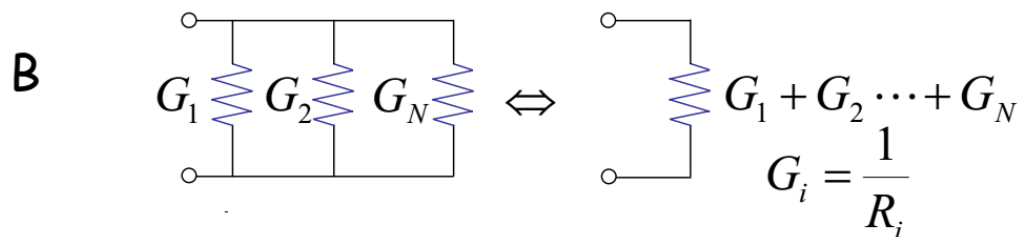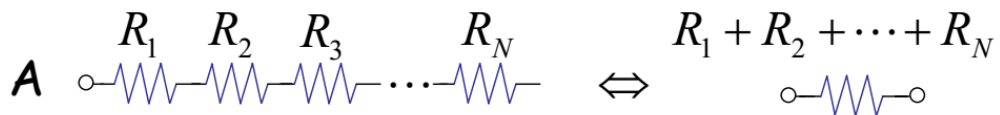







# Example

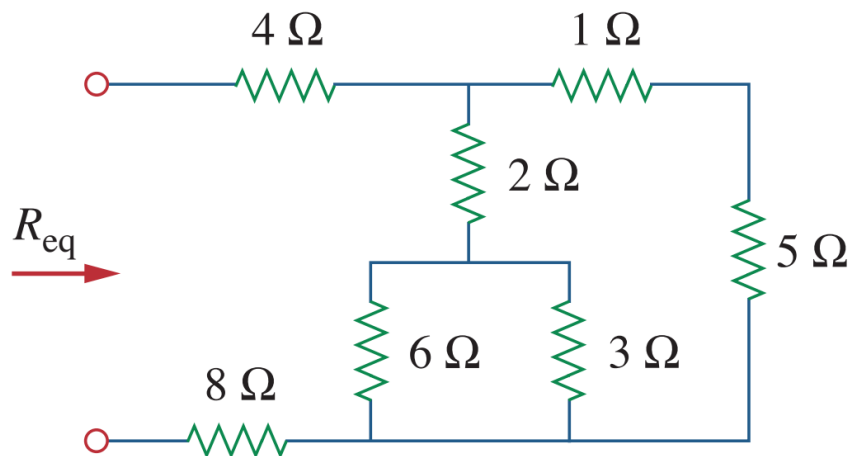




# Practice

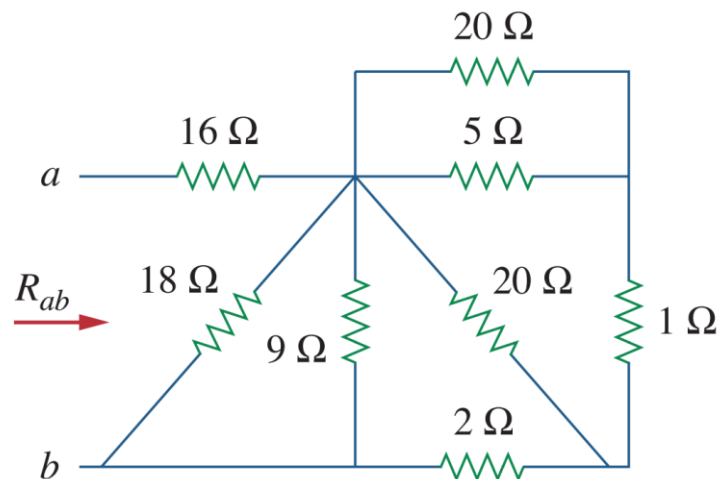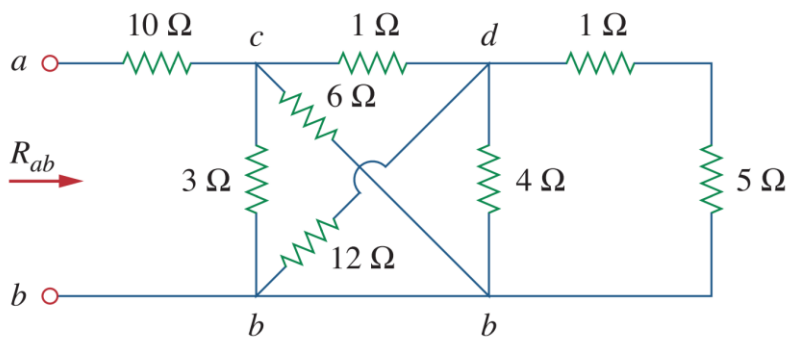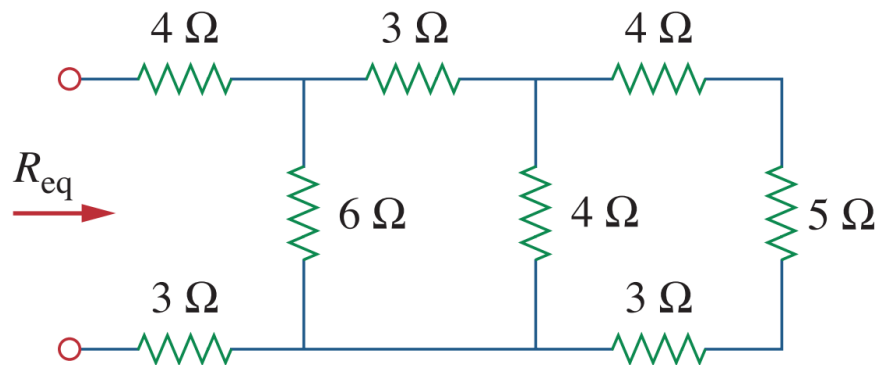

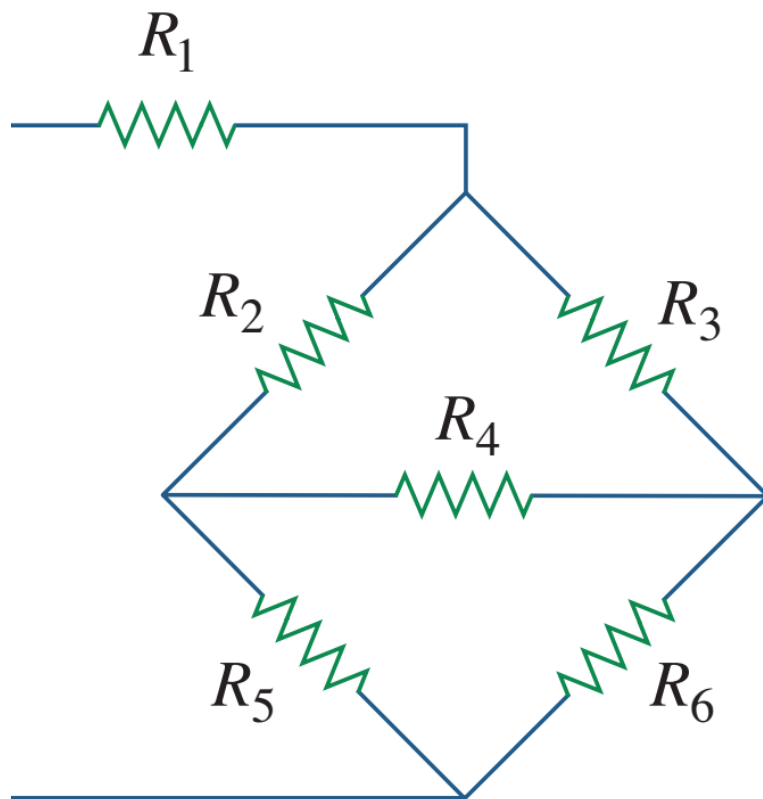



# Delta-wye conversion

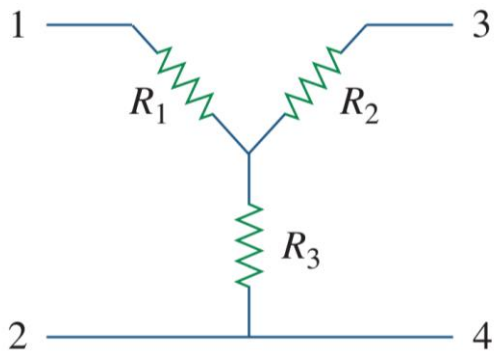

$$R_{12}(Y) = R_1 + R_3 \quad (2.46)$$

$$R_{12}(\Delta) = R_b \parallel (R_a + R_c)$$

Setting  $R_{12}(Y) = R_{12}(\Delta)$  gives

$$R_{12} = R_1 + R_3 = \frac{R_b(R_a + R_c)}{R_a + R_b + R_c} \quad (2.47a)$$

Similarly,

$$R_{13} = R_1 + R_2 = \frac{R_c(R_a + R_b)}{R_a + R_b + R_c} \quad (2.47b)$$

$$R_{34} = R_2 + R_3 = \frac{R_a(R_b + R_c)}{R_a + R_b + R_c} \quad (2.47c)$$


Subtracting Eq. (2.47c) from Eq. (2.47a), we get

$$R_1 - R_2 = \frac{R_c(R_b - R_a)}{R_a + R_b + R_c} \quad (2.48)$$

Adding Eqs. (2.47b) and (2.48) gives


$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c} \quad (2.49)$$
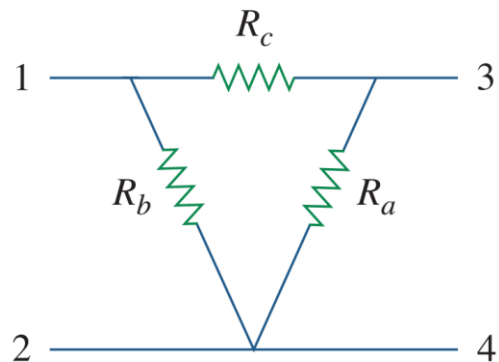
$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c} \quad R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$





# Wye-delta conversion

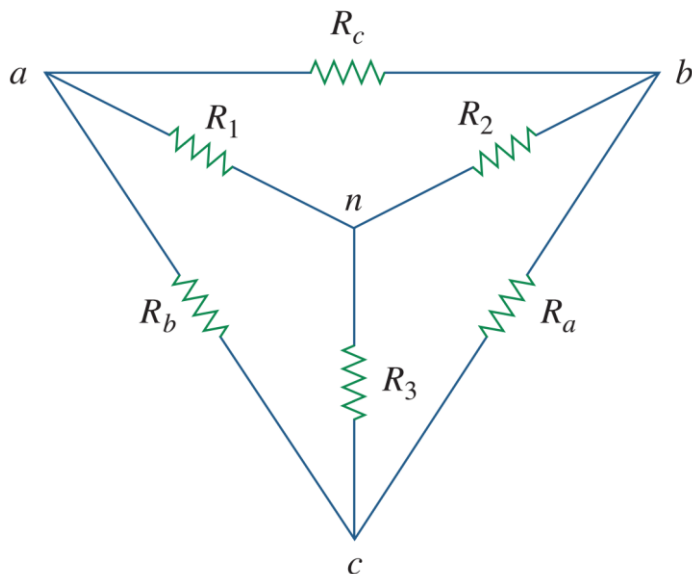

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

The Y and  $\Delta$  networks are said to be *balanced* when

$$R_1 = R_2 = R_3 = R_Y, \quad R_a = R_b = R_c = R_\Delta \quad (2.56)$$

Under these conditions, conversion formulas become

$$R_Y = \frac{R_\Delta}{3} \quad \text{or} \quad R_\Delta = 3R_Y \quad (2.57)$$





# Outline

- Basic Laws
  - Ohm's Law
  - Kirchhoff's Laws -- KCL, KVL
- Circuit Analysis
  - Nodal Analysis
  - Mesh Analysis



# Circuit Analysis

- Two techniques will be presented in this part:
  - Nodal analysis, which is based on **KCL**
  - Mesh analysis, which is based on **KVL**




# Nodal Analysis – Three Steps

- Given a circuit with  $n$  nodes, the nodal analysis is accomplished via three steps:
  1. Select a node as the reference (i.e., ground) node. Assign the node voltages to the remaining  $(n-1)$  nodes. Voltages are relative to the reference node.
  2. Apply KCL to the  $(n-1)$  nodes, expressing branch current in terms of the node voltages (using the  $I$ - $V$  relationships of branch elements).
  3. Solve the resulting simultaneous equations to obtain the unknown node voltages.





# Nodal Analysis: Example #1

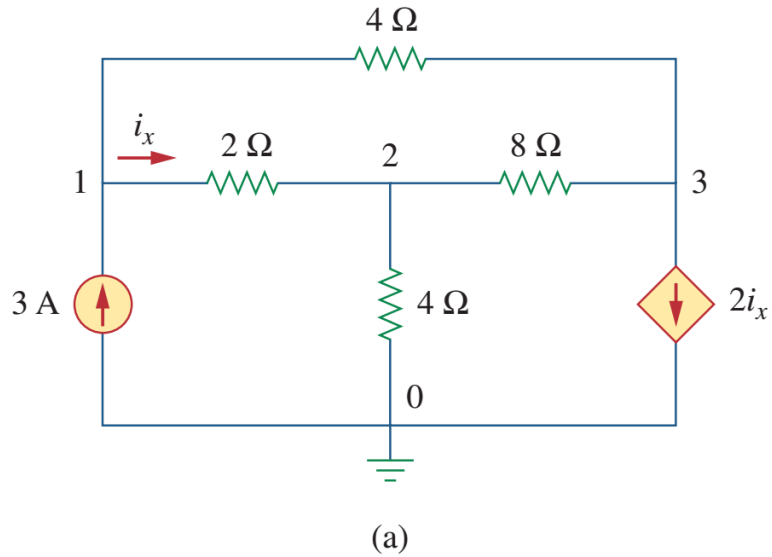




# Nodal Analysis: Example #1

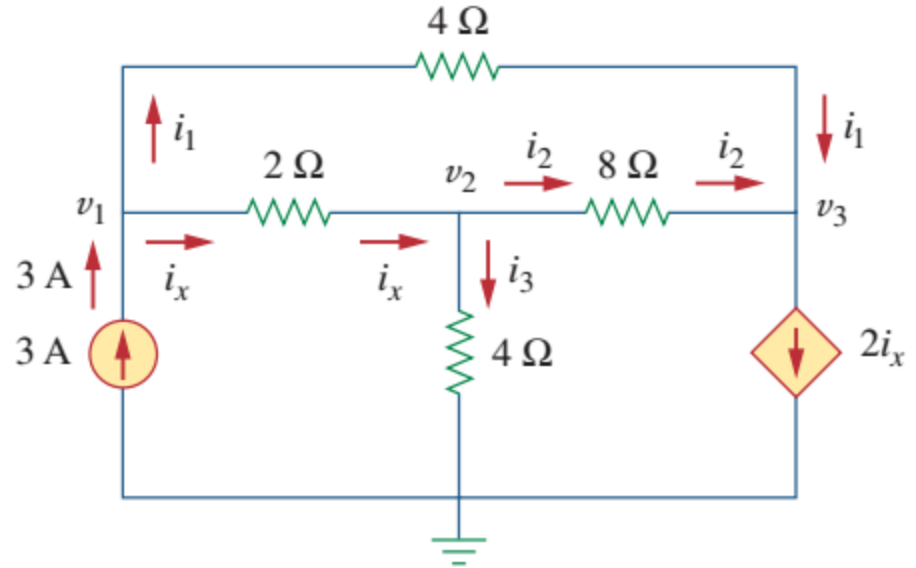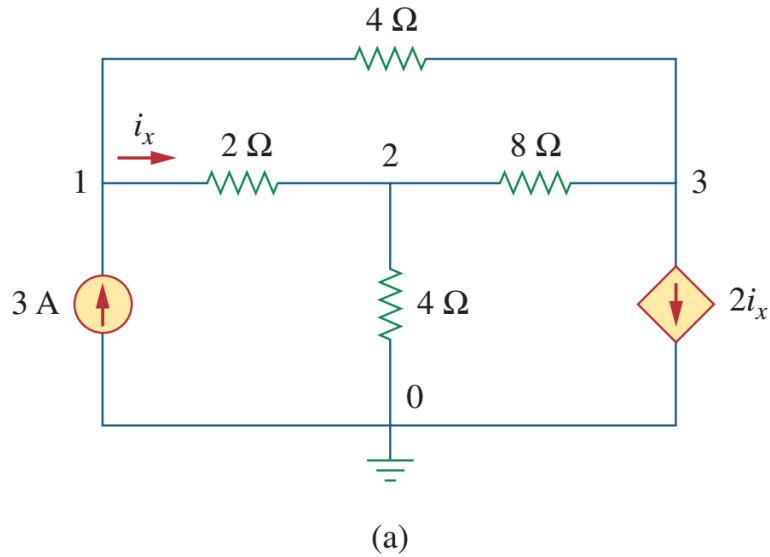



# Nodal Analysis with Voltage Sources


## Case I:

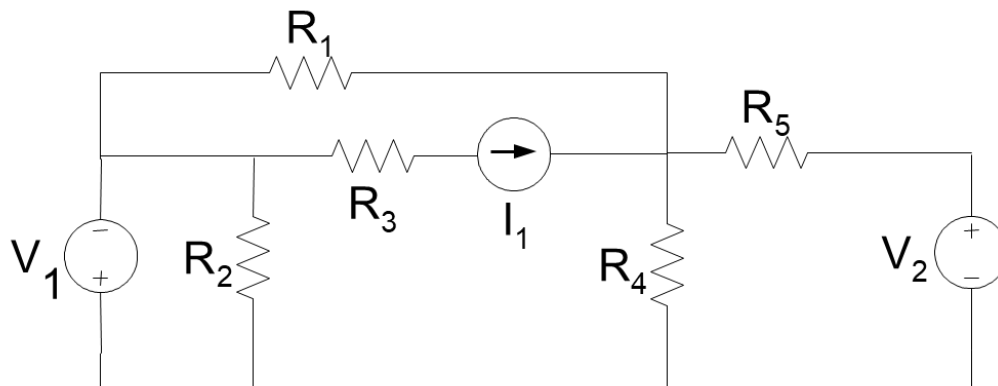

# Nodal Analysis: Supernode
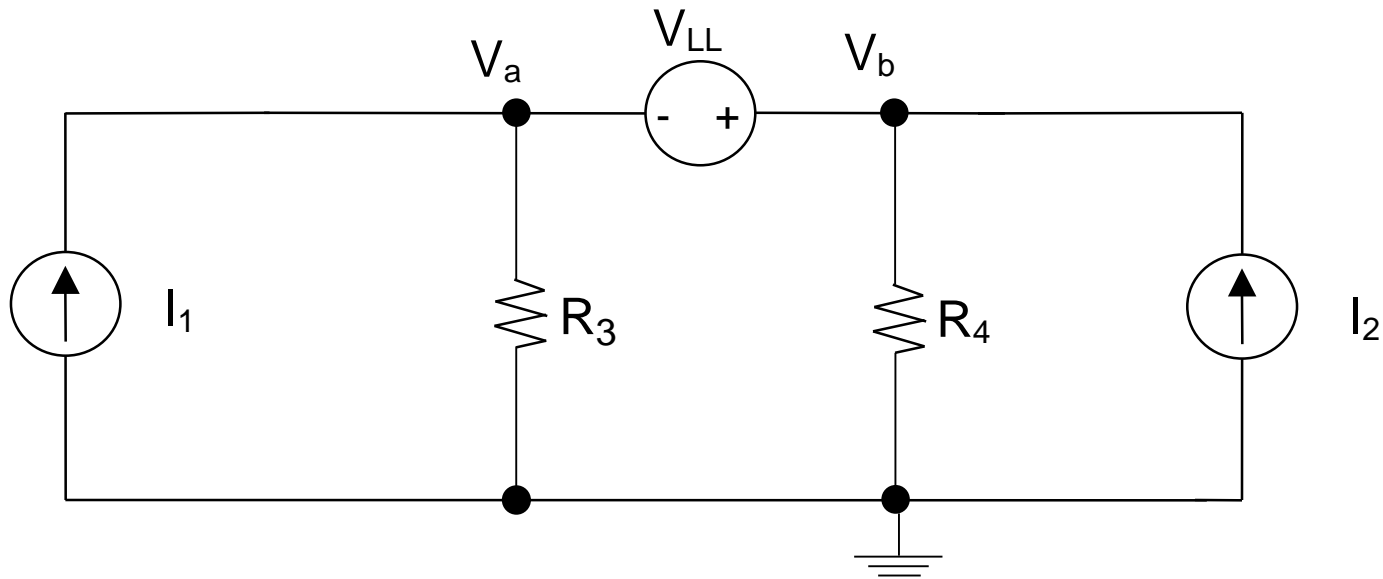
## Case II

A “floating” voltage source is one for which **neither** side is connected to the reference node, e.g.  $V_{LL}$  in the circuit below:




A supernode is formed by enclosing a (dependent or independent) voltage source connected between two nonreference nodes and any elements connected in parallel with it.


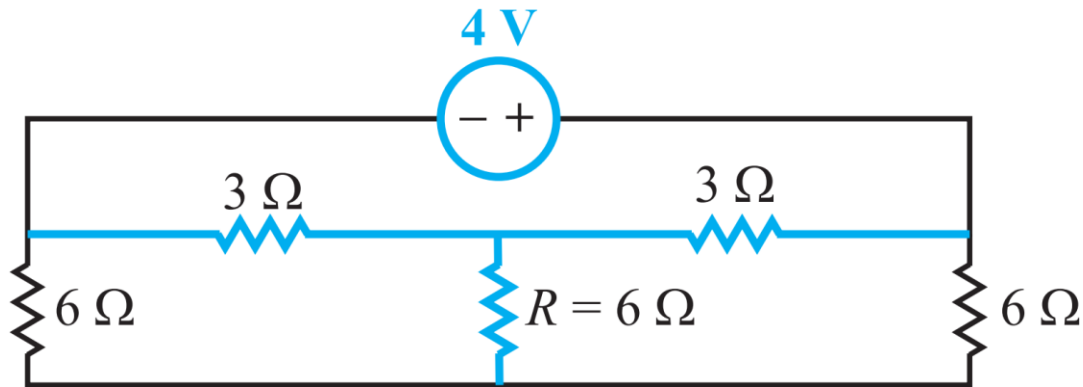
## Exercise

- Find the power supplied by the voltage source.





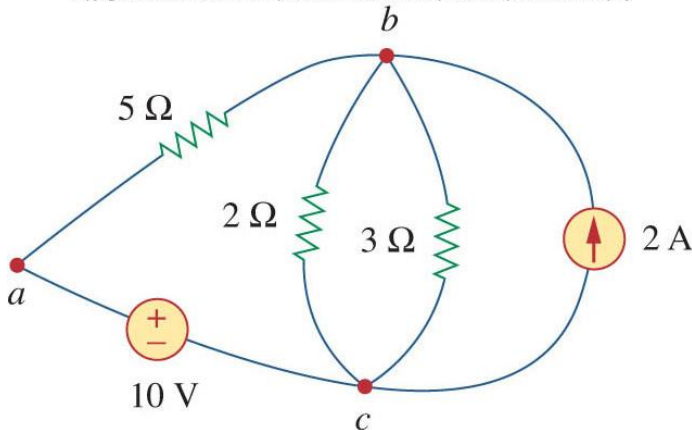
# Mesh Analysis--Loop, Independent Loop, Mesh

- A loop is a closed path.
- A loop is independent if it contains at least one branch which is not a part of any other independent loop.
- A mesh is a loop that does not contain any other loop within it.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



- $b$  – number of branches
- $n$  – number of nodes
- $l_{ind}$  – number of ind. loops


Mesh = Independent loop?

$$l_{ind} = b - (n - 1)$$


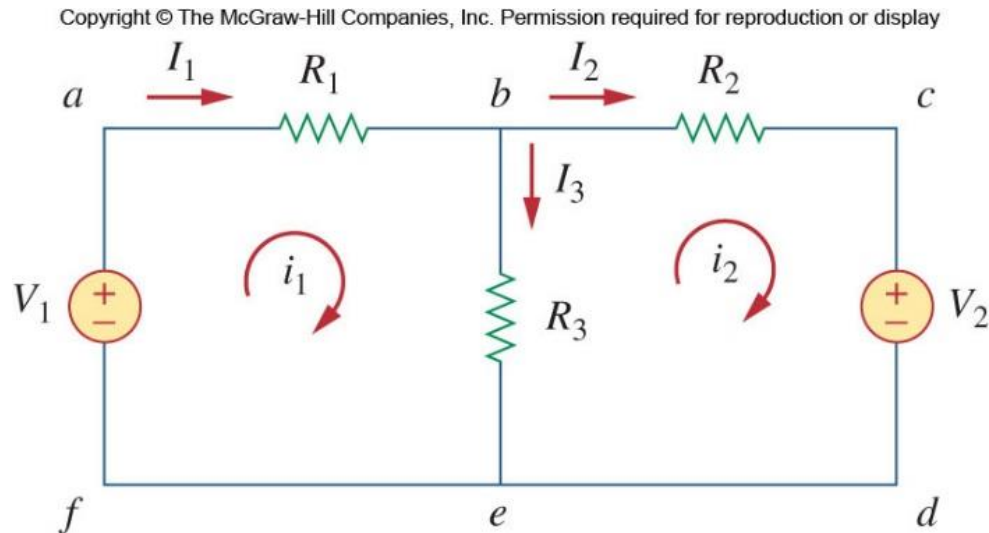
# Mesh Analysis

- Another general procedure for analyzing circuits is to use the mesh currents as the circuit variables.




- Mesh analysis uses KVL to find unknown currents.



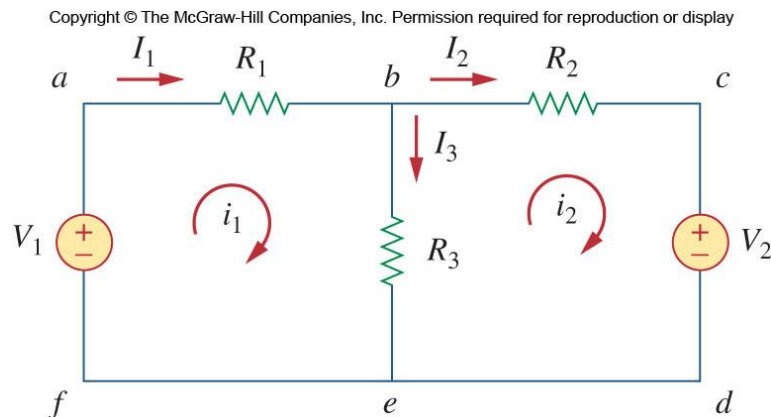
# Mesh Analysis Steps

- Mesh analysis follows these steps:
  1. Assign mesh currents  $i_1, i_2, \dots, i_x$  to the  $x$  meshes
  2. Apply KVL to each of the  $x$  mesh currents.
  3. Solve the resulting  $x$  simultaneous equations to get the mesh currents.






# Example

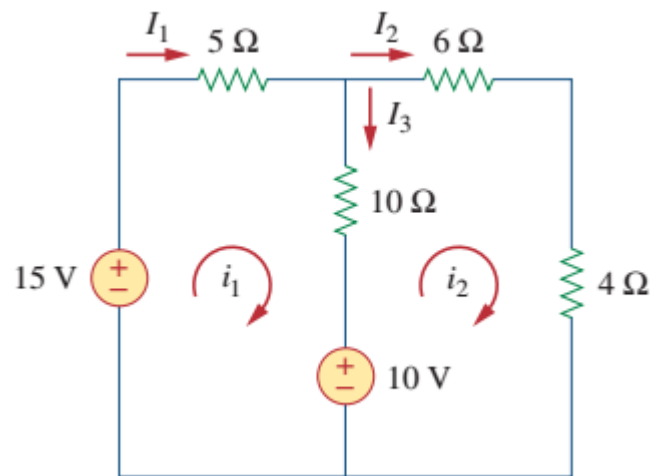

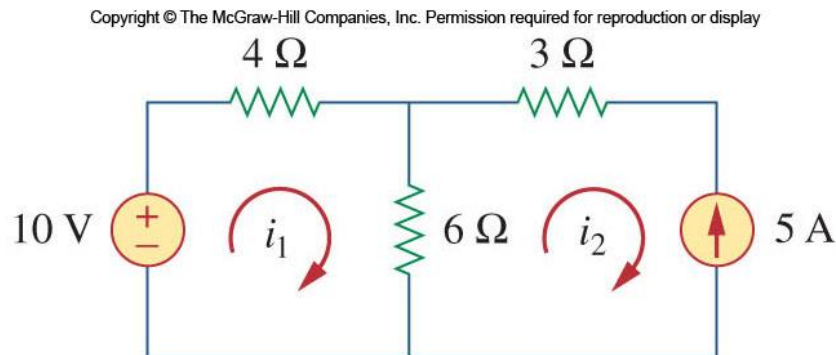
# Mesh Analysis with Current Sources

- The presence of a current source makes the mesh analysis simpler in that it reduces the number of equations.
  - If the current source is located on only one mesh, the current for that mesh is defined by the source. For example:







If the current source is located...

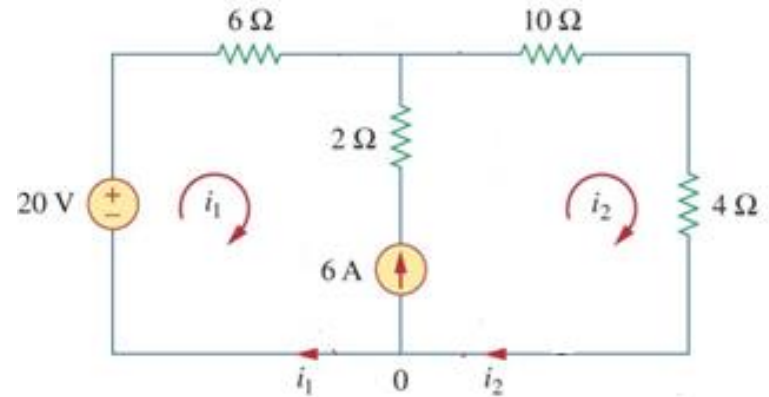




# Supermesh

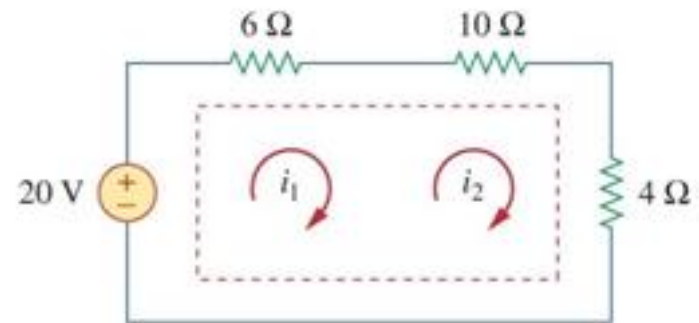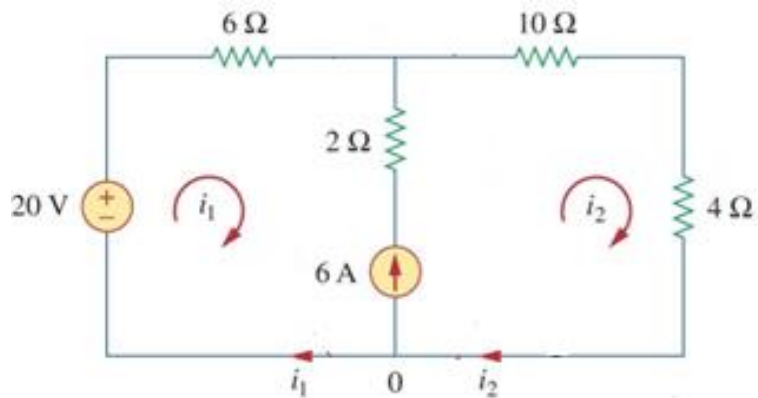

# Summary
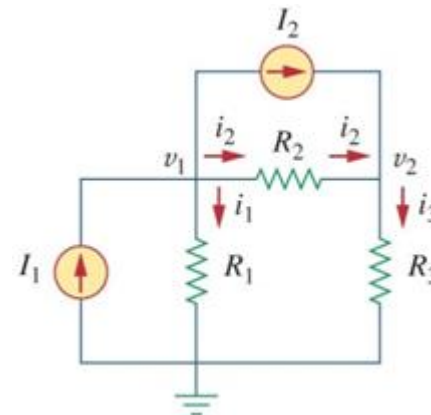
## • Node Analysis

- Node voltage is the unknown
- Solve by KCL
- Special case: Floating voltage source



## • Mesh Analysis

- Mesh current is the unknown
- Solve by KVL
- Special case: Current source

