

## **Homework 1**


Due date: Oct. 19<sup>th</sup>, 2023

Turn in your hard-copy hand-writing homework in class


Rules:

- Work on your own. Discussion is permissible, but extremely similar submissions will be judged as plagiarism.
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.

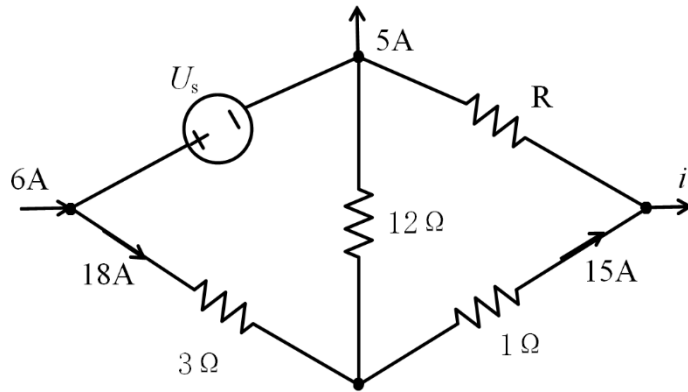1. (a) Use Kirchhoff's law to find  $U_s$  and  $i$ .  
(b) Calculate resistance  $R$ .



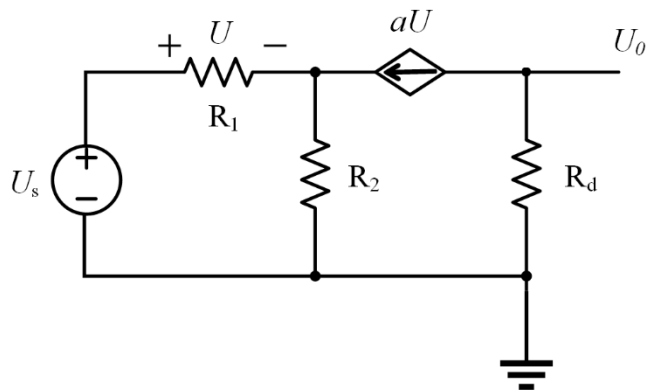
2. Use Kirchhoff's law to calculate  $U_o/U_s$  in terms of  $a$ ,  $R_1$ ,  $R_2$ , and  $R_d$ . Except for  $U$ , all other variables are known quantities.




3. For the circuit below, using  $\Delta$ -Y conversion

(a) Calculate the  $U$ .

(b) Calculate the  $U_{ab}$ .

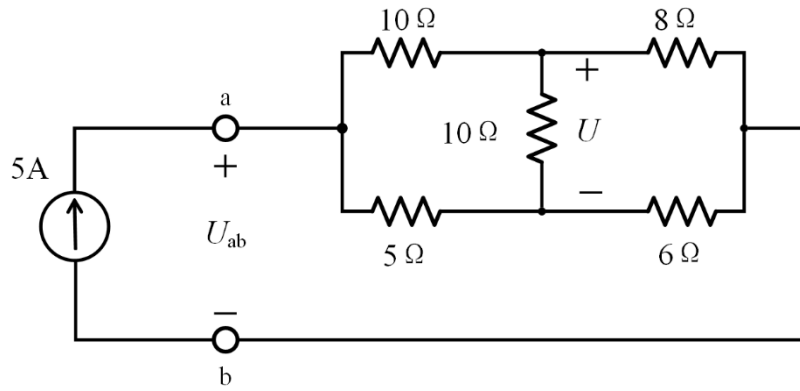

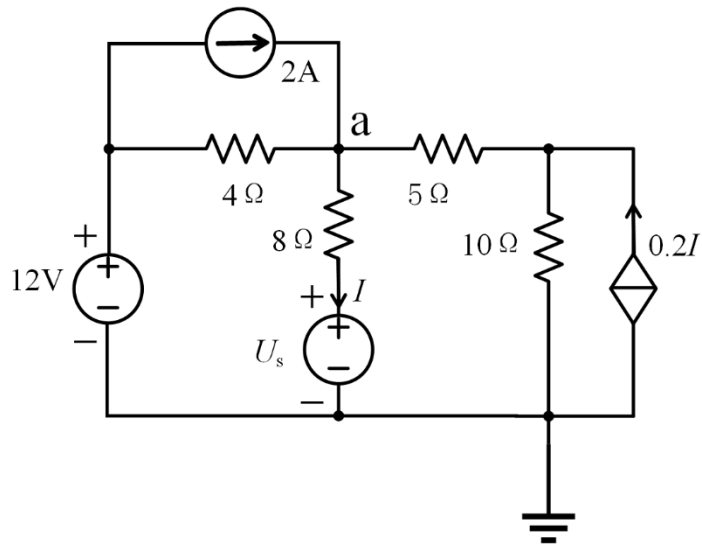
4. The node voltage  $U_a$  equals 15V, using nodal analysis method to obtain  $U_s$  and  $I$ .




5. For the circuit below,

(a) apply nodal analysis method to find  $V_a$ ,  $V_b$ .

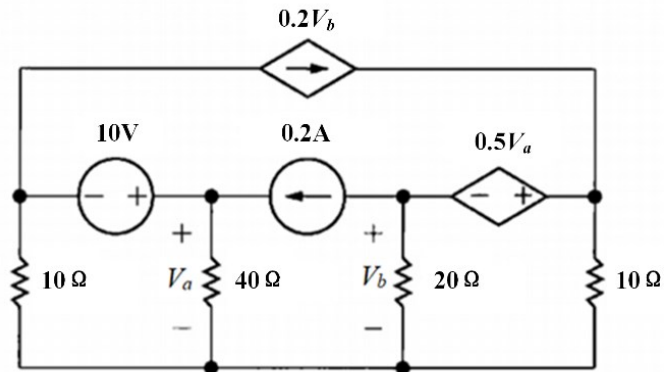(b) find the power delivered by each source (2 voltage sources and 2 current sources).



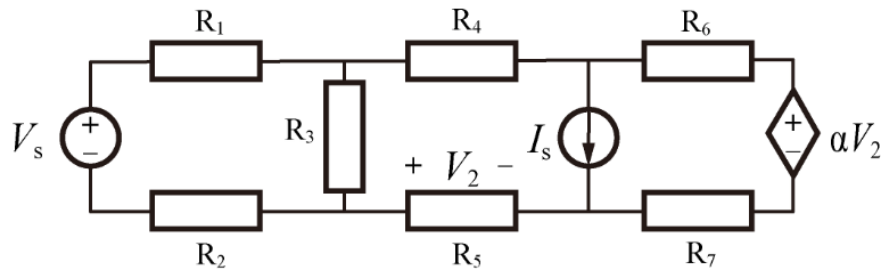6. Use mesh current analysis method, calculate the absorbed power of current source and voltage source, given  $R_1 = R_2 = R_3 = R_4 = R_5 = R_6 = R_7 = 1\Omega$ ,  $\alpha = 4$ ,  $I_s = 1A$ ,  $V_s = 1V$



7.  $R_1 = R_2 = R_3 = R_4 = 10\Omega$ ,  $\beta = 2$ , use the mesh current method to find  $V_s/i$

