

Student Name: \_\_\_\_\_

Student Number: \_\_\_\_\_

School: \_\_\_\_\_

Year of Entrance: \_\_\_\_\_

## ShanghaiTech University Midterm Examination Cover Sheet

EE111 Fall 2023/2024 Exam Time 2023/11/18 8:15am-9:55am

6 problems in total (1 A4 crib sheet allowed)

Answer the Questions in English

Two-decimal policy applies for the final answer

Academic Year: 2023 to 2024

Term: Fall

Course-offering School: SIST

Instructor: Dr. Xinbo ZOU

Course Name: Electrical Circuits

Course Number: EE111.01

### Exam Instructions for Students:

1. All examination rules must be strictly obeyed throughout the entire test, and any form of cheating is prohibited.
2. Other than allowable materials, students taking closed-book tests must place their books, notes, tablets and any other electronic devices in places designated by the examiners.
3. Students taking open-book tests may use allowable materials authorized by the examiners. They must complete the exam independently without discussion with each other or exchange of materials.

### For Marker's Use:

Section	1	2	3	4	5	6	Total
Marks							
Recheck							

Marker's Signature:

Date:

Rechecker's Signature:

Date:

Q1. (15 points) For the following circuit, apply **mesh** analysis method to find current  $I$  and the power absorbed by the **independent source**.


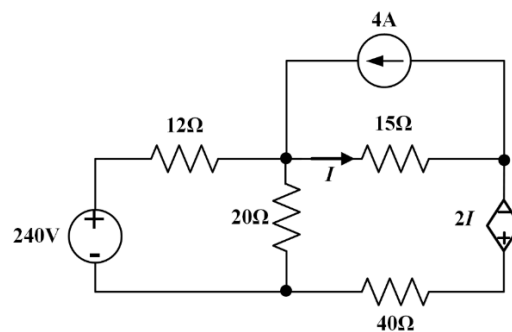


Fig.Q1

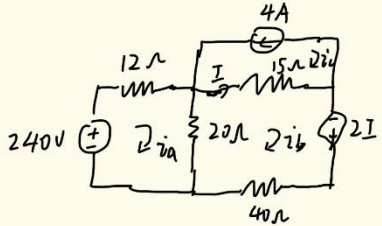

$$\begin{cases} -240 + 12i_a + 20i_a - 20i_b = 0 & 2 \\ (20 + 40 + 15)i_b - 20i_a - 15i_c - 2I = 0 & 2 \\ i_c = -4 & 2 \\ I = i_b - i_c & 2 \end{cases}$$

解得:  $i_a = 8.51A$ ,  $i_b = 1.62A$ ,  $i_c = -4A$

$I = i_b - i_c = 5.62A$

$P_V = -240 \times 8.51 = -2042.4W$

$P_A = -4 \times I \times 15 = -337.2W$

Q2. (15 points) Use **nodal analysis** method to calculate the voltage for node  $a$ ,  $b$  and  $c$ , namely  $v_a$ ,  $v_b$ , and  $v_c$ .

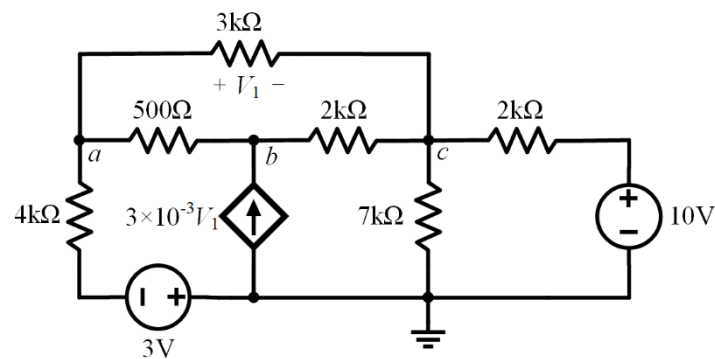


Fig.Q2

$$\begin{cases} \frac{V_a + 3}{4k} + \frac{V_a - V_b}{0.5k} + \frac{V_a - V_c}{3k} = 0 & 3 \\ \frac{V_b - V_a}{0.5k} + \frac{V_b - V_c}{2k} - 3 \times 10^{-3} V_1 = 0 & 3 \\ \frac{V_c}{7k} + \frac{V_c - 10}{2k} + \frac{V_c - V_a}{3k} + \frac{V_c - V_b}{2k} = 0 & 3 \\ V_1 = V_a - V_c & 2 \end{cases}$$

$$\begin{cases} 31V_a - 24V_b - 4V_c = 9 \\ -10V_a + 5V_b + 5V_c = 0 \\ -14V_a - 21V_b + 62V_c = 210 \end{cases} \Rightarrow V_a = 17V, V_b = 20V, V_c = 14V \quad 2$$

Q3. (15 points) For the following circuit, using **Thevenin equivalent circuit** to determine the **value of  $R$**  when maximum power could be transferred to it, and calculate the **maximum power  $P_R$**

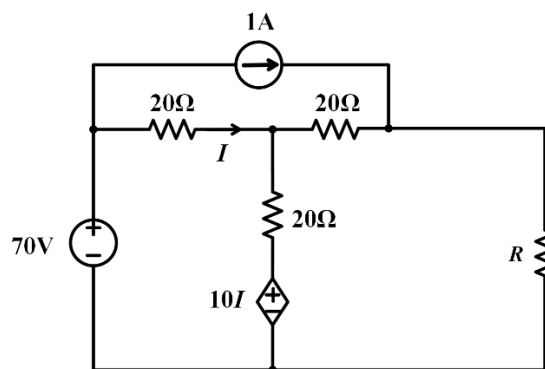


Fig.Q3

3.

$$\begin{aligned} V_o &= 20(I_1 - I) + 20I_1 + 10(I_1 - I) \\ I_1 &= 2A \quad \checkmark \\ V_{oc} &= 20(1) + 20(1) + 10(1 - 1) \\ &= 70 \quad 3' \end{aligned}$$

$$\begin{aligned} 70 - 10I &= 40I_v - 20 - 20I_{sc} \\ 10I &= 40I_{sc} - 20I_v - 20 \\ I &= I_v - 1 \\ \begin{cases} I_v = 3A \\ I_{sc} = 2.5A \end{cases} & \quad 4' \end{aligned}$$

$$R_{eq} = \frac{V_{oc}}{I_{sc}} = 28\Omega \quad 1'$$

$$R = R_{eq} = 28\Omega \quad 1'$$

$$P_R = \frac{V_{oc}^2}{4R} = 43.75W \quad 4'$$

Q4. (15 points) The following operational amplifier is working in its linear mode. Find the expression of  $v_o$  using  $v_1$ ,  $v_2$ ,  $R_a$ ,  $R_b$ ,  $R_c$ , and  $R_d$ .

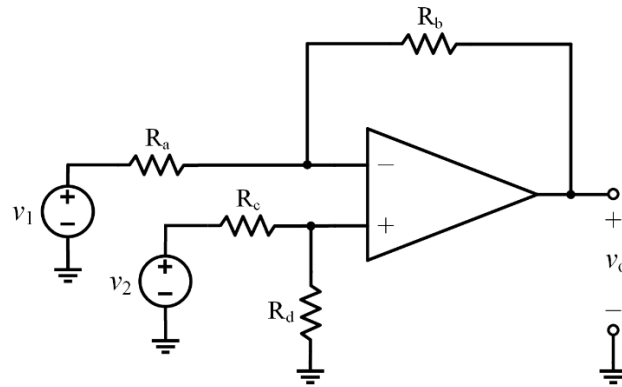


Fig.Q4

$$\left( V_o - \frac{V_2 R_d}{R_c + R_d} \right) \cdot \frac{1}{R_b} = - \left( V_1 - \frac{V_2 R_d}{R_c + R_d} \right) \frac{1}{R_a} \quad 10$$

$$V_o = \frac{R_d (R_a + R_b)}{R_a (R_c + R_d)} V_2 - \frac{R_b}{R_a} V_1 \quad 5$$

Q5. (20 points) In the circuit below, the switch has been open for a long time and reaches steady state before  $t=0$ . At  $t=0$ , the switch is turned to node  $a$  and remains there for **15ms**. Then it is turned to node  $b$ . Given no initial charge stored in the capacitor, please find:

(a)  $v_c(t)$  for  $t > 0$ . (15 points)

(b) Sketch the plot of  $v_c(t)$  versus time  $t$ . (5 points)

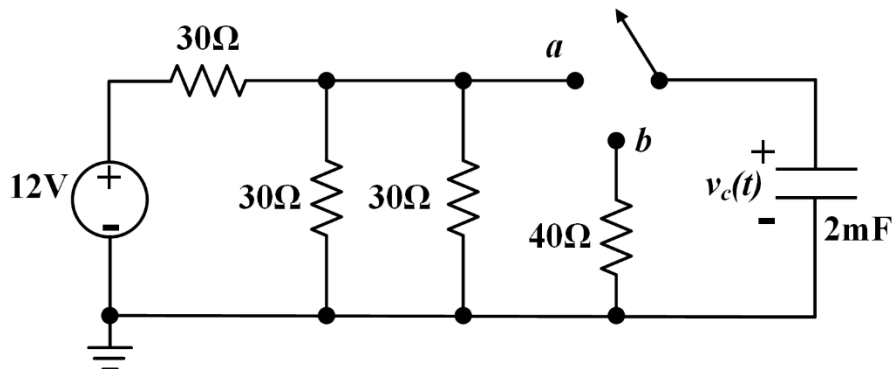


Fig.Q5

Natural response:

Using Thevenin:

$$V_{oc} = 12 \times \frac{30 \parallel 30}{30 \parallel 30 + 30} = 4V$$

$$R_{eq} = 30 \parallel 30 \parallel 30 = 10\Omega$$

When  $t < 0$ ,  $V_{C(0^-)} = 0V$

$t = 0^+$ ,  $V_{C(0^+)} = V_{C(0^-)} = 0V$

$t > 0$ ,  $V_{C(\infty)} = 4V$

$$\tau = R_{eq} \cdot C = 10 \times 10 \times 10^{-6} F = 0.1ms$$

$$V_{C(t)} = 4 - 4e^{-50t} \quad (t > 0)$$

When  $t = 15ms$ ,  $V_{C(15ms)} = 4 - 4e^{-50 \times 0.015} = 2.11V$

$$\tau' = 40 \times 10 \times 10^{-6} F = 0.4ms$$

$$V_{C(t)} = 2.11 e^{-\frac{t-0.015}{0.0004}} = 2.11 \cdot e^{-2500(t-0.015)} = 2.545 e^{-2500t}$$

Q6. (20 points) For the following circuit, the switch has been at node **a** for a long time before  $t=0$ .

At  $t = 0$ , the switch is turned to node **b**. Please find

- the current on the inductance  $i_L(t)$  for  $t \geq 0$ . (10 points)
- the voltage on the inductance  $v_L(t)$  for  $t \geq 0$  (5 points)
- the voltage on the  $2\Omega$ -resistor  $v(t)$  for  $t \geq 0$  (5 points)


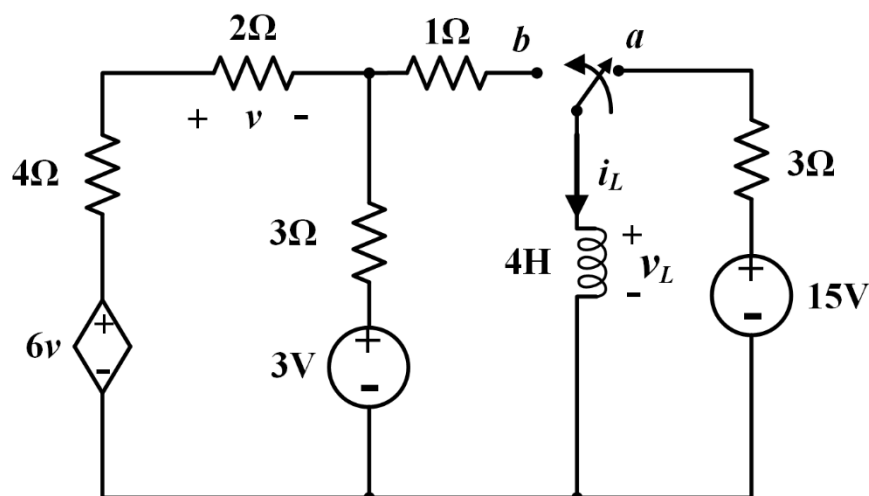




Fig.Q6

6. (a)

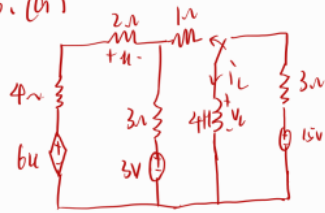


$$t < 0: i_{L(0^-)} = \frac{15}{3} = 5 \text{ A}$$
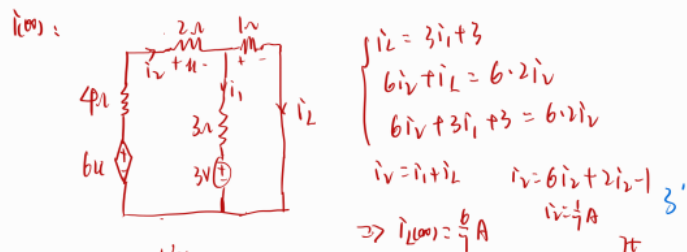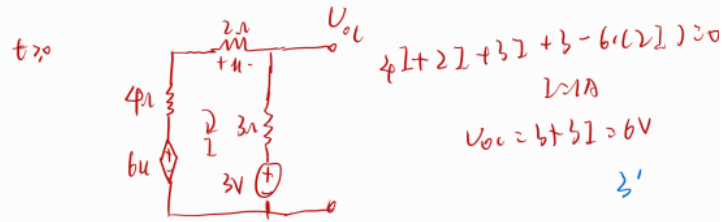
$$t = 0: i_{L(0^+)} = i_{L(0^-)} = 5 \text{ A}$$



$$R_{eq} = \frac{V_{OC}}{i_L(\infty)} = 7\Omega \quad \tau = \frac{L}{R} = \frac{4}{7} \text{ s}$$
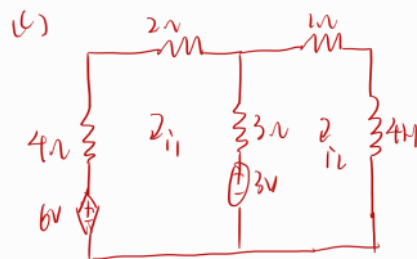
$$\phi) V_L(t) = L \frac{di_L}{dt} = -7e^{-\frac{7}{4}t} \text{ V}$$



$$-6 \times 2i_1 + 4i_1 + 2i_1 + 3(i_1 - i_L) + 3 = 0$$

$$i_1 = 1 - i_L$$

$$i_1 = \frac{1}{7} - \frac{2}{7}e^{-\frac{7}{4}t}$$

$$V_L(t) = i_L R = \frac{2}{7} - \frac{58}{7}e^{-\frac{7}{4}t} \text{ V}$$