

## **Homework 5**


Due date: Dec. 5<sup>th</sup>, 2023

Turn in your hard-copy hand-writing homework in class

Rules:

- Work on your own. Discussion is permissible, but extremely similar submissions will be judged as plagiarism.
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.

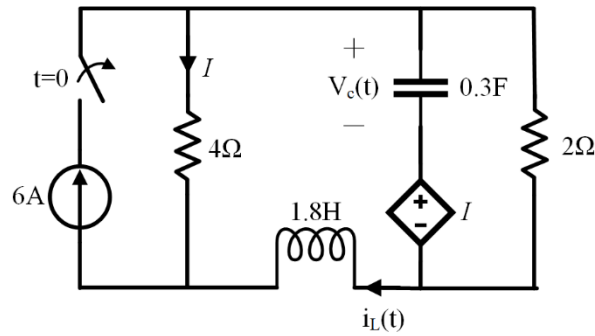1. Assume the circuit has reached steady state at  $t < 0$ , find  $v_c(0^+)$ ,  $dv_c(0^+)/dt$ ,  $i_L(0^+)$ ,  $di_L(0^+)/dt$ .



$$i_L(0^+) = i_L(0^-) = \frac{6 \times 4}{4+2} = 4 \text{ A},$$

$$V_c(0^+) = V_c(0^-) = 2 \times 4 - 2 = 6 \text{ V}$$

$$\text{when } t > 0, \quad I = -4 \text{ A}, \quad V_{2\Omega} = -4 \times 2 = -8 \text{ V}, \quad I_{2\Omega} = \frac{-8}{2} = -4 \text{ A}$$


$$i_L(0^+) = 4 - 1 = 3 \text{ A}$$

$$V_{4\Omega} + V_L(0^+) + V_{2\Omega} = 0, \quad \therefore V_L(0^+) = -18 \text{ V}$$

$$\frac{dv_c(0^+)}{dt} = \frac{i_L(0^+)}{C} = 10$$

$$\frac{di_L(0^+)}{dt} = \frac{V_L(0^+)}{L} = -10$$

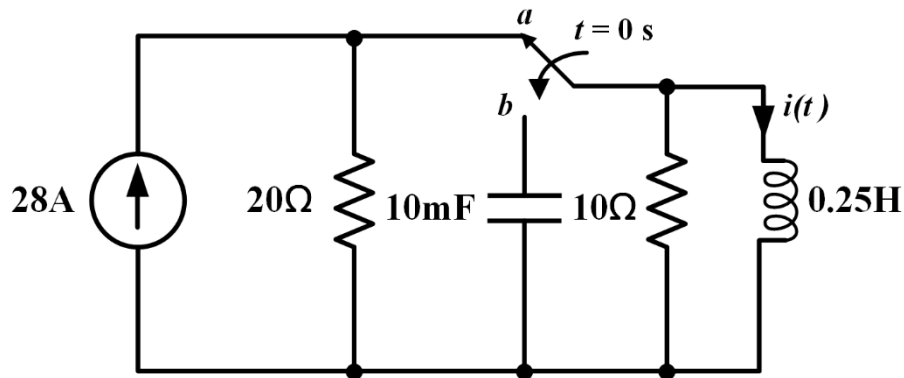2. When  $t < 0$ , no energy is stored in the capacitor, the switch has been placed at node **a** for a long time. The switch moves from node **a** to node **b** at  $t = 0$  immediately. Determine  $i(t)$  for  $t \geq 0$ .



2.

$t < 0 : i(t) = 28 \text{ A} \quad V_C(t) = 0 \text{ V}$

$t > 0 : i(t) = i(t) = 28 \text{ A} \quad V_C(t) > V_C(0) > 0 \quad \text{4'}$

10mF

$5^r + 10 + 400 = 0 \quad d = \frac{1}{20} = 5 \quad \omega_0 = \frac{1}{\sqrt{LC}} = 20$

$\therefore d < \omega_0$

$\omega_d = \sqrt{\omega_0^2 - d^2} = 19.36$


$i(t) = e^{-5t} (B_1 \cos(19.36t) + B_2 \sin(19.36t)) \quad \text{6'}$

when  $t = 0^+ \quad i(0) = 28 \text{ A} = B_1$

$\frac{di(t)}{dt} = \frac{V_C}{L} = 0 = -5B_1 + 19.36B_2 = 0 \Rightarrow \begin{cases} B_1 = 28 \\ B_2 = 7.13 \end{cases} \quad \text{5'}$

$\therefore i(t) = e^{-5t} (28 \cos(19.36t) + 7.13 \sin(19.36t)) \text{ A.}$

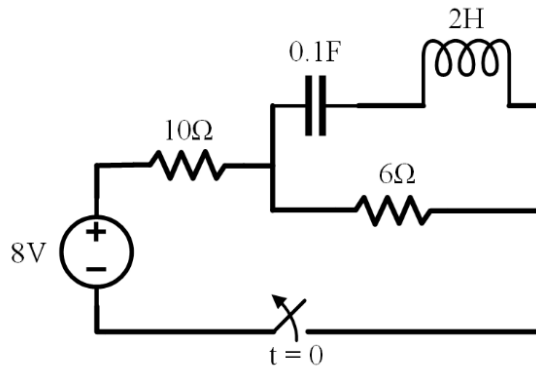3. Assume the circuit has reached steady state at  $t < 0$ , calculate the current of a 6ohm resistor for  $t > 0.6$ .



3.

$$\begin{cases} i = C \frac{dV_C}{dt} \\ V_L = L \frac{di}{dt} \end{cases} \Rightarrow 6i + V_L + V_C = 0$$

 $t < 0$ 

$$i(0^-) = 0A$$

$$V_C(0^-) = 3V$$

$$t > 0, i(0^+) = i(0^-) = 0A$$

$$V_C(0^+) = V_C(0^-) = 3V$$

$$V_C(0^+) + V_L(0^+) = 0$$

$$\therefore V_L(0^+) = -3V$$

$$i = C \frac{d(-V_L)}{dt} + C \frac{d(-6i)}{dt} = -C \frac{dV_L}{dt} - 6C \frac{di}{dt}$$

$$LC \frac{d^2 i}{dt^2} + 6C \frac{di}{dt} + i = 0$$

$$\frac{d^2 i}{dt^2} + 3 \frac{di}{dt} + 5i = 0$$

$$\therefore i = e^{-1.5t} (A_1 \cos 1.66t + A_2 \sin 1.66t)$$

$$\frac{V_L}{L} = \frac{di}{dt} = -1.5 e^{-1.5t} (A_1 \cos 1.66t + A_2 \sin 1.66t) + e^{-1.5t} (-1.66 A_1 \sin 1.66t + 1.66 A_2 \cos 1.66t)$$

代入边界条件:


$$\begin{cases} A_1 = 0 \\ 1.66 A_2 = -3/2 \end{cases}$$

$$\therefore A_2 = -0.9$$

$$i = -0.9 e^{-1.5t} \sin 1.66t, t > 0$$

$$i = -0.9 e^{-1.5(t-0.6)} \sin 1.66t, t > 0.6$$

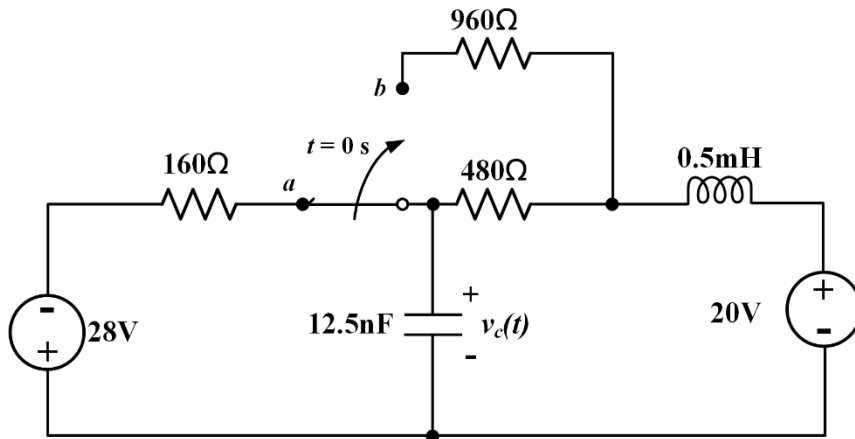4. For the following circuit, the switch has been placed at node **a** for a long time. At  $t = 0$  s, the switch is switched from **a** to **b** immediately. Please find the voltage on the capacitor  $v_c(t)$  for  $t \geq 0$  s.



4.  $t < 0$  :  $V_c(0^-) = 20 - 20 + 28 \times \frac{480}{160 + 480} = -16V$   $I_L(0^-) = \frac{20 + 28}{160 + 480} = \frac{2}{40} A$  4'

$t > 0$  :  $960\Omega \parallel 480\Omega = 320\Omega$

$\alpha = \frac{R}{L} = 3.2 \times 10^5$   $\omega_0 = \frac{1}{\sqrt{LC}} = 2 \times 10^5$   
 $\alpha < \omega_0$


$s_{1,2} = -\alpha \pm j\sqrt{\omega_0^2 - \alpha^2} = -3.2 \times 10^5 \pm j2.4 \times 10^5$  6'

$V_c(t) = 20 + (B_1 \cos 2.4 \times 10^5 t + B_2 \sin 2.4 \times 10^5 t) e^{-3.2 \times 10^5 t}$

$\begin{cases} V_c(0) = -16 = 20 + B_1 \\ \frac{dV_c}{dt} \big|_{t=0} = 6 \times 10^6 = 2.4 \times 10^5 B_2 - 3.2 \times 10^5 B_1 \end{cases} \Rightarrow \begin{cases} B_1 = -36 \\ B_2 = -23 \end{cases}$


$\therefore V_c(t) = 20 + (-36 \cos 2.4 \times 10^5 t - 23 \sin 2.4 \times 10^5 t) e^{-3.2 \times 10^5 t}$  5'

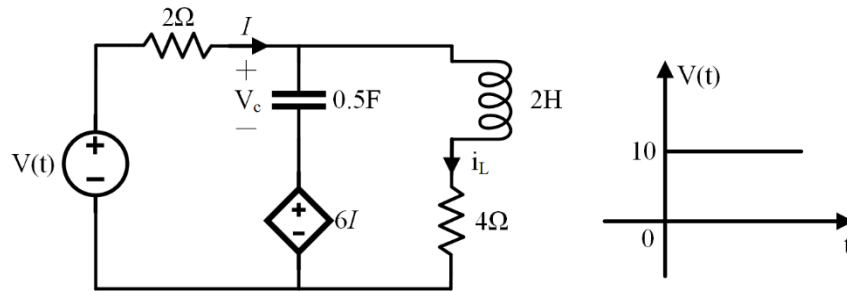5. Assume  $V_c(0^+) = 4V$ ,  $i_L(0^+) = 0A$ . find  $V_c(t)$  and  $i_L(t)$ .




$$\begin{aligned}
 5. \quad & \begin{cases} i_L = I - C \frac{dV_c}{dt} \\ V_c + 6I = 4i_L + L \frac{di_L}{dt} \Rightarrow \\ 2I + V_c + 6I = 10 \end{cases} \quad 3 \\
 & V_c(0^+) = 4 \\
 & i_L(0^+) = 0 \quad 2 \\
 & i_L(0^+) = \frac{3}{4} \\
 & L \frac{d^2 V_c}{dt^2} + (4L + \frac{L}{8}) \frac{dV_c}{dt} + \frac{3}{4} V_c + \frac{5}{2} = 0 \\
 & \frac{d^2 V_c}{dt^2} + 2.25 \frac{dV_c}{dt} + \frac{3}{4} V_c = -\frac{5}{2} \quad 2 \\
 & V_c = C_1 e^{-0.41t} + C_2 e^{-1.84t} - \frac{10}{3} \quad 2 \\
 & i_L = (-0.41 C_1 e^{-0.41t} - 1.84 C_2 e^{-1.84t}) \cdot \frac{1}{2} \quad 2 \\
 & \text{代入边界条件:} \\
 & \begin{cases} C_1 + C_2 - \frac{10}{3} = 4 \\ -0.41 C_1 - 1.84 C_2 = \frac{3}{2} \end{cases} \Rightarrow \begin{cases} C_1 = 10.48 \\ C_2 = -3.15 \end{cases} \quad 2 \\
 & i_L(t) = \frac{10 - V_c}{8} - C \frac{dV_c}{dt} \\
 & = 0.74 e^{-0.41t} - 2.5 e^{-1.84t} + 1.67 \quad 2
 \end{aligned}$$

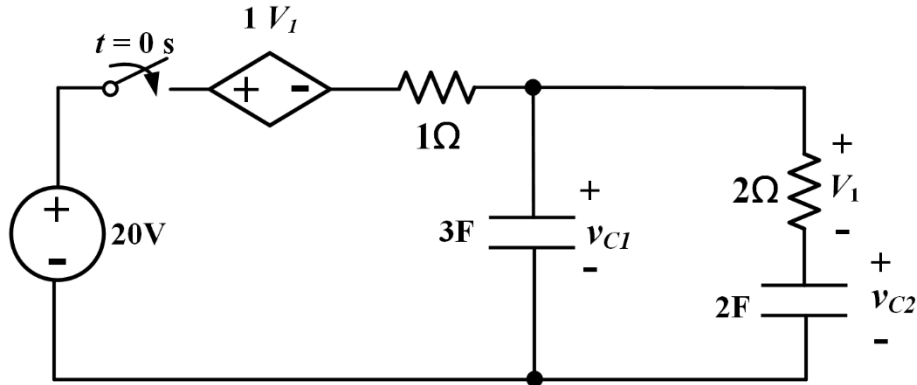6. For the following circuit, the switch closes at  $t = 0$ s immediately. Please find the voltage on the capacitors  $v_{C1}(t)$  and  $v_{C2}(t)$  for  $t > 0$ s, respectively. Note that the switch has been open for a long time before  $t = 0$ s.



$b. \quad t < 0: v_{C1}(0^-) = v_{C2}(0^-) = 0 \quad 1'$   
 $t > 0: V_{C1} = v_{C1} - V_1 = v_{C1} - 2x2 \frac{dv_{C1}}{dt} \Rightarrow v_{C1} = v_{C1} + 4 \frac{dv_{C1}}{dt}$   
 $\Rightarrow \frac{dv_{C1}}{dt} = \frac{dv_{C1}}{dt} + 4 \frac{d^2 v_{C1}}{dt^2} \quad 3'$   
 $\bar{I}_1 = 3 \frac{dv_{C1}}{dt} + 2 \frac{dv_{C1}}{dt} = 12 \frac{dv_{C1}}{dt} + 5 \frac{dv_{C1}}{dt}$   
 $20 = V_1 + \bar{I}_1 + v_{C1}$   
 $\Rightarrow 12 \frac{dv_{C1}}{dt} + 13 \frac{dv_{C1}}{dt} + v_{C1} = 20$   
 $\frac{dv_{C1}}{dt} + \frac{13}{12} \frac{dv_{C1}}{dt} + v_{C1} = \frac{5}{5} \quad 5'$   
 $\alpha = \frac{13}{24} \quad \omega_0 = \sqrt{\frac{1}{12}} \quad \therefore \alpha > \omega_0 \quad s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -\frac{1}{12}$   
 $v_{C1}(t) = A_1 e^{-\frac{1}{12}t} + A_2 e^{-t} + 20 \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -1 \quad 4'$   
 $\begin{cases} v_{C1}(0) = 0 = A_1 + A_2 + 20 \\ \frac{dv_{C1}}{dt} = 0 = -\frac{1}{12}A_1 - A_2 \end{cases} \Rightarrow \begin{cases} A_1 = -21.81 \\ A_2 = 1.81 \end{cases} \quad 2'$   
 $v_{C1}(t) = 20 - 21.81 e^{-\frac{1}{12}t} + 1.81 e^{-t} \quad 4'$   
 $v_{C1} = 4v_{C1} + v_{C1} = 20 - 12.67 e^{-\frac{1}{12}t} - 5.43 e^{-t} \quad 4'$

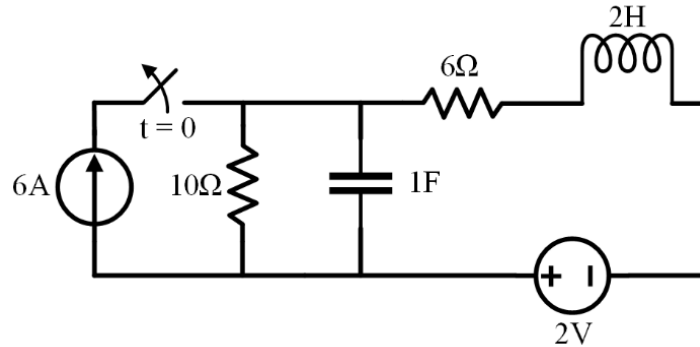7. Assume the circuit has reached steady state at  $t < 0$ , calculate the current of a 6ohm resistor for  $t > 0$  for  $t > 0$ .



7.  $\begin{cases} V_c = (i_L - C \frac{dV_c}{dt}) \times 10 \\ 2 + V_L + 6i_L + V_c = 0 \\ \frac{dV_L}{dt} + 6 \frac{di_L}{dt} + \frac{dV_c}{dt} = 0 \\ V_L = L \frac{di_L}{dt} \end{cases}$

$\Rightarrow \frac{1}{10}(-2 - V_L - 6i_L) = i_L + C \frac{dV_L}{dt} + 6C \frac{di_L}{dt}$

$10CL \frac{d^2 i_L}{dt^2} + (60L + L) \frac{di_L}{dt} + 16i_L + 2 = 0$

$20 \frac{d^2 i_L}{dt^2} + 62 \frac{di_L}{dt} + 16i_L = -2$

$i_L = C_1 e^{-0.28t} + C_2 e^{-2.82t} - \frac{1}{8}$

$V_L = L \frac{di_L}{dt} = -0.56C_1 e^{-0.28t} - 5.64C_2 e^{-2.82t}$

$i_L(0^-) = -\frac{6 \times 10}{10+6} - \frac{2}{10+6} = -3.875 A$

$V_c(0^-) = -\frac{2 \times 10}{10+6} + 6 \times (10/16) = 21.25 V$

$\therefore V_c(0^+) = V_c(0^-), i_L(0^+) = i_L(0^-)$

$V_L(0^+) = 2 + V_c(0^+) + 6i_L(0^+) = 0$

代入边界条件:


$\begin{cases} C_1 + C_2 - \frac{1}{8} = -3.875 \\ -0.56C_1 - 5.64C_2 = 0 \end{cases}$

$\therefore \begin{cases} C_1 = -4.16 \\ C_2 = 0.41 \end{cases}$

$i_R = i_L = -4.16 e^{-0.28t} + 0.41 e^{-2.82t} - \frac{1}{8}$



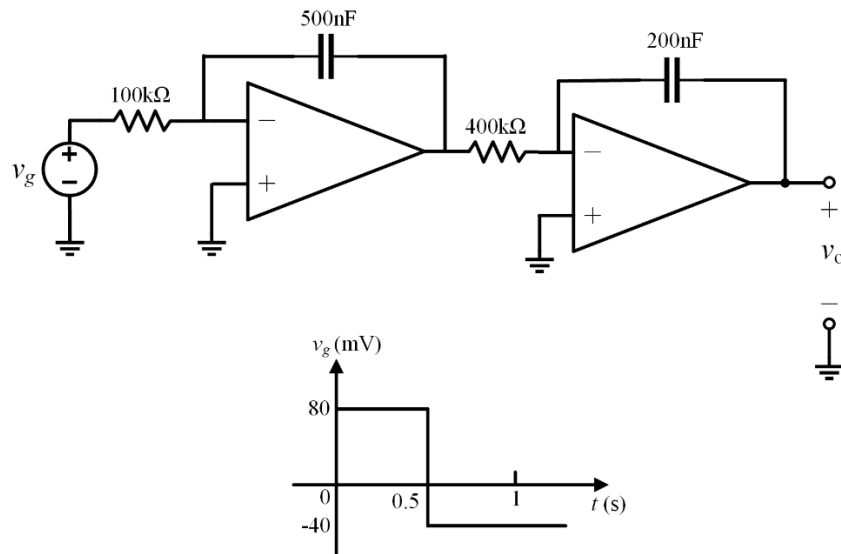8. The waveform of voltage source  $v_g$  as shown and the initial value of the capacitance are 0, find  $v_o(t)$  for  $t \geq 0$ .



$$\begin{cases} \frac{V_g}{100\text{k}} = C_1 \frac{dV_{c1}}{dt} & 2 \\ -\frac{V_{c1}}{400\text{k}} = C_2 \frac{dV_{c2}}{dt} & 2 \end{cases} \Rightarrow V_o = -V_{c2} \quad 2$$

$$V_{c1} = \frac{V_g}{100\text{k} \times C_1} t + A_1 = 20 V_g t + A_1 \quad 2$$

$$V_{c2} = -125 V_g t^2 - 12.5 A_1 t + A_2 \quad 2$$

$$\therefore V_{c1}(0^+) = V_{c2}(0^+) = 0 \quad 1$$

$$\therefore A_1 = A_2 = 0, \therefore V_o = -V_{c2} = 10t^2, 0 \leq t < 0.5 \quad 2$$

$$\therefore V_{c1}(0.5^-) = 0.8\text{V}, V_{c2}(0.5^-) = -2.5\text{V} \quad 2$$

$$V_{c1}(0.5^+) = V_{c1}(0.5^-), V_{c2}(0.5^+) = V_{c2}(0.5^-) \quad 1$$

$$\text{Let } \begin{cases} -0.4 + A_1 = 0.8 \\ 1.25 - 6.25 A_1 + A_2 = -2.5 \end{cases} \Rightarrow \begin{cases} A_1 = 1.2 \\ A_2 = 3.75 \end{cases} \quad 2$$

$$\therefore V_o = -5t^2 + 15t - 3.75, t > 0.5 \quad 2$$