

## Homework 3


Due time: 10 p.m. Nov. 2<sup>nd</sup>, 2024

Turn in your hard-copy hand-writing homework at the entrance of  
Room 3-324 SIST #3 Building.

Rules:


- Work on your own. Discussion is permissible, but extremely similar submissions will be judged as plagiarism.
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in **English only**. No Chinese submission will be accepted.
- All final answers must be rounded to **two decimal places**, and include the **appropriate units**.

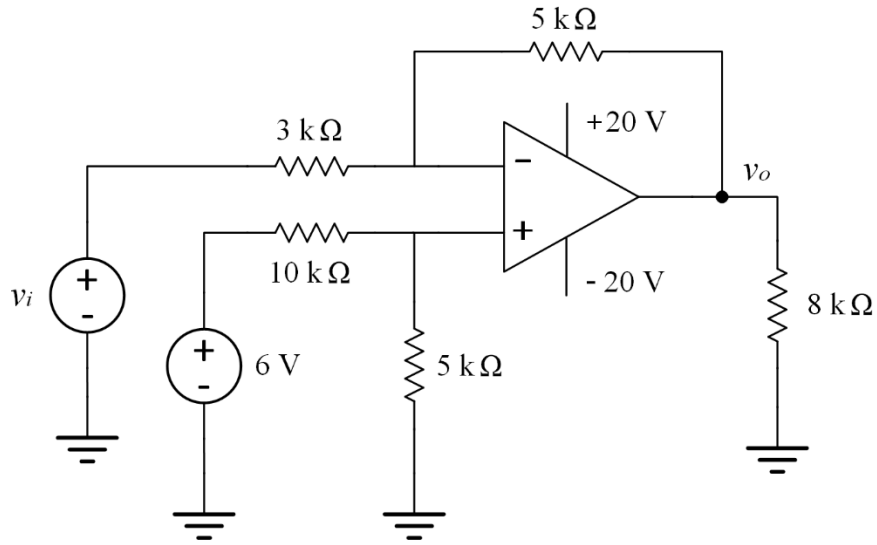1. Consider the circuit given below, the ideal operational amplifier is working in the linear region. Find the relationship between  $v_o$  and  $v_i$ .




2. The op amp in the circuit below is working in the linear region, calculate:


- a.  $V_a$
- b.  $V_o$
- c.  $I_o$

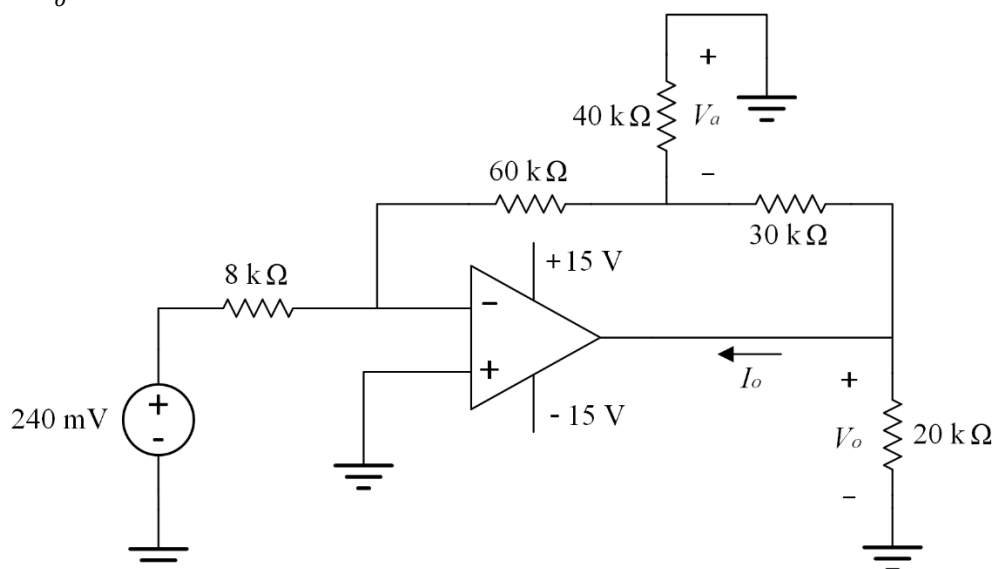

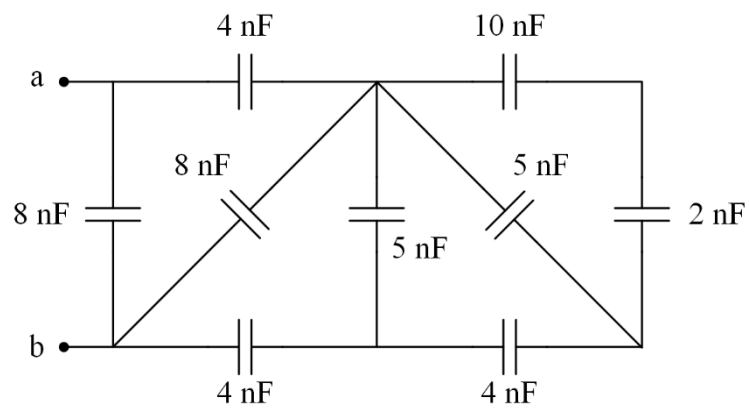
3. Find the equivalent capacitance  $C_{ab}$  of the circuit.



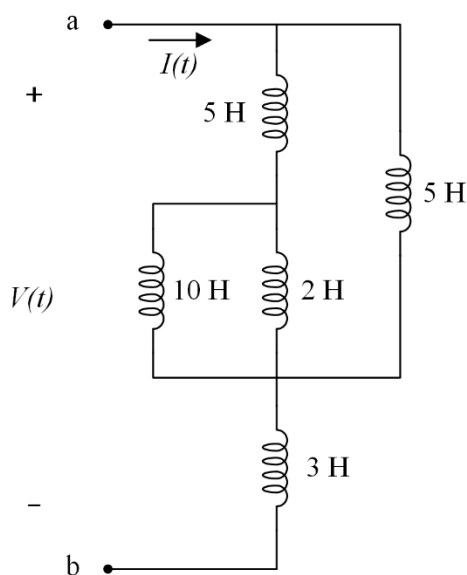
4. For the circuit below,  $I(0^-) = 0$  A, and let  $V(t) = 8e^{-3t}$  V. The initial energy stored in all inductors is 0 J.
- Calculate the equivalent inductance  $L_{ab}$ .
  - Find  $I(t)$  for  $t > 0$ .



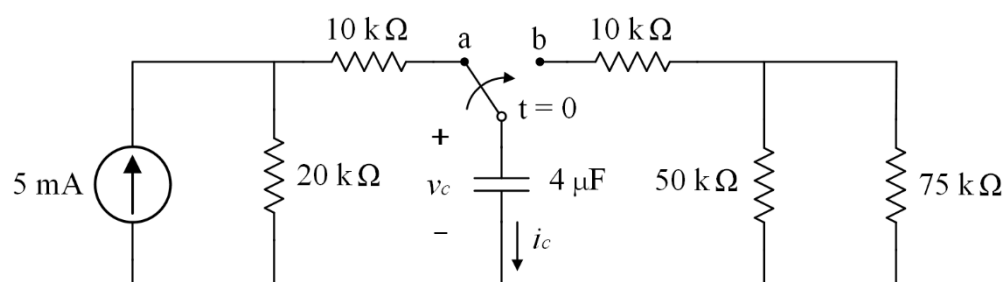
5. In the circuit shown, the switch is instantly moved from node **a** to **b** at  $t = 0$ . Assume the circuit was in steady state for  $t < 0$ . Determine the expressions for  $v_c(t)$  and  $i_c(t)$  for  $t > 0$ .



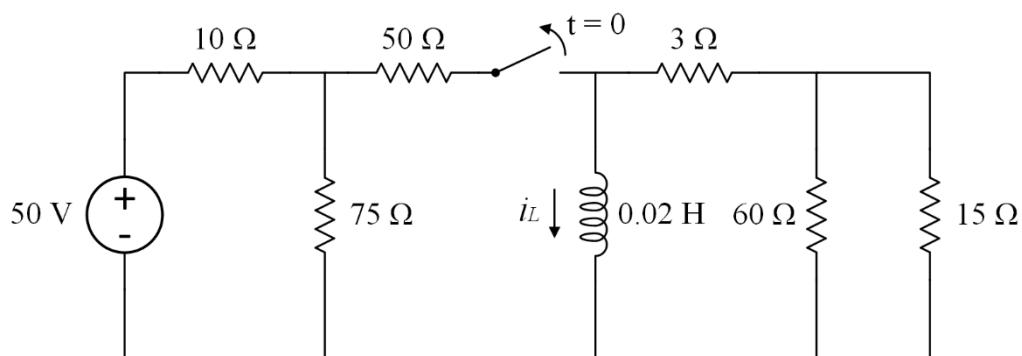6. For the circuit below, the switch has been closed for a long time. At  $t = 0$ , the switch is opened.
- Determine  $i_L(t)$  for  $t > 0$ .
  - Calculate the initial energy stored in the inductor. Then, find the percentage of this initial energy that is eventually dissipated in the  $15\ \Omega$  resistor.



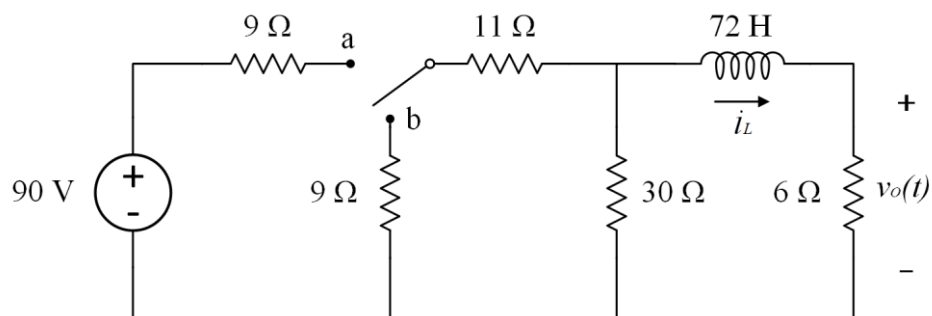7. For the circuit below, the switch has remained in position **a** for a long time. At  $t = 0$ , the switch is instantly moved to position **b**. After 12 s, the switch is moved back to position **a** instantaneously.
- Find  $v_o(t)$  for  $t > 0$ .
  - Sketch the curve of  $i_L(t)$  as a function of  $t$ .





8. For the op amp in the given circuit operating in the linear region, find  $v_o(t)$  for  $t > 0$ .

