

## **Homework 2**

Due date: Oct. 31<sup>st</sup>, 2023

Turn in your hard-copy hand-writing homework in class


Rules:

- Work on your own. Discussion is permissible, but extremely similar submissions will be judged as plagiarism.
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.

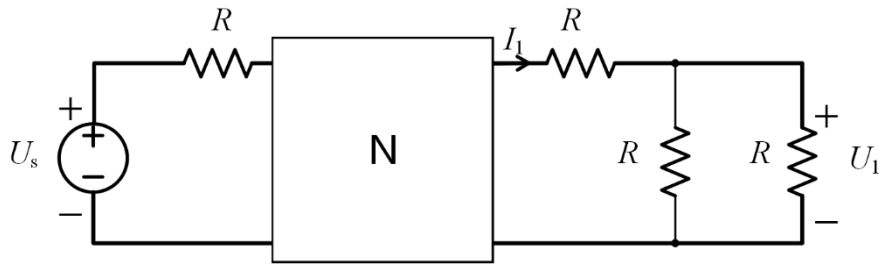1. N is a linear resistive network with sources inside.

When  $U_s = 6V$ ,  $I_1 = 1A$ ,  $U_1 = 2V$ ; When  $U_s = 10V$ ,  $I_1 = 2A$ .

Use linear property to find  $I_1$  and  $U_1$  if  $U_s = 12V$ . **10'**




$$I_1, U_1 = 0.5RI_1, \text{ from } I_1 = 1A, U_1 = 2V \Rightarrow R = 4\Omega$$

$$\therefore I_1 = k + k_1 U_s, \quad \begin{cases} 1 = k + 6k_1 \\ 2 = k + 10k_1 \end{cases} \Rightarrow \begin{cases} k = 0.5 \\ k_1 = 0.125 \end{cases} \quad 5'$$

$$\text{When } U_s = 12V, \quad I_1 = 0.5 + 0.125 \times 12 = 2.5A \quad U_1 = 0.5RI_1 = 5V \quad 5'$$

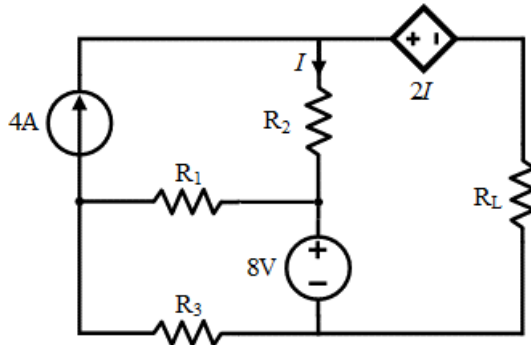2.  $R_1=R_2=2\Omega$ ,  $R_3=1\Omega$ ,  $R_L=2\Omega$

- Calculate the current of  $R_L$  when an independent current source acts alone. 5'
- Calculate the current of  $R_L$  when an independent voltage source acts alone. 5'
- Calculate the current on  $R_L$  using the superposition theorem. 5'



a.

$$\frac{IR_2 - 2I}{R_L} + I = 4 \quad 2$$

$$I = 4A$$

$$\underline{\underline{v_{RL} = 0A}} \quad 2$$

b.

$$-I \cdot (R_2 + R_L) + 2I = 8 \quad 2$$


$$I = -4A$$

$$v_{RL} = -I = 4A \quad 2$$

c.  $I_{RL} = 0 + 4 = 4A \quad 3$

3. (a) Apply superposition to find  $U_0$  in the circuit below when  $R_L=250\Omega$ .5'

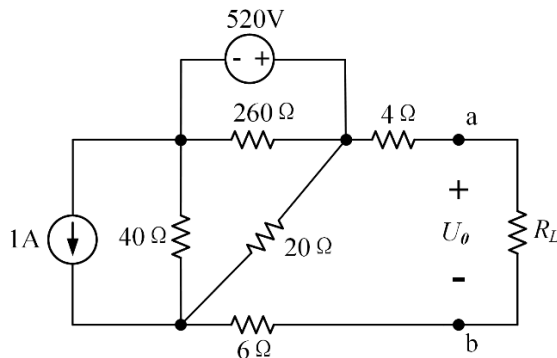(b) Find the Thevenin equivalent circuit for the left hand side circuit of node a and node b.10'




3. a. when the independent current source acts:



$$I_{ab} = \frac{\frac{40}{3}}{40 + \frac{40}{3} + 6 + 250} \times 1 = \frac{V}{41} \text{ A}$$

$$U_{ab} = -I_{ab} \cdot 150 = -\frac{500}{41} \text{ V} = -12.19 \text{ V}$$

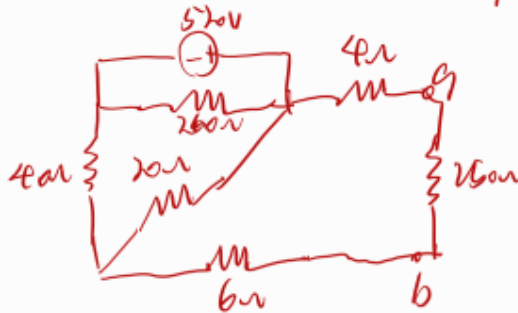when the independent voltage source acts:



$$I = \frac{520}{40 + \frac{20 \times 260}{20 + 260}} \times \frac{20}{20 + 260} = \frac{26}{41} \text{ A}$$


$$U'_{ab} = \frac{26}{41} \times 150 = \frac{6500}{41} \text{ V} = 158.54 \text{ V}$$

$$\therefore U_0 = U_{ab} + U'_{ab} = \frac{6000}{41} \text{ V} = 146.34 \text{ V}$$

b.  $R_{eq} = 4 + 6 + \frac{40 \times 20}{40 + 20} = \frac{70}{3} \Omega = 23.3 \Omega$


$$-16 \times 2 + 40(I+1) + 20I = 0 \quad I = 8 \text{ A} \quad U_{oc} = 20 \times 8 = 160 \text{ V}$$

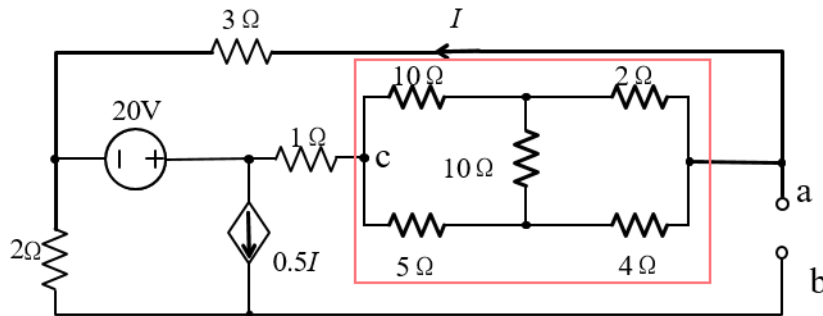4. a. Find the equivalent resistance  $R_{ac}$  5'  
 b. Find the Thevenin equivalent circuit between node a and b 15'



4. a.  $\Delta \rightarrow Y$   $R_{eq} = 2 + [(1+2) || (1+2)] = 14/3 = 5\Omega$  5'

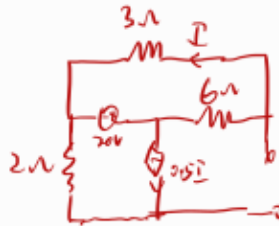b  $I = \frac{20V}{6+5\Omega} = \frac{20}{11} A$   $V_{oc} = I \times 3\Omega - 0.5I \times 2\Omega = 3 \times \frac{20}{11} - 0.5 \times \frac{20}{11} \times 2 = \frac{60}{11} - \frac{20}{11} = \frac{40}{11} V$  5'



$3\Omega \times I = 6\Omega \times I_v$   $I_v = 0.5I$

$I_3 = I + I_v - 0.5I = I$  5'





$R_{eq} = \frac{V_1}{I_1} = \frac{6V \times I_v + 2\Omega \times I_3}{I + I_v} = \frac{3I + 2I}{1.5I} = \frac{5I}{1.5I} = \frac{10}{3}\Omega$  5'



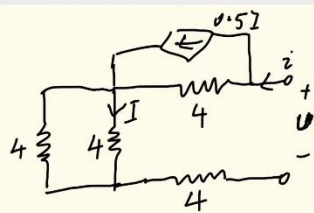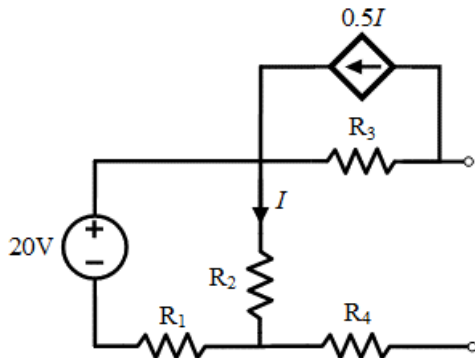5.  $R_1 = R_2 = R_3 = R_4 = 4\Omega$ .


Find the Norton equivalent circuit of the two port network. 15'




$$\begin{cases} (v - 0.5I)R_3 + IR_2 + vR_4 = U \\ \frac{IR_2}{R_1} + I = v \end{cases} \quad 4$$

$$\therefore v = 2I$$
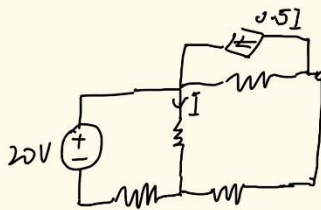
$$R_{eq} = \frac{U}{I} = 9\Omega \quad 2$$






$\Rightarrow$

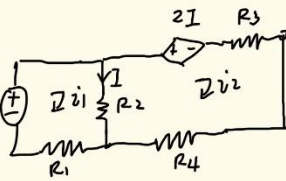

$$\begin{cases} (R_1 + R_2)v_1 - v_2 R_2 = 20 \\ (R_2 + R_3 + R_4)v_2 + 2I \\ -v_1 R_2 = 0 \end{cases} \quad 4$$

$$\begin{aligned} I &= v_1 - v_2 \\ \therefore v_1 &= \frac{25}{9} \quad v_2 = \frac{5}{9} \end{aligned} \quad \begin{matrix} 2 \\ 2 \end{matrix}$$

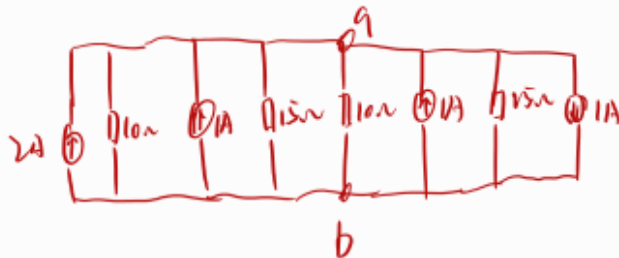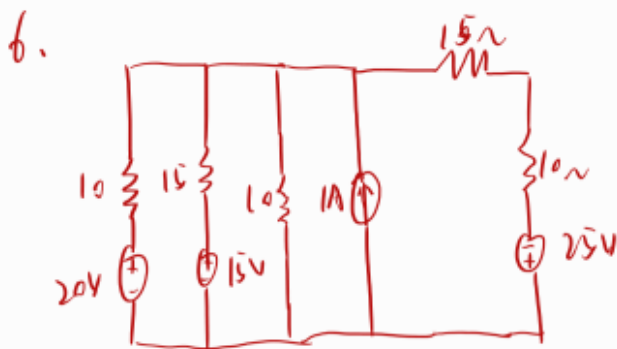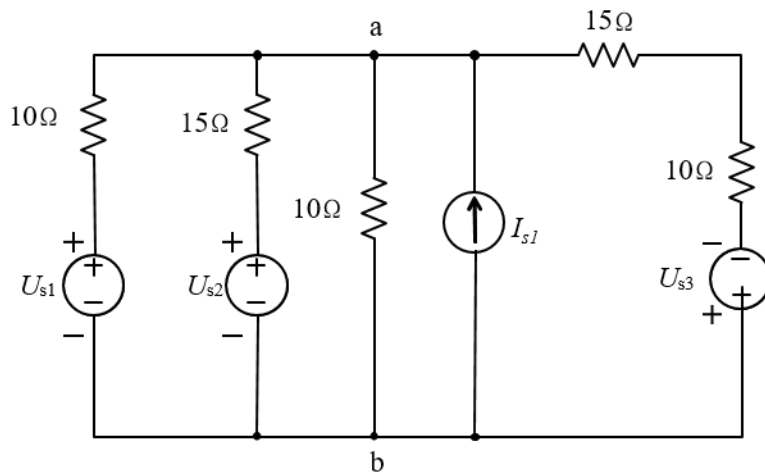6.  $U_{s1} = 20V$ ,  $U_{s2} = 15V$ ,  $U_{s3} = 25V$ ,  $I_{s1} = 1A$ , using source transfer to calculate  $U_{ab}$  10'



$$I_{total} = 2 + 1 + 1 - 1 = 3A \quad 5'$$




$$I_{ab} = 3 \times \frac{\frac{150}{31}}{10 + \frac{150}{31}} = \frac{45}{46} = 0.98A$$

$$U_{ab} = 10 \times \frac{45}{46} = 9.78V \quad 5'$$

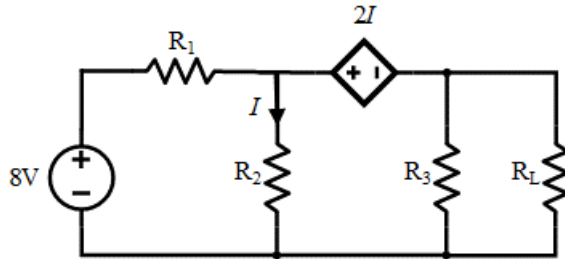7.  $R_1 = 2\Omega$ ,  $R_2 = 6\Omega$ ,  $R_3 = 1\Omega$


- Determine the value of  $R_L$  when maximum power could be transferred to it, and calculate the maximum power  $P_{RL}$ . **10'**
- Calculate the ratio of  $P_{RL}$  to the output power of the independent voltage source. **5'**




equivalent circuit


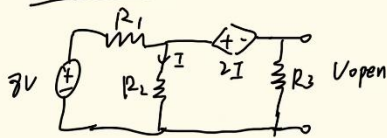
$$R_{eq} = R_3 // \left( \frac{R_2 - 2}{R_2/R_1 + 1} \right) = 0.5\Omega \quad 2$$



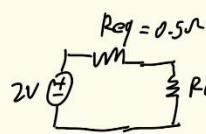
$$\begin{cases} V_{open} + 2I = IR_2 \\ 8 = IR_2 + R_1 \left( \frac{V_{open}}{R_3} + I \right) \end{cases} \quad 3$$



$$\therefore V_{open} = 2V$$

$$\text{when } R_L = 0.5\Omega, P_{av} = \frac{2^2}{4 \cdot 0.5} = 2W \quad 2$$

来自华为笔记

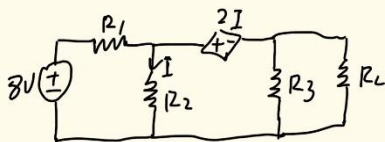

$$\left[ \frac{(IR_2 - 2I)}{R_3 // R_L} + I \right] R_1 + IR_2 = 8V \quad 3$$

$$\therefore I = \frac{13}{4} A$$

$$P_{out} = 8 \cdot \frac{13}{4} = 26W$$

$$\eta = \frac{P_{RL}}{P_{out}} = \frac{1}{13} \quad 2$$