

Homework 1


Due date: Oct. 8th, 2024 at 10 p.m.

Turn in your hard-copy hand-writing homework at the entrance of the School of Information, Room 3-324.

Rules:

- Work on your own. Discussion is permissible, but extremely similar submissions will be judged as plagiarism.
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.

1. Find v_o using Kirchhoff's laws.

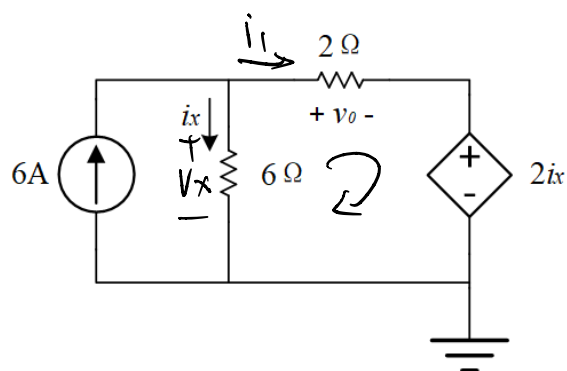

$$-v_x + v_o + 2i_x = 0 \quad \text{KVL.}$$



$$v_x = 6i_x \quad \text{Ohm.}$$

$$i_1 = \frac{v_o}{2} \quad \text{Ohm.}$$

$$6 = i_x + i_1 \quad \text{KCL.}$$

$$\Rightarrow v_o = 8 \text{ V.}$$

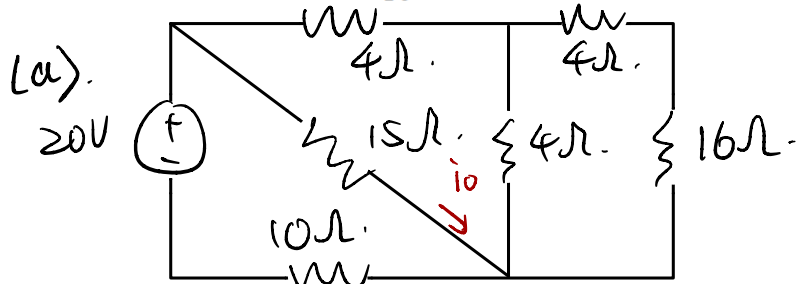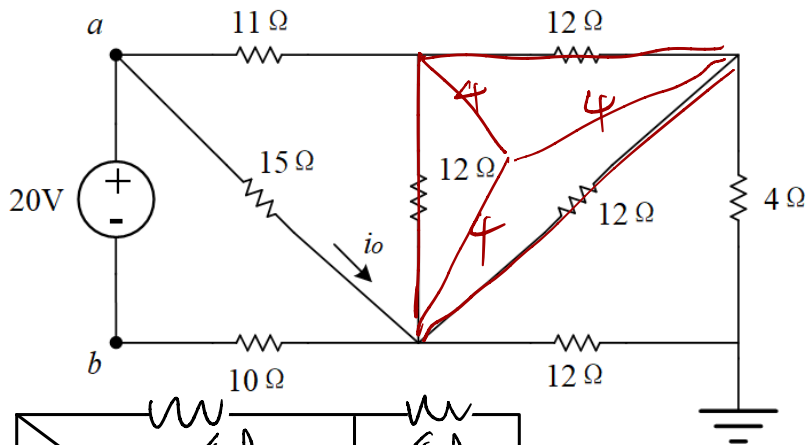2. (a) Use Delta-to-Y or Y-to-Delta transformation to find the i_o in the circuit.
 (b) Calculate the equivalent resistance R_{ab} .



$$R_Y = \frac{R_0}{3} = 4\Omega.$$



$$4 + 16 = 20\Omega.$$

$$11 + 4 = 15\Omega.$$

$$20 \parallel 4 = \frac{10}{3}\Omega.$$


$$15 + \frac{10}{3} = \frac{55}{3}\Omega.$$
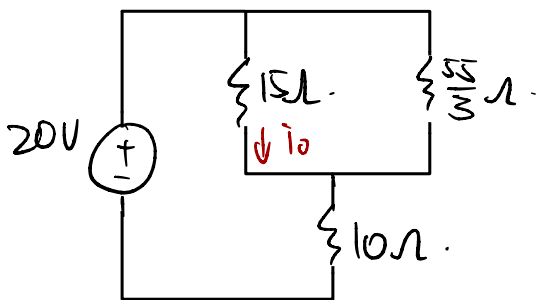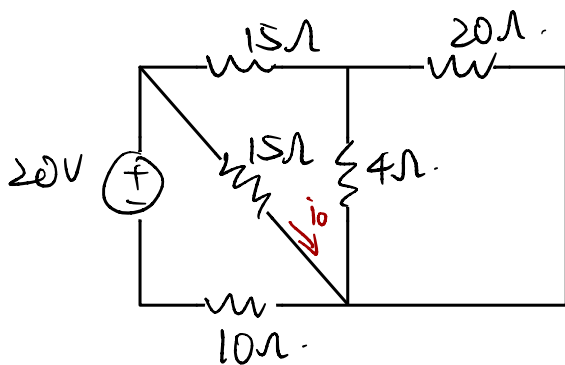
$$\frac{55}{3} \parallel 15 = 8.25\Omega.$$




$$V_o = \frac{8.25}{8.25 + 10} \times 20 = 9.04\text{ V}.$$
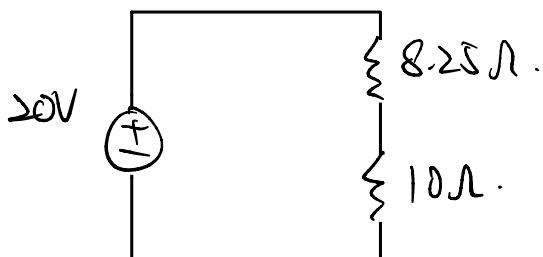
$$i_o = \frac{V_o}{R_o} = \frac{9.04}{15} = 0.60\text{ A}.$$



(b). $R_{ab} = 10 + 8.25$
 $= 18.25\Omega.$

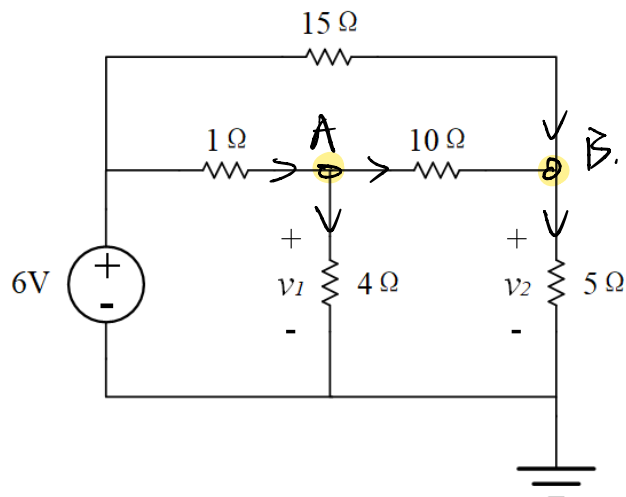
3. Use nodal analysis method to find v_1 and v_2 in the circuit.



$$\text{KCL: } \begin{cases} \frac{6 - v_1}{1} = \frac{v_1}{4} + \frac{v_1 - v_2}{10} & \text{Node A} \\ \frac{6 - v_2}{15} + \frac{v_1 - v_2}{10} = \frac{v_2}{5} & \text{Node B} \end{cases}$$

$$\Rightarrow \begin{cases} v_1 = 4.62 \text{ V} \\ v_2 = 2.35 \text{ V} \end{cases}$$

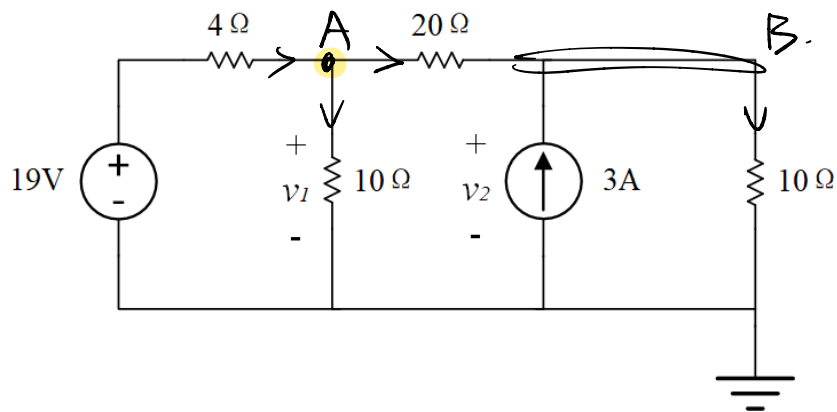
4. Use nodal analysis method to find v_1 and v_2 in the circuit.



$$\text{KCL: } \begin{cases} \frac{19 - v_1}{4} = \frac{v_1}{10} + \frac{v_1 - v_2}{20} & \text{Node A} \\ \frac{v_1 - v_2}{20} + 3 = \frac{v_2}{10} & \text{Node B} \end{cases}$$

$$\Rightarrow \begin{cases} v_1 = 15 \text{ V} \\ v_2 = 25 \text{ V} \end{cases}$$

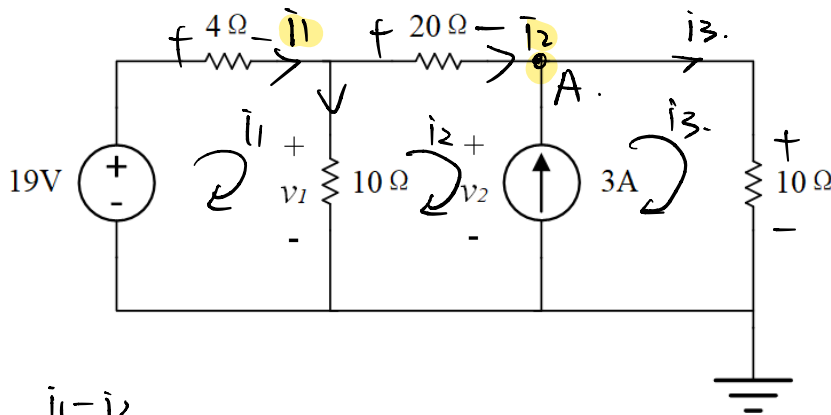5. For the circuit below, use mesh current analysis method to find v_1 and v_2 in the circuit.



$$v_1 = \frac{i_1 - i_2}{10}$$

Assume the voltage on the current source is V_2 .

$$\text{KVL: } -19 + 4 \cdot i_1 + 10(i_1 - i_2) = 0 \quad \text{Mesh 1.}$$

$$-10(i_1 - i_2) + 20 \cdot i_2 + V_2 = 0 \quad \text{Mesh 2.}$$

$$-V_2 + 10 \cdot i_3 = 0 \quad \text{Mesh 3.}$$

$$\text{KCL: } i_2 + 3 = i_3 \quad \text{Node A.}$$


$$\Rightarrow \begin{cases} v_1 = 15\text{V.} \\ v_2 = 25\text{V.} \end{cases}$$

6. For the circuit below:

(a) Use the nodal method to find V_o in the circuit.

(b) Draw or copy the circuit on your own answer sheet, and use the mesh method to find V_o in the circuit.

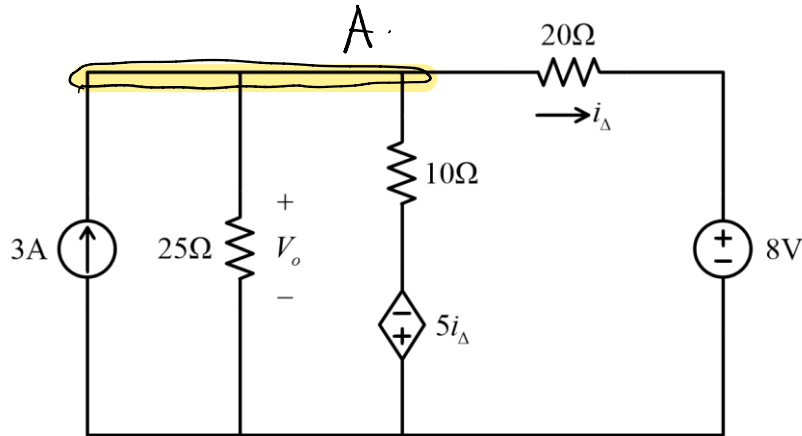(c) Find the power absorbed by the dependent source.




$$(a). \begin{cases} \text{KCL: } -3 + \frac{V_o}{25} + \frac{V_o + 5i_\Delta}{10} + \frac{V_o - 8}{20} = 0, & \text{Node A.} \\ \text{Ohm: } i_\Delta = \frac{V_o - 8}{20}. \end{cases}$$

$$\Rightarrow V_o = 16.74 \text{ V}$$

$$(b). \begin{cases} \text{KVL: } -25(3 - i_1) + 10(i_1 - i_2) - 5i_\Delta = 0, & \text{Mesh 1.} \\ 5i_\Delta - 10(i_1 - i_2) + 20i_2 + 8 = 0, & \text{Mesh 2.} \\ i_\Delta = i_2. \\ V_o = 25(3 - i_1). \end{cases}$$


$$\Rightarrow V_o = 16.74 \text{ V.}$$

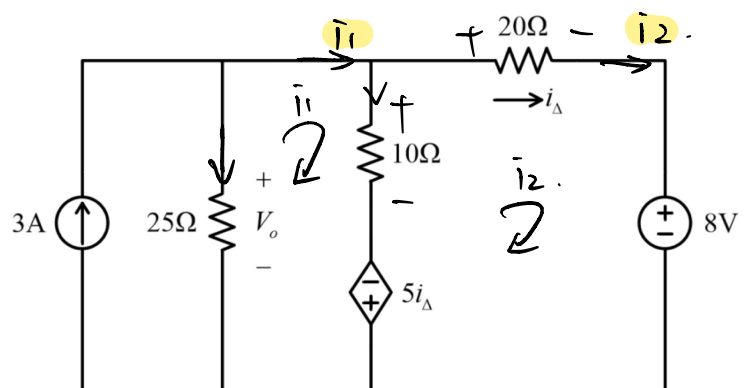

$$(c). \quad \bar{i}_{ds} = \frac{V_o + 5i_o}{10} \Rightarrow \bar{i}_x = 0.44 \text{ A.}$$

$$\Rightarrow \bar{p}_{ds} = (-5i_o) \cdot \bar{i}_{ds} = -4.14 \text{ W.}$$

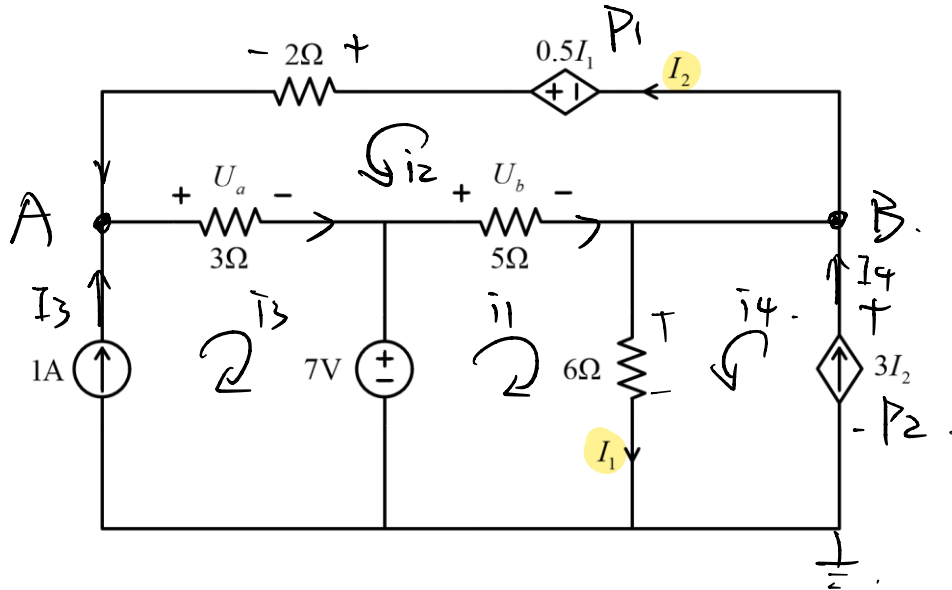7. Use mesh analysis to find U_a , U_b and the power delivered by the two controlled sources.



Assume $I_3 = 1A$, $I_4 = 3I_2$.

$$\text{KVL: } -0.5I_1 + 2 \cdot I_2 + 3 \cdot (I_2 + I_3) + 5 \cdot (I_1 + I_2 - I_4) = 0. \text{ Mesh 1.}$$

$$5 \cdot (I_1 + I_2 - I_4) + 6I_1 - 7 = 0. \text{ Mesh 2.}$$

$$\text{Also. } U_a = 3 \cdot (I_2 + I_3).$$

$$U_b = 5 \cdot (I_1 + I_2 - I_4).$$

$$\Rightarrow \begin{cases} I_1 = 6.5A \\ I_2 = 6.45A \\ U_a = 22.35V \\ U_b = -32V \end{cases} \Rightarrow \begin{cases} P_1 = 0.5I_1 \times I_2 = 20.96W \\ P_2 = 3I_2 \times 6I_1 = 754.65W \end{cases}$$