




# Outline

- Capacitors and inductors
- Natural response of RC/RL circuits
- Step response of RC/RL circuits
- Others
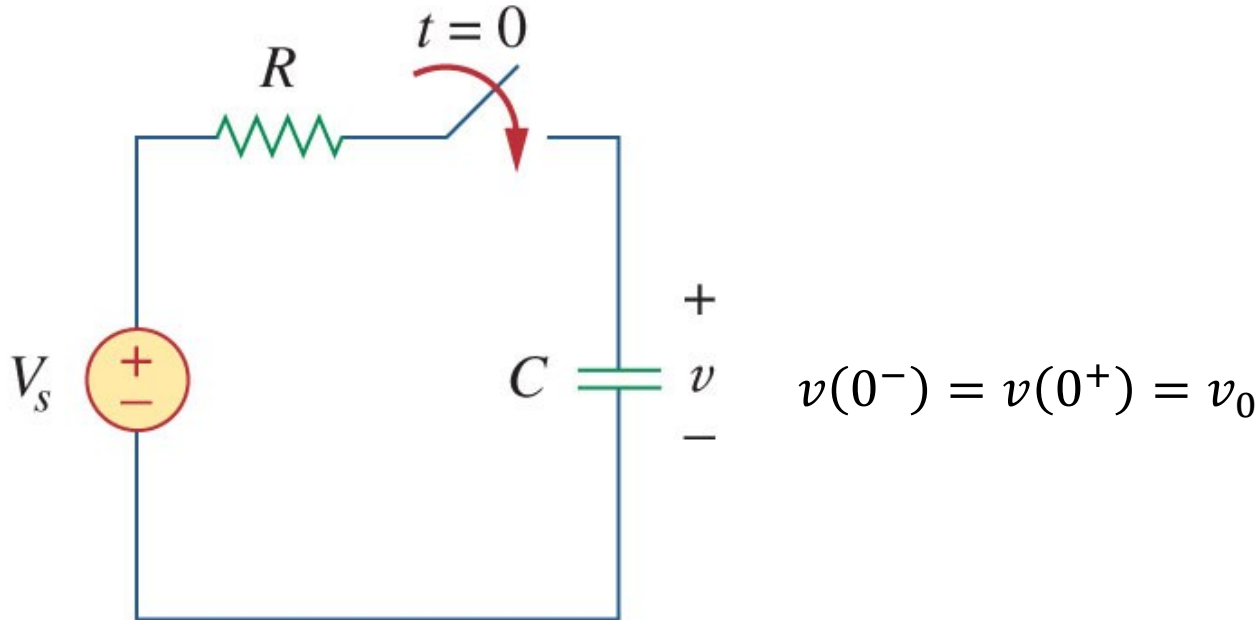
# Step Response of RC Circuit

- When a **DC source** is suddenly applied to a RC circuit, the circuit response is known as the step response.


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display


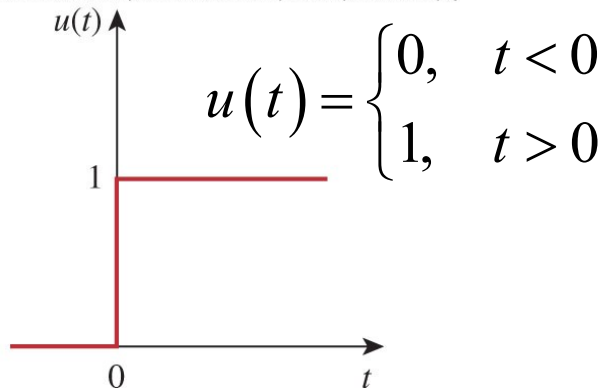
# The unit step function $u(t)$


- A step function is one that maintains a constant value before a certain time and then changes to another constant afterwards.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display




switching time may be shifted to  $t = t_0$  by
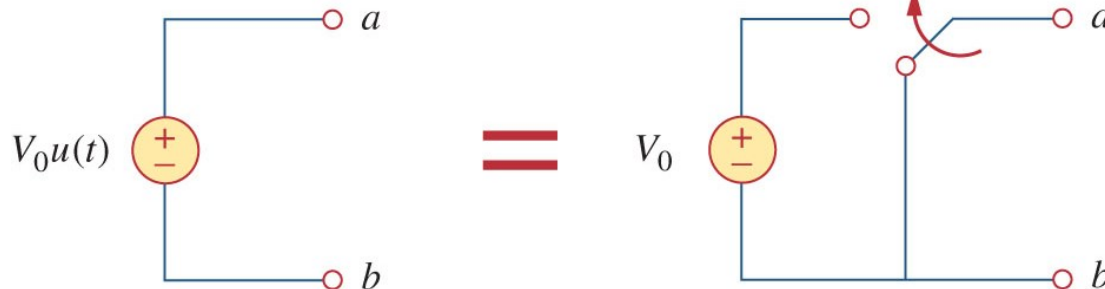
$$u(t - t_0) = \begin{cases} 0, & t < t_0 \\ 1, & t > t_0 \end{cases}$$



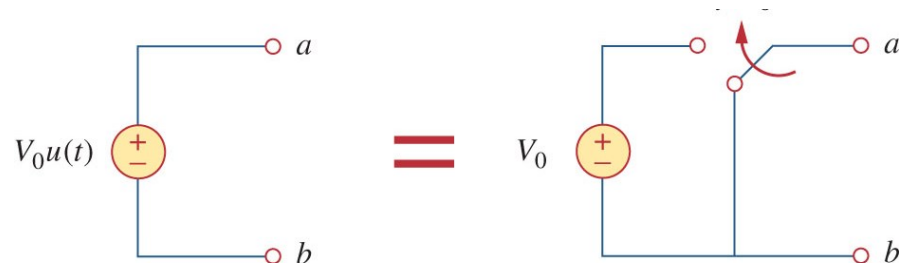
# Equivalent Circuit of Unit Step


- The unit step function has an equivalent circuit to represent when it is used **to switch on** a source.



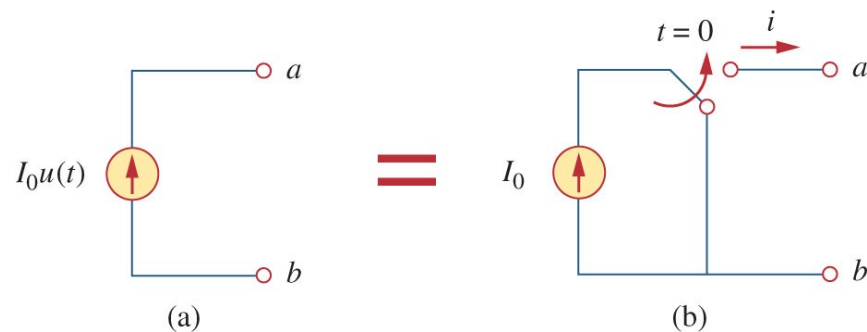Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



# Step Response of the RC Circuit

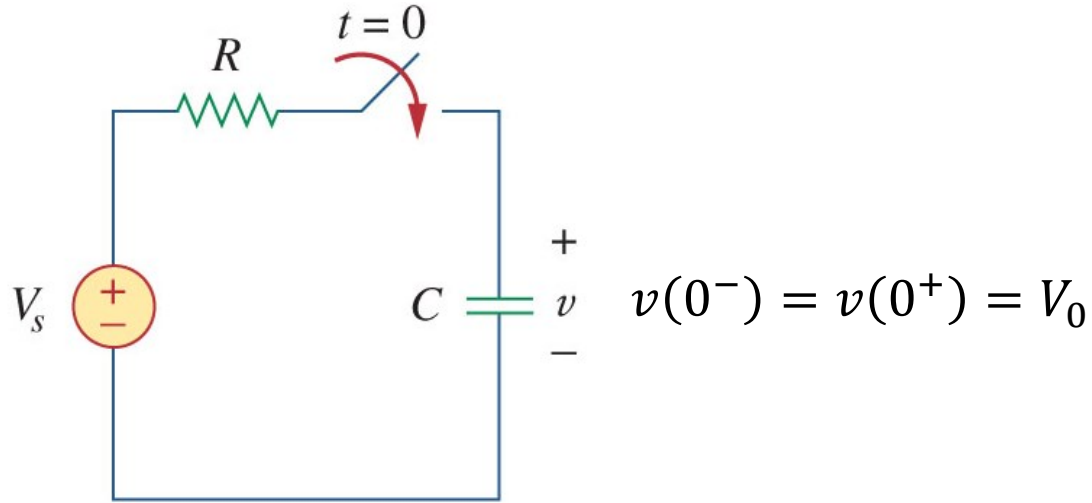





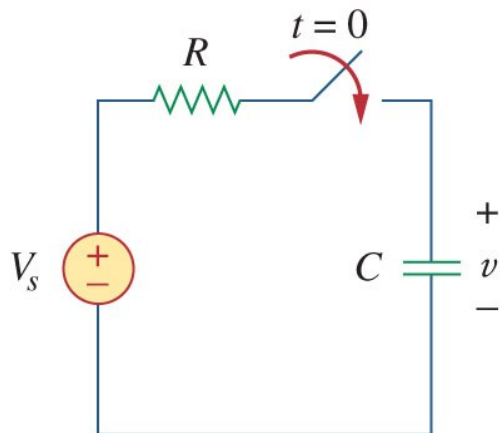
# Step Response of the RC Circuit


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



$$v(0^-) = v(0^+) = V_0$$

$$v(t) = \begin{cases} V_0, & t < 0 \\ V_s + (V_0 - V_s)e^{-t/\tau} & t > 0 \end{cases}$$

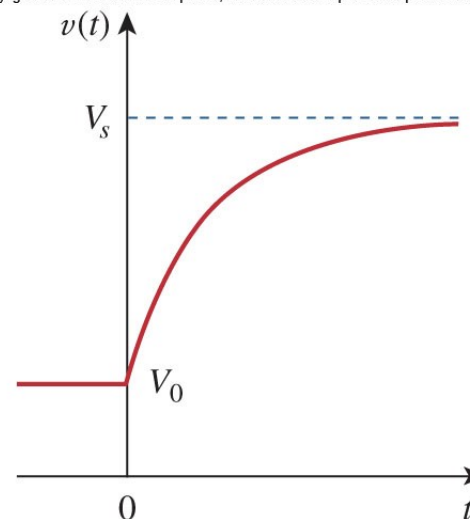Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display




- This is known as the complete response, or total response.


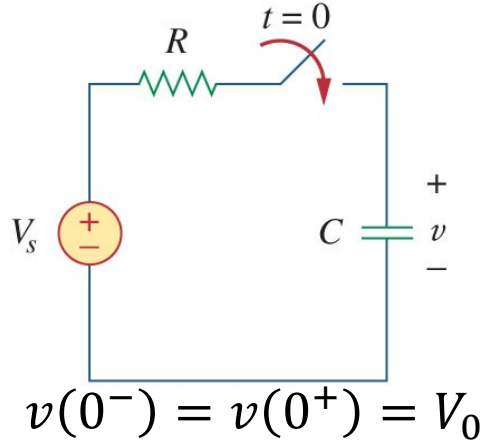
# Complete response

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display




- The complete response

$$v(t) = \begin{cases} V_0, & t < 0 \\ V_s + (V_0 - V_s)e^{-t/\tau} & t > 0 \end{cases}$$

can be written as:

$$v = v_n + v_f$$

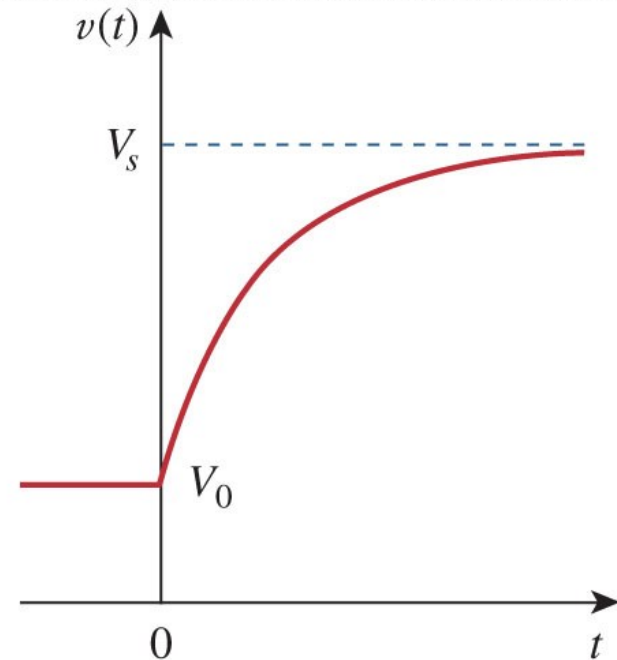Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display







$$\text{Complete response} = \underset{\text{stored energy}}{\text{natural response}} + \underset{\text{independent source}}{\text{forced response}}$$

or

$$v = v_n + v_f$$

where


$$v_n = V_o e^{-t/\tau}$$

and

$$v_f = V_s(1 - e^{-t/\tau})$$
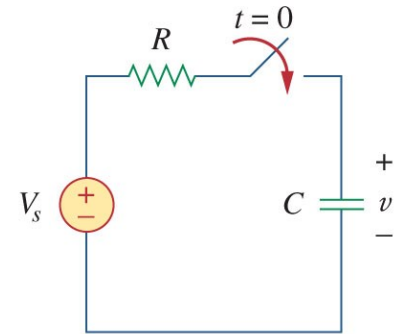
## Another Perspective

$$v(t) = \begin{cases} V_0, & t < 0 \\ V_s + (V_0 - V_s)e^{-t/\tau} & t > 0 \end{cases}$$




- Another way to look at the response is to break it up into the transient response and the steady state response:

$$v(t) = \underbrace{v(\infty)}_{\text{steady } v_{ss}} + \underbrace{[v(0) - v(\infty)]e^{-t/\tau}}_{\text{transient } v_t}$$
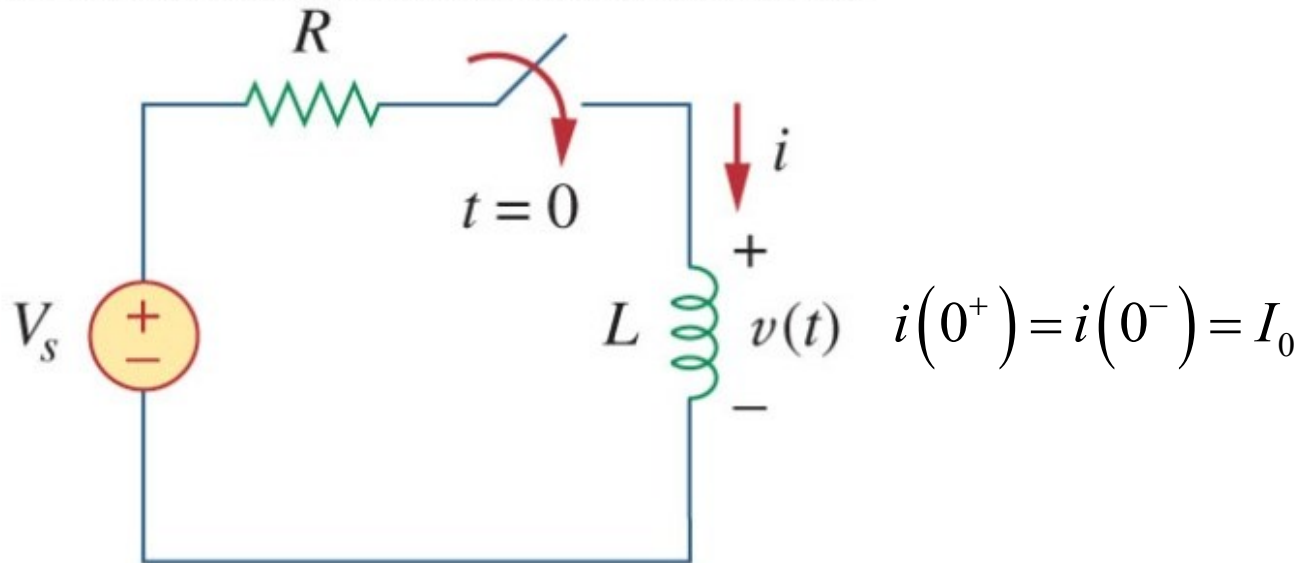
# Step Response of the RL Circuit

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display









# General Procedure of Finding RC/RL Response with D.C. sources

## 1. Identify the variable of interest

- For RL circuits, it is usually the inductor current  $i_L(t)$ .
- For RC circuits, it is usually the capacitor voltage  $v_c(t)$ .

## 2. Determine the initial value of the variable at $T_0$

- Recall that  $i_L(t)$  and  $v_c(t)$  are continuous variables:

$$i_L(T_0^+) = i_L(T_0^-) \quad \text{and} \quad v_c(T_0^+) = v_c(T_0^-)$$



## 3. Determine the final value of the variable (as $t \rightarrow \infty$ )

If needed, recall that an inductor behaves like a short circuit & that a capacitor behaves like an open circuit in steady state (e.g.,  $t \rightarrow \infty$ ).

## 4. Calculate the time constant for the circuit


- $\tau = \mathbf{CR}$  for an RC circuit where  $R$  is the Thévenin equivalent resistance “seen” by the capacitor.
- $\tau = \mathbf{L/R}$  for an RL circuit, where  $R$  is the Thévenin equivalent resistance “seen” by the inductor.

# Response Form of Basic First-Order Circuits

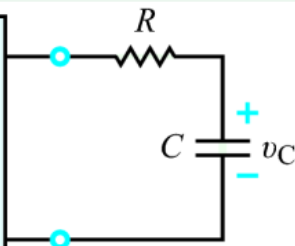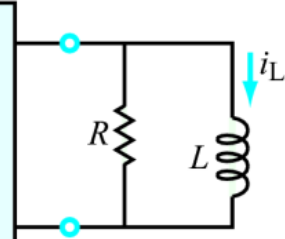Circuit	Diagram	Response
RC	<p><b>Input:</b> dc circuit with switch action @ <math>t = T_0</math></p> 	$v_C(t) = \left\{ v_C(\infty) + [v_C(T_0) - v_C(\infty)]e^{-(t-T_0)/\tau} \right\}$ $(\tau = RC)$
RL	<p><b>Input:</b> dc circuit with switch action @ <math>t = T_0</math></p> 	$i_L(t) = \left\{ i_L(\infty) + [i_L(T_0) - i_L(\infty)]e^{-(t-T_0)/\tau} \right\}$ $(\tau = L/R)$
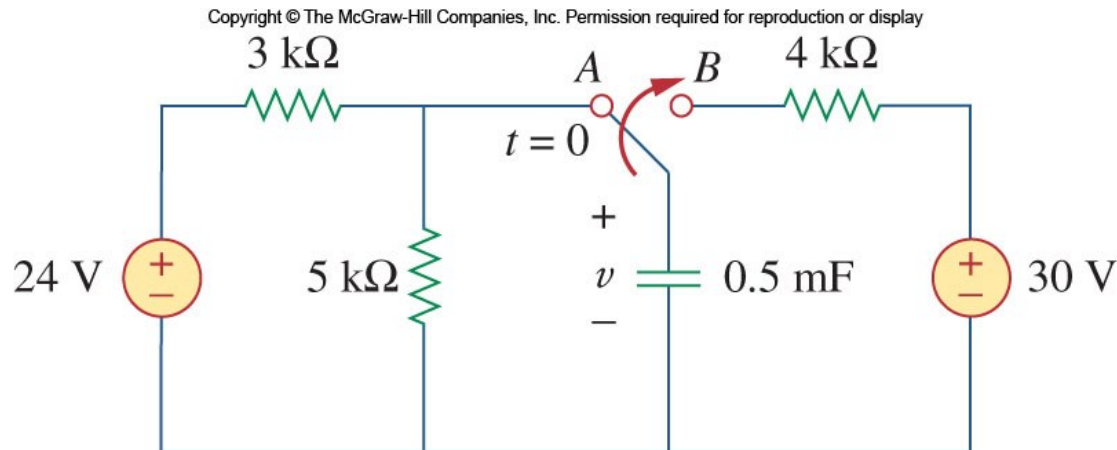
## Example

- The switch has been in position A for a long time. At  $t = 0$ , the switch moves to B. Find  $v(t)$ .





## Example

- Find  $i(t)$  in the circuit for  $t > 0$ . Assume that the switch has been closed for a long time.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display

