

Homework 8


Due date: 11:00 pm, Jan. 14th, 2023

Turn in your hard-copy hand-writing homework to Room 324 #3 SIST


Rules:

- Work on your own. Discussion is permissible, but extremely similar submissions will be judged as plagiarism.
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.

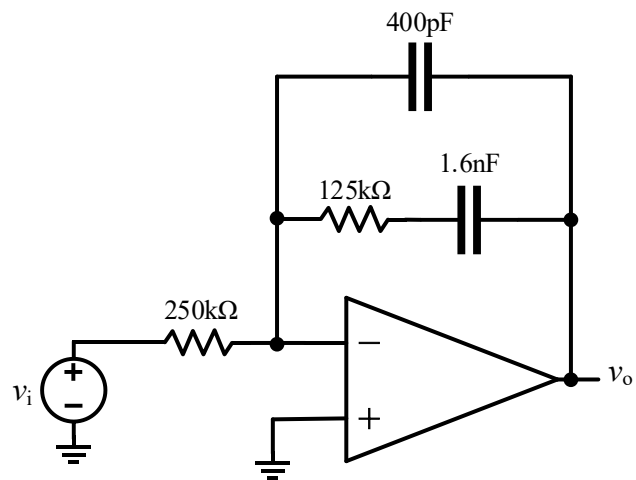
1. Please find the transfer function of v_o/v_i .



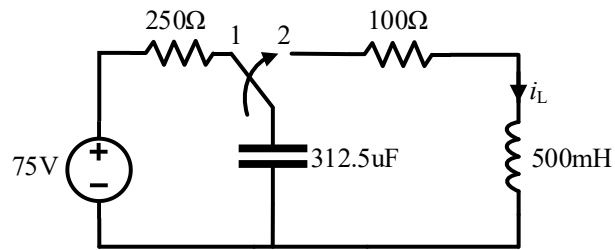
2. For the following circuit, the switch had been at node **1** for a long time before $t=0$ s. When $t=0$ s, the switch was turned to node **2** immediately. If no initial energy was stored for the inductor, please use **Laplace domain method** to find $i_L(t)$ for $t>0$ s.



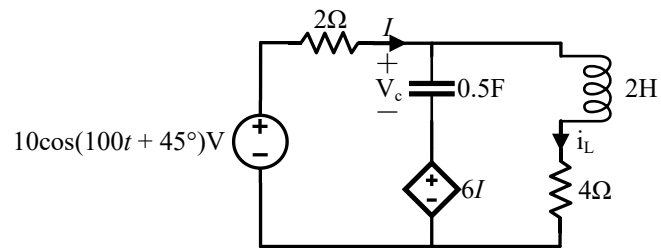3. Given no initial energy was stored for the energy storage elements, find steady-state response v_c by **Laplace domain method** and **phasor domain method**.



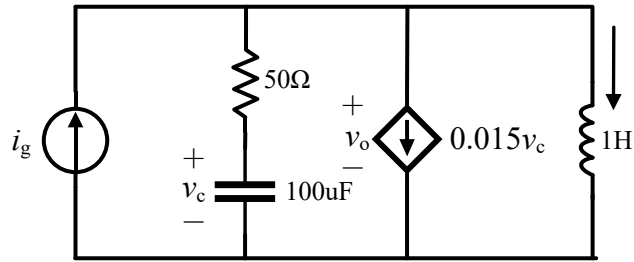
4. When $t=0$, the current through the inductor is 5mA and no initial energy is stored for the capacitor. If $i_g=20u(t)$ mA, find $v_o(t)$ for $t>0$ by **Laplace domain method**.



5. For the following circuit, $v_s(t)=10\cos(200t)$ V, and the switch closed immediately at $t=0$ s. There is no energy stored for the inductors before $t=0$ s. Please

(a) Use **phasor method** to find the **steady-state** for the voltage of $v(t)$.

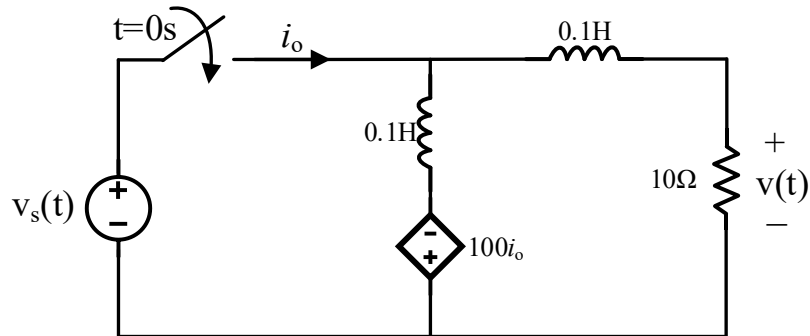(b) Use **Laplace domain method** to find **complete response** of $v(t)$ for $t>0$ and compare the results from (a).



6. For the following circuit, the switch had been at node **a** for a long time before $t=0$ s. When $t=0$ s, the switch was turned to node **b** immediately. Please use (a) **Laplace domain method** and (b) **time domain method** to find $i_L(t)$ for $t>0$ s.

