



# Lecture 14

## -- Laplace Transform in Circuit Analysis



## V-I relations of R,L,C

• R 
$$U_R(s) = RI_R(s)$$

• C 
$$V(s) = \frac{1}{sC} I(s) + \frac{V_0}{s}$$


$$I(s) = sCV(s) - CV_0$$

• L 
$$I(s) = \frac{1}{sL} V(s) + \frac{I_0}{s}$$

$$V(s) = sLI(s) - LI_0$$

# S-domain circuit models for a capacitor

## s-Domain Circuit Models


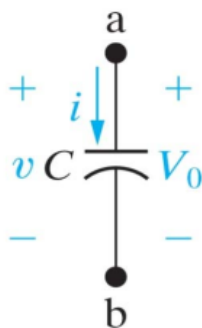


$$i(t) = C \frac{dv(t)}{dt}$$

For a capacitor  
(with initial conditions)


$$I(s) = sCV(s) - CV_0$$
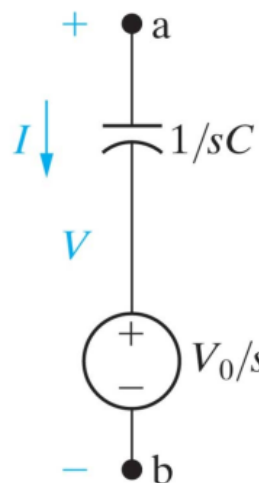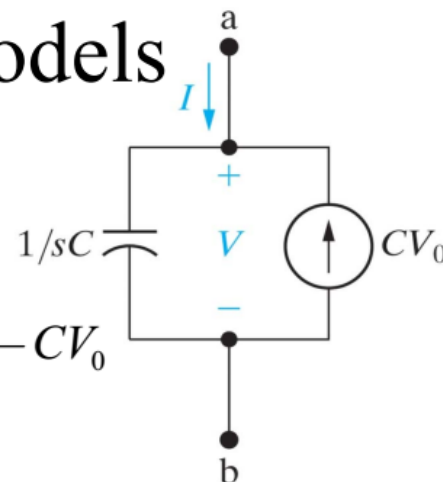
$$V(s) = \frac{1}{sC} I(s) + \frac{V_0}{s}$$




# S-domain circuit models for an inductor

## s-Domain Circuit Models

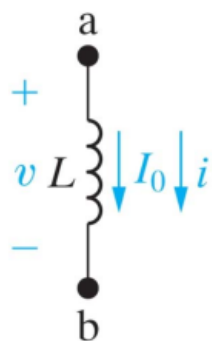


For an inductor  
(with initial conditions)
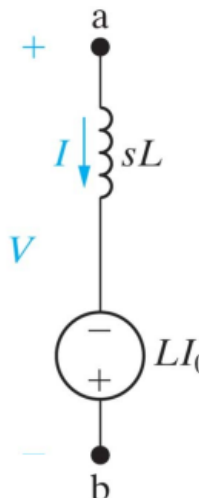
$$v(t) = L \frac{di(t)}{dt} \quad \Rightarrow \quad V(s) = sLI(s) - LI_0$$










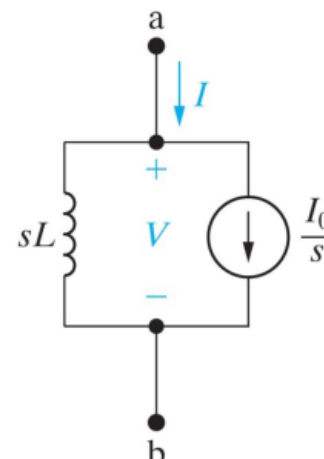
$$I(s) = \frac{1}{sL} V(s) + \frac{I_0}{s}$$





Time domain

s-domain

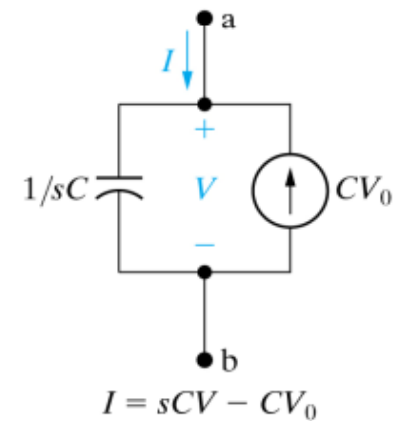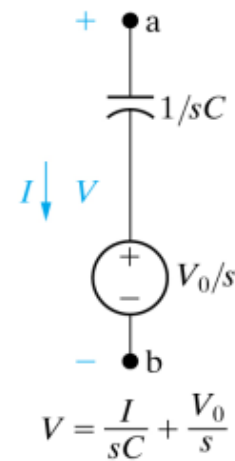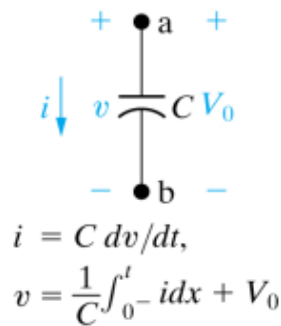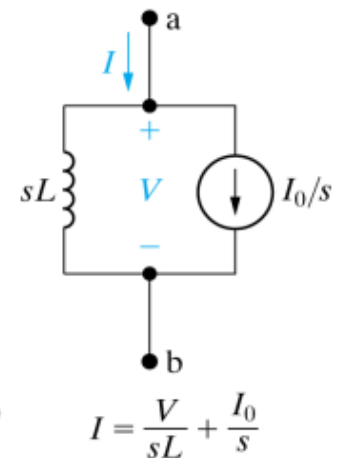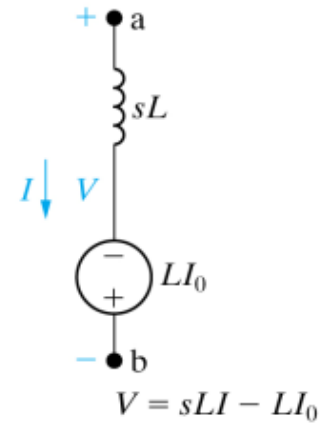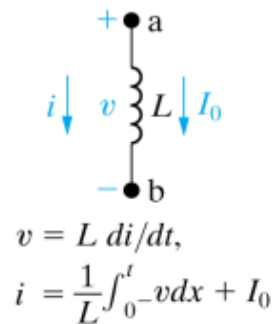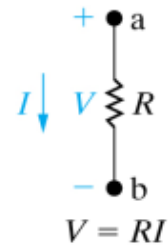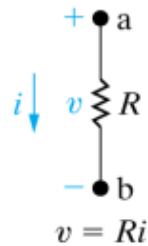



## D.C. sources and Dependent Sources

- The models for dependent sources are easy to develop, drawing from the simple fact that if the Laplace transform of  $f(t)$  is  $F(s)$ , then the Laplace transform of  $af(t)$  is  $aF(s)$  — the linearity property.

$$\mathcal{L}[av(t)] = aV(s)$$

$$\mathcal{L}[ai(t)] = aI(s)$$



# Steps in Applying the Laplace transform

- Transform the circuit from the time domain to the Laplace ( $s$ ) domain, including initial conditions.  
--The elegance of using the Laplace transform in circuit analysis lies in (1) transforming the differential equation into an *algebraic* equation; and (2) automatic inclusion of initial conditions in the transformation process, thus providing a complete (**transient and steady-state**) solution.
- Solve the circuit using nodal analysis, mesh analysis, source transformation, superposition, or any other analysis technique with which we are familiar.
- Take the inverse transform of the solution and thus obtain the solution in the time domain.



## Example 1

Assuming no initial energy storage, find  $i_1(t)$  and  $i_2(t)$  for  $t > 0$ .

