

## Homework 5

Due time: 10 p.m. Dec. 3<sup>rd</sup>, 2024

Turn in your hard-copy hand-writing homework at the entrance of Room 3-324 SIST  
#3 Building.

Rules:


- Work on your own. Discussion is permissible, but extremely similar submissions will be judged as plagiarism.
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.
- All final answers must be rounded to **two decimal places**.

1. The expression for the steady-state voltage and current in the terminals of the circuit seen in the figure are

$$v_g = 300 \cos(5000\pi t + 78^\circ) V$$

$$i_g = 6 \sin(5000\pi t + 123^\circ) A$$

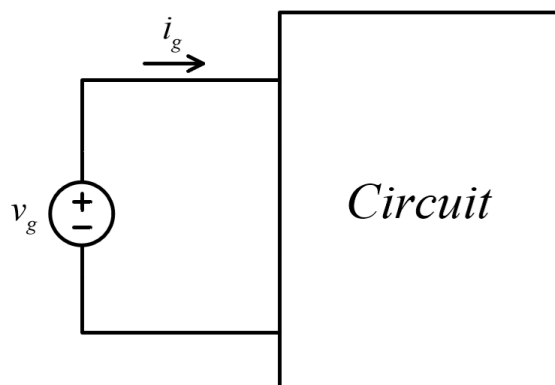- (a) Transform the expressions of  $v_g$  and  $i_g$  into **phasor** form.  
(b) What is the impedance seen by the source?



(a)

$$V_g = 300 \angle 78^\circ V$$

$$I_g = 6 \angle 33^\circ A$$


(b)

$$Z = \frac{V_g}{I_g} = \frac{300 \angle 78^\circ}{6 \angle 33^\circ} = 50 \angle 45^\circ \Omega$$

2. For the circuit shown below:

(a) Find the frequency (in radians per second) at which the impedance  $Z_{ab}$  is purely resistive.

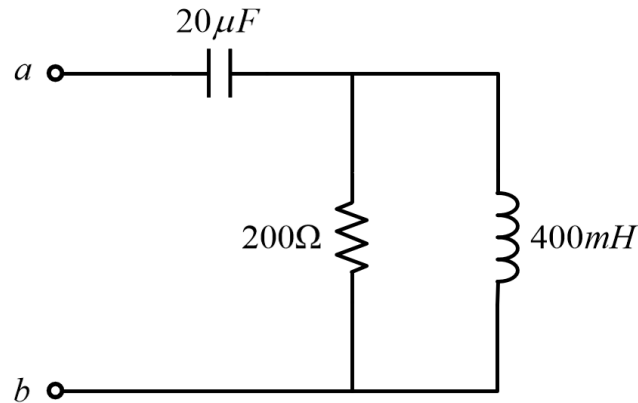(b) Find the value of  $Z_{ab}$  at the frequency of (a).



(a)

$$\begin{aligned} \frac{1}{j\omega C} + R || j\omega L &= \frac{1}{j\omega C} + \frac{j\omega RL}{j\omega L + R} \\ &= \frac{j\omega L + R - \omega^2 RLC}{j\omega C(j\omega L + R)} \\ &= \frac{(R - \omega^2 RLC + j\omega L)(-\omega^2 LC - j\omega RC)}{(-\omega^2 LC + j\omega RC)(-\omega^2 LC - j\omega RC)} \end{aligned}$$

Set the imaginary part to 0:

$$-\omega^3 L^2 C - \omega R^2 C + \omega^3 R^2 C^2 L = 0$$

$$\omega^2 = \frac{R^2}{R^2 LC - L^2} = 250000$$

$$\omega = 500 \text{ rad/s}$$


(b)

$$Z_{ab}(500) = -j100 + \frac{200 \cdot (j200)}{200 + j200} = 100 \Omega$$

3. The frequency of the sinusoidal voltage source in the circuit is adjusted until  $i_g$  is in phase with  $v_g$ .

(a) What is the value of  $\omega$  in radians per second.

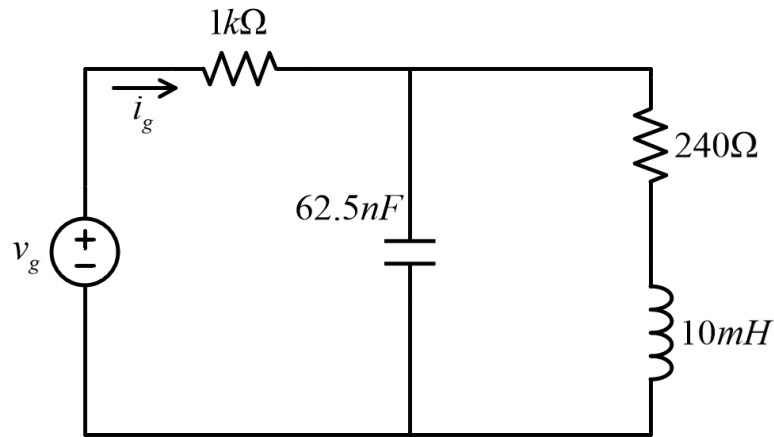(b) If  $V_g = 15\cos\omega t$  V (where  $\omega$  is the frequency found in (a)), what is the steady-state expression for  $i_g$  in **time domain**?



(a)

$$Z_{eq} = \frac{1}{j\omega C} || (R + j\omega L)$$

$$= \frac{(R + j\omega L)(1 - \omega^2 LC - j\omega RC)}{(1 + \omega^2 LC)^2 + \omega^2 R^2 C^2}$$

The voltage and current are in phase when the impedance to the left of the  $1k\Omega$  resistor is purely real. Set the imaginary part of  $Z_{eq}$  to zero:

$$-\omega R^2 C + \omega L - \omega^3 L^2 C = 0$$

$$\omega = 32000 \text{ rad/s}$$


(b)

$$Z_t = 1000 + (-j500) || (240 + j320) = 1666.67 \Omega$$

$$I_g = \frac{V_g}{Z_t} = 9 \angle 0^\circ \text{ mA}$$

$$i_g = 9 \cos(32000t) \text{ mA}$$

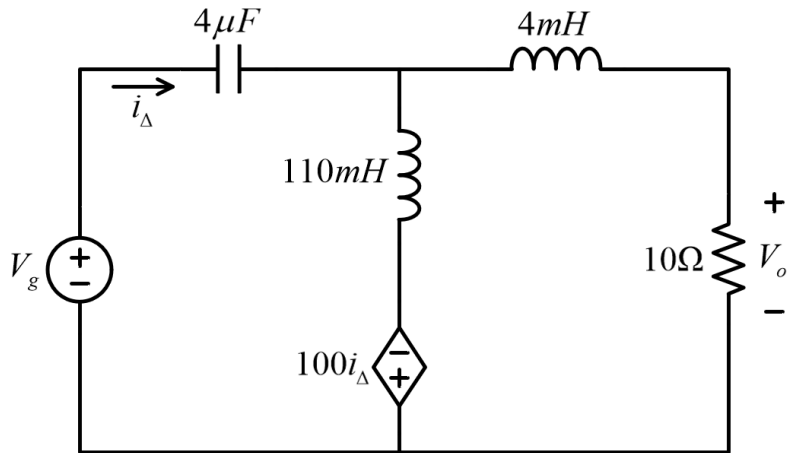4. Use the nodal or mesh method to find  $V_o$  in **phasor domain** in the circuit if  $V_g = 75\cos 5000t$  V.



$$j\omega L_1 = j5000(4 \times 10^{-3}) = j20 \, \Omega$$

$$j\omega L_2 = j5000(110 \times 10^{-3}) = j550 \, \Omega$$

$$\frac{1}{j\omega C} = \frac{-j}{(5000)(4 \times 10^{-6})} = -j50 \, \Omega$$

Mesh method:

The current in the left mesh is  $i_\Delta$ , assume the current in the right mesh is  $i_a$ .

$$75\angle 0^\circ = j500I_\Delta - 100I_\Delta - j550I_\Delta$$


$$0 = (10 + j20)I_a + 100I_\Delta + j550(I_a - I_\Delta)$$

Solving,

$$I_a = j2.5 \, A$$

$$V_o = 10I_a = j25 = 25\angle 90^\circ \, V$$

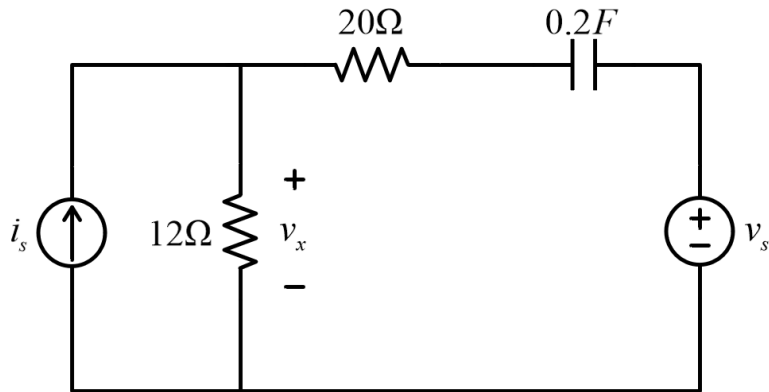5. Use the superposition principle to obtain the steady-state expression for  $v_x$  in **time domain** in the circuit. Assume  $v_s = 50\sin 2t \text{ V}$  and  $i_s = 12\cos(6t + 10^\circ) \text{ A}$ .



Step 1. Only  $i_s$ .

$$\omega = 6 \text{ rad/s}$$

$$I_s = 12\angle 10^\circ \text{ A}$$

$$Z_c = \frac{1}{j\omega C} = -j0.83 \Omega$$

$$Z = 12 \parallel (20 - j0.83) = 7.50\angle -0.89^\circ \Omega$$

$$V_{x1} = I_s \cdot Z = 90.05\angle 9.11^\circ \text{ V}$$

Step 2. Only  $v_s$ .

$$\omega = 2 \text{ rad/s}$$

$$V_s = 50\angle -90^\circ \text{ V}$$


$$Z_c = \frac{1}{j\omega C} = -j2.5 \Omega$$

$$V_{x2} = \frac{12}{12 + 20 - j2.5} \cdot V_s = 18.69\angle -85.53^\circ \text{ V}$$


Step 3. Superposition.

$$v_x(t) = 90.05 \cos(6t + 9.11^\circ) + 18.69 \cos(2t - 85.53^\circ) \text{ V}$$

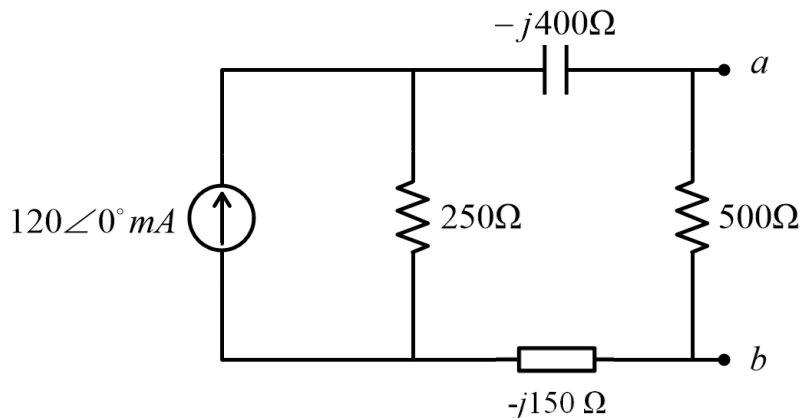6. Use source transformations to find the Thevenin equivalent circuit with respect to the terminals a, b for the circuits shown below.



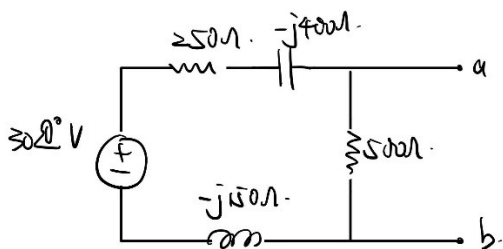
$$250 \cdot 0.12\angle 0^\circ = 30\angle 0^\circ \text{ V}$$



$$250 - j400 - j150 = 250 - j550 \Omega$$

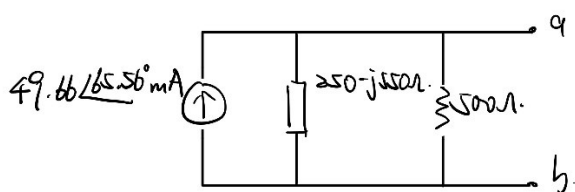
$$\frac{30\angle 0^\circ}{250 - j550} = 49.6\angle 65.56 \text{ mA}$$



$$R_{th} = (250 - j550) \parallel 500 = 324.79\angle -29.30^\circ \Omega$$

$$V_{th} = 49.6\angle 65.56^\circ \cdot 324.79\angle -29.30^\circ = 16.13\angle 36.26^\circ \text{ V}$$

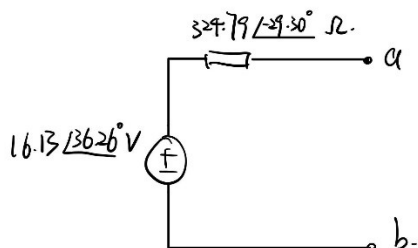
The Thevenin equivalent circuit is shown below:







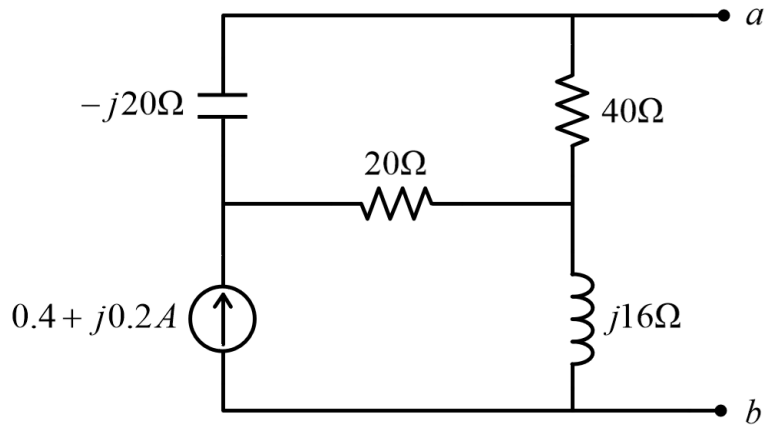7. Find the Thevenin equivalent circuit with respect to the terminals a, b for the circuit.



Open circuit voltage:

Assume the current in the upper mesh is  $I_a$ :

$$-j20I_a + 40I_a + 20(I_a - 0.4 - j0.2) = 0$$

Solving:

$$I_a = \frac{20(0.4 + j0.2)}{60 - j20} = 0.1 + j0.1 \text{ A}$$

$$V_{oc} = 40I_a + j16(0.4 + j0.2) = 0.8 + j10.4 = 10.43 \angle 85.60^\circ \text{ V}$$

Short circuit current:

Mesh:

$$-j20I_a + 40(I_a - I_{sc}) + 20(I_a - 0.4 - j0.2) = 0$$


$$40(I_{sc} - I_a) + j16(I_{sc} - 0.4 - j0.2) = 0$$

Solving:


$$I_{sc} = 0.3 + j0.5 \text{ A}$$

$$Z_{th} = \frac{V_{oc}}{I_{sc}} = 16 + j8 = 17.89 \angle 26.57^\circ \Omega$$

The Thevenin equivalent circuit:

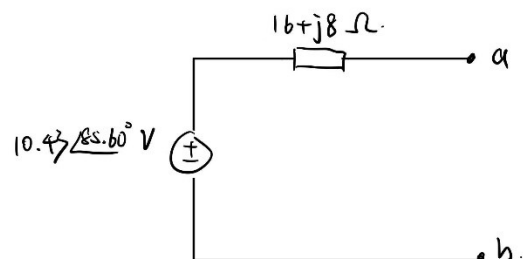

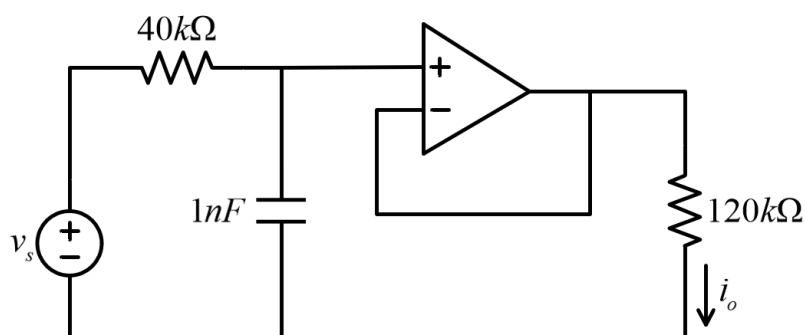8. Compute  $i_o(t)$  in the operational amplifier circuit if  $v_s = 4 \cos(10^4 t)$  V.



$$V_s = 4 \angle 0^\circ \text{ V}$$

$$Z_c = \frac{1}{j\omega C} = -j100 \text{ k}\Omega$$

KCL:

$$\frac{V_s - V_o}{40 \text{ k}\Omega} = \frac{V_o}{-j100 \text{ k}\Omega}$$

Solving:

$$V_o = 3.71 \angle -21.80^\circ \text{ V}$$

$$I_o = \frac{V_o}{120 \text{ k}\Omega} = 3.09 \times 10^{-5} \angle -21.80^\circ \text{ A}$$

$$i_o(t) = 3.09 \times 10^{-5} \cos(10^4 t - 21.80^\circ) \text{ A}$$