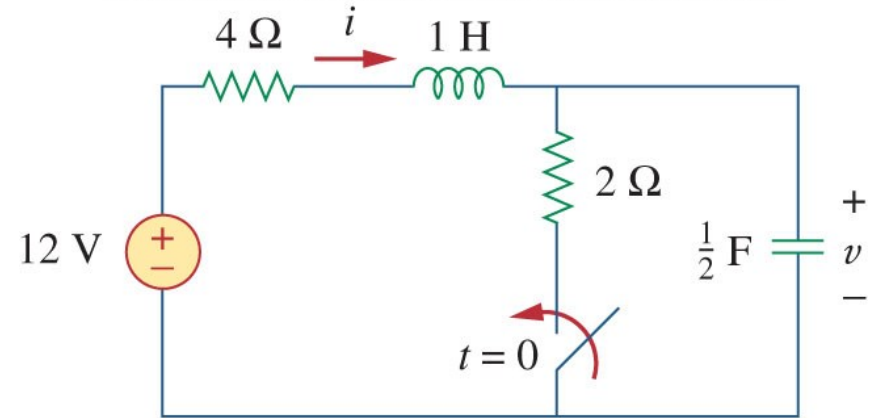





- Use mesh analysis method to find the complete response $v(t)$ for $t > 0$ in the circuit.





Find $v(t)$ for $t > 0$

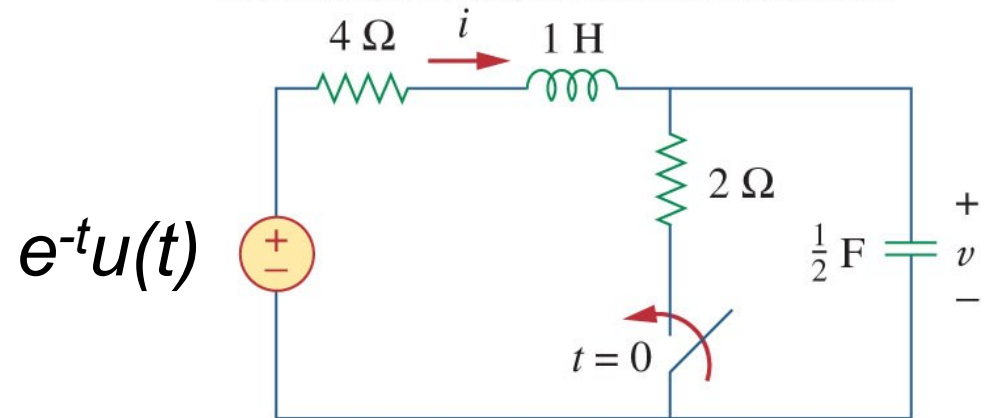Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display






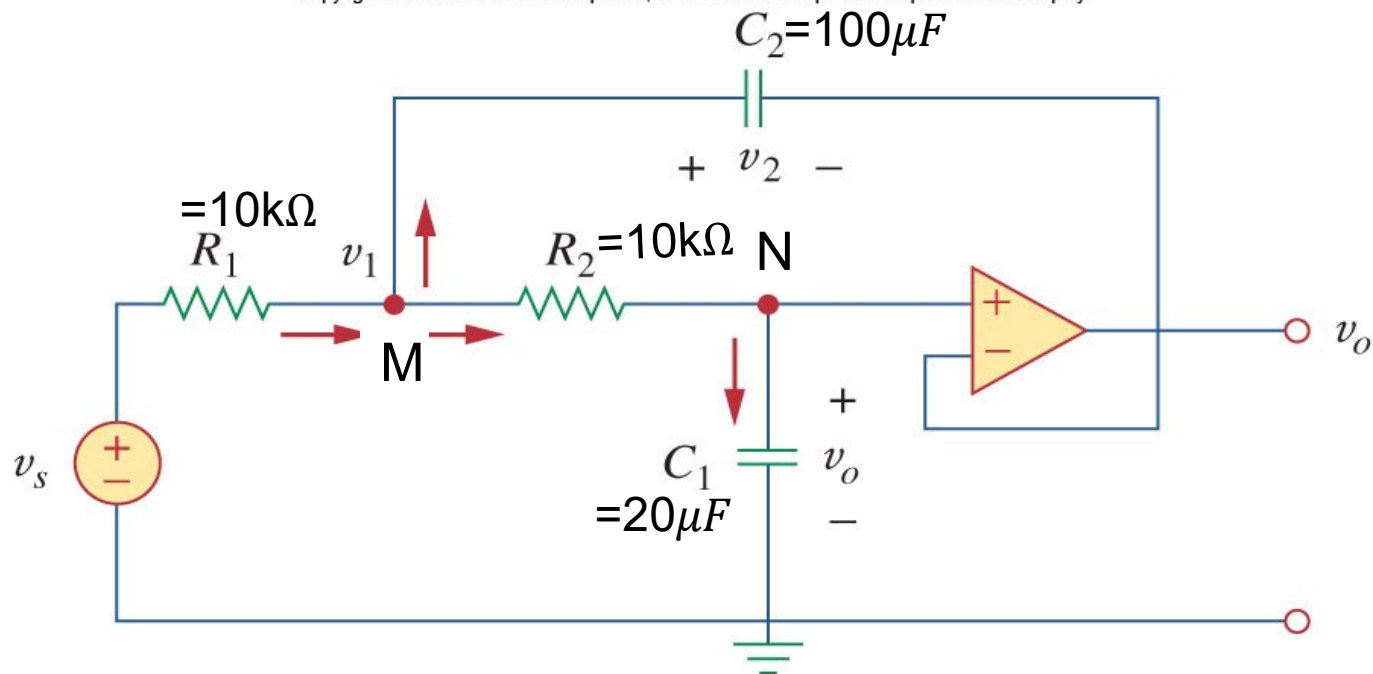Example of 2nd-order op-amp circuits

- Find v_o for $t > 0$
when $v_s = 10u(t)mV$.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display




$$\text{Initial conditions: } v_o(0^+) = 0, C_1 \frac{dv_o(0^+)}{dt} = \frac{v_1(0^+) - v_o(0^+)}{R_2} = \frac{v_2(0^+)}{R_2} = 0$$



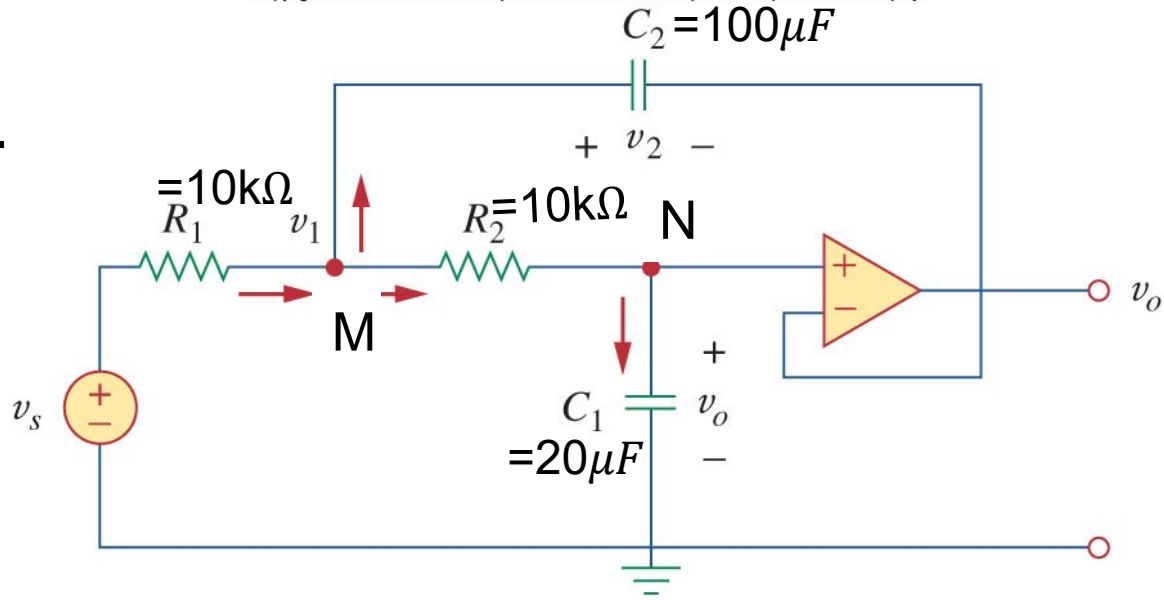Example of 2nd-order op-amp circuits

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display

- Find v_o for $t > 0$
when $v_s = 10u(t)mV$.



KCL at node M:

$$\frac{v_s - v_1}{R_1} = C_2 \frac{dv_2}{dt} + \frac{v_1 - v_o}{R_2}$$

KCL at node N:

$$C_1 \frac{dv_o}{dt} = \frac{v_1 - v_o}{R_2}$$


and we have $v_1 - v_2 = v_o$

$$\Rightarrow \frac{d^2 v_o}{dt^2} + \left(\frac{1}{R_1 C_2} + \frac{1}{R_2 C_2} \right) \frac{dv_o}{dt} + \frac{v_o}{R_1 R_2 C_1 C_2} = \frac{v_s}{R_1 R_2 C_1 C_2}$$



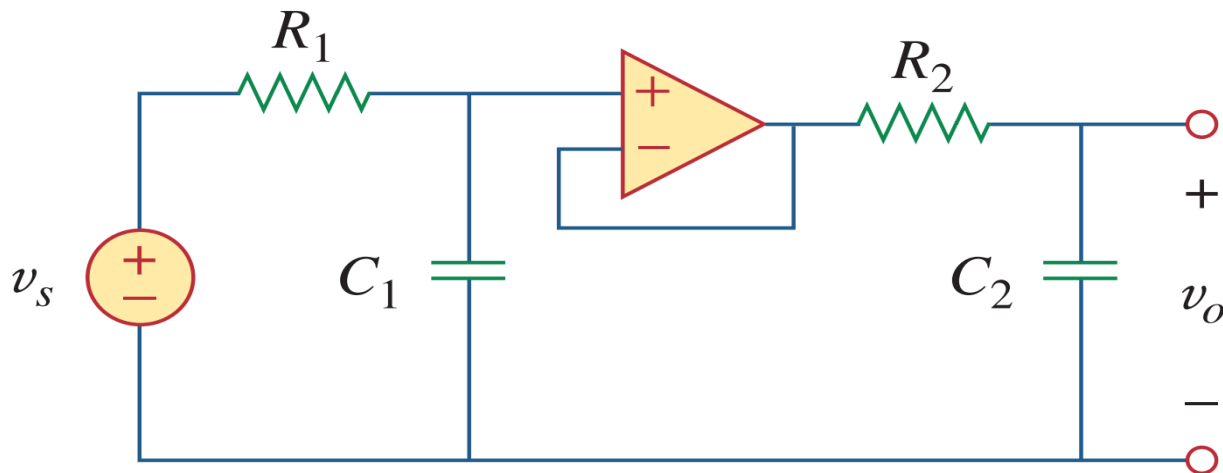Example


In the op amp circuit shown in Fig. 8.34, $v_s = 10u(t)$ V, find $v_o(t)$ for $t > 0$. Assume that $R_1 = R_2 = 10 \text{ k}\Omega$, $C_1 = 20 \text{ }\mu\text{F}$, and $C_2 = 100 \text{ }\mu\text{F}$.





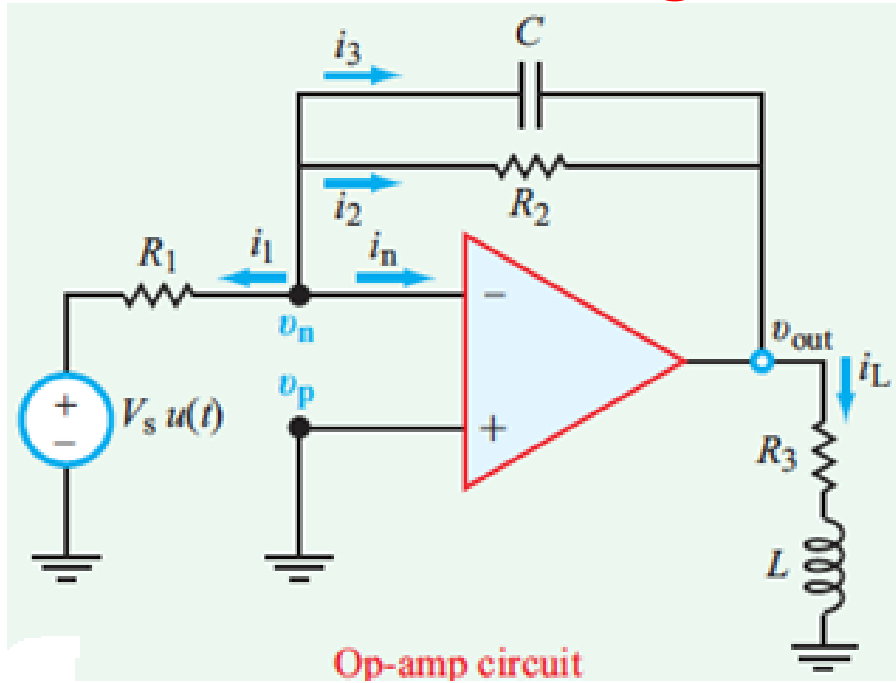
Example-2

find current through the inductor for $t > 0$





Example-2

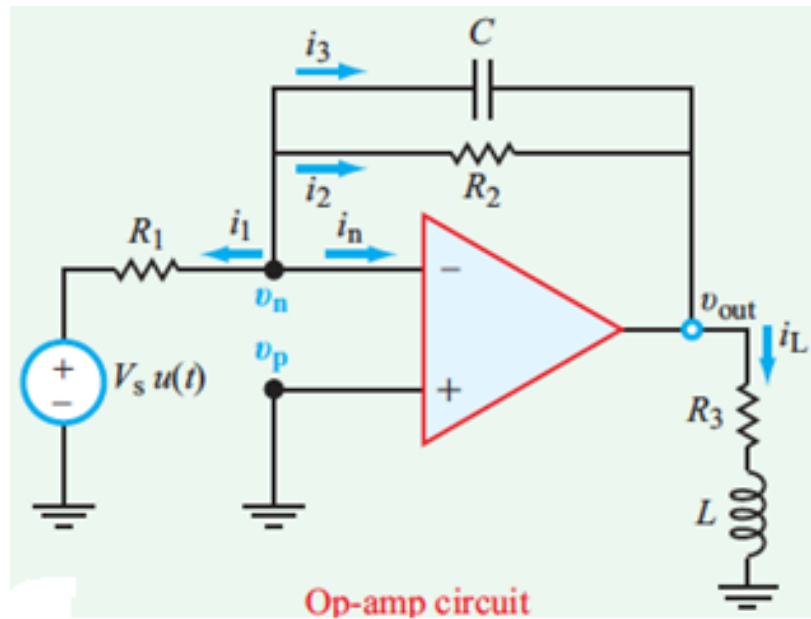

$$i_L(0) = i_L(0^-) = 0, \quad i_L'(0) = \frac{1}{L} v_L(0) = 0.$$

$$\frac{R_3}{R_2} i_L + \left(\frac{L}{R_2} + R_3 C \right) \frac{di_L}{dt} + LC \frac{d^2 i_L}{dt^2} = -\frac{V_s}{R_1}$$