

Homework 7


Due date: Jan. 2nd, 2024

Turn in your hard-copy hand-writing homework in class


Rules:

- Work on your own. Discussion is permissible, but extremely similar submissions will be judged as plagiarism.
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.

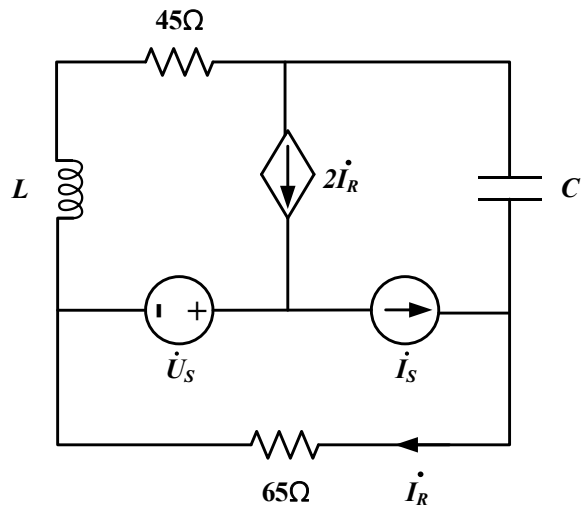1. For the circuit below, $\dot{U}_s = 100 \angle 0^\circ$ V (rms), $\dot{I}_s = 2 \angle 0^\circ$ A (rms), $\omega L = 30 \Omega$, $1/\omega C = 90 \Omega$, find the complex power delivered by **voltage and current source**.




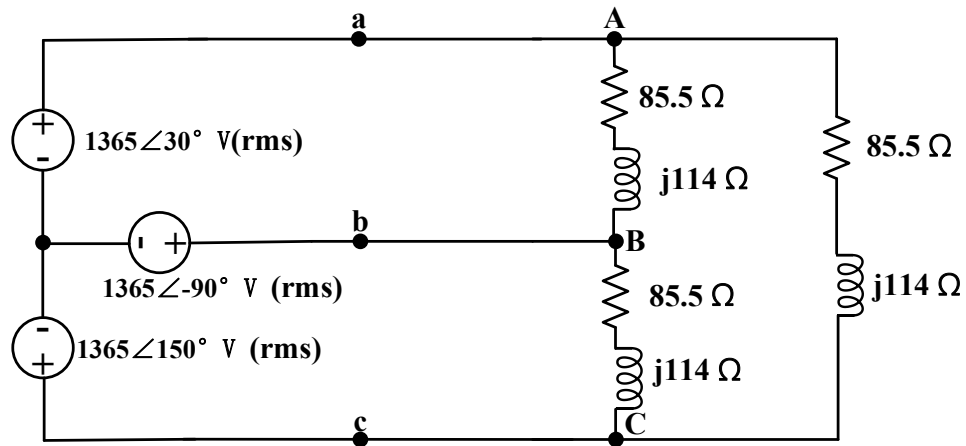2. For the circuit below, find \dot{I}_{AB} , \dot{I}_{BC} , \dot{I}_{CA} , and \dot{V}_{CA} in the circuit.




3. Consider the following three-phase circuit. $R=20\ \Omega$, $jX_L=j5\ \Omega$, $Z=(1+j0.5)\ \Omega$.

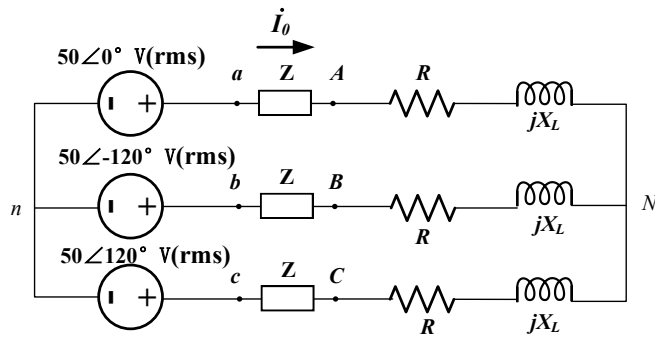- (1) Calculate the **line current** I_θ .
- (2) Calculate **the voltage** U_{AB} .
- (3) Calculate the total complex power absorbed by **all the loads including Z, R and jX_L** .




4. For the circuit below, $\dot{U}_s = 80 \angle 30^\circ \text{ V}$ (*Phasor expressed by amplitude*), find

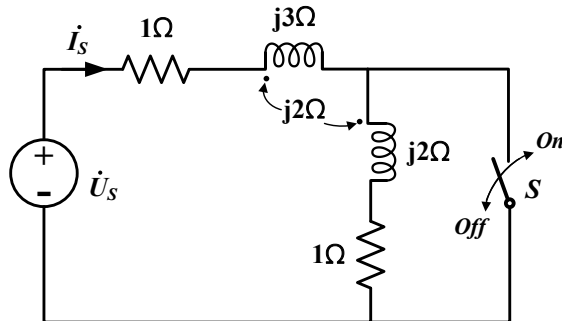- (1) The current \dot{I}_s for switch S is off.
- (2) The complex power delivered by **voltage source** when S is off.
- (3) The current \dot{I}_s when the switch S is on.



5. For the circuit below, please find:

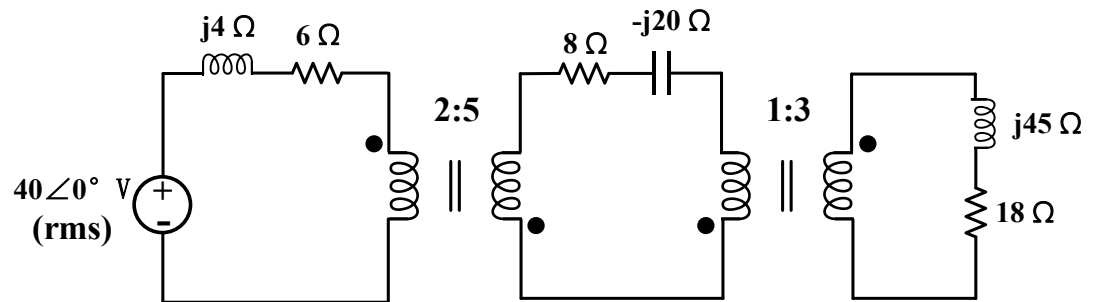- (a) The average power released by the source.
- (b) The average power delivered to the 18Ω resistor.



6. For the following circuit, please find current I_0

