





# Outline

- Capacitors and inductors
- Natural response of RC/RL circuits
- Step response of RC/RL circuits
- Others
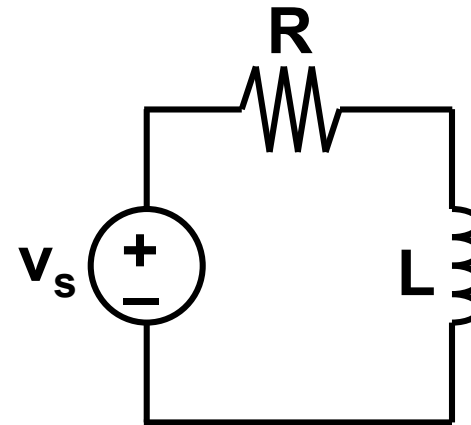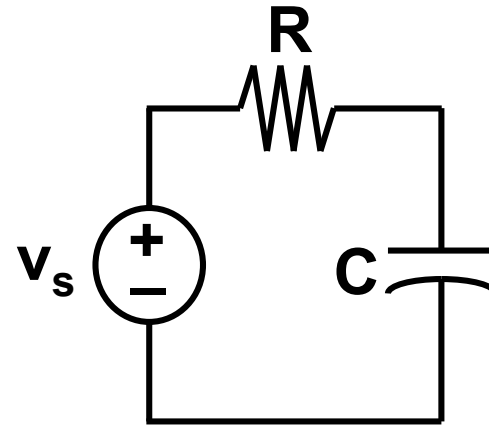
## RC and RL Circuits

- A circuit that contains only source(s), resistor(s) and a capacitor is called an **RC circuit**.
- A circuit that contains only source(s), resistor(s) and an inductor is called an **RL circuit**.





# Natural Response


Behavior (*i.e.*, current and voltage) when stored energy in the inductor or capacitor is released to the resistive part of the network (containing no independent sources).

## Natural Response of a Charged Capacitor

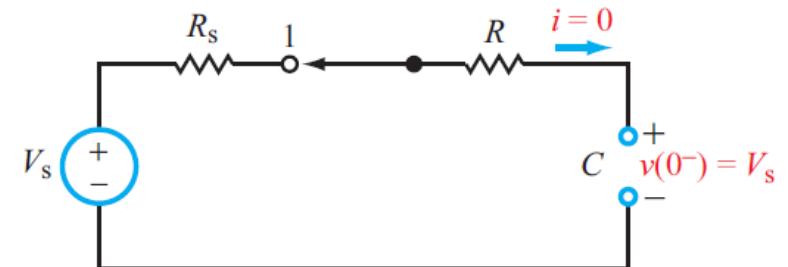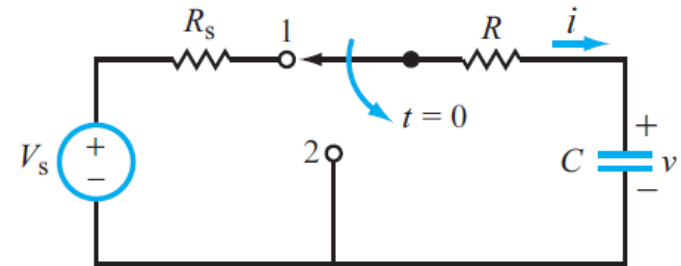(a)  $t = 0^-$  is the instant just before the switch is moved from terminal 1 to terminal 2;




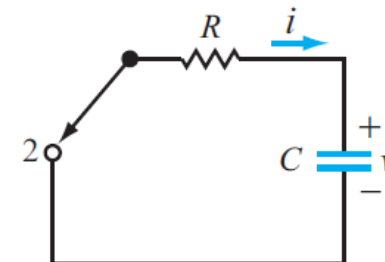(b)  $t = 0$  is the instant just after it was moved,  $t = 0$  is synonymous with  $t = 0^+$ .







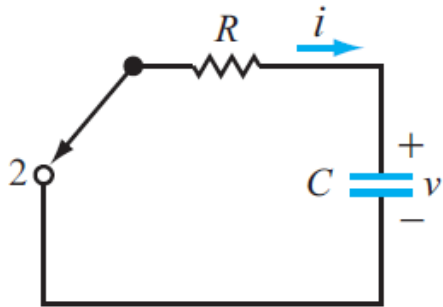
# Natural Response of a Charged Capacitor





# Natural Response of RC Circuit

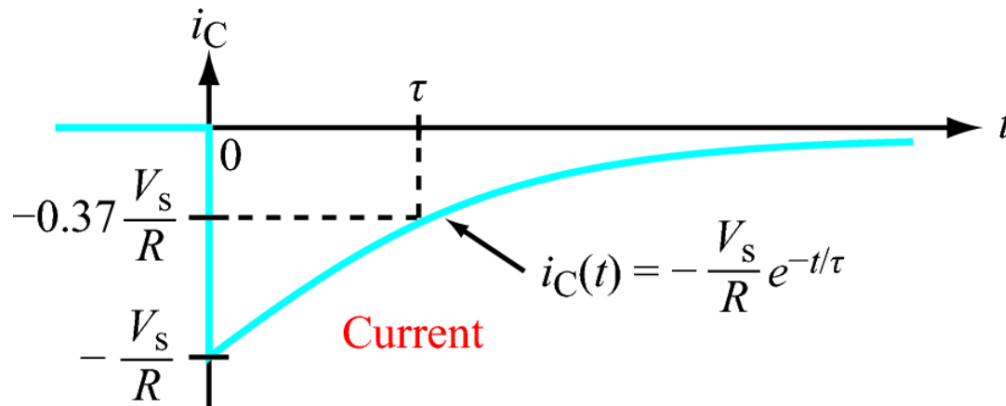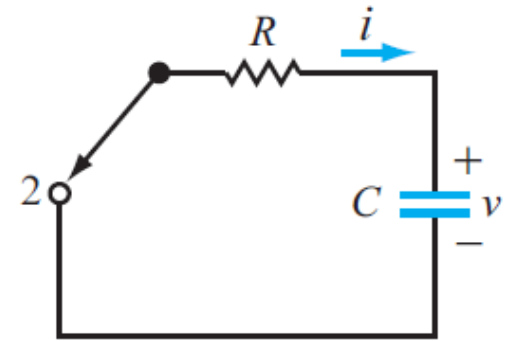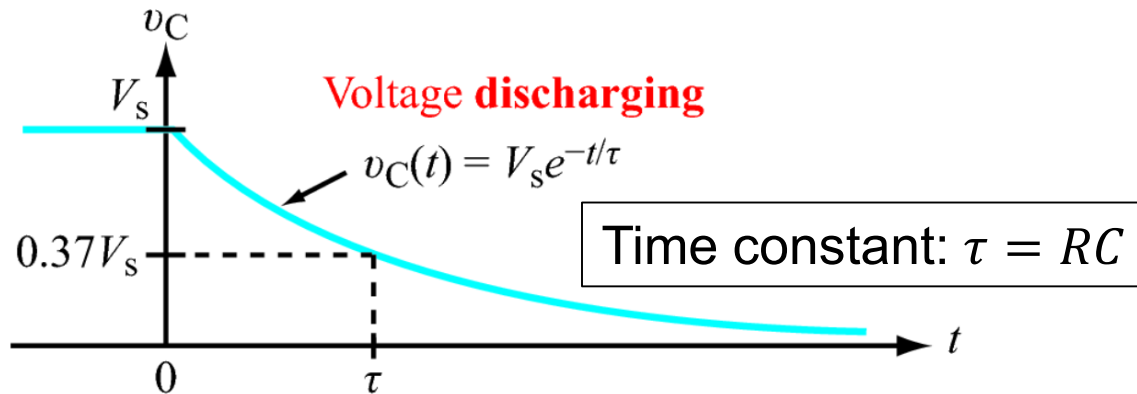
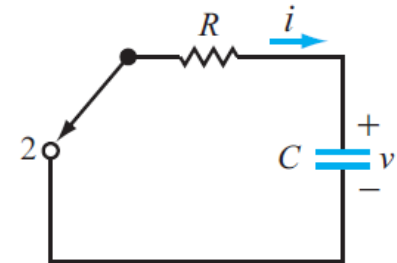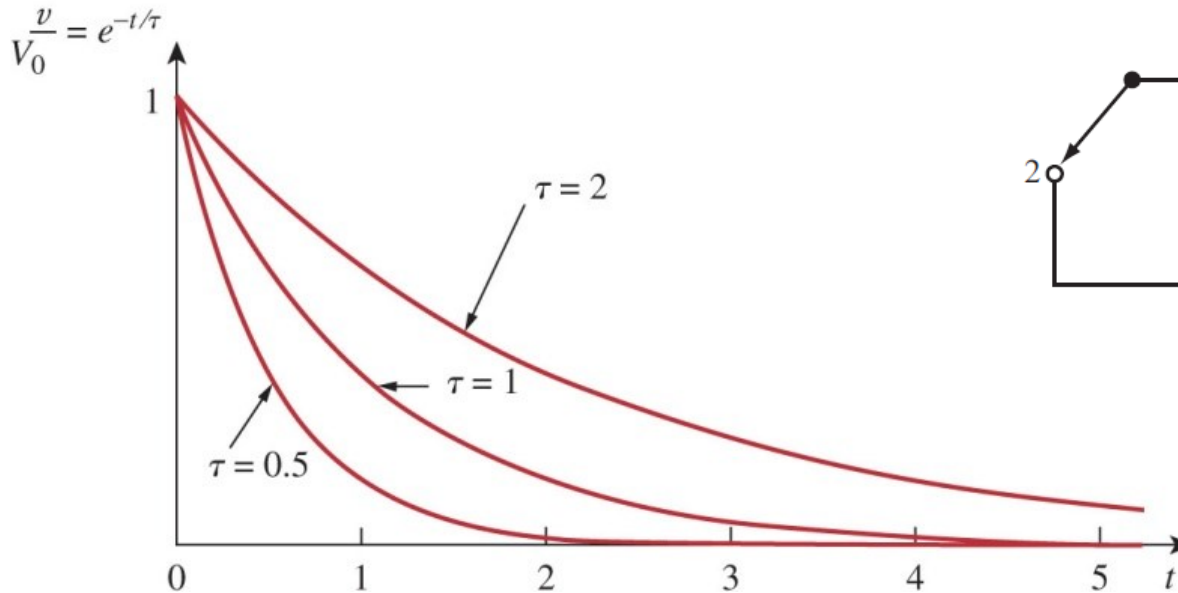
# Time Constant $\tau (= RC)$




- A circuit with a small time constant has a fast response and vice versa.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display






# Natural Response of the RL Circuit

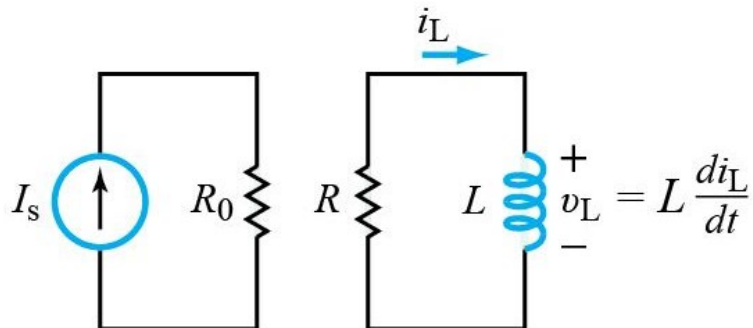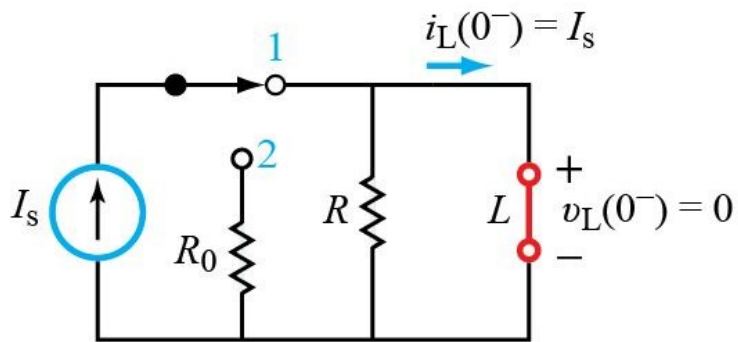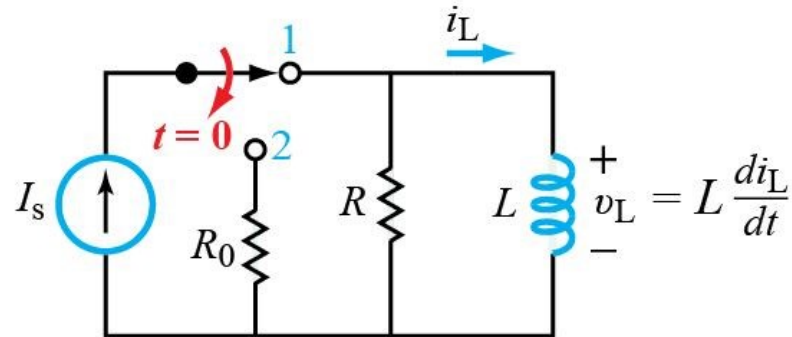




# Natural Response of the RL Circuit

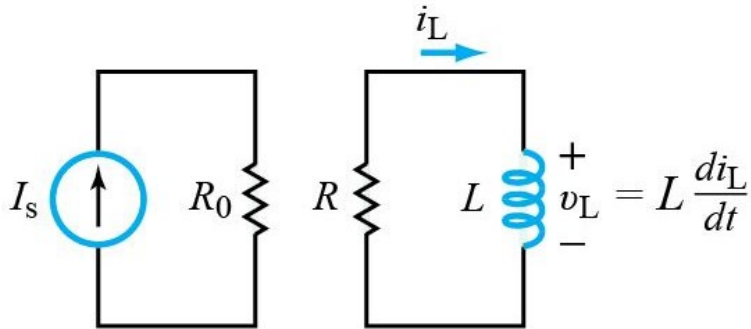






# Natural Response of the RL Circuit

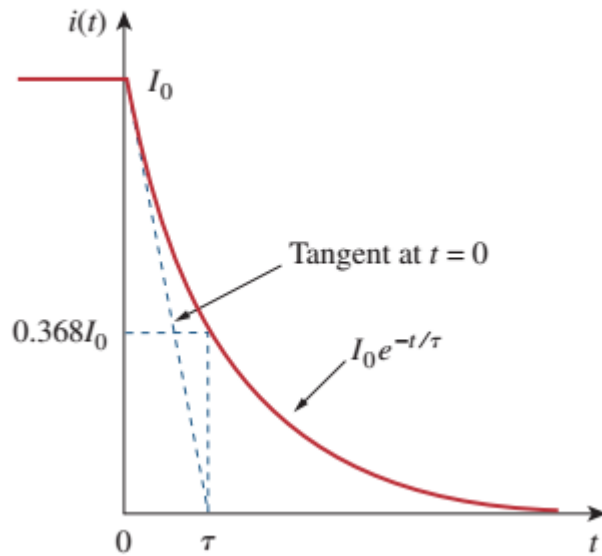

# Natural Response Summary

## RC Circuit

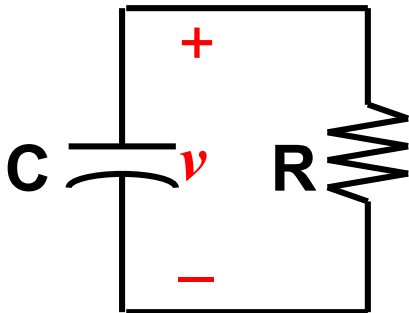


- **Capacitor voltage** cannot change instantaneously

$$v(0^-) = v(0^+)$$

$$v(t) = v(0)e^{-t/\tau}$$

- time constant  $\tau = RC$

## RL Circuit

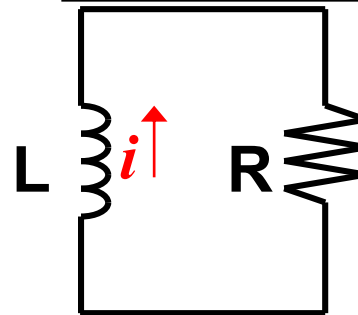

- **Inductor current** cannot change instantaneously

$$i(0^-) = i(0^+)$$

$$i(t) = i(0)e^{-t/\tau}$$


- time constant  $\tau = \frac{L}{R}$


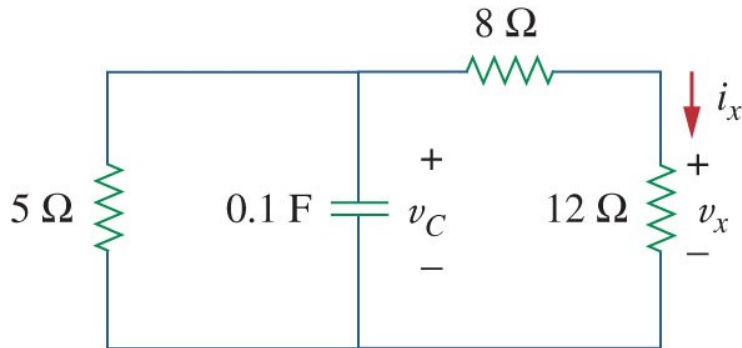
## Example

- In the circuit below, let  $v_C(t = 0) = 15\text{V}$ . Find  $v_C$ ,  $v_x$ , and  $i_x$  for  $t > 0$ .

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display






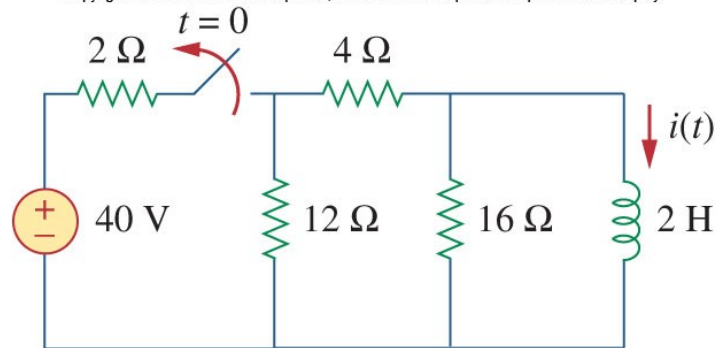
## Example

- The switch in the circuit below has been closed for a long time. At  $t = 0$ , the switch is opened. Calculate  $i(t)$  for  $t > 0$ .

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



When  $t < 0$

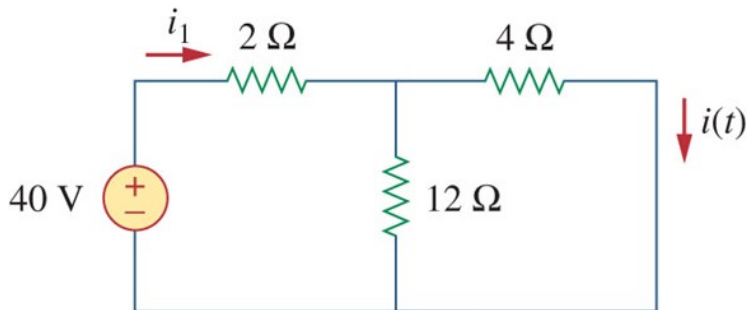

When  $t > 0$

