

1. Given that the voltage and current of two-terminal elements adopt the passive sign convention, the instantaneous values are expressed as:

(1)  $v(t) = 15\cos(400t + 30^\circ)$  V,  $i(t) = 3\sin(400t + 30^\circ)$  A;

(2)  $v(t) = 8\sin(500t + 50^\circ)$  V,  $i(t) = 2\sin(500t + 140^\circ)$  A;

(3)  $v(t) = 8\cos(250t + 60^\circ)$  V,  $i(t) = 5\sin(250t + 150^\circ)$  A;

(a) Transform the three voltage & current pairs into phasors.

(b) Try to determine whether the element is a resistor, inductor or capacitor, and determine its value ( $R=?$ ,  $C=?$ ,  $L=?$ ) for (1), (2), and (3), respectively.

1) (1)  $\dot{V} = 15\angle 30^\circ$  (V)

$i(t) = 3\cos(400t - 60^\circ)$  (A)

$\Rightarrow \dot{I} = 3\angle -60^\circ$  (A)

(2)  $v(t) = 8\cos(500t - 40^\circ)$

$\Rightarrow \dot{V} = 8\angle -40^\circ$  (V)

$i(t) = 2\cos(500t + 50^\circ)$  (A)

$\Rightarrow \dot{I} = 2\angle 50^\circ$  (A)

(3)  $\dot{V} = 8\angle 60^\circ$  (V)

$i(t) = 5\cos(250t + 60^\circ)$  (A)

$\Rightarrow \dot{I} = 5\angle 60^\circ$  (A)

(1)  $30 - (-60) = 90^\circ$

$\Rightarrow$  voltage leads current by  $90^\circ$

$\Rightarrow$  inductor

$$L = \frac{\dot{V}}{j\omega \dot{I}} = \frac{15\angle 30^\circ}{j400(3\angle -60^\circ)} = 12.5 \text{ mH}$$

(2)  $-40 - 50 = -90^\circ$

$\Rightarrow$  voltage lags current by  $90^\circ$

$\Rightarrow$  capacitor

$$C = \frac{\dot{I}}{j\omega \dot{V}} = \frac{2\angle 50^\circ}{j500(8\angle -40^\circ)} = 0.5 \text{ mF}$$


(3)  $60 - 60 = 0$

$\Rightarrow$  voltage and current in same phase

$\Rightarrow$  resistor

$$R = \frac{\dot{V}}{\dot{I}} = \frac{8\angle 60^\circ}{5\angle 60^\circ} = 1.6 \Omega$$

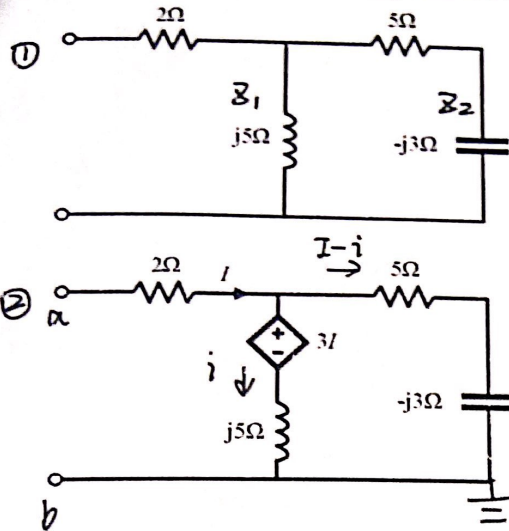2. Find the equivalent impedance for the following two circuits.



$$\textcircled{1} Z_{eq} = 2 + j5 \parallel (5 - j3) = 2 + \frac{j5(5 - j3)}{5 + j2} = 7.11 \angle 27.43^\circ (\Omega)$$

$$\textcircled{2} 3\tilde{I} + j5\tilde{i} = 5(\tilde{I} - \tilde{i}) - j3(\tilde{I} - \tilde{i})$$

$$\Rightarrow \tilde{i} = \frac{-2\tilde{I} + j3\tilde{I}}{-5 + 3j - 5j} = \frac{j3 - 2}{-5 - 2j} \tilde{I}$$


$$V_{ab} = 5\tilde{I} + j5\tilde{i}$$

$$= (8.30 \angle 4.76) \tilde{I} \text{ (A)}$$

$$\Rightarrow Z_{eq} = \frac{V_{ab}}{\tilde{I}} = 8.30 \angle 4.76 (\Omega)$$

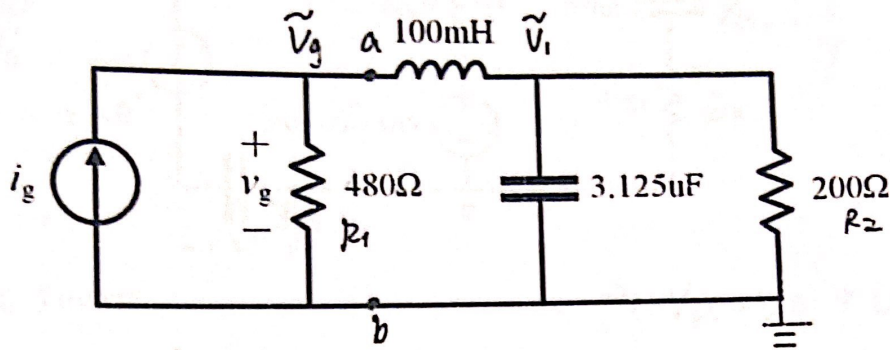3. Given  $i_g = 60 \cos(\omega t)$  mA.

If  $i_g$  is in phase with  $v_g$ , calculate the angular frequency of the current source and find the expression for  $v_g$ .



$$\tilde{i}_g = 60 \angle 0^\circ = 0.06 \angle 0^\circ \text{ (A)}$$

$$\begin{aligned} Z_{eq}' &= (Z_L + Z_C \parallel Z_{R2}) = 0.1j\omega + \frac{1}{\frac{1}{3.125 \times 10^{-6}j\omega} + \frac{1}{200}} \\ &= 0.1j\omega + \frac{200}{1 + 6.25 \times 10^{-4}j\omega} \\ &= 0.1j\omega + \frac{200(1 - 6.25 \times 10^{-4}j\omega)}{1 + 6.25^2 \times 10^{-8}\omega^2} \end{aligned}$$

$\therefore$  in phase  $\therefore \text{Im}(Z_{eq}') = 0$

$$0.1\omega + \frac{-0.125\omega}{1 + 6.25^2 \times 10^{-8}\omega^2} = 0 \Rightarrow \omega = 800 \text{ rad/s}$$

$$Z_L = j\omega L = 0.1j\omega = 80j \Omega$$

$$Z_C = \frac{1}{j\omega C} = \frac{-3.2 \times 10^5 j}{\omega} = -400j \Omega$$


$$Z_{ab}(\text{right}) = Z_L + Z_C \parallel Z_{R2} = 160 \Omega$$

$$\Rightarrow \tilde{V}_g = \tilde{i}_g \times 480 \parallel Z_{ab}(\text{right}) = 7200 \angle 0^\circ \text{ (V)}$$

$$\begin{aligned} \Rightarrow V_g &= 7200 \cos(800t) \text{ (mV)} \\ &= 7.2 \cos(800t) \text{ (V)} \end{aligned}$$



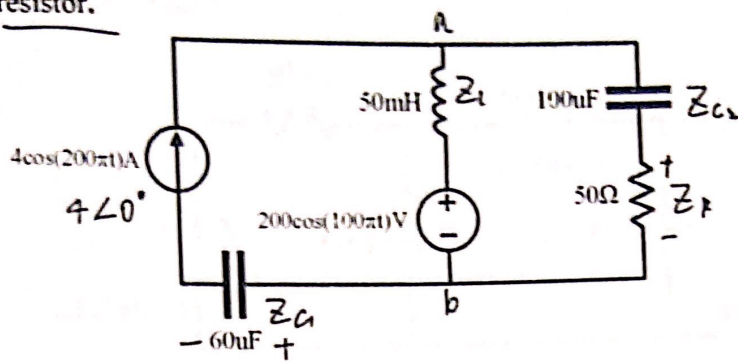4. Use superposition method to find the Time Domain voltage expression for the resistor.



① current source

$$\Rightarrow V_R = V_{R1} + V_{R2}$$

$$Z_{eq_{(ab)}} = Z_L \parallel (Z_{C2} + Z_R)$$

$$Z_{C1} = \frac{1}{j\omega C_1} = j - 26.53 \Omega$$

$$Z_L = j\omega L = j 31.42 \Omega$$

$$Z_{C2} = \frac{1}{j\omega C_2} = j - 15.92 \Omega$$

$$Z_R = 50 \Omega$$

$$\Rightarrow Z_{eq_{(ab)}} = 18.01 + j 25.84 \Omega$$

$$\tilde{V}_{R1} = \tilde{I} \cdot Z_{eq_{(ab)}} \cdot \frac{Z_R}{Z_{C2} + Z_R} = 120.05 \angle 72.79^\circ (V)$$

$$\Rightarrow V_{R1} = 120.05 \cos(200\pi t + 72.79^\circ) (V)$$

② voltage source

$$Z'_L = j\omega' L = 15.71 \angle 90^\circ \Omega$$


$$Z'_{C1} = \frac{1}{j\omega' C_1} = 31.83 \angle -90^\circ \Omega$$

$$Z_R = 50 \Omega$$

$$\Rightarrow \tilde{V}_{R2} = 200 \angle 0^\circ \times \frac{Z_R}{Z'_L + Z'_{C1} + Z_R} = 190.35 \angle 17.87^\circ (V)$$

$$\Rightarrow V_{R2} = 190.35 \cos(100\pi t + 17.87^\circ)$$

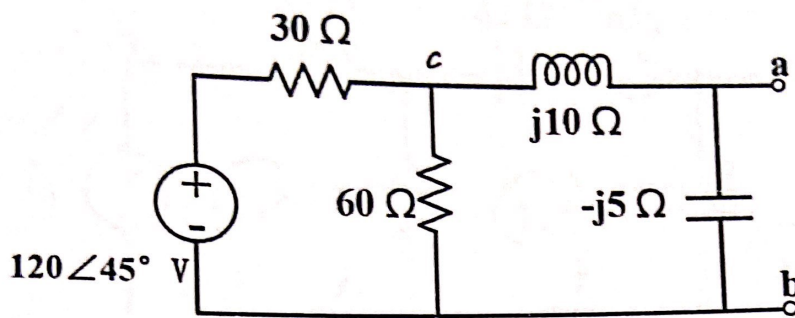5. For the circuit below, please find the Thevenin equivalent circuit with respect to node a and node b.



$$Z_{cb} = 60 \parallel (j10 - j5)$$

$$= \frac{60 \times j5}{60 + j5} = 4.98 \angle 85.24^\circ \Omega$$


$$\Rightarrow V_{TH} = V_{oc}$$

$$= 120 \angle 45^\circ \times \frac{4.98 \angle 85.24^\circ}{30 + 4.98 \angle 85.24^\circ} \times \frac{-j5}{j10 - j5} = 19.39 \angle -59.03^\circ \text{ (V)}$$


$$Z_{TH} = (30 \parallel 60 + j10) \parallel (-j5)$$

$$= 5.42 \angle -77.47^\circ \Omega$$

$\Rightarrow$  Thevenin equivalent:

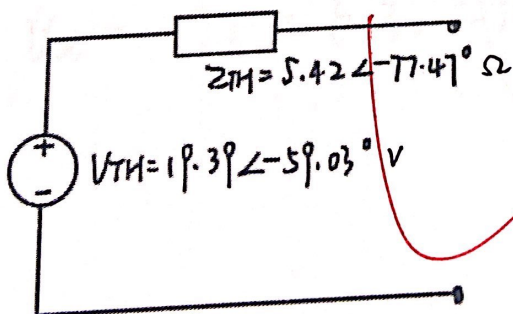

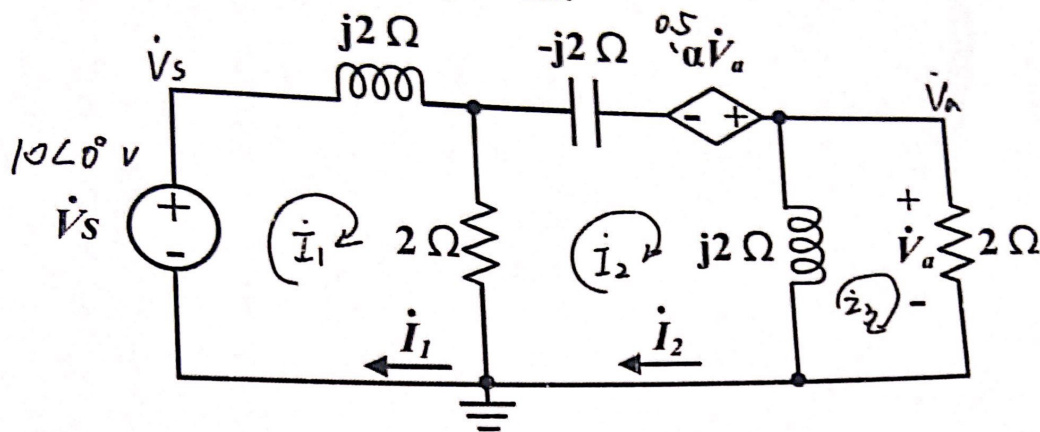6. Use nodal or mesh methods to find  $\dot{V}_a$ ,  $\dot{I}_1$  and  $\dot{I}_2$  for the circuit below, assuming that  $\dot{V}_s = 10 \angle 0^\circ \text{ V}$ ,  $\alpha = 0.5$ .



mesh analysis:

$$\begin{cases} -\dot{V}_s + j2\dot{I}_1 + 2(\dot{I}_1 - \dot{I}_2) = 0 \\ 2(\dot{I}_2 - \dot{I}_1) - j2\dot{I}_2 - \alpha\dot{V}_a + j2(\dot{I}_2 - \dot{I}_3) = 0 \\ j2(\dot{I}_3 - \dot{I}_2) + 2\dot{I}_3 = 0 \\ \dot{V}_a = 2\dot{I}_3 \end{cases}$$

$$\Rightarrow \begin{cases} \dot{I}_1 = 6.52 \angle -57.53^\circ \text{ (A)} \\ \dot{I}_2 = 4.47 \angle -26.57^\circ \text{ (A)} \end{cases}$$

$$\dot{I}_3 = \frac{j2\dot{I}_2}{j2+2} = 3.16 \angle 18.43^\circ \text{ (A)}$$

$$\Rightarrow \dot{V}_a = 2\dot{I}_3 = 6.32 \angle 18.43^\circ \text{ (V)}$$