



# Lecture 3

## Circuit Theorems




# Outline

- Linearity property
- Superposition
- Thevenin's theorem
- Source transformation
- Norton's theorem
- Power transfer
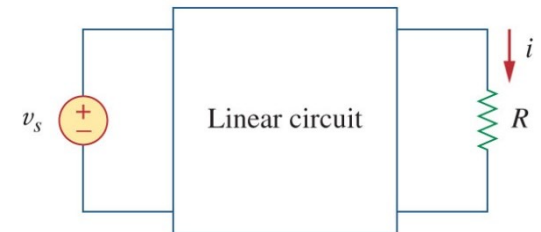
# Linear Circuit


- A linear circuit consists of only linear elements (resistors, capacitors and inductors), linear dependent sources, and independent sources.
- In a circuit,
  - Excitation: Sources
  - Response: Voltage or current in the branches

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display






# Linearity Property

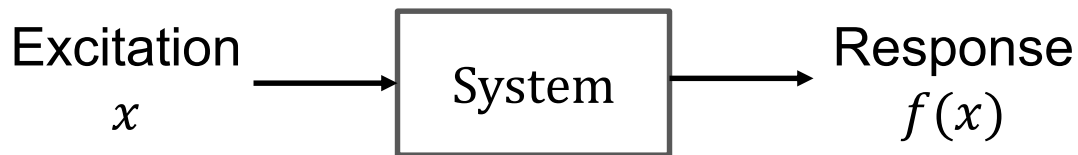

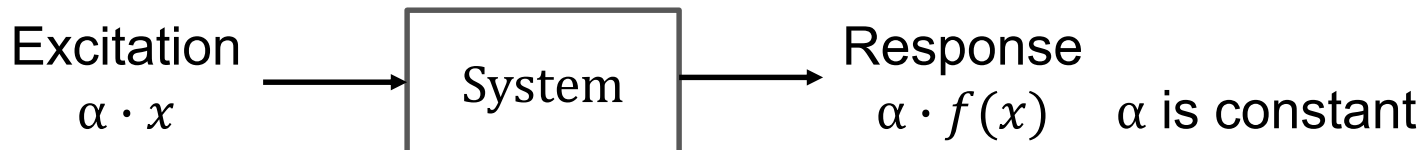- Linearity is a combination of
  - homogeneity (scaling) property




- additivity property





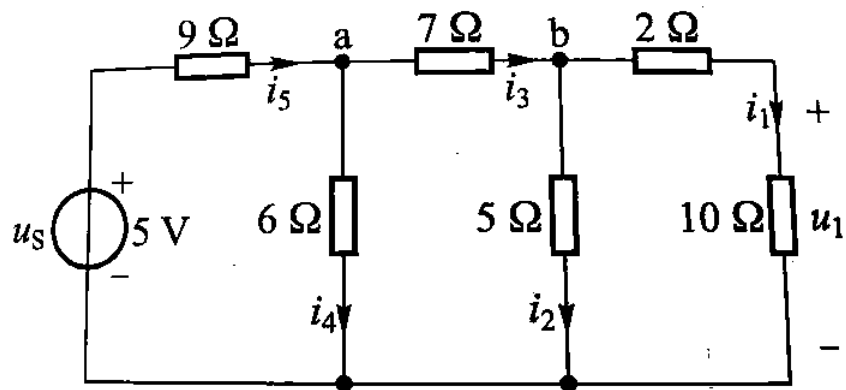
## Example of homogeneity (scaling) property



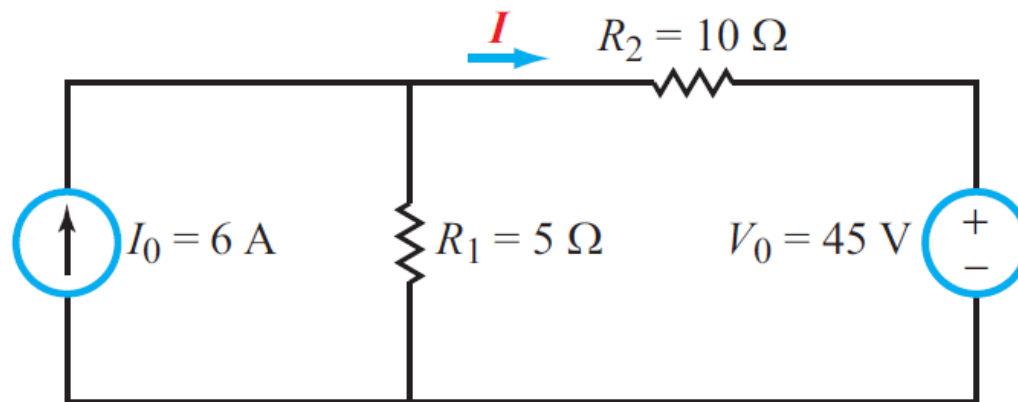
# Superposition

- The superposition principle states that the voltage across (or current through) an element in *a linear circuit* is the algebraic sum of the voltages across (or currents through) that element due to each independent source acting alone.



# Applying Superposition

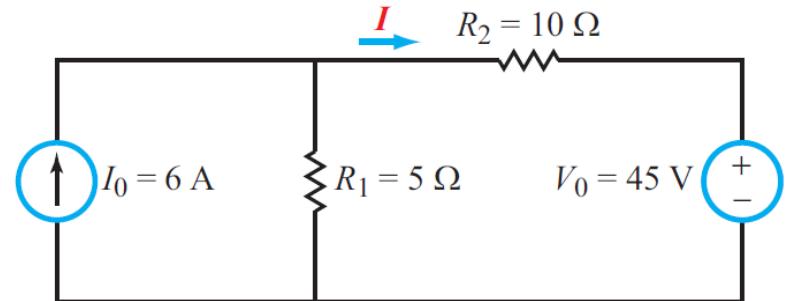

- The steps are:
  1. Turn off all other **independent** sources except for the source of interest. Find the output (voltage or current) due to that **active** source.
    - “Turn off” means to replace **independent** voltage source by short circuit ( $0\text{ V}$ ), **independent** current source by open circuit ( $0\text{ A}$ ).
  2. Repeat step 1 for **each independent** source.
  3. Find the total contribution by adding algebraically **all** the contributions due to the **independent** sources.

Note that


- 1) Using superposition means applying one independent source at a time.
- 2) **Dependent sources are left alone.**


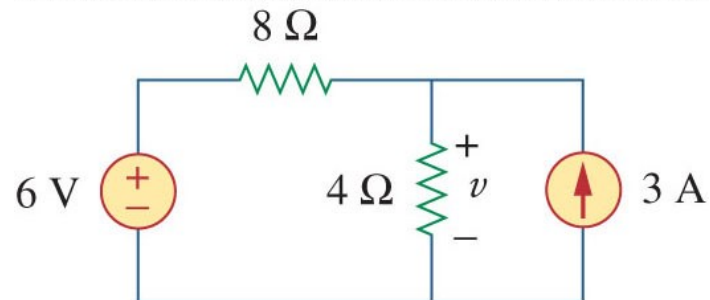
# Open Circuit and Short Circuit

- Turn off an independent voltage source means
  - $v=0$
  - Replace by wire
  - Short circuit
- Turn off an independent current source means
  - $i=0$
  - Cut off the branch
  - Open circuit

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display








## Example: Superposition


Calculate  $I$

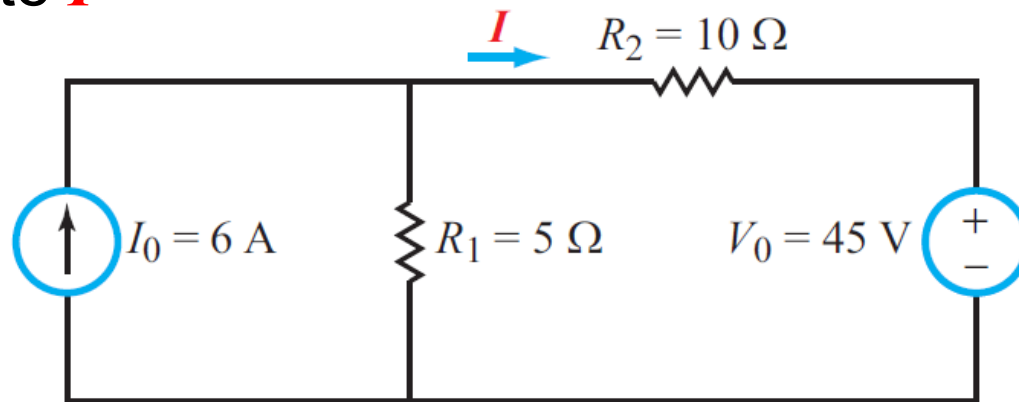




## Example: Superposition

Calculate  $I$

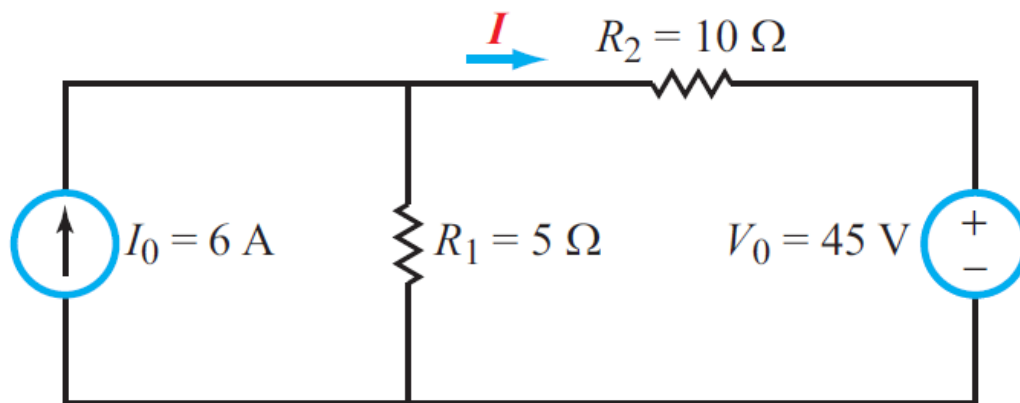


Contribution from  $I_0$  alone

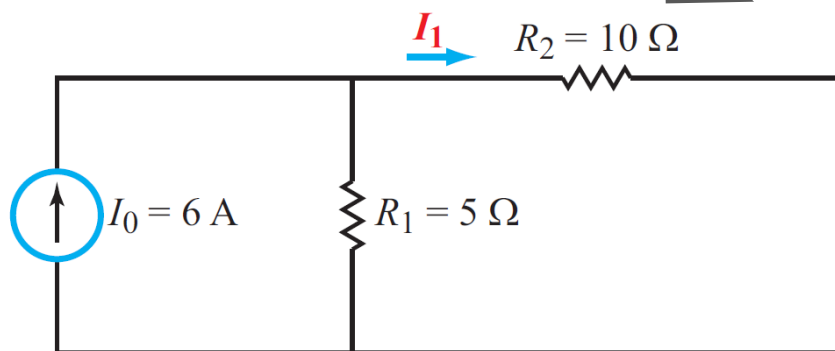

$$I_1 = 2\text{ A}$$

Contribution from  $V_0$  alone

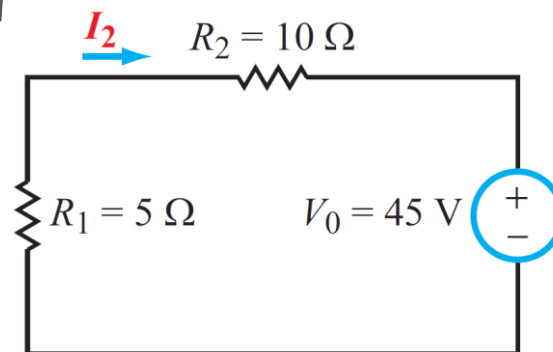


$$I_2 = -3\text{ A}$$

$$I = I_1 + I_2 = 2 - 3 = -1\text{ A}$$


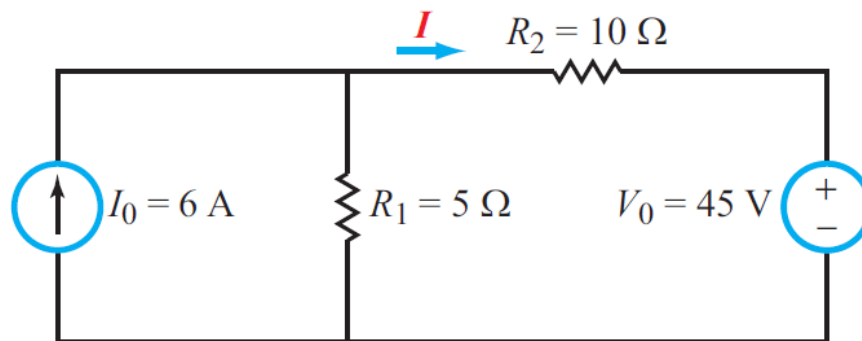
## Why Superposition?

- It is useful to evaluate the sensitivity of a response to specific sources in the circuit.
- Because it entails solving a circuit multiple times, this source-superposition method may not be attractive.




$$I = aI_0 + bV_0$$


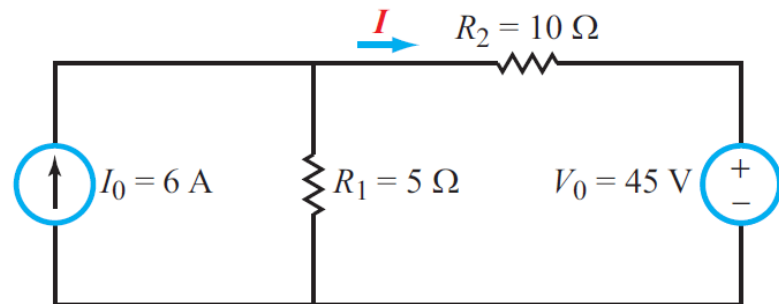
## How about Power absorbed by $R_2$

- Power due to  $I_0$ ,  $P_1 = ?$
- Power due to  $V_0$ ,  $P_2 = ?$
- Power due to both  $V_0$  and  $I_0$ ,  $P = ?$







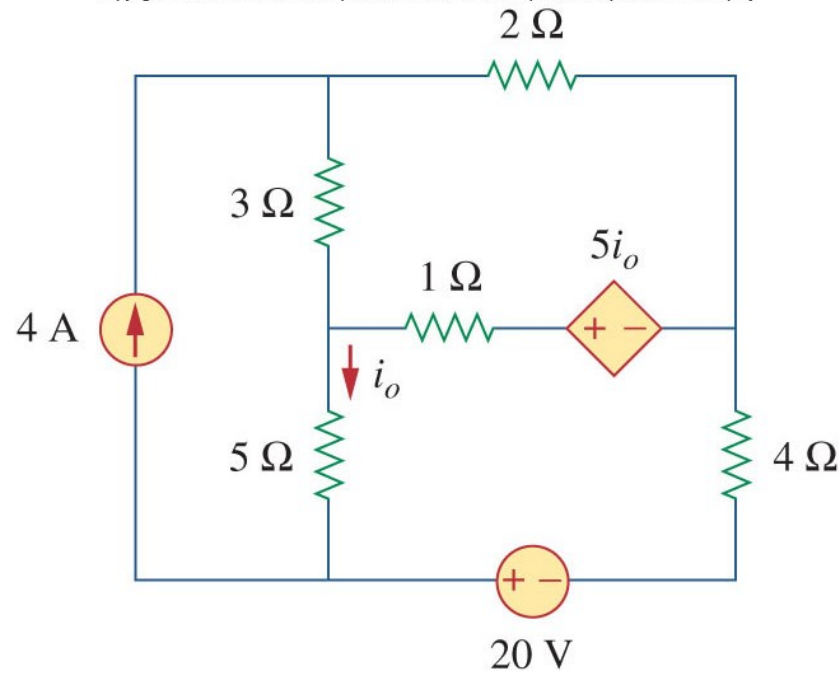
# Practice 1

- Find  $i_o$  in the circuit shown below.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



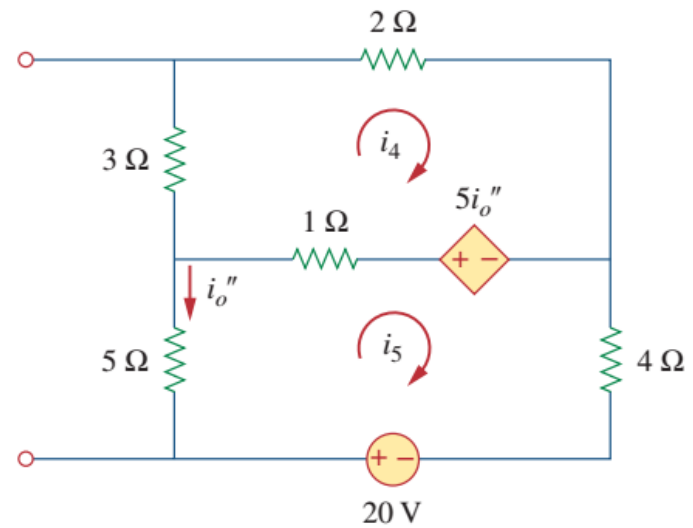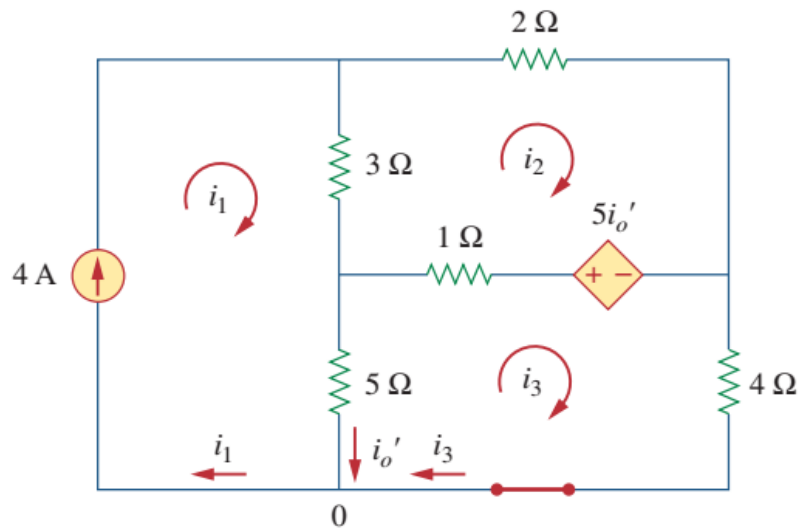



## Practice 2

- Express node voltage  $e_1$  as a function of two voltage sources  $V_1$ ,  $V_2$  and one current source  $I$ .

