

Homework 1


Due date: Oct. 19th, 2023

Turn in your hard-copy hand-writing homework in class


Rules:

- Work on your own. Discussion is permissible, but extremely similar submissions will be judged as plagiarism.
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.

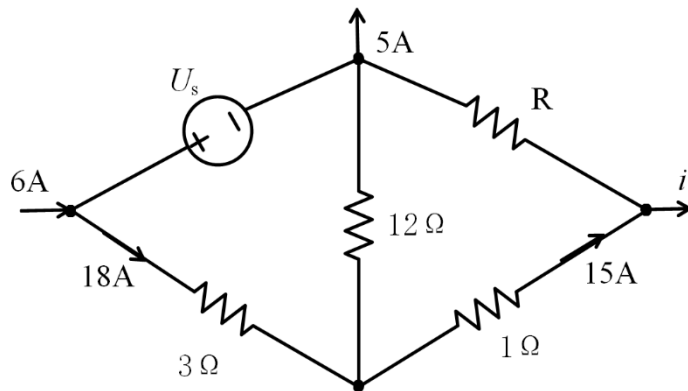1. (a) Use Kirchhoff's law to find U_s and i . **10'**
- (b) Calculate resistance R . **5'**



Answer:

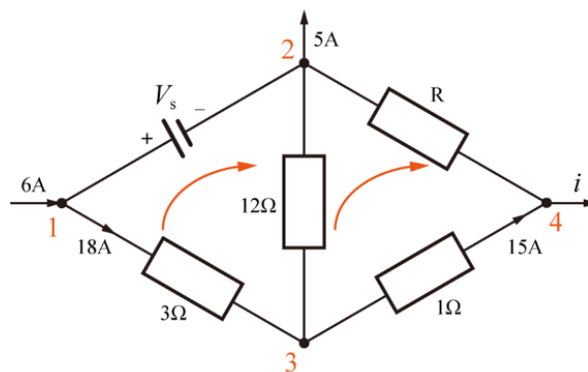

As shown in the figure, list the current equations for each node and define the current entering the node as positive and the current leaving the node as negative:

node 1: $6A - 18A + i_{V_s} = 0$

node 2: $-i_{V_s} - 5A + i_R + i_{12\Omega} = 0$

node 3: $18A - i_{12\Omega} - 15A = 0$

node 4: $-i + 15A - i_R = 0$

So: $i_{V_s} = 12A$, $i_R = 14A$, $i_{12\Omega} = -3A$, $i = 1A$

List the circuit voltage equation in the reference direction of the figure:


$V_s - V_{12\Omega} - V_{3\Omega} = 0 \dots V_{12\Omega} - V_R - V_{1\Omega} = 0$

$V_{12\Omega} = 3A \times 12\Omega = 36V \dots V_{3\Omega} = 18A \times 3\Omega = 54V$


$V_{1\Omega} = 15A \times 1\Omega = 15V \rightarrow \dots V_R = 14A \times R = 14R$

So: $V_s = 90V \dots R = 21/14\Omega = 1.5\Omega$

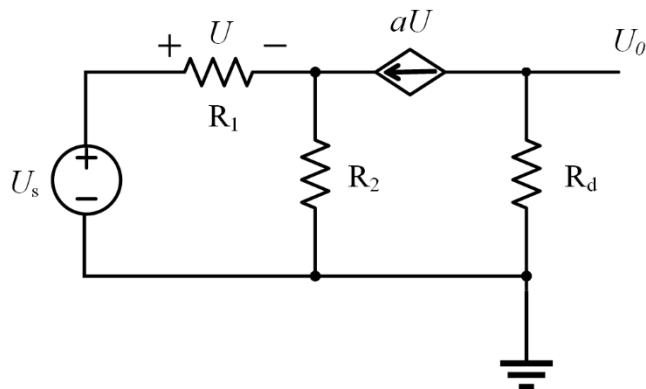2. Use Kirchhoff's law to calculate U_o/U_s in terms of a , R_1 , R_2 , and R_d . Except for U , all other variables are known quantities. **10'**



Answer ☐

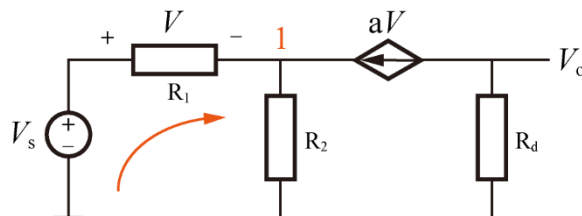

Kirchhoff's current law ☐

$$\text{node 1} \quad i_{R1} + aV - i_{R2} = 0$$

Kirchhoff's voltage Law ☐

$$-V_s + V + V_{R2} = 0$$

Ohm's law ☐

$$V_{R2} = i_{R2} \times R_2$$

$$V = i_{R1} \times R_1$$

$$\text{So} \quad V_s = (1 + R_2/R_1 + aR_2)V \quad V_o = -aVR_d$$


$$V_o/V_s = (-aR_d)/(1 + R_2/R_1 + aR_2)$$

The dimension of a is S.

3. For the circuit below, using Δ -Y conversion

(a) Calculate the U . 10'

(b) Calculate the U_{ab} . 5'

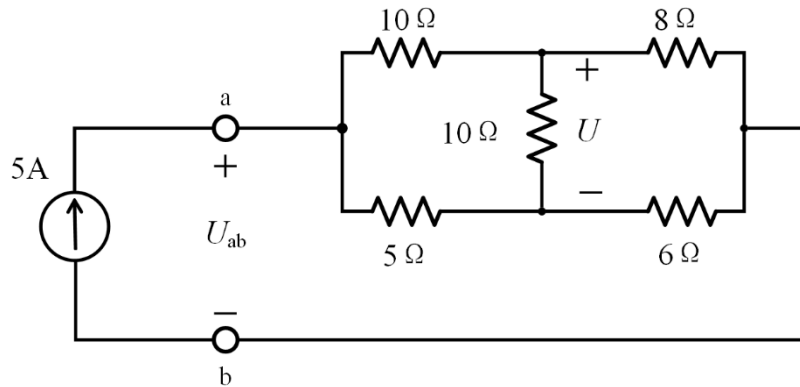

transfer $\Delta \rightarrow Y$:

$$R_1 = R_3 = \frac{5 \times 10}{10 + 10 + 5} \Omega = 2 \Omega, \quad R_2 = \frac{10 \times 10}{10 + 10 + 5} \Omega = 4 \Omega$$

$$I_1 = \frac{2 \times 6}{8 + 4 + 2 + 6} \times 5A = 2A, \quad I_2 = \frac{8 + 4}{8 + 4 + 2 + 6} \times 5A = 3A$$


$$\therefore U = 8I_1 - 6I_2 = 16 - 18 = -2V$$

$$R_{ab} = 2 + \frac{12 \times 8}{12 + 8} = 6.8 \Omega$$

$$\therefore U_{ab} = 5 R_{ab} = 34V$$

4. The node voltage U_a equals 15V, using nodal analysis method to obtain U_s and I .

10'

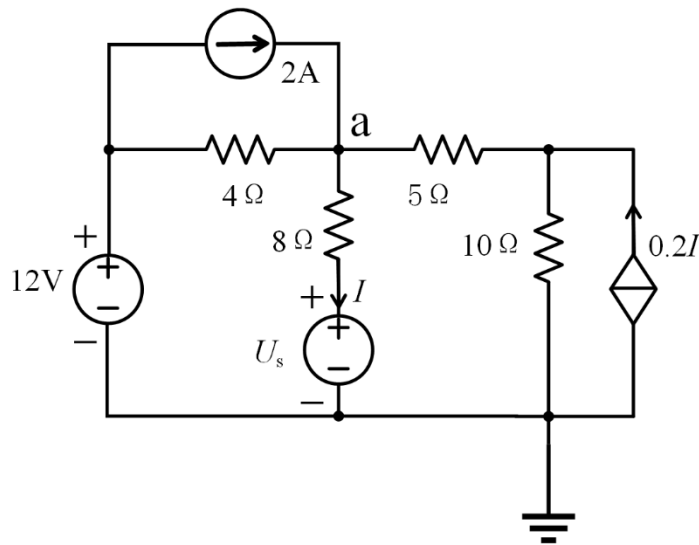

$$\begin{cases} -\frac{12}{4} + (\frac{1}{4} + \frac{1}{8} + \frac{1}{5}) U_b - \frac{1}{5} U_c = 2 + \frac{U_s}{8} \end{cases}$$

$$\begin{cases} -\frac{1}{5} U_b + (\frac{1}{5} + \frac{1}{10}) U_c = 0.2 \times \frac{U_b - U_s}{8} \end{cases}, \text{ when } U_b = 12 \text{ V.}$$



$$\begin{cases} 8.625 - 0.2 U_c = 5 + 0.125 U_s \\ -0.3 + 0.3 U_c = 0.125 - 0.025 U_s \end{cases} \Rightarrow U_s = \frac{165}{13} \text{ V} = 12.69 \text{ V}$$

$$I = \frac{12 - U_s}{8} = 0.288 = \frac{12}{52} \text{ A}$$

5. For the circuit below,

(a) apply nodal analysis method to find V_a , V_b . 10'

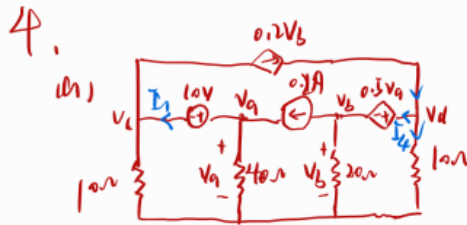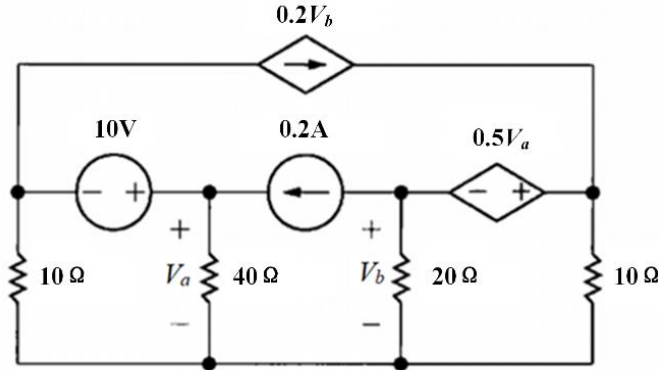(b) find the power delivered by each source (2 voltage sources and 2 current sources). 10'



$$\begin{cases} \frac{V_a - 10}{10} + 0.2V_b + \frac{V_a}{40} = 0.2 \\ 0.1 + \frac{V_b}{20} + \frac{V_b + 0.5V_a}{10} = 0.2V_b \end{cases} \Rightarrow \begin{cases} V_a = \frac{46}{13} = 3.54 \text{ V} \\ V_b = \frac{68}{13} = 5.23 \text{ V} \end{cases}$$

(b)

$$\text{for } 0.2V_b: V_c = V_a + 10 = \frac{114}{13} \text{ V}, V_d = V_b + 0.5V_a = \frac{76}{13} \text{ V}$$


$$P_{0.2V_b} = 0.2 \times \frac{68}{13} \times \left(\frac{114}{13} - \frac{76}{13} \right) = \frac{2584}{169} \text{ W}, \text{ delivered } \frac{2584}{169} \text{ W}$$

$$\text{for } 10\text{V}: P_{10\text{V}} = 10 \times I_1 = \frac{20}{13} \text{ W}, \text{ delivered } -\frac{20}{13} \text{ W}$$

$$\text{for } 0.2\text{A}: P_{0.2\text{A}} = 0.2 \times \left(\frac{68}{13} - \frac{16}{13} \right) = 0.8 \text{ W}, \text{ delivered } -0.8 \text{ W}$$


$$\text{for } 0.5V_a: P_{0.5V_a} = 0.5 \times V_a \times \left(\frac{V_d}{10} - 0.1V_b \right) = \frac{48}{169} \text{ W}, \text{ delivered } \frac{48}{169} \text{ W}$$

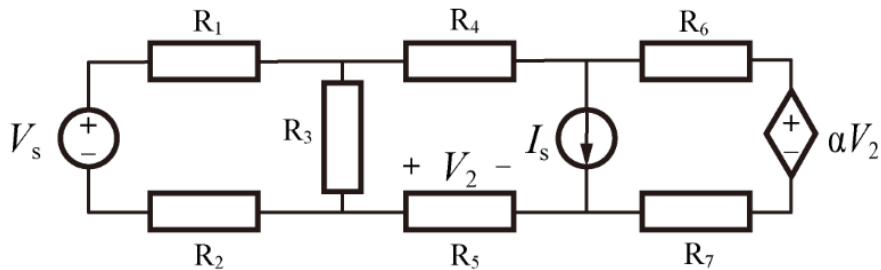6. Use mesh current analysis method, calculate the absorbed power of current source and voltage source, given $R_1 = R_2 = R_3 = R_4 = R_5 = R_6 = R_7 = 1\Omega$, $\alpha = 4$, $I_s = 1A$, $V_s = 1V$ 20'



Answer:

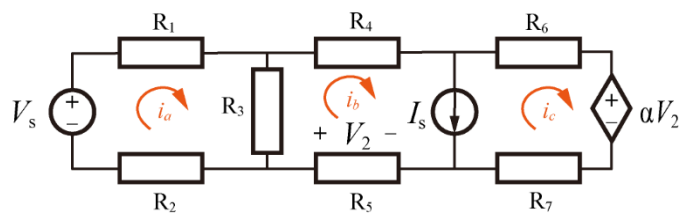Define the voltage of the current source as V:



$$-V_s + i_a R_1 + (i_a - i_b) R_3 + i_a R_2 = 0$$

$$(i_b - i_a) R_3 + i_b R_4 - V + i_b R_5 = 0$$

$$V + i_c R_6 + \alpha V_2 + i_c R_7 = 0$$

Additional equations:

$$V_2 = -i_b R_5$$

$$i_b = i_c + I_s$$

$$\text{So: } i_a = 1.5A, i_b = 3.5A, i_c = 2.5A, V = -9V$$


$$P_{V_s} = i_a \times V_s = -1.5W$$

$$P_{I_s} = I_s \times V = -9W$$

$$P_{\alpha V} = -35W$$

6. $R_1 = R_2 = R_3 = R_4 = 10\Omega$, $\beta = 2$, use the mesh current method to find V_s/i

10'

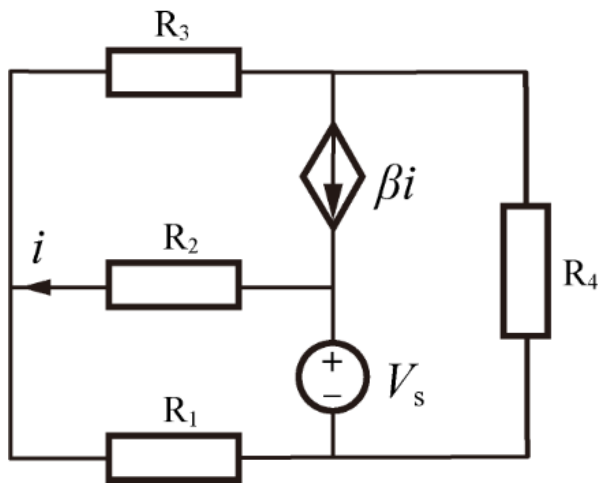

Answer:

Define the voltage of the controlled current source as V :

$$i_a R_3 + V + (i_a - i_b) R_2 = 0$$

$$(i_b - i_a) R_2 + V_s + i_b R_1 = 0$$

$$-V_s - V + i_c R_4 = 0$$

Additional equations:

$$i_a - i_b = i$$

$$i_a - i_c = \beta i$$

$$\text{eliminate the } V, i_a, i_b, i_c, \text{ to get: } V_s/i = \frac{(R_1+R_2)(R_3+R_4) - (\beta R_4 - R_2)R_1}{R_1+R_3+R_4} = 10$$