

Student Name: _____
Student Number: _____
School: _____
Year of Entrance: _____

ShanghaiTech University Final Examination Cover Sheet

EE111 Fall 2023/2024 Exam 2024/1/18 From 8:00am-10:00am

7 Problems in total (3 A4 crib sheets allowed)

Answer the Questions in English

Two-decimal policy applies for the final answer

Academic Year: 2023 to 2024 Term: Fall
Course-offering School: SIST
Instructor: Dr. Xinbo ZOU
Course Name: Electrical Circuits
Course Number: EE111.01

Exam Instructions for Students:

1. All examination rules must be strictly obeyed throughout the entire test, and any form of cheating is prohibited.
2. Other than allowable materials, students taking closed-book tests must place their books, notes, tablets and any other electronic devices in places designated by the examiners.
3. Students taking open-book tests may use allowable materials authorized by the examiners. They must complete the exam independently without discussion with each other or exchange of materials.

For Marker's Use:


Problem	1	2	3	4	5	6	7	Total
Marks								
Recheck								

Marker's Signature:
Date:

Rechecker's Signature:
Date:

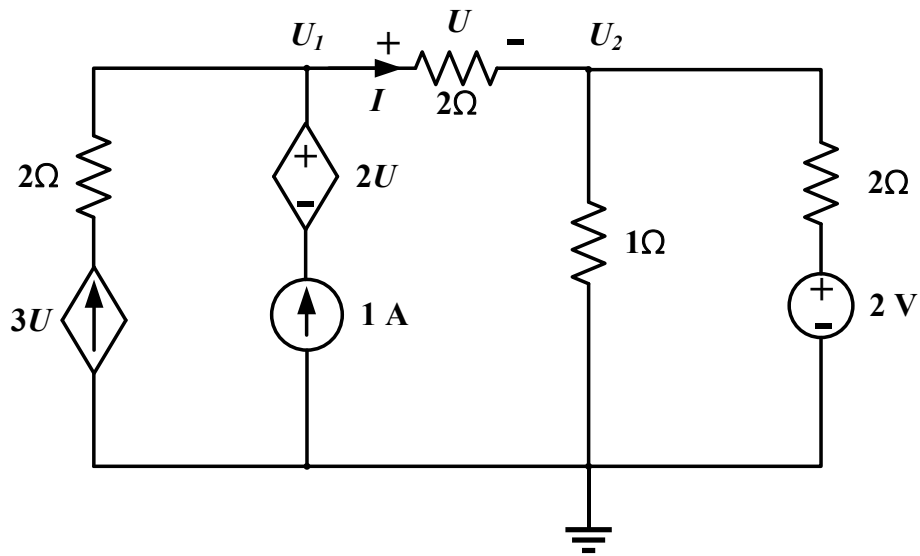
Q1 (13 points).

For the following circuit, U denotes the voltage across the resistor at the top of circuit graph. U_1 and U_2 denote the node voltage. Please use **nodal** method to derive current I .



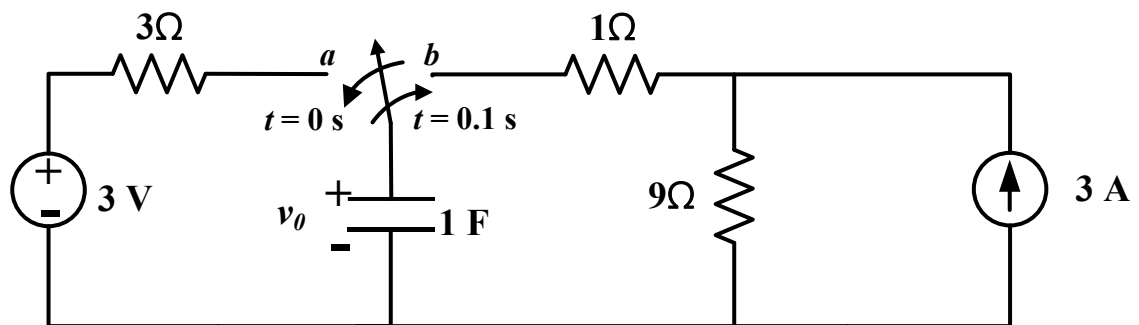
Q2(12 points). **(First-Order Circuit)**

There is no energy stored in the capacitor for $t < 0$. At $t=0$, the switch moves to node a . Then, at $t = 0.1$ s, the switch moves to node b . Find the expression of v_o for $t > 0$.



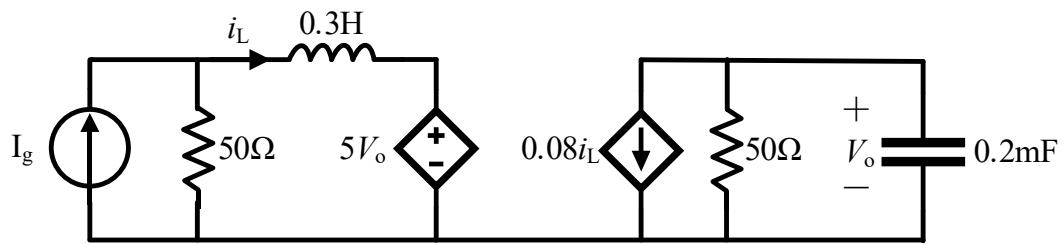Q3 (15 points). (AC circuit steady-state analysis)

Given $I_g = 10\cos(100t - 90^\circ)$, use **phasor domain method** to find steady-state response of V_o .




Q4 (12 points).

For the three-phase circuit below, $\mathbf{Z}_{\Delta} = 21 + j24 \Omega$, please

(a) find the total complex power absorbed by the **load** (the part in the dashed box).

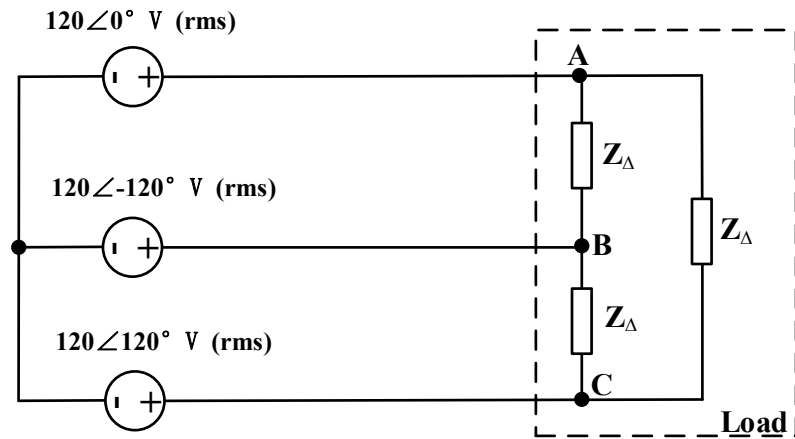
(b) find average power absorbed by **each of** the delta-connected impedance \mathbf{Z}_{Δ} .



Q5 (15 points).


In the circuit below, use **mesh current method** to find

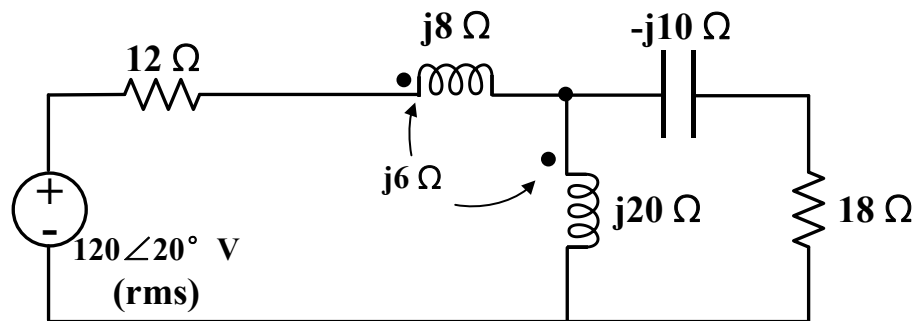- (a) Mesh current.
- (b) Complex power released by the voltage source.
- (c) The average power delivered to the 18Ω -resistor.



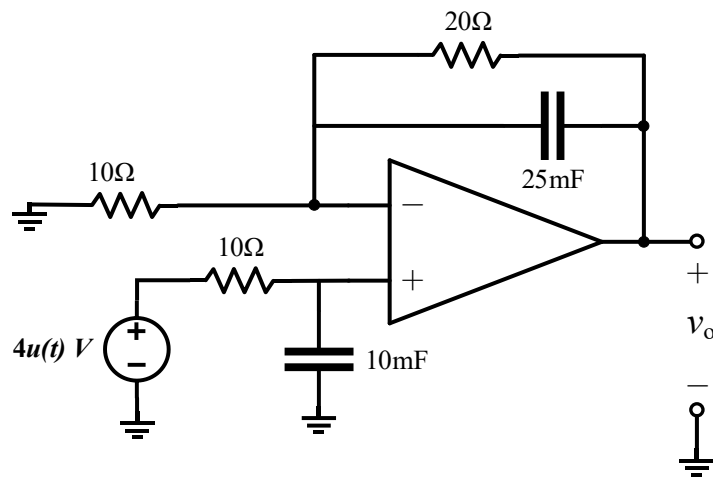Q6 (15 points). **(General 2nd-order circuits)**

Given no initial energy was stored for the energy storage elements, *use Laplace domain method OR time-domain analysis method* to find output voltage v_o for $t > 0$.




Q7(18 points)

When $t=0$, the current through the inductor is **6A** and no initial energy is stored for the capacitor.

(1) Find $i_L(t)$ for $t > 0$ by **Laplace domain method**.

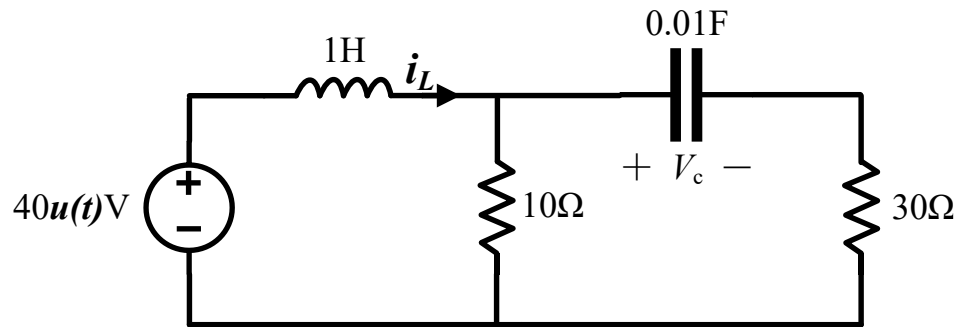(2) Find $i_L(t)$ for $t > 0$ by **time-domain method**.



Scratch Paper -1

Scratch Paper -2

Scratch Paper -3