



Lecture 14


-- Laplace Transform in Circuit Analysis

Example 2

Find (1) the voltage across the capacitor

(2) current through the inductor

assuming that $v_s(t) = 10u(t)$ V, and assume that at $t = 0$, -1 A flows through the inductor and $+5$ V is across the capacitor.


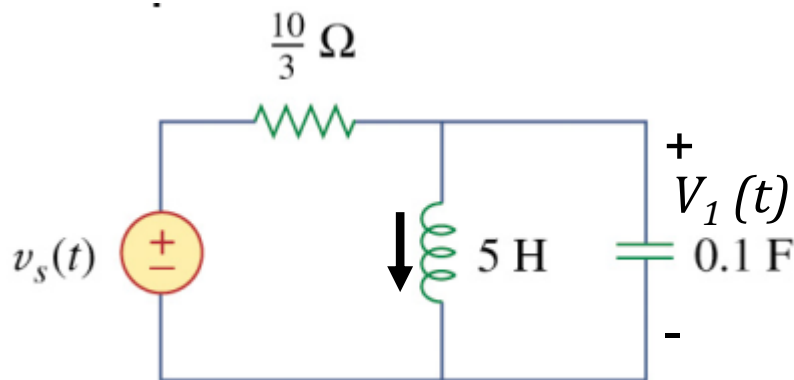


Example 2

Find (1) the voltage across the capacitor


(2) current through the inductor

assuming that $v_s(t) = 10u(t)$ V, and assume that at $t = 0$, **-1 A** flows through the inductor and +5 V is across the capacitor.

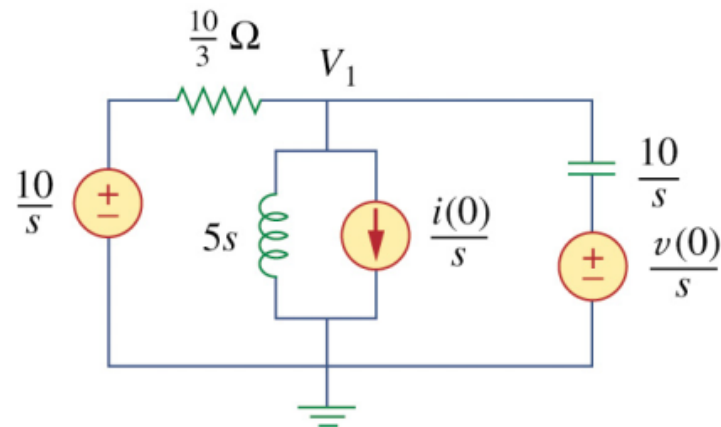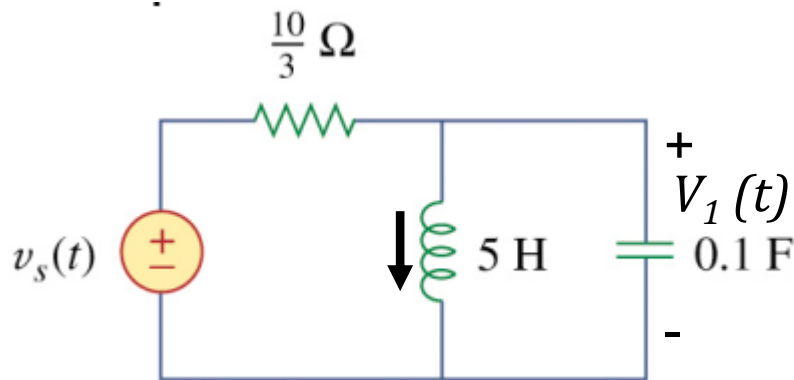

Example 3


- Use Thevenin's equivalent circuit w.r.t. terminals a - b to find current $i_C(t)$ for $t > 0$.

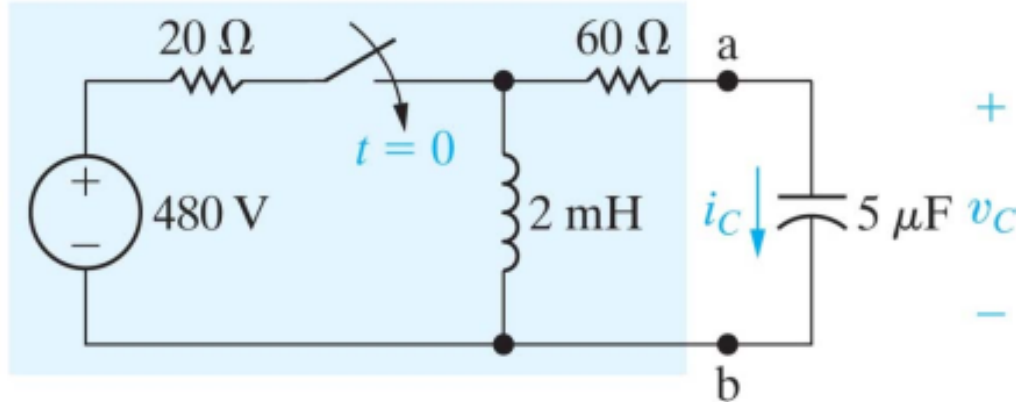



Example 4

- Find $v_o(t)$ for $t > 0$

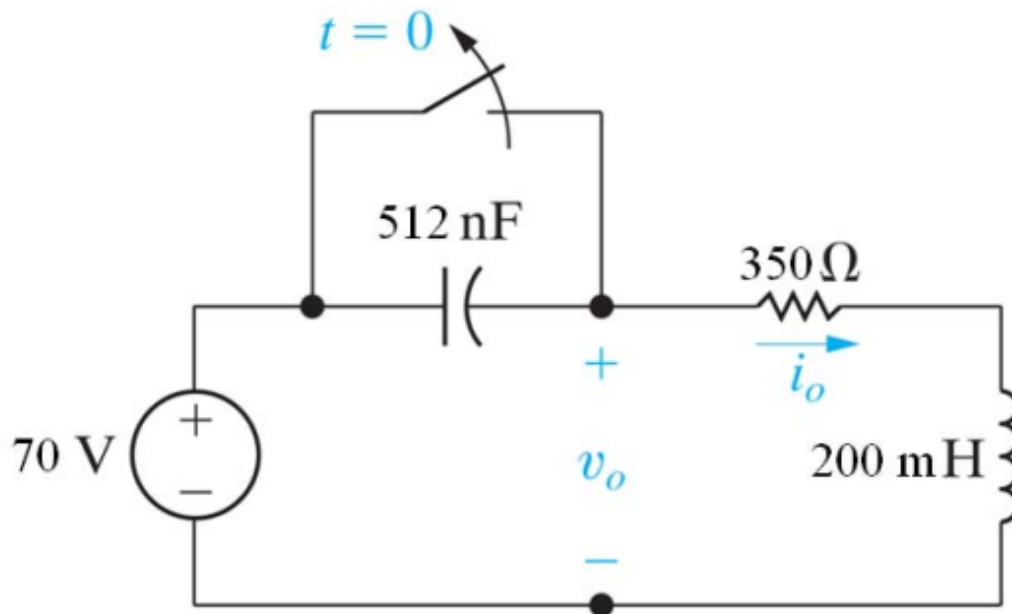



$$V_0(s) = \frac{70s - 268,125}{s^2 + 1750s + 9,765,625} = \frac{K_1}{(s + 875 - j3000)} + \frac{K_2}{(s + 875 + j3000)}$$

$$K_1 = \left. \frac{70s - 268,125}{(s + 875 + j3000)} \right|_{s=-875+j3000} = \frac{70(-875 + j3000) - 268,125}{[(-875 + j3000) + 875 + j3000]} = 65.1\angle 57.48^\circ$$

$$K_2 = \left. \frac{70s - 268,125}{(s + 875 - j3000)} \right|_{s=-875-j3000} = \frac{70(-875 - j3000) - 268,125}{[(-875 - j3000) + 875 - j3000]} = 65.1\angle -57.48^\circ$$

$$V_0(s) = \frac{65.1\angle 57.48^\circ}{(s + 875 - j3000)} + \frac{65.1\angle -57.48^\circ}{(s + 875 + j3000)}$$


$$v_0(t) = 2(65.1)e^{-875t} \cos(3000t + 57.48^\circ) = 130.2e^{-875t} \cos(3000t + 57.48^\circ)u(t) \text{ V}$$


Example 5

- Example---Find i_x (S.S.) assuming no initial energy stored

Using (1) phasor method


(2) Laplace transform method

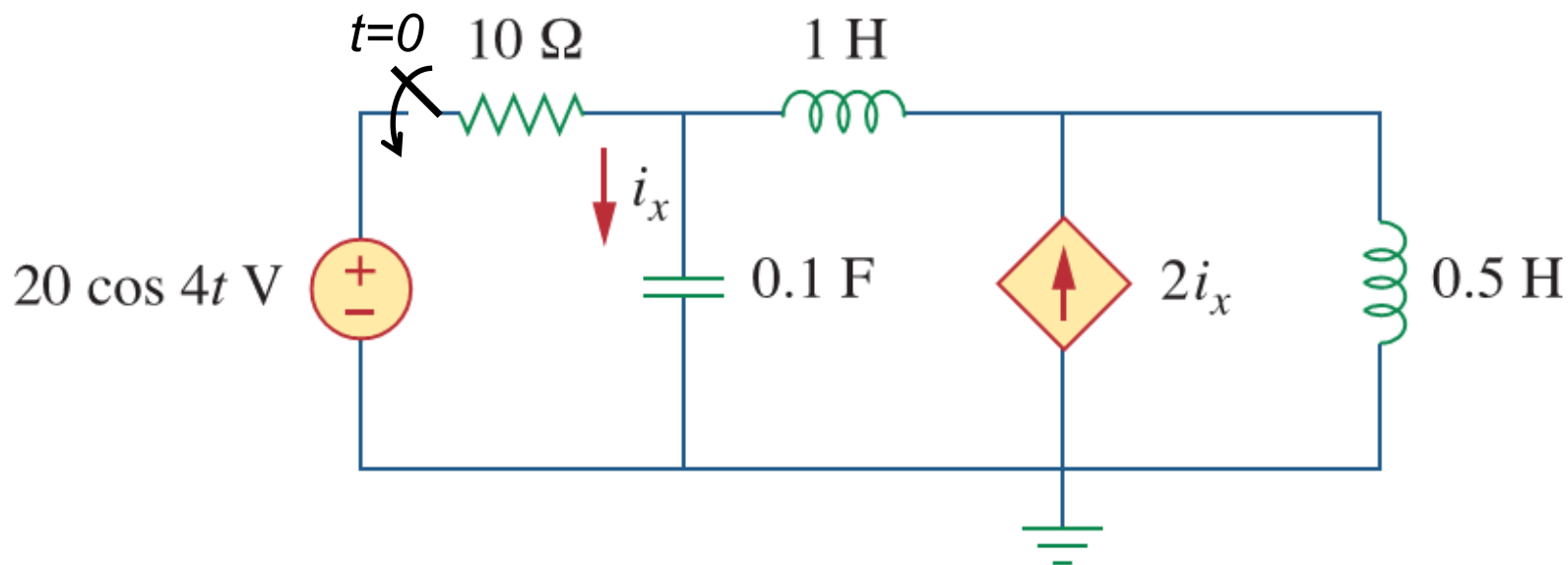

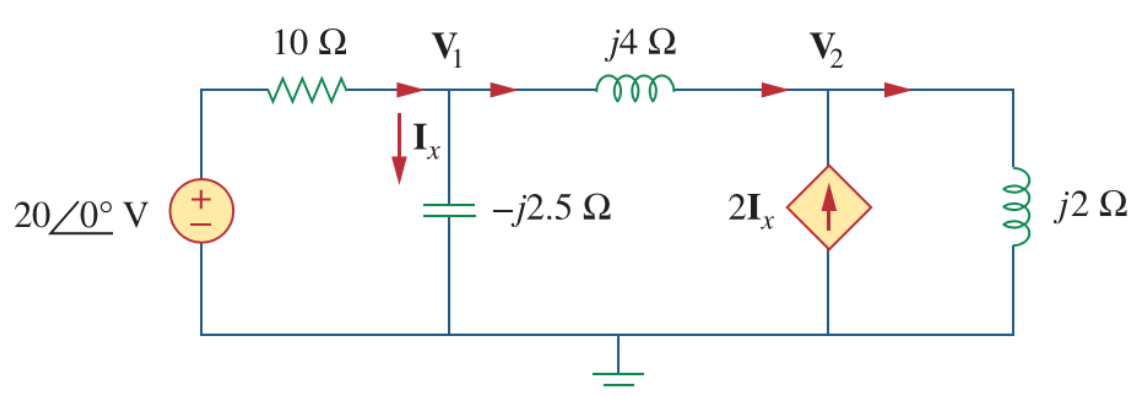

$$\frac{20 - \mathbf{V}_1}{10} = \frac{\mathbf{V}_1}{-j2.5} + \frac{\mathbf{V}_1 - \mathbf{V}_2}{j4}$$
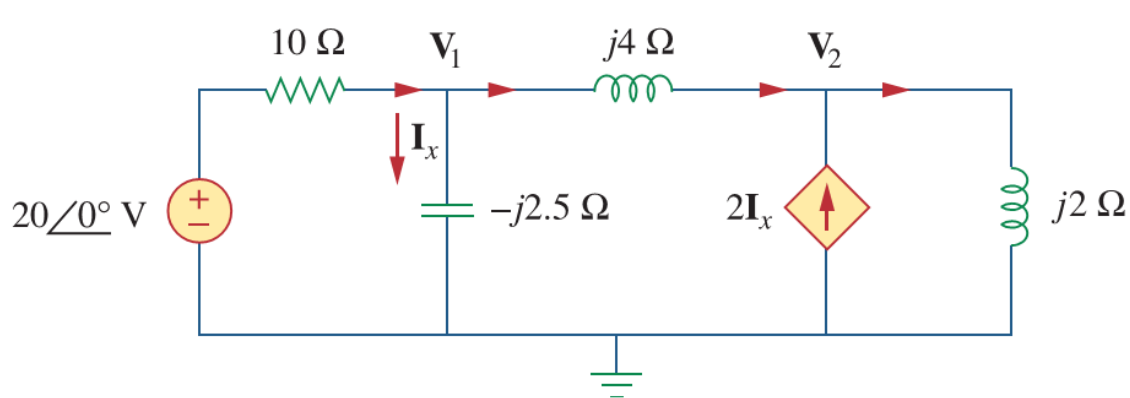
$$2\mathbf{I}_x + \frac{\mathbf{V}_1 - \mathbf{V}_2}{j4} = \frac{\mathbf{V}_2}{j2}$$



$$\frac{20 - \mathbf{V}_1}{10} = \frac{\mathbf{V}_1}{-j2.5} + \frac{\mathbf{V}_1 - \mathbf{V}_2}{j4}$$
$$2\mathbf{I}_x + \frac{\mathbf{V}_1 - \mathbf{V}_2}{j4} = \frac{\mathbf{V}_2}{j2}$$

$$i_x = 7.59 \cos(4t + 108.4^\circ) \text{ A}$$



Example 6

- There is no initial energy stored in this circuit. Find $i(t)$ if
- $v(t) = e^{-0.6t} \sin 0.8t$ V.