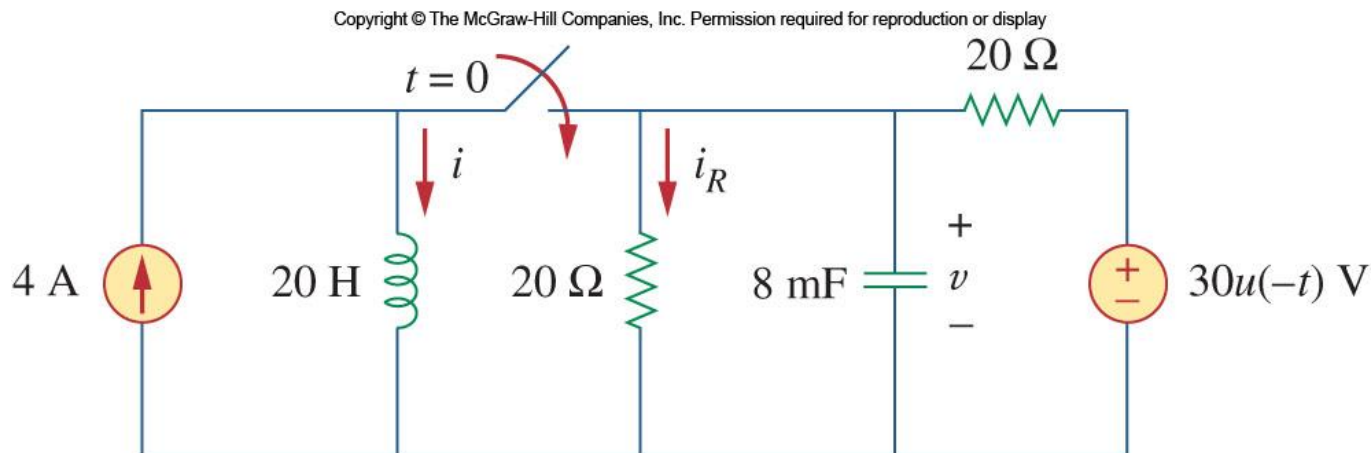





## Example

- Find  $i(t)$  and  $i_R(t)$  for  $t > 0$ .






## Example

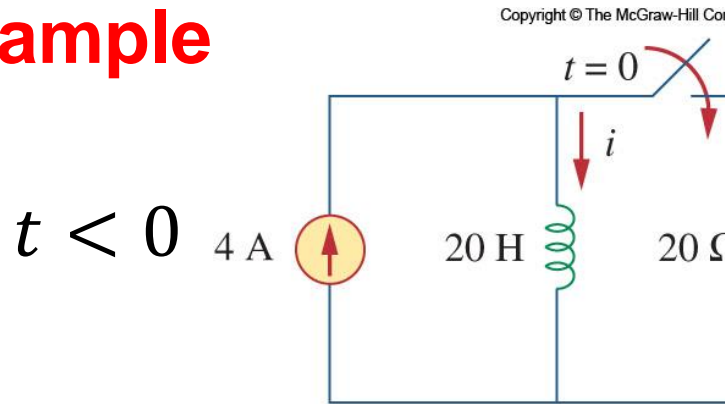


Initial values :  $i(0^+) = 4A$

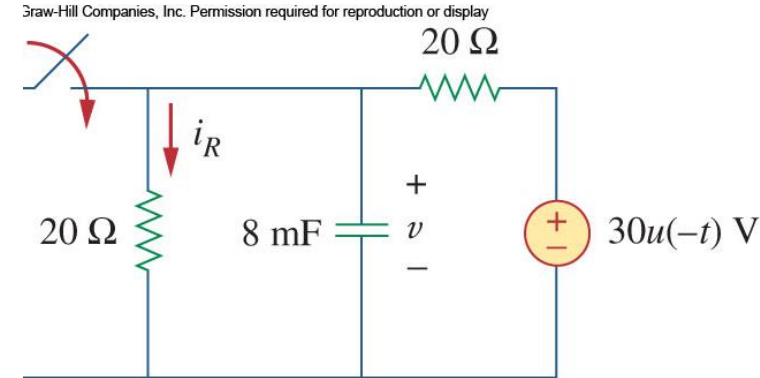

$$v(0^+) = \frac{20}{20 + 20} \times 30V = 15V$$


$t = 0^+$

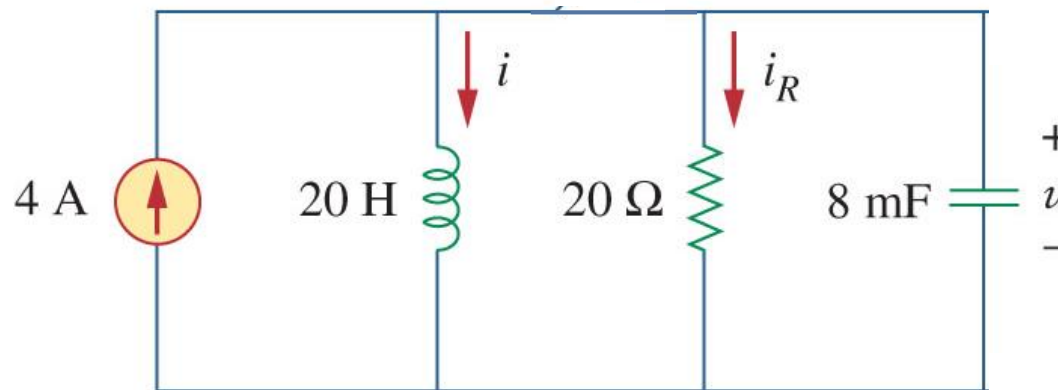

$$v(0^+) = 15V = L \frac{di(0^+)}{dt}$$



$$t = 0^+$$

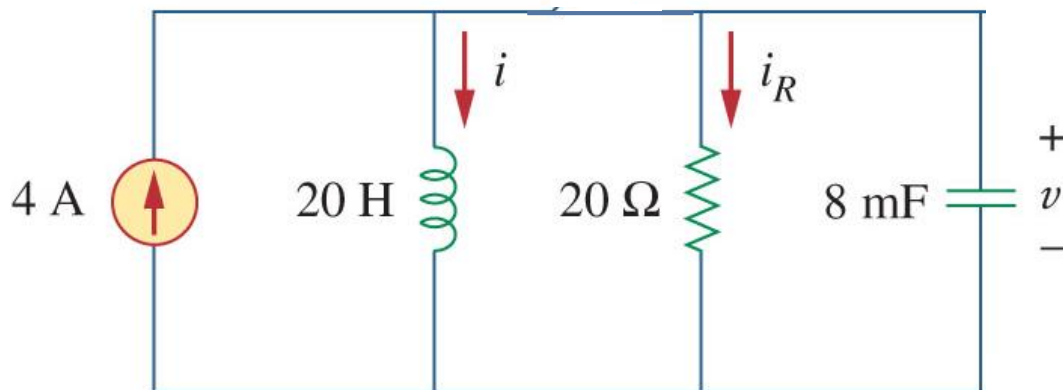

$$\text{For } t > 0, \alpha = \frac{1}{2RC} = \frac{1}{2 \times 10 \times 8 \times 10^{-3}} = 6.25, \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{20 \times 8 \times 10^{-3}}} = 2.5$$

$$s_{1,2} = -6.25 \pm 5.7282$$

$$i(t) = I_{s.s.} + A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

Apply

$$i(0^+) = 4A$$
$$\frac{di(0^+)}{dt}$$





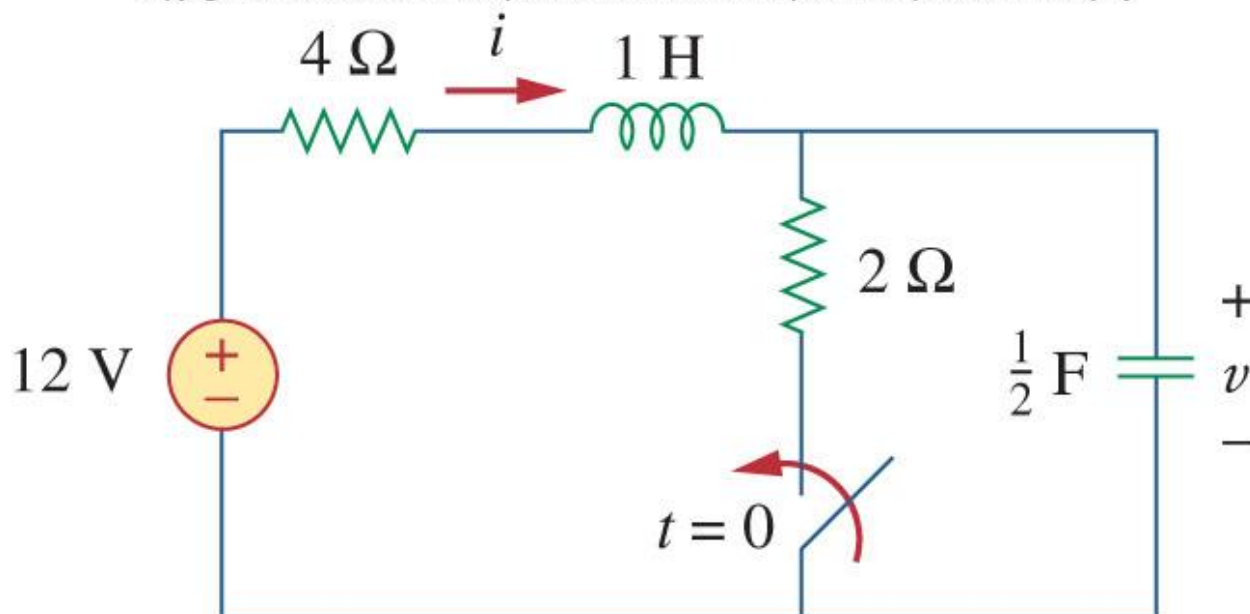
# General Second-Order Circuits

- An example

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display





## General Second-Order Circuits

- The principles of solving the series/parallel forms of RLC circuits can **be applied/extended** to **general second-order circuits**, by taking the following six steps:

1. First determine the initial conditions,  $x(0)$  and  $dx(0)/dt$ .

2. Applying KVL and KCL, to find a **general second-order differential equation** about  $x(t)$ .

Then solve the equation:

3. Depending on the roots of C.E. , the form of general solution  $x_{g.s.}(t)$  **(3 cases)** of homogeneous equation can be determined.

4. We obtain the **particular solution** by observation/calculation, **specially** for a DC/step response  $x_{p.s.}(t) = x(\infty)$

5. The complete response = general solution + particular solution.

$$x(t) = x_{P.S.}(t) + x_{G.S.}(t)$$

6. Using the initial conditions to determine the constants of  $x(t)$ .



$x(t)$  = unknown variable (voltage or current)

**Differential equation:**

$$x'' + ax' + bx = c$$

**Initial conditions:**

$$x(0) \text{ and } x'(0)$$

**Final condition:**

$$x(\infty) = \frac{c}{b}$$

$$\alpha = \frac{a}{2}$$

$$\omega_0 = \sqrt{b}$$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

**Overdamped Response**  $\alpha > \omega_0$

$$x(t) = [A_1 e^{s_1 t} + A_2 e^{s_2 t} + x(\infty)]$$




# General RLC Circuits


- Find the complete response  $v(t)$  for  $t > 0$  in the circuit.
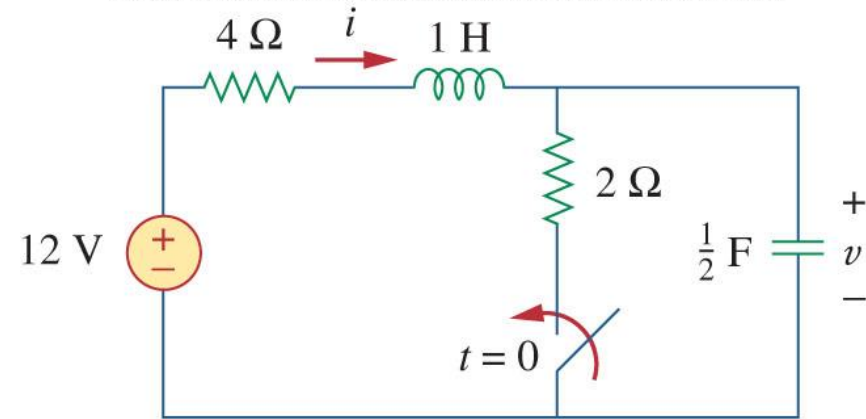
## 1. Initial conditions

$$v(0^+) = v(0^-) = 12V, i(0^+) = i(0^-) = 0$$



$t = 0$

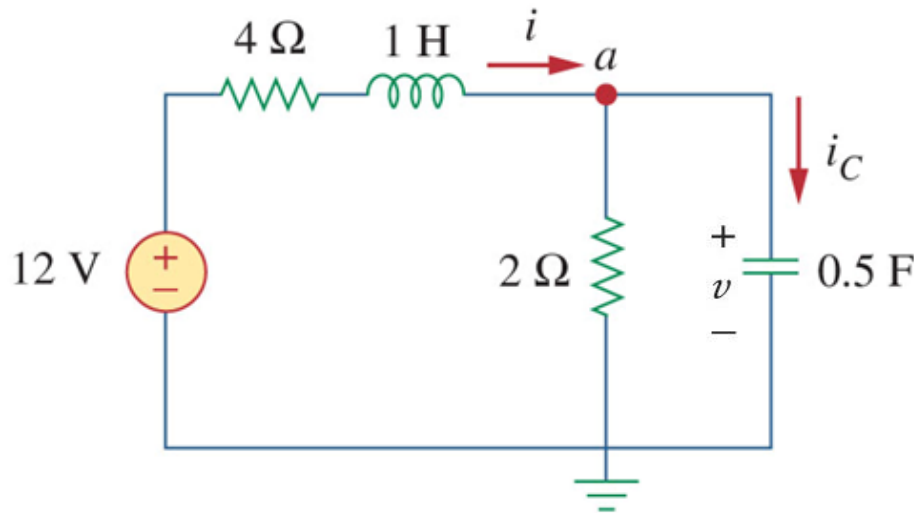



$$\frac{dv(0^+)}{dt} = \frac{i_C(0^+)}{C} = \frac{-12/2}{0.5} = -12 V/s$$




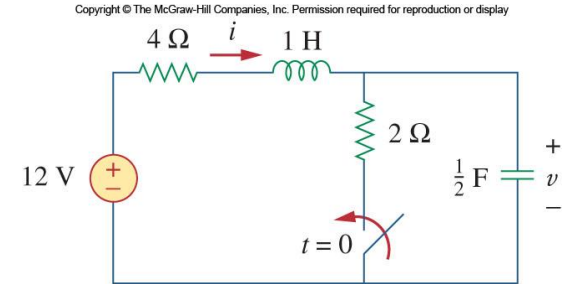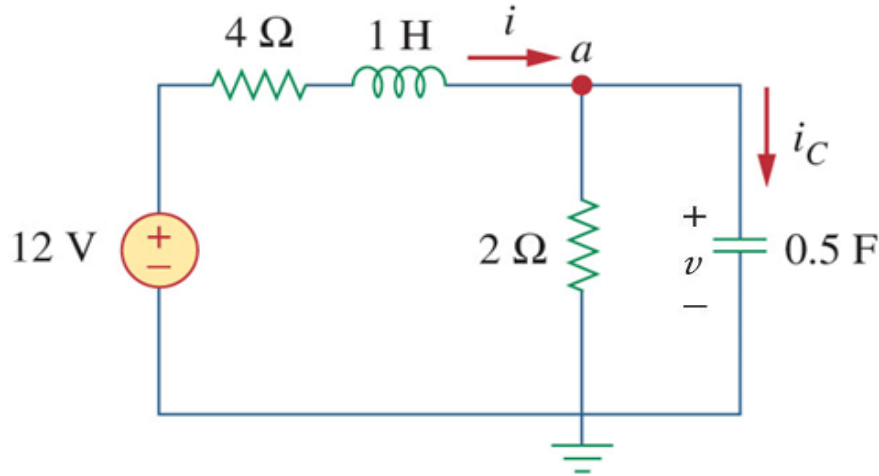
# General RLC Circuits

- Find the complete response  $v(t)$  for  $t > 0$



- To find a **general** second-order differential equation about  $x(t)$



$$\frac{d^2v}{dt^2} + 5 \frac{dv}{dt} + 6v = 24$$

3. General Solution:

➡ General Solution  $v_t(t) = A_1 e^{-2t} + A_2 e^{-3t}$


4. Particular Solution : Steady-state response  $v_{ss}(t) = 4V$

5. Put together :  $v(t) = 4 + A_1 e^{-2t} - A_2 e^{-3t}$

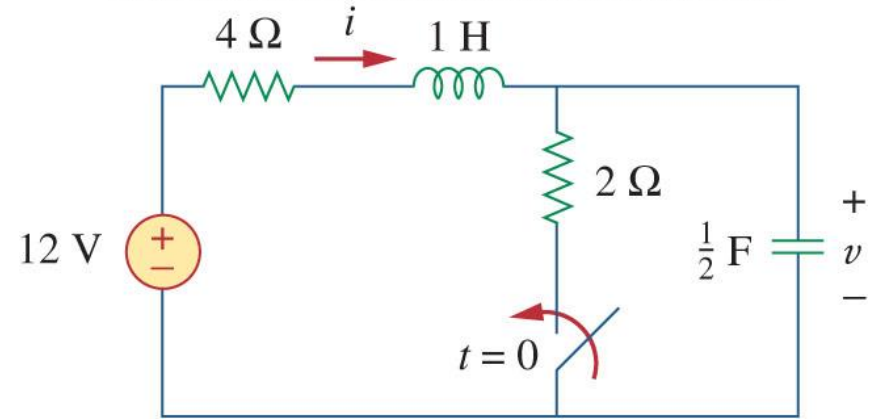6. Using initial conditions to determine  $A_1$  ,  $A_2$



- Use mesh analysis method to find the complete response  $i(t)$  for  $t > 0$  in the circuit.





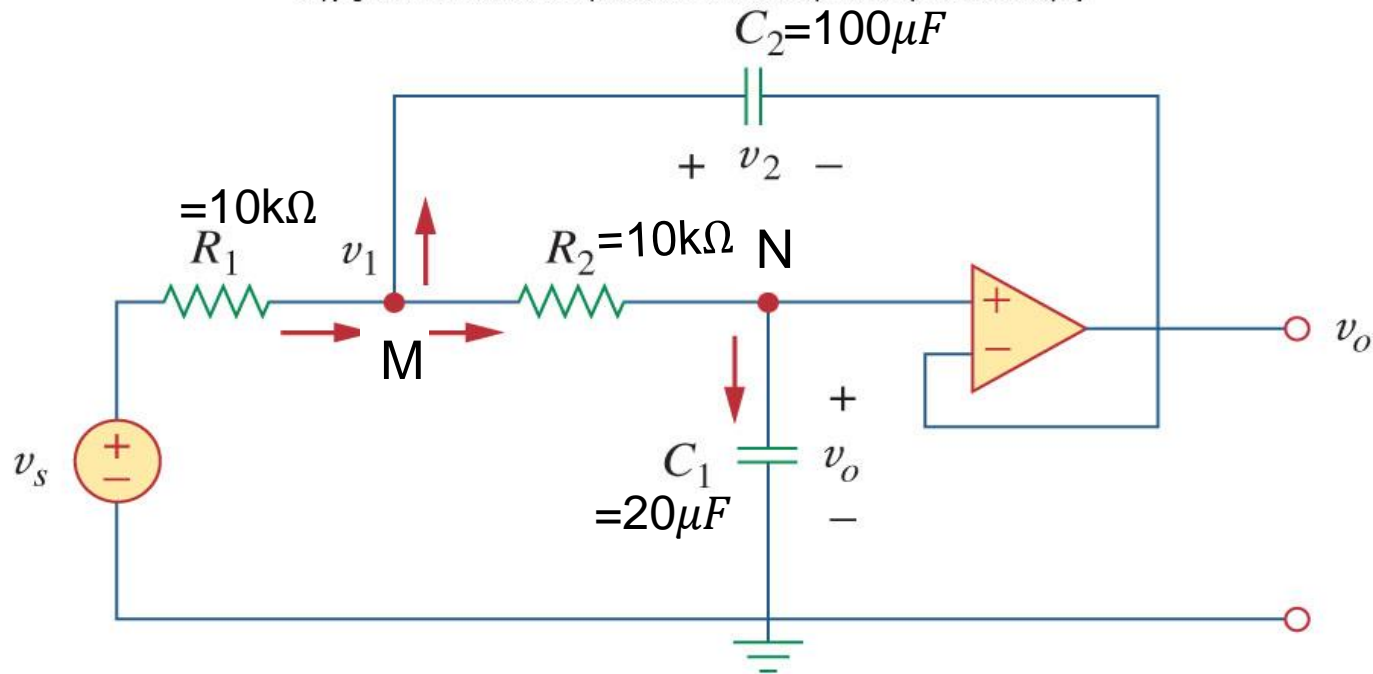
## Example of 2<sup>nd</sup>-order op-amp circuits

- Find  $v_o$  for  $t > 0$   
when  $v_s = 10u(t)\text{mV}$ .

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display




$$\text{Initial conditions: } v_o(0^+) = 0, C_1 \frac{dv_o(0^+)}{dt} = \frac{v_1(0^+) - v_o(0^+)}{R_2} = \frac{v_2(0^+)}{R_2} = 0$$


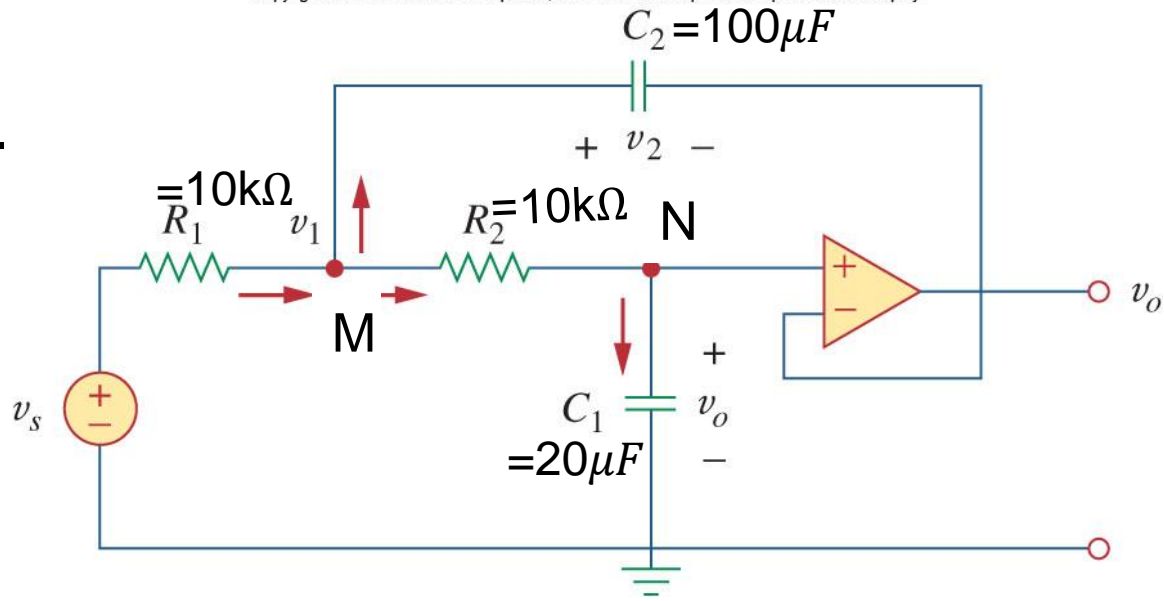
## Example of 2<sup>nd</sup>-order op-amp circuits

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display

- Find  $v_o$  for  $t > 0$   
when  $v_s = 10u(t)mV$ .



KCL at node M:

$$\frac{v_s - v_1}{R_1} = C_2 \frac{dv_2}{dt} + \frac{v_1 - v_o}{R_2}$$

KCL at node N:

$$C_1 \frac{dv_o}{dt} = \frac{v_1 - v_o}{R_2}$$

and we have  $v_1 - v_2 = v_o$

$$\Rightarrow \frac{d^2 v_o}{dt^2} + \left( \frac{1}{R_1 C_2} + \frac{1}{R_2 C_2} \right) \frac{dv_o}{dt} + \frac{v_o}{R_1 R_2 C_1 C_2} = \frac{v_s}{R_1 R_2 C_1 C_2}$$

