



Outline


- Linearity property
- Superposition
- Thevenin's theorem
- Norton's theorem
- Source transformation
- Power transfer




Norton's Theorem

Norton's theorem states that all linear circuits can be simplified to an equivalent circuit with a single current source in parallel with a single resistor connected to a load.

Norton equivalent
circuit

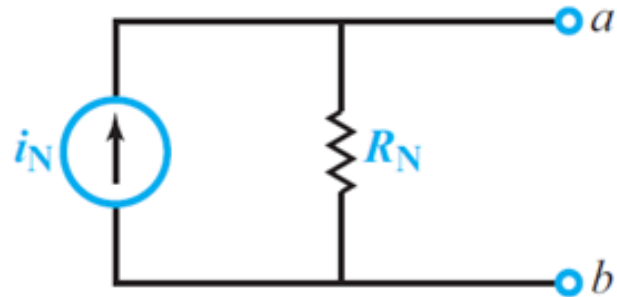


Source Transformation

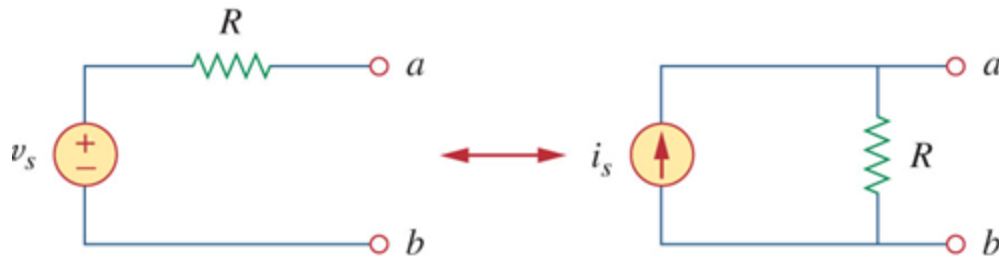

- A source transformation is the process of replacing “a voltage source v_s in series with a resistor R ” **by** “a current source i_s in parallel with a resistor R ”, or vice versa. $V_s/i_s = R$
- These transformations work because the two sources have equivalent behavior at their terminals:
 - If the sources are turned off, resistance at the terminals are both R
 - If the terminals are short circuited, the currents is the same.




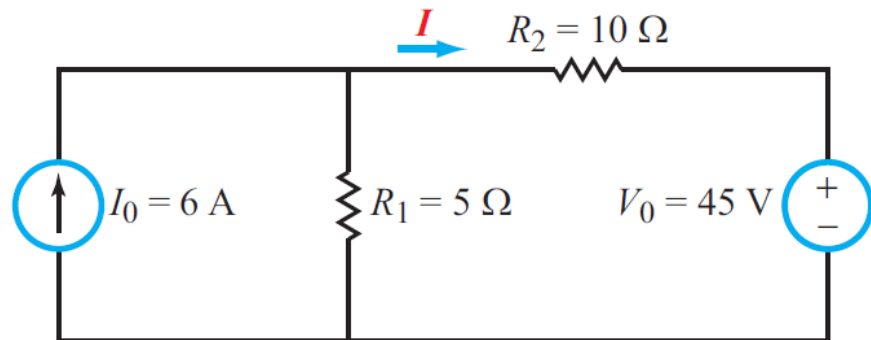- Q1: If $R_2 = 1\Omega$, $I = ?$
- Q2: What if $R_2 = 5\Omega$?







Max Power Transfer

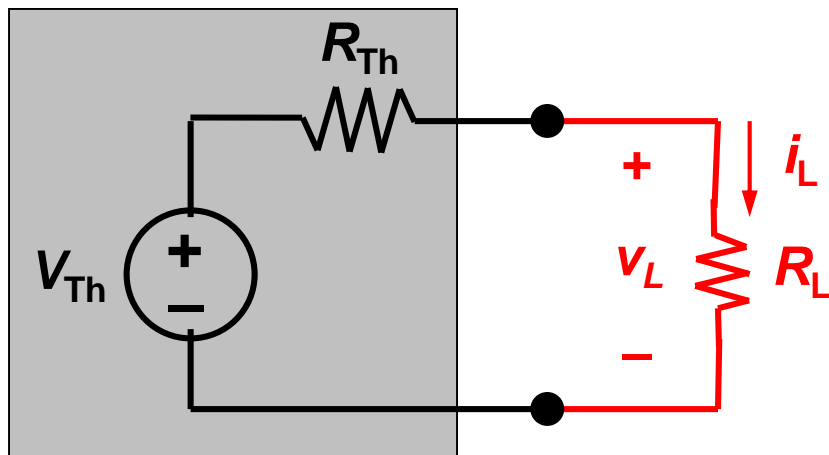

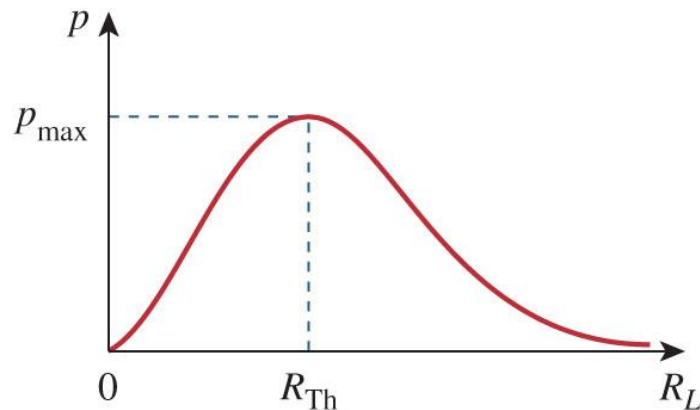Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



Example

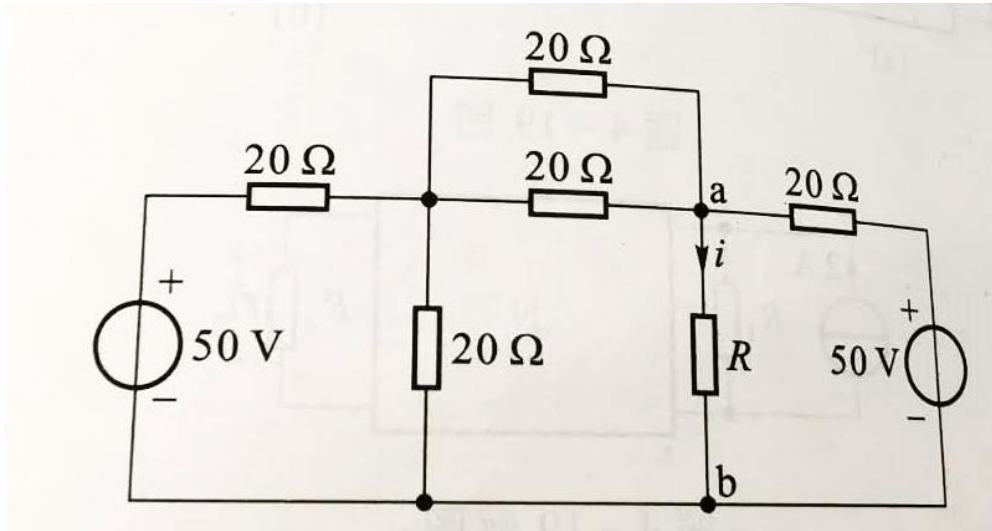

- (1) Calculate the value of R , at which maximum power transferred to R holds.
- (2) Calculate the percentage/ratio: P_R/P_{total}