





# Steps in Applying the Laplace transform

- Transform the circuit from the time domain to the Laplace ( $s$ ) domain, including initial conditions.  
--The elegance of using the Laplace transform in circuit analysis lies in (1) transforming the differential equation into an *algebraic* equation; and (2) automatic inclusion of initial conditions in the transformation process, thus providing a complete (**transient and steady-state**) solution.
- Solve the circuit using nodal analysis, mesh analysis, source transformation, superposition, or any other analysis technique with which we are familiar.
- Take the inverse transform of the solution and thus obtain the solution in the time domain.


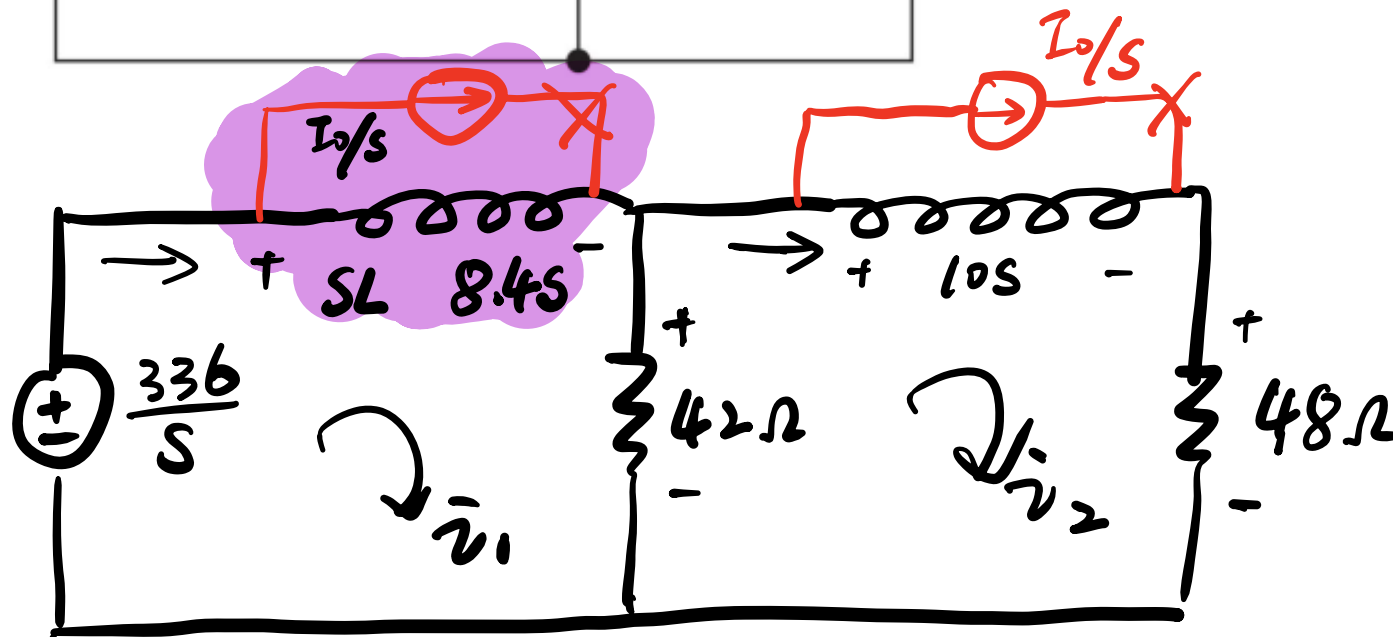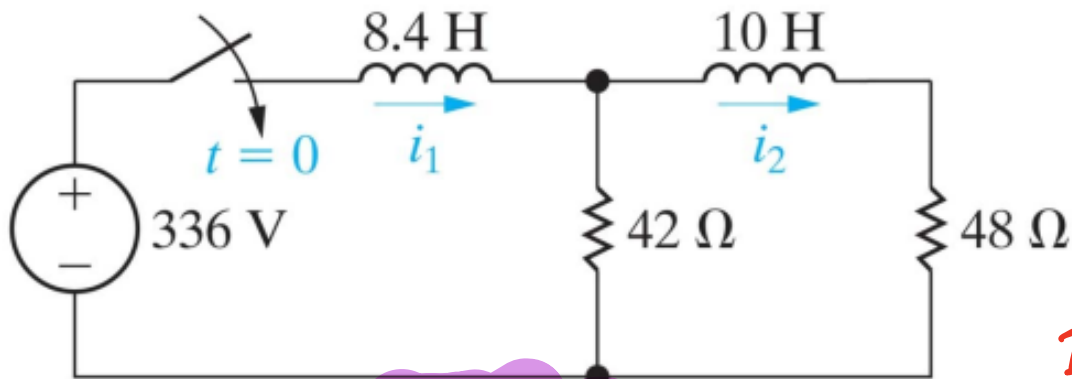
## Example 1

Assuming no initial energy storage, find  $i_1(t)$  and  $i_2(t)$  for  $t > 0$ .



$$\frac{336}{s} = 8.4s \cdot \dot{v}_1 + 42(v_1 - v_2) \quad (1)$$

$$42(v_1 - v_2) = 10s \cdot \dot{v}_2 + 48v_2 \quad (2)$$

By (2)  $v_1 = \frac{10s + 48}{42} \dot{v}_2$

$$\dot{v}_2 = \frac{168}{s^3 + 14s^2 + 24s} = \frac{168}{s(s+2)(s+12)}$$

$$= \frac{k_1}{s} + \frac{k_2}{s+2} + \frac{k_3}{s+12}$$

$$\frac{168}{s(s+2)(s+12)} \cdot s = \frac{k_1 \cdot s}{s} + \frac{k_2 \cdot s}{s+2} + \frac{k_3 \cdot s}{s+12}$$

$$k_1 = \frac{168}{(s+2)(s+12)} \Big|_{s=0} = 7$$

$$k_2 = -8.4 \quad k_3 = 1.4$$

$$\dot{v}_2 = \frac{7}{s} + \frac{-8.4}{s+2} + \frac{1.4}{s+12} \quad \text{S. Domain}$$


$$\hookrightarrow \dot{v}_2(t) = [7 + (-8.4 \cdot e^{-2t}) + 1.4e^{-12t}] \underline{u(t)} \quad \underline{A.}$$

$$\hat{v}_1 = \frac{90+10s}{42} \cdot \frac{168}{s^3+14s^2+24s}$$

$$= \frac{40s+360}{\underline{s^3+14s^2+24s}} = \frac{k_1'{}^{15}}{s} + \frac{k_2'{}^{-14}}{s+2} + \frac{k_3'{}^{-1}}{s+12}$$

$$\hat{v}_1^{-1} \\ \hat{v}_1(t) = (15 - 14e^{-2t} - e^{-12t}) u(t) \quad \underline{A.}$$

T.D. ↻

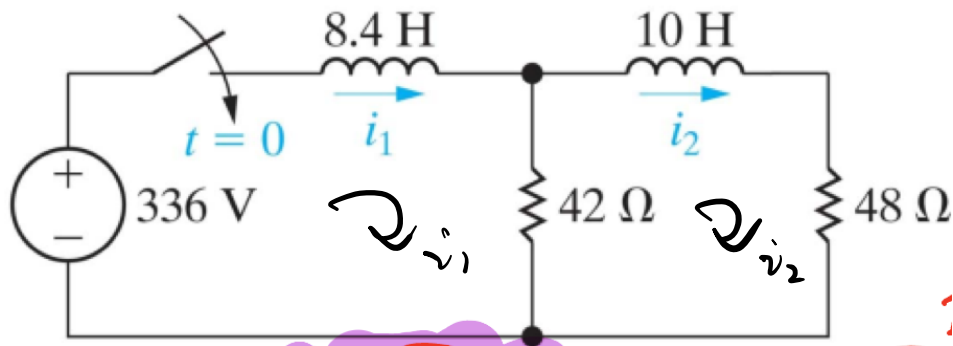

$$336 = 8.4 \frac{dv_1}{dt} + 42(v_1 - v_2) \quad \textcircled{1}$$

$$42(v_1 - v_2) = 10 \frac{dv_2}{dt} + 48v_2 \quad \textcircled{2}$$

By ②  $42v_1 = 10 \frac{dv_2}{dt} + 90v_2$

$$\ddot{z}_2 + 14\dot{z}_2' + 24z_2 = 168$$

---

$$S^2 + 14S + 24 = 0$$

$$\text{C.E. } (S+2)(S+12) = 0$$

---




# Steps in Applying the Laplace transform

- Transform the circuit from the time domain to the Laplace ( $s$ ) domain, including initial conditions.  
--The elegance of using the Laplace transform in circuit analysis lies in (1) transforming the differential equation into an *algebraic* equation; and (2) automatic inclusion of initial conditions in the transformation process, thus providing a complete (**transient and steady-state**) solution.
- Solve the circuit using nodal analysis, mesh analysis, source transformation, superposition, or any other analysis technique with which we are familiar.
- Take the inverse transform of the solution and thus obtain the solution in the time domain.




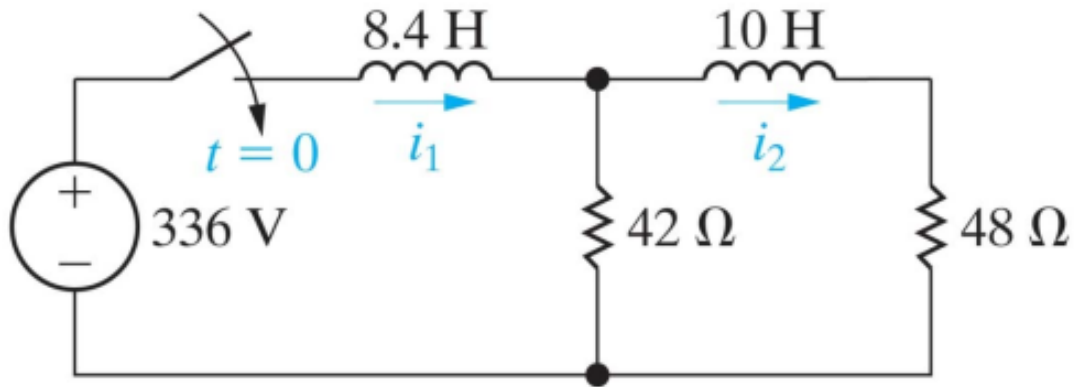
## Example 1

Assuming no initial energy storage, find  $i_1(t)$  and  $i_2(t)$  for  $t > 0$ .


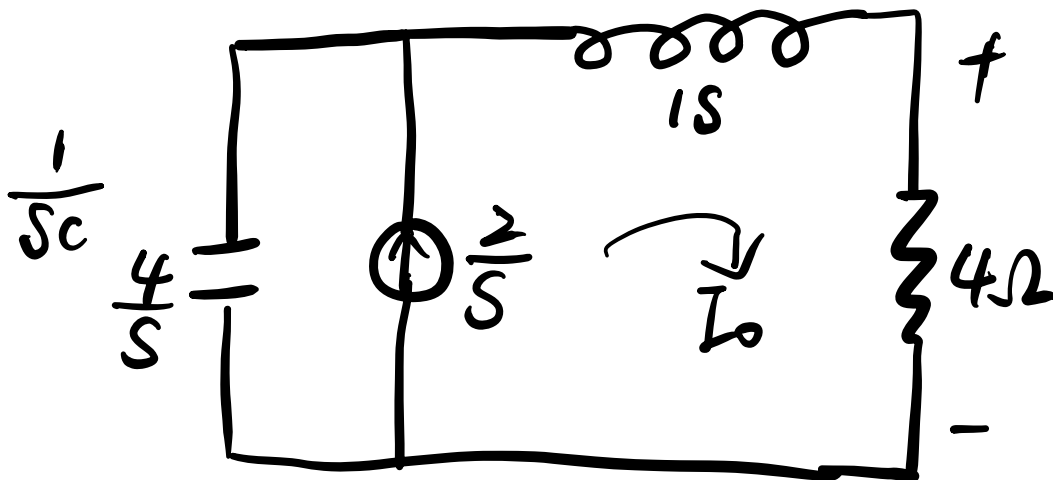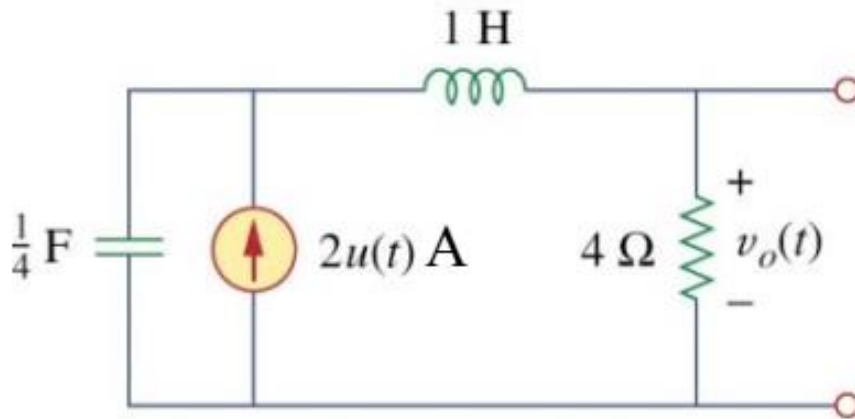
## Example 2

Determine  $v_o(t)$  for  $t > 0$  assuming zero initial conditions:







$$I_o(s) = \frac{\frac{4}{s}}{\frac{4}{s} + s + 4} \times \frac{2}{s} = \frac{8}{s(s+2)^2}$$

$$V_o(s) = I_o(s) \cdot 4 = \frac{32}{s(s+2)^2}$$

$$= \frac{A^8}{s} + \frac{B^{-8}}{\underbrace{s+2}} + \frac{C^{-16}}{(s+2)^2}$$


$$B = \left[ V_o(s) \cdot (s+2)^2 \right]' \bigg|_{s=-2} = \left( \frac{32}{s} \right)' = -\frac{32}{s^2} = -8$$



$$V(t) = \underbrace{(8 - 8 \cdot e^{-2t} - 16t \cdot e^{-2t})}_{\text{T.S.}} u(t)$$
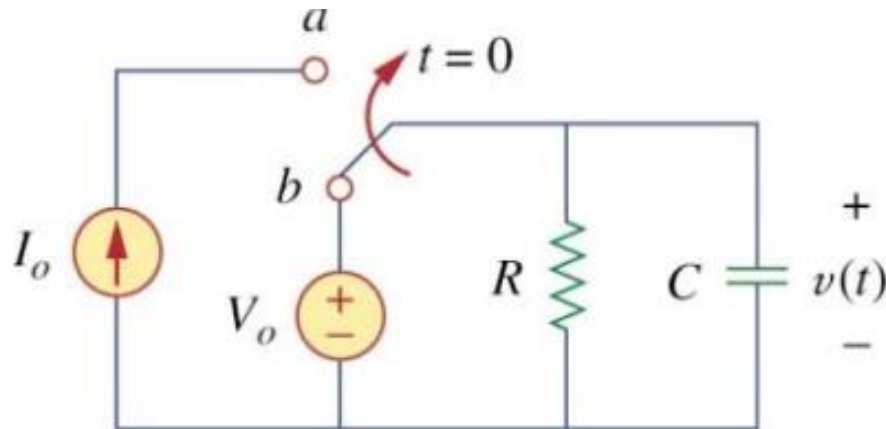
## Example 3


- The switch has been in position  $b$  for a long time. It is moved to position  $a$  at  $t = 0$ . Determine  $v(t)$  for  $t > 0$ .


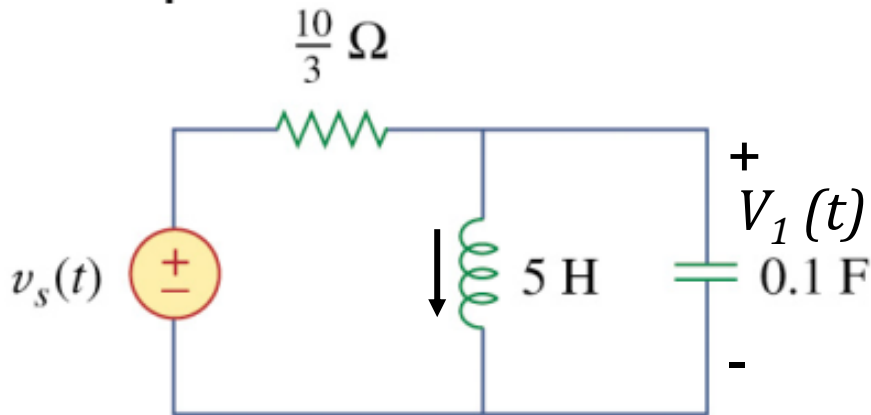
## Example 4

- Find (1) the voltage across the capacitor  
(2) current through the inductor



assuming that  $v_s(t) = 10u(t)$  V, and assume that at  $t = 0$ ,  $-1$  A flows through the inductor and +5 V is across the capacitor.


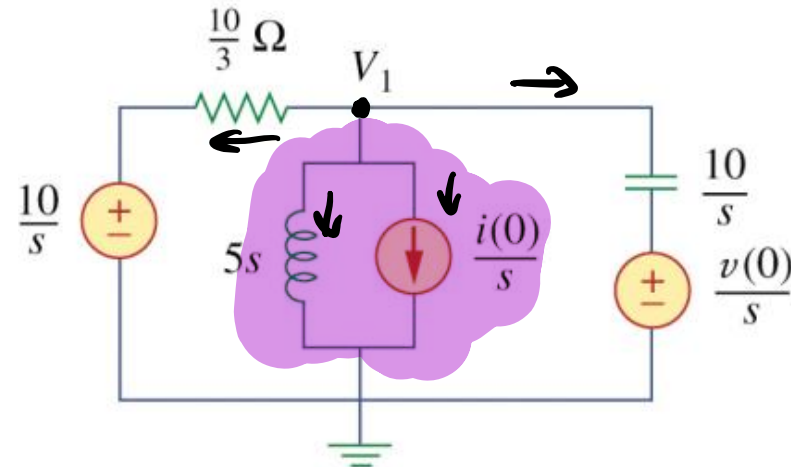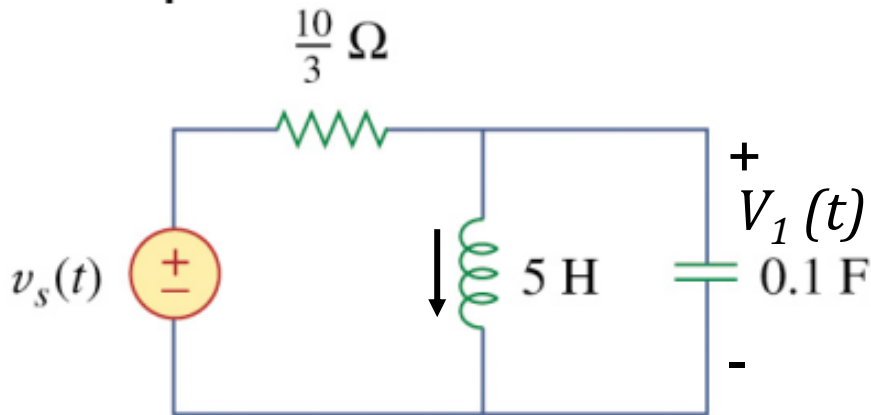
## Example 4

- Find (1) the voltage across the capacitor  
(2) current through the inductor

assuming that  $v_s(t) = 10u(t)$  V, and assume that at  $t = 0$ ,  $-1$  A flows through the inductor and  $+5$  V is across the capacitor.



$$\frac{V_1 - \frac{10}{s}}{\frac{10}{3}} + \frac{V_1 - 0}{5s} + \frac{-1}{s} + \frac{V_1 - \frac{5}{s}}{10/s} = 0$$

$$V_1 = \frac{40 + 5s}{(s+1)(s+2)} = \frac{35}{s+1} - \frac{30}{s+2}$$



$$V_1(t) = (35 \cdot e^{-t} - 30 e^{-2t}) u(t) \quad V$$

$$\tilde{i}_L(s) = \frac{V_1}{5s} + \frac{-1}{s} \quad \leftarrow$$


$$= \frac{40 + 5s}{5s(s+1)(s+2)} - \frac{1}{s}$$

$$= \frac{3}{s} - \frac{7}{s+1} + \frac{3}{s+2}$$

$$i_L(t) = (3 - 7 \cdot e^{-t} + 3 \cdot e^{-2t}) u(t) \quad A.$$
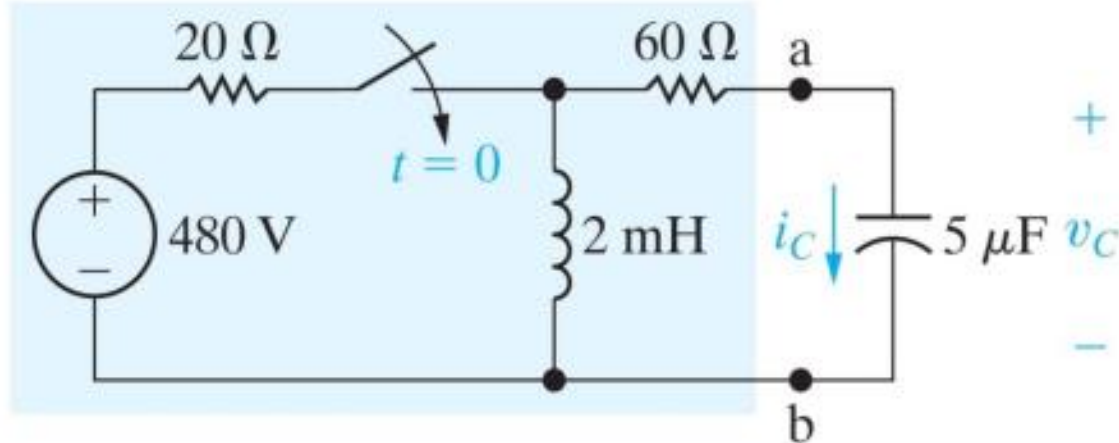
## Example 5

- Use Thevenin's equivalent circuit w.r.t. terminals  $a$ - $b$  to find current  $i_C(t)$  for  $t > 0$ .




## Example 6

- Find  $v_o(t)$  for  $t > 0$

$$V_c(0) = V_o = 0 \text{ V}$$

$$v_L(0) = I_o = 0.2 \text{ A}$$

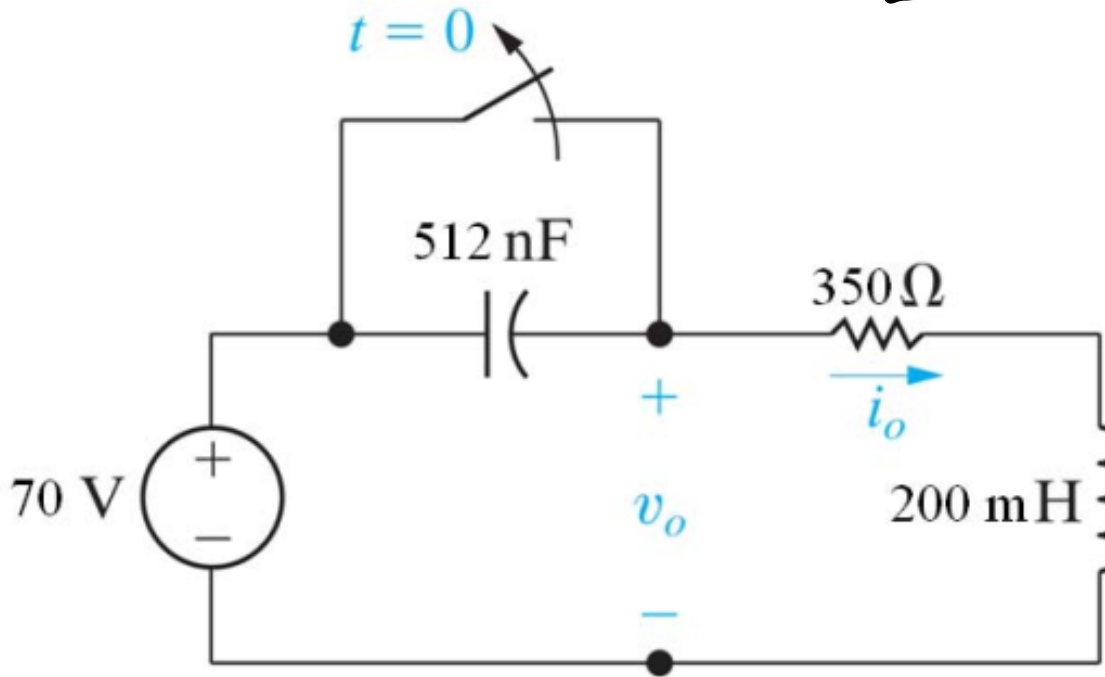

$$\alpha = \frac{R}{2L}$$



$$875$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$= -875 \pm 3000j$$



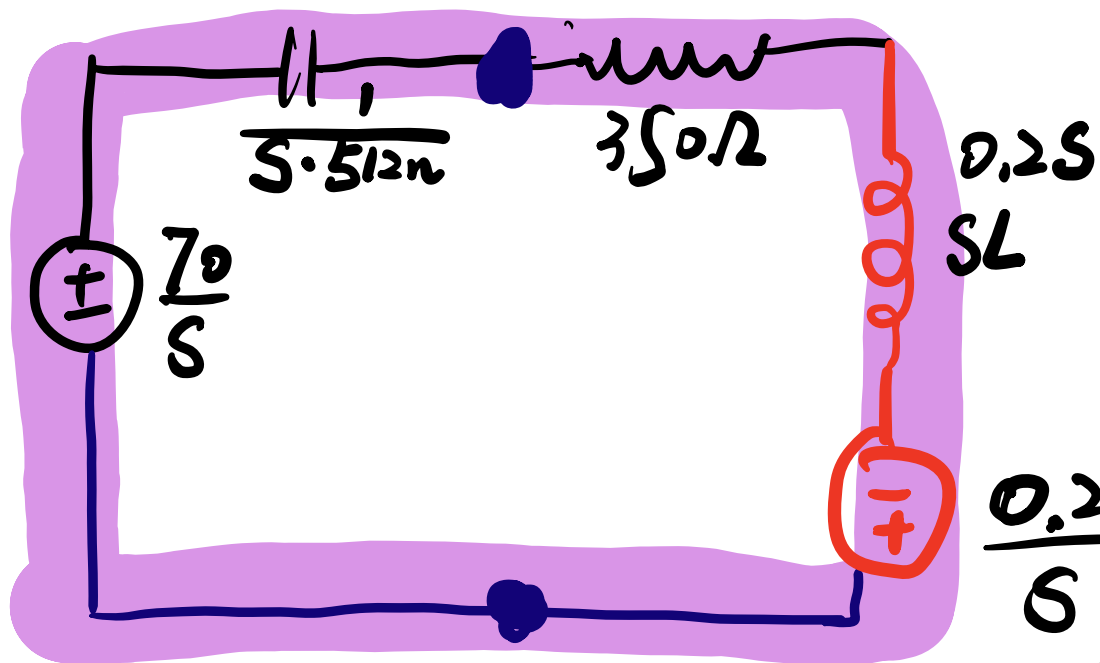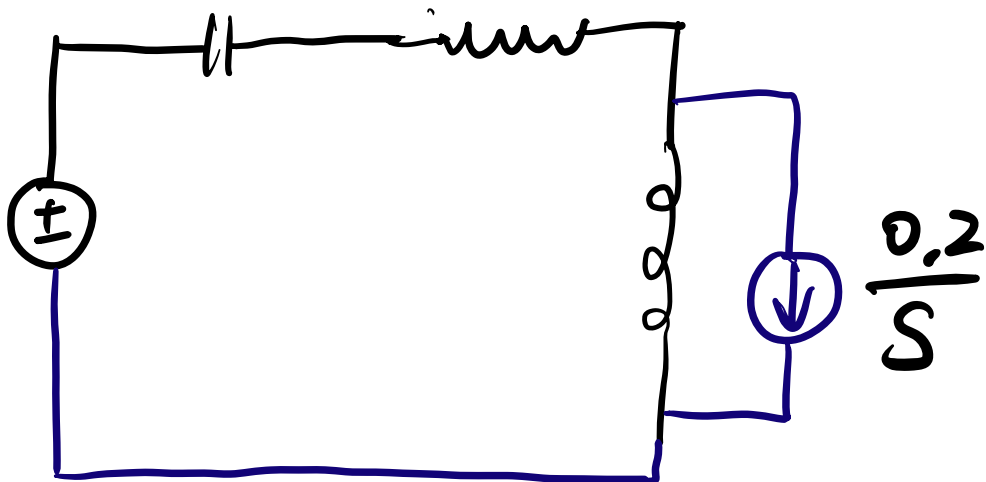

$$\frac{0.2}{S} \times 0.2S = 0.04$$



$$s - (\alpha + j\omega)$$

$$V_0(s) = \frac{70s - 268,125}{s^2 + 1750s + 9,765,625} = \frac{K_1}{(s + 875 - j3000)} + \frac{K_2}{(s + 875 + j3000)}$$

$$K_1 = \left. \frac{70s - 268,125}{(s + 875 + j3000)} \right|_{s=-875+j3000} = \frac{70(-875 + j3000) - 268,125}{[(-875 + j3000) + 875 + j3000]} = 65.1 \angle 57.48^\circ$$

$$K_2 = \left. \frac{70s - 268,125}{(s + 875 - j3000)} \right|_{s=-875-j3000} = \frac{70(-875 - j3000) - 268,125}{[(-875 - j3000) + 875 - j3000]} = 65.1 \angle -57.48^\circ$$


$$V_0(s) = \frac{65.1 \angle 57.48^\circ}{(s + 875 - j3000)} + \frac{65.1 \angle -57.48^\circ}{(s + 875 + j3000)}$$


$$v_0(t) = 2(65.1)e^{-875t} \cos(3000t + 57.48^\circ) = 130.2e^{-875t} \cos(3000t + 57.48^\circ)u(t) \text{ V}$$

$\uparrow$   $\uparrow$   $\uparrow$   $\uparrow$   
 $16.1$   $\alpha$   $\omega$   $\phi_k$

## Example 7

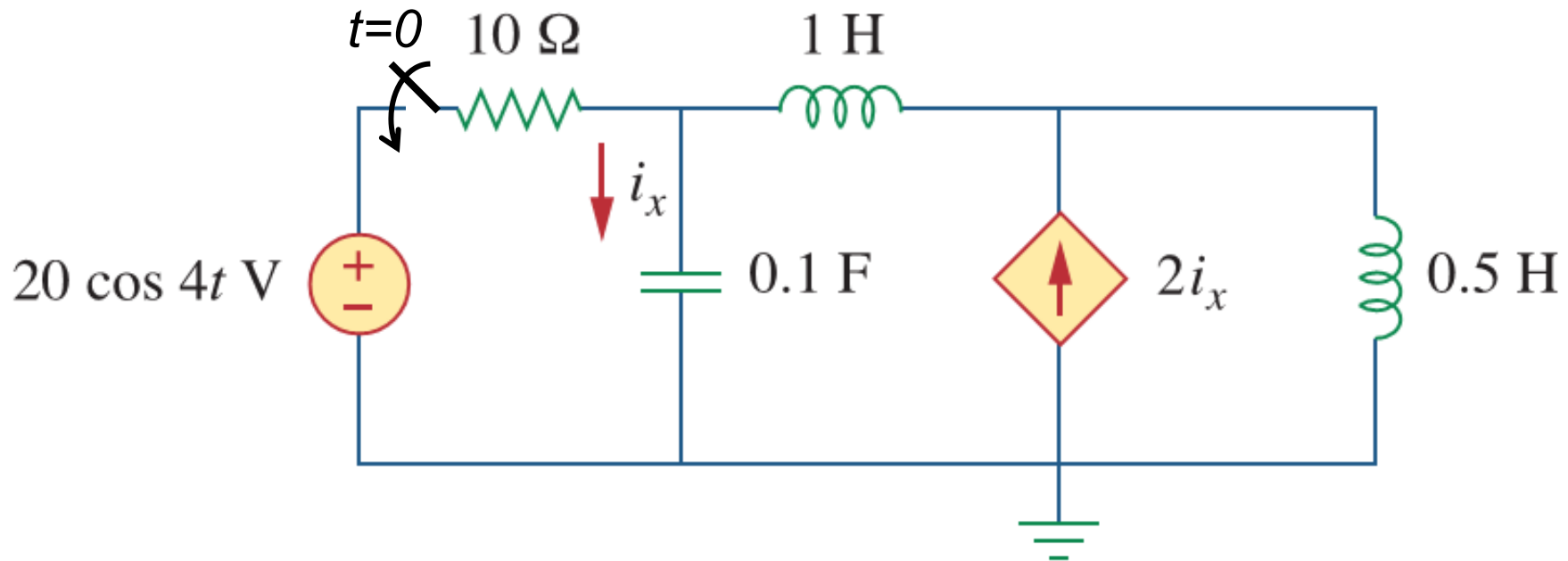
- Example---Find  $i_x$  (s.s.) assuming no initial energy stored  
**Using phasor method and Laplace transform method**



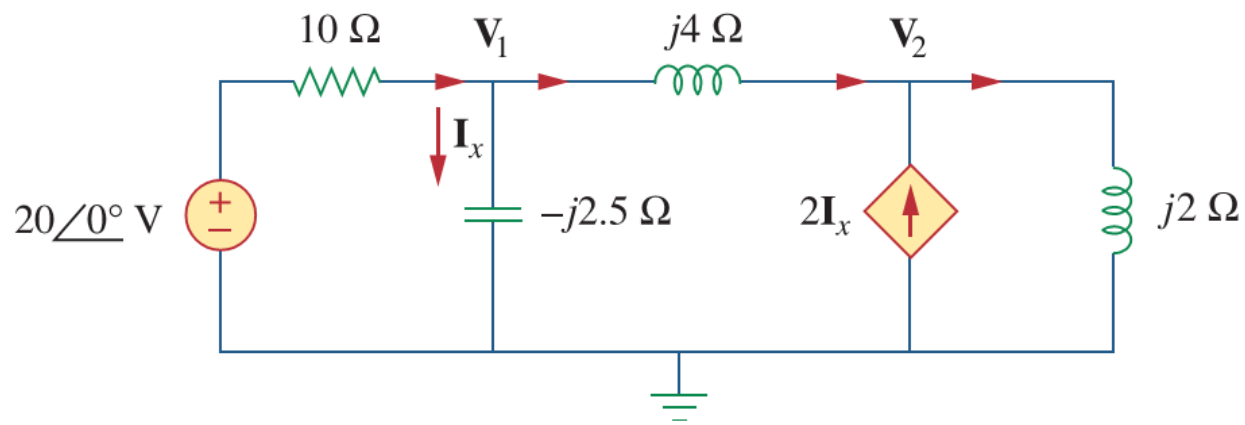



$$\frac{20 - \mathbf{V}_1}{10} = \frac{\mathbf{V}_1}{-j2.5} + \frac{\mathbf{V}_1 - \mathbf{V}_2}{j4}$$
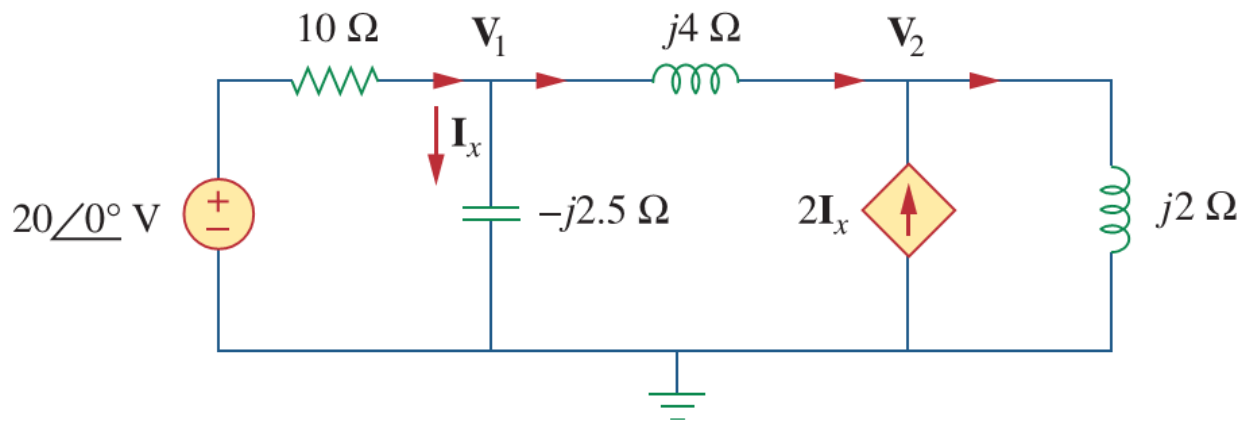
$$2\mathbf{I}_x + \frac{\mathbf{V}_1 - \mathbf{V}_2}{j4} = \frac{\mathbf{V}_2}{j2}$$



$$\frac{20 - V_1}{10} = \frac{V_1}{-j2.5} + \frac{V_1 - V_2}{j4}$$
$$2\mathbf{I}_x + \frac{V_1 - V_2}{j4} = \frac{V_2}{j2}$$
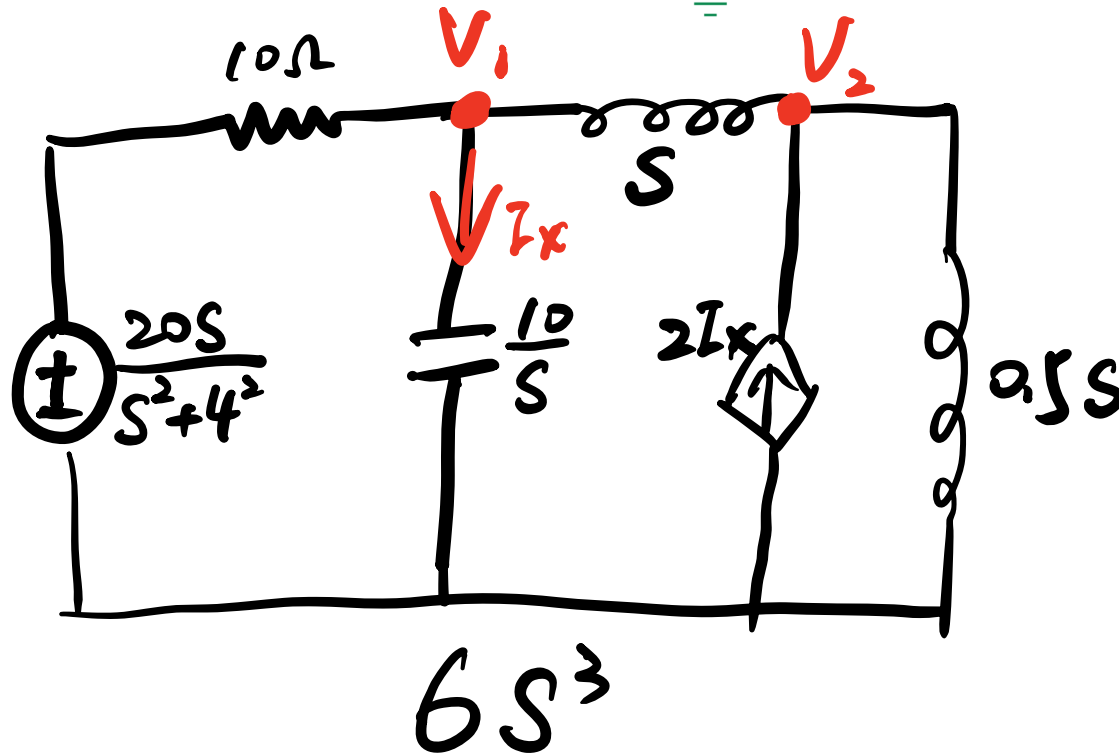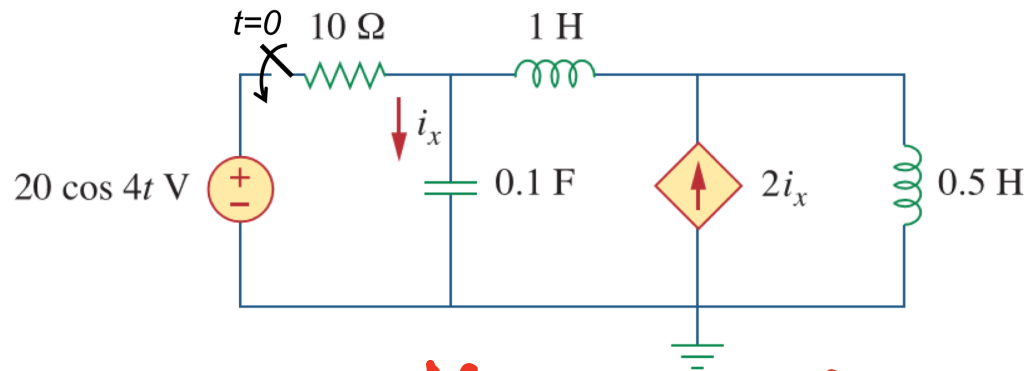
$$i_x = 7.59 \cos(4t + 108.4^\circ) \text{ A}$$



$$I_x = \frac{20s}{(s^2 + 4^2)(s^2 + 3s + 20)}$$



$$\underline{I}_x = \underbrace{\frac{k_1}{s-4j} + \frac{k_1^*}{s-(-4j)}}_{\text{Red wavy line}} + \underbrace{\frac{k_2}{s-(-1.5+4.2j)} + \frac{k_2^*}{s-(-1.5-4.2j)}}_{\text{Blue wavy line}}$$

$$\alpha_1 = 0 \quad \omega_1 = 4$$

$$\alpha_2 = -1.5 \quad \omega_2 = 4.2$$

$$k_1 = 3.79 \angle 108.43^\circ$$

$$k_2 = 5.0 \angle -146.2^\circ$$

$$\begin{aligned} \underline{i}_x(t) &= \left[ 2|k_1| e^{\alpha_1 t} \cos(\omega_1 t + \varphi_{k_1}) + 2|k_2| e^{\alpha_2 t} \cos(\omega_2 t + \varphi_{k_2}) \right] u(t) \\ &= \left[ 7.58 \cos(4t + 108.43^\circ) + 10 e^{-1.5t} \cos(4.2t - 146.2^\circ) \right] u(t) \end{aligned}$$