

Homework 2

Due date: Oct. 31st, 2023

Turn in your hard-copy hand-writing homework in class


Rules:

- Work on your own. Discussion is permissible, but extremely similar submissions will be judged as plagiarism.
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.

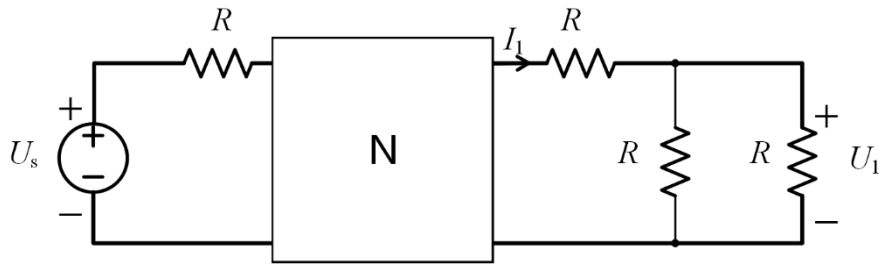1. N is a linear resistive network with sources inside.


When $U_s = 6\text{V}$, $I_1 = 1\text{A}$, $U_1 = 2\text{V}$; When $U_s = 10\text{V}$, $I_1 = 2\text{A}$.

Use linear property to find I_1 and U_1 if $U_s = 12\text{V}$.



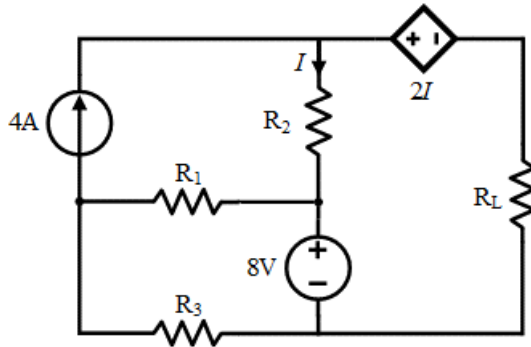
2. $R_1=R_2=2\Omega$, $R_3=1\Omega$, $R_L=2\Omega$

- Calculate the current of R_L when an independent current source acts alone.
- Calculate the current of R_L when an independent voltage source acts alone.
- Calculate the current on R_L using the superposition theorem.




3. (a) Apply superposition to find U_0 in the circuit below when $R_L=250\Omega$.

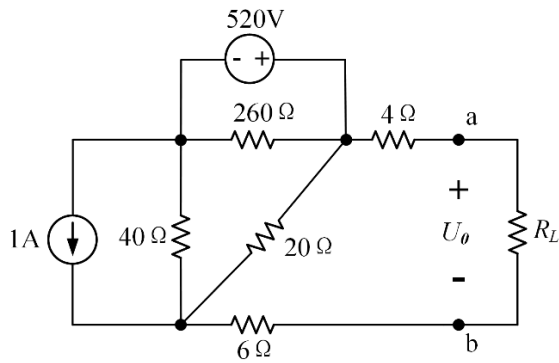(b) Find the Thevenin equivalent circuit for the left hand side circuit of node a and node b.




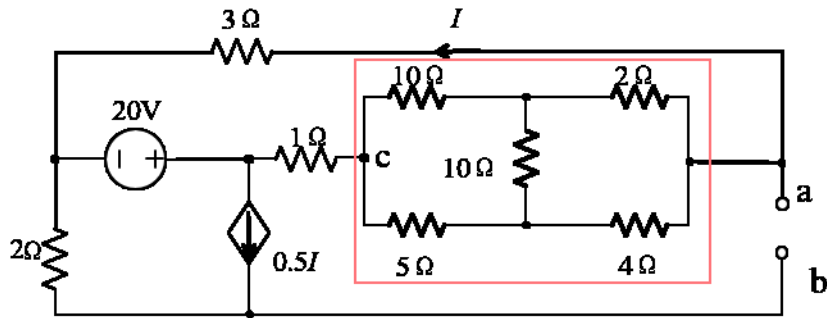4. a. Find the equivalent resistance inside rectangle drawn with red lines.
b. Find the Thevenin equivalent circuit between node **a** and **b**




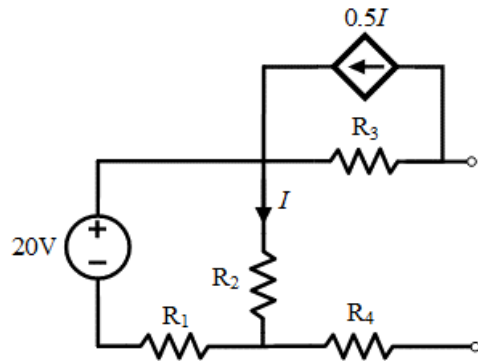5. $R_1 = R_2 = R_3 = R_4 = 4\Omega$.

Find the Norton equivalent circuit of the two port network.



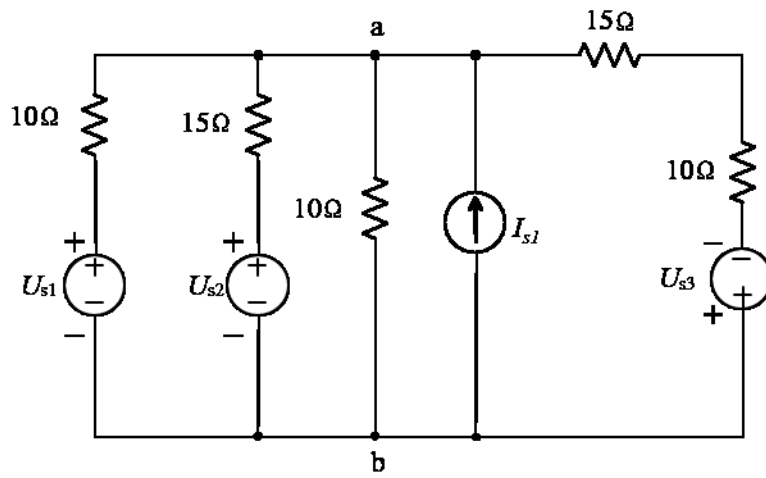6. $U_{s1} = 20\text{V}$, $U_{s2} = 15\text{V}$, $U_{s3} = 25\text{V}$, $I_{s1} = 1\text{A}$, using source transfer to calculate U_{ab}



7. $R_1 = 2\Omega$, $R_2 = 6\Omega$, $R_3 = 1\Omega$

- Determine the value of R_L when maximum power could be transferred to it, and calculate the maximum power P_{RL} .
- Calculate the ratio of P_{RL} to the output power of the independent voltage source.

