

Homework 4

Due date: Nov. 14th, 2023


Turn in your hard-copy hand-writing homework to Room 324 #3 SIST

信息学院 3 号楼 324

Rules:


- Work on your own. Discussion is permissible, but extremely similar submissions will be judged as plagiarism.
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.

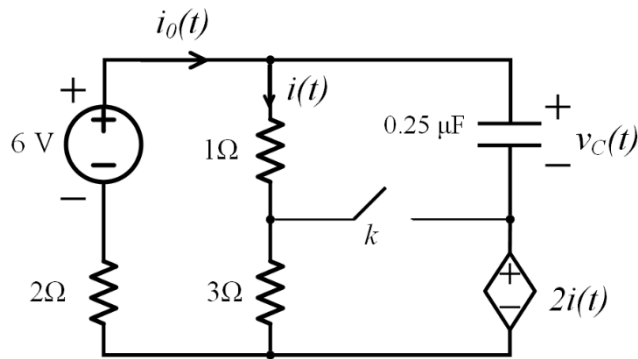1. For the circuit below, the switch has been open for a long time. The switch is closed at $t = 0$ s immediately. Determine $i_o(t)$, $i(t)$ and $v_C(t)$ in the circuit for $t > 0$.



$$1. \quad t < 0. \quad i = \frac{6}{1+1+3} = 1 \text{ A} \quad v_C(0^-) = (1+3)i - 2i = 2 \text{ V}$$
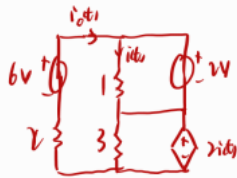
$$t = 0^+ \quad v_C(0^+) = v_C(0^-) = 2 \text{ V}$$



$$i(0^+) = \frac{2}{1} = 2 \text{ A}$$

$$2 + 2i(0^+) + 2i(0^+) = 6 \text{ V} \Rightarrow i(0^+) = 0 \text{ A}$$

$t \rightarrow \infty$



$$i(\infty) = i(0^+)$$

$$2 \times 1 + 2i + 2i = 6 \text{ V} \quad i = 1.1 \text{ A}$$

$$i(\infty) = i(0^+) = 1.1 \text{ A}$$



$$\begin{cases} v = 1 \cdot i' \\ (1' - i') \cdot 3 = 2i' + v \end{cases}$$

$$\Rightarrow \frac{v}{i'} = 0.4 \Omega$$


$$R_{eq} = 0.4 \Omega$$

$$\tau = R_{eq}C = 0.15 \mu\text{F} \times 0.4 \Omega = 10^{-7} \text{ s}$$


$$i(t) = 1.1 + 0.8e^{-10^7 t} \text{ A} \quad (t \geq 0)$$

$$i_o(t) = 1.1 - 1.2e^{-10^7 t} \text{ A} \quad (t \geq 0)$$

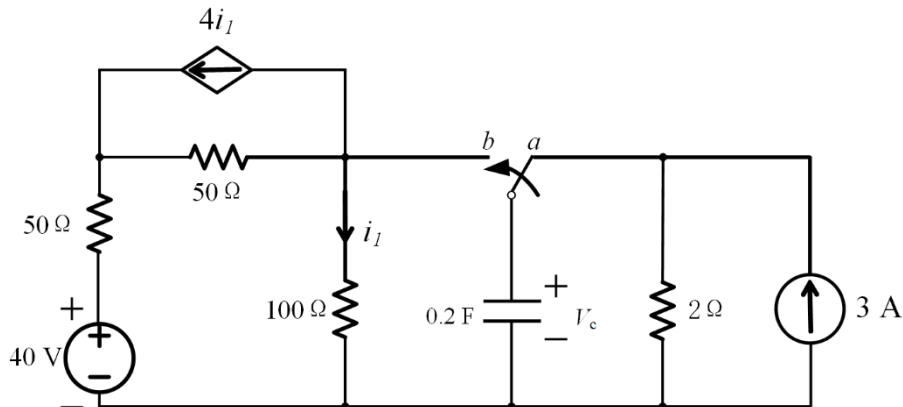
2. When $t=0$ s, the switch changes from node a to node b immediately. Assume that the circuit reaches steady state before $t=0$. Determine $v_c(t)$, in the circuit for $t > 0$.



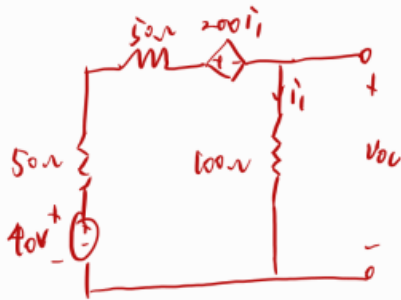$t < 0: V_{100\Omega} = 2 \times 3 = 6V$
 $t = 0: V_c(0^+) = V_c(0^-) = 6V$



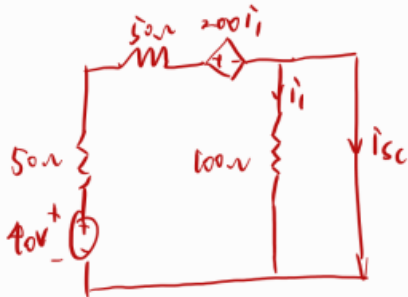$V_o = 100\Omega \times i_l = 100i_l$
 $100i_l + (50 + 50)i_l = 40 - 200i_l$
 $i_l = 0.1A$
 $V_o = 100 \times 0.1A = 10V$




$i_l = 0 \therefore i_{sc} = \frac{40}{50+50} = 0.4A$
 $R_{eq} = \frac{V_o}{i_{sc}} = \frac{10}{0.4} = 25\Omega$
 $\tau = R_{eq} \cdot C = 5s$

$V_c(\infty) = 10V$
 $\therefore V_c(t) = 10 - 4e^{-0.2t} V \quad (t > 0)$

3.

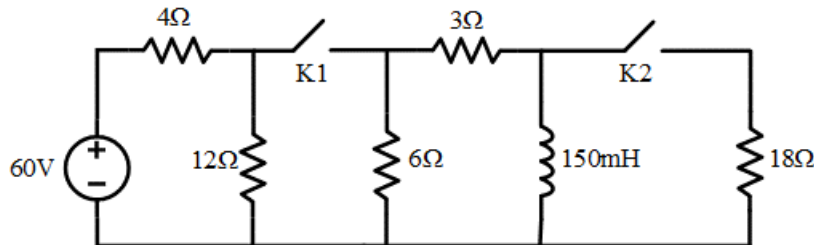- a. assuming that K1 and K2 have been closed for a long time, K1 opens at $t=0$ and K2 opens at $t=35\text{ms}$, calculate the inductance currents for $t > 0$.
- b. What is the ratio between energy consumed by the 18Ω resistor and energy stored in the inductor?



$$a. I(0) = 6\text{A}$$

当 K1 打开时:

$$R_{eq} = (2+6) \parallel 18 = \frac{9 \times 18}{9+18} = 6\Omega$$

$$\tau = \frac{L}{R} = \frac{150}{6} \times 10^{-3} = 25\text{ms}$$

$$\therefore i_L(t) = 6e^{-40t} \text{ A}, \quad 0 \leq t \leq 35\text{ms}$$

$$b. i_L(35) = 6e^{-40 \times 35 \times 10^{-3}} = 6e^{-1.4} \text{ A}$$

$$R_{eq} = 3+6 = 9\Omega, \quad \tau = \frac{L}{R} = \frac{150}{9} \times 10^{-3} = \frac{50}{3} \times 10^{-3} \text{ms}$$

$$i_L(t) = 1.48e^{-60 \times (t - 0.035)} \text{ A}, \quad t \geq 35\text{ms}$$

来自华为笔记

$$c. W_{L0} = \frac{1}{2} L I_{L0}^2 = \frac{1}{2} \times 150 \times 10^{-3} \times 36 = 2.7\text{J}$$

$$i_L(t) = 6e^{-40t} \text{ A}, \quad 0 \leq t \leq 35\text{ms}$$

$$i_{18\Omega}(t) = 6e^{-40t} \cdot \frac{9}{9+18} = 2e^{-40t}, \quad 0 \leq t \leq 35\text{ms}$$

$$p_{18\Omega}(t) = i^2 R = 4 \cdot e^{-80t} \cdot 18 = 72e^{-80t}$$


$$W_{18\Omega} = \int_0^{35\text{ms}} p_{18\Omega}(t) dt = \frac{72}{-80} e^{-80t} \Big|_0^{35\text{ms}} = 0.85\text{J}$$

$$\therefore \eta = \frac{W_{18\Omega}}{W_{L0}} = \frac{0.85}{2.7} \times 100 = 31.31\%$$

来自华为笔记

4.

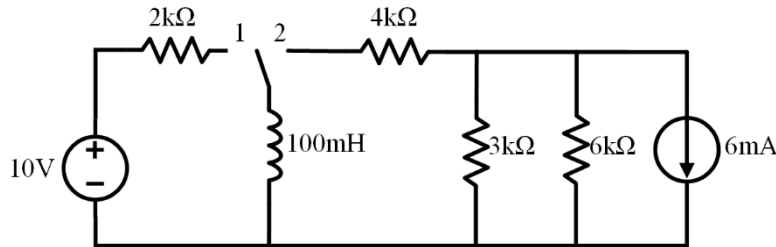- a. The switch has been placed at terminal 2 for a long time. When $t=0$, the switch is placed at terminal 1. Calculate the inductance current at $t=0.6\text{ms}$.
- b. If at $t=0.6\text{ms}$, the switch was placed back to terminal 2. Calculate the inductance current for $t > 0.6\text{ms}$.



$$\begin{aligned}
 \text{a. } I_{L(\infty)} &= \frac{6\text{mA} \cdot 2\text{k}\Omega}{4\text{k}\Omega + 2\text{k}\Omega} = 2\text{mA}, \quad R_{eq} = 2\text{k}\Omega \\
 I_{L(0)} &= -\frac{10}{2\text{k}} = -5\text{mA}, \quad \tau = \frac{L}{R_{eq}} = \frac{100\text{m}}{2\text{k}} = 5 \times 10^{-5}\text{s} \\
 i_L(t) &= I_{L(\infty)} + [I_{L(0)} - I_{L(\infty)}]e^{-\frac{t}{\tau}} = -5 + 7e^{-2 \times 10^4 t} \text{ mA}, \quad t > 0 \\
 i_L(0.6 \times 10^{-3}) &= -5 \text{ mA}
 \end{aligned}$$


$$\text{b. } I_{L(0)} = -5\text{mA}, \quad I_{L(\infty)} = 2\text{mA}, \quad R_{eq} = 6\text{k}\Omega, \quad \tau = \frac{L}{R_{eq}} = \frac{100\text{m}}{6\text{k}}$$

$$i_L(t) = 2 - 7e^{-6 \times 10^4 (t - 0.6 \times 10^{-3})} \text{ mA}, \quad t > 0.6\text{ms}$$

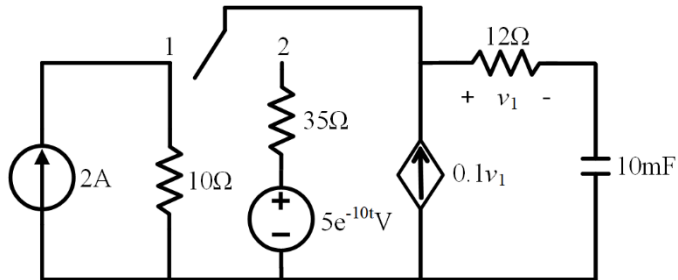5.


When $t < 0$, the switch is set to terminal 1 and the circuit reaches steady state.

When $t > 0$, the switch is set to terminal 2. Calculate the capacitance voltage for $t > 0$.



when switch is set to 1, $U_C(0) = 20V$

when switch is set to 2.

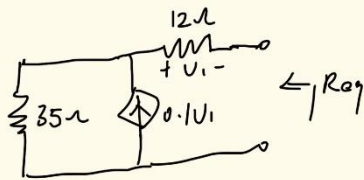

$$(i - 12i \times 0.1)35 + 12i = U$$

$$R_{eq} = \frac{U}{i} = 5\Omega, \tau = \frac{1}{20}$$

$$(12 \cdot C \frac{dU_C}{dt} + U_C) + (C \frac{dU_C}{dt} - 12C \frac{dU_C}{dt})35 = 5e^{-10t}$$

$$5C \frac{dU_C}{dt} + U_C = 5e^{-10t}$$

$$\frac{1}{20} \frac{dU_C}{dt} + U_C = 5e^{-10t}$$

$$\text{设 } U_C^* = Ae^{-10t}, \text{ 代入解得 } A = 10$$

$$\text{通解 } U_C = Be^{-\frac{t}{20}} = Be^{-20t}$$

$$\therefore U_C = 10e^{-10t} + Be^{-20t}, \text{ 由 } U_C(0) = 20 \text{ 得}$$

$$U_C = 10e^{-10t} + 10e^{-20t}, t > 0$$