





Lecture 10

- Three-Phase Circuits

Single phase vs. Polyphase

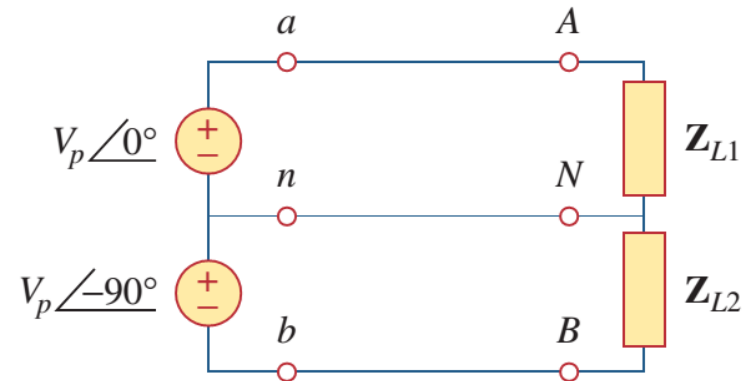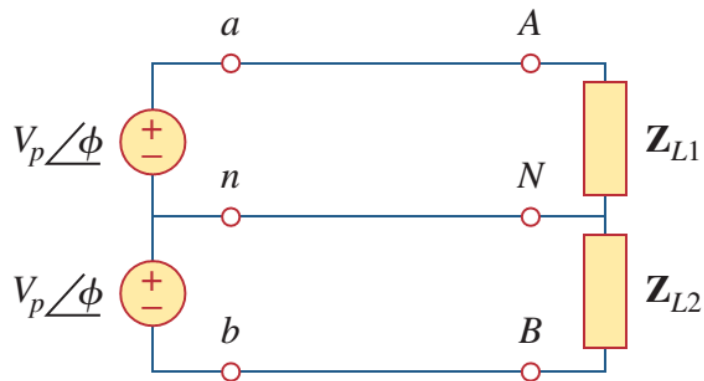- Single-phase power supply
 - For example, two 120V sources with the same phase are connected in series.
 - This allows for appliances to use either 120 or 240V
- Circuits that operate with multiple sources, at the same frequency but *at different phases* are called polyphase.






Outline--Three-Phase Circuits

- Balanced Three-Phase System
 - Balanced sources
 - Balanced loads
- Circuit analysis
 - Phase voltage/current
 - Line voltage/current


Balanced Three-Phase Sources

Connecting the Sources

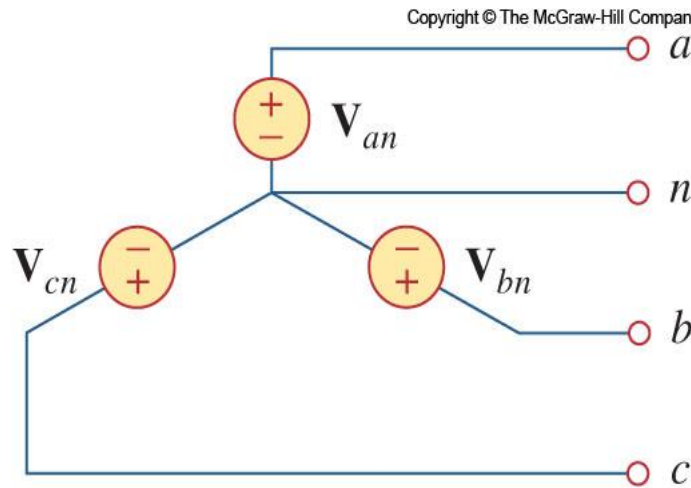- Three phase voltage sources can be connected by either four or three wire configurations.
 - Four-wire system accomplished using a Y(Wye) connected source.
 - Three-wire configuration accomplished by Delta connected source.



(a)

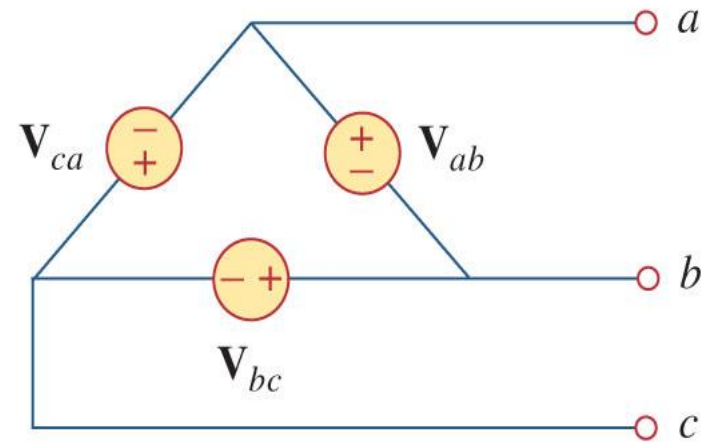

(b)


$$V_{an} = V_p \angle 0^\circ$$

$$V_{bn} = V_p \angle -120^\circ$$

$$V_{cn} = V_p \angle -240^\circ = V_p \angle +120^\circ$$

Balanced Three-Phase Sources

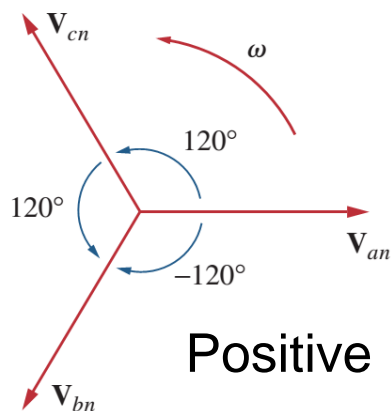
- Balanced phase voltage are equal in magnitude and are out of phase with each other by 120deg
- It's easy to know $V_{an} + V_{bn} + V_{cn} = 0$
- Two sequences for the phases:



$$V_{an} = V_p \angle 0^\circ$$

$$V_{bn} = V_p \angle -120^\circ$$
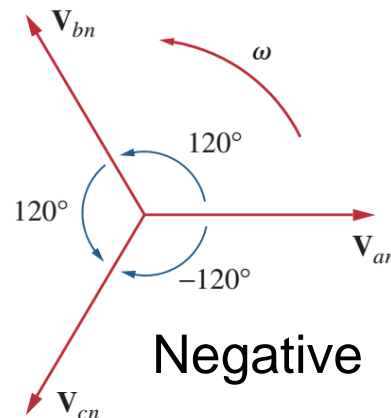
$$V_{cn} = V_p \angle -240^\circ = V_p \angle +120^\circ$$






$$V_{an} = V_p \angle 0^\circ$$

$$V_{cn} = V_p \angle -120^\circ$$

$$V_{bn} = V_p \angle -240^\circ = V_p \angle +120^\circ$$


Three-Phase Sources

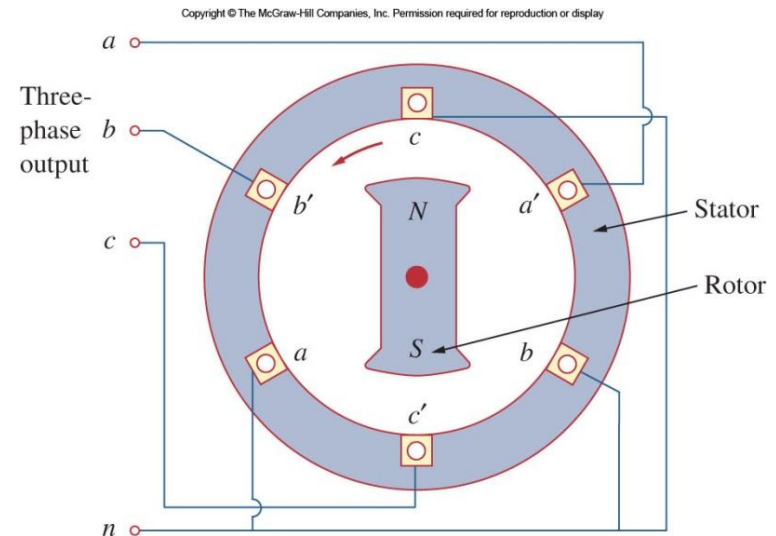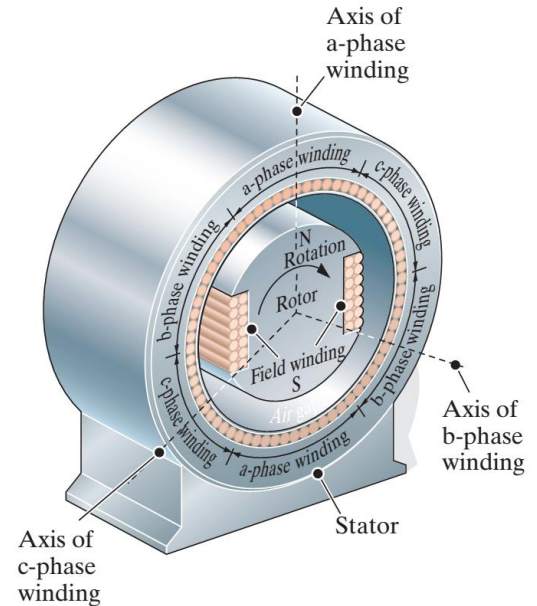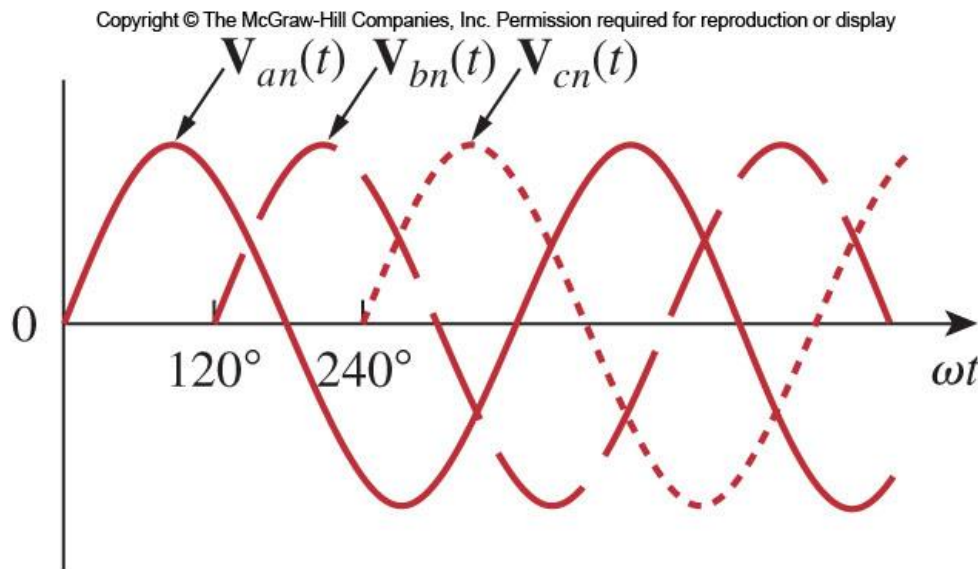- Three phase voltages are typically produced by a three-phase AC generator.
- The output voltages look like below.







Three-phase four-wire system in China

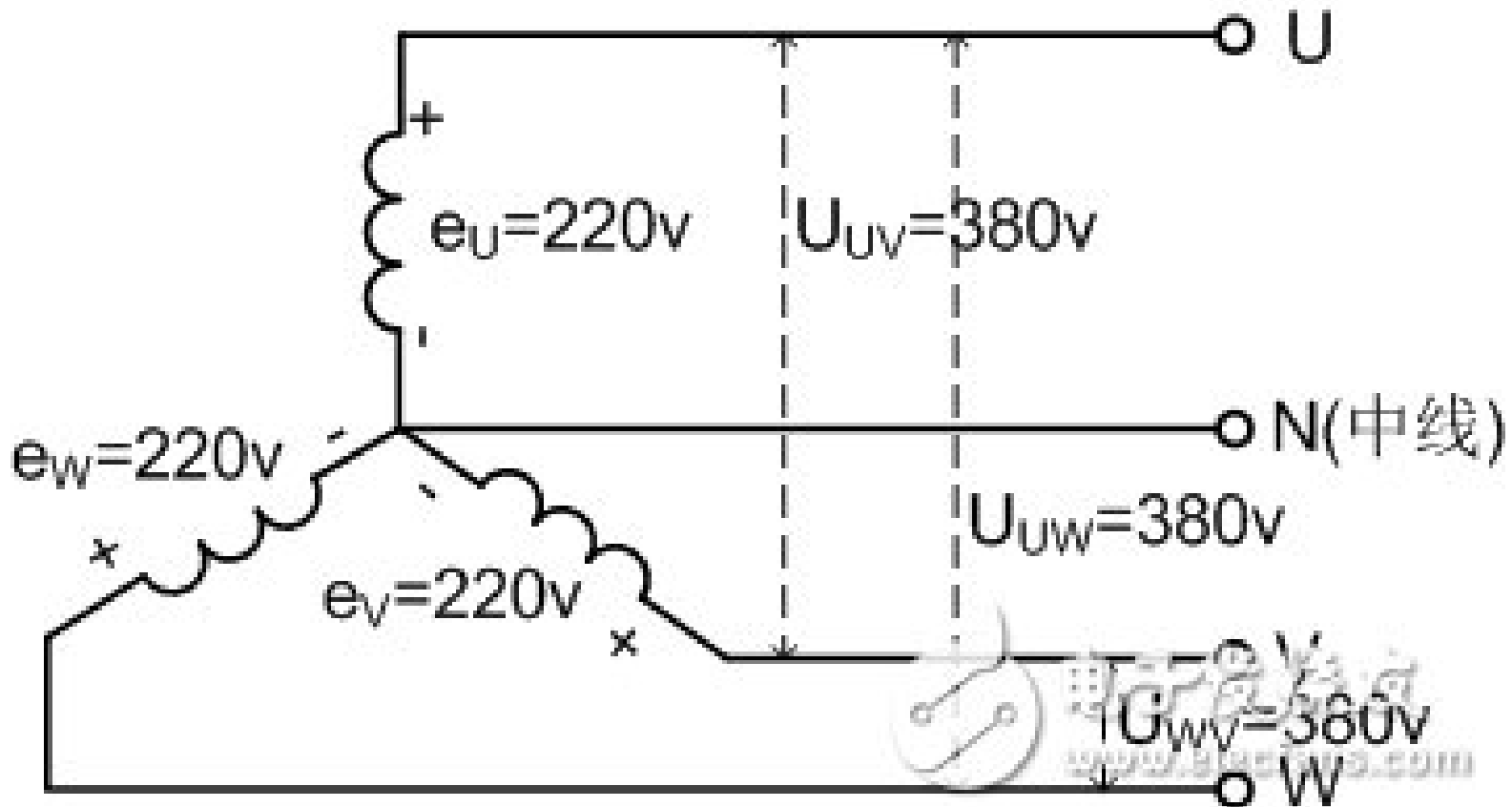

Balanced Loads

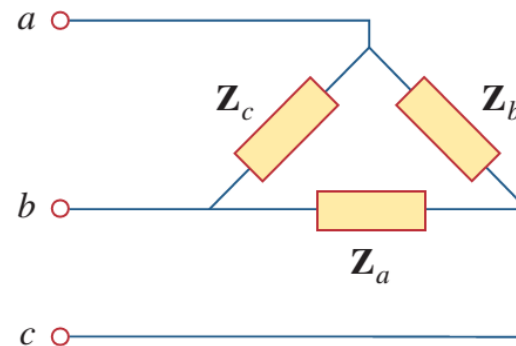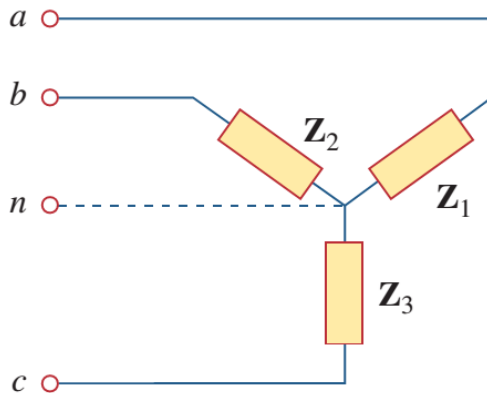
- A balanced load means the same impedance for each load.
-- Impedance are equal in magnitude and in phase
- They may also be connected in either Delta or wye
 - For a balanced wye connected load: $Z_1 = Z_2 = Z_3 = Z_Y$
 - For a balanced delta connected load: $Z_a = Z_b = Z_c = Z_\Delta$



- The load impedance per phase for the above configurations can be **interchanged**.



Source-Load configurations

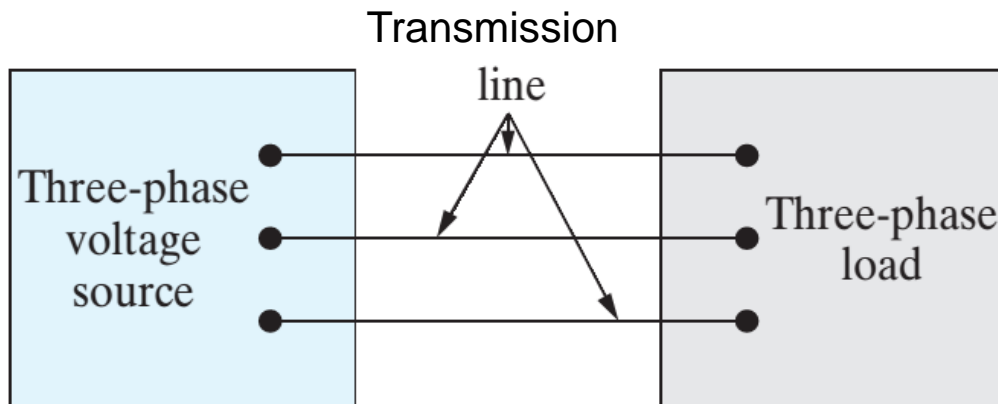


Source	Load
Y	Y
Y	Δ
Δ	Y
Δ	Δ



Source-Load Configurations

Y-Y

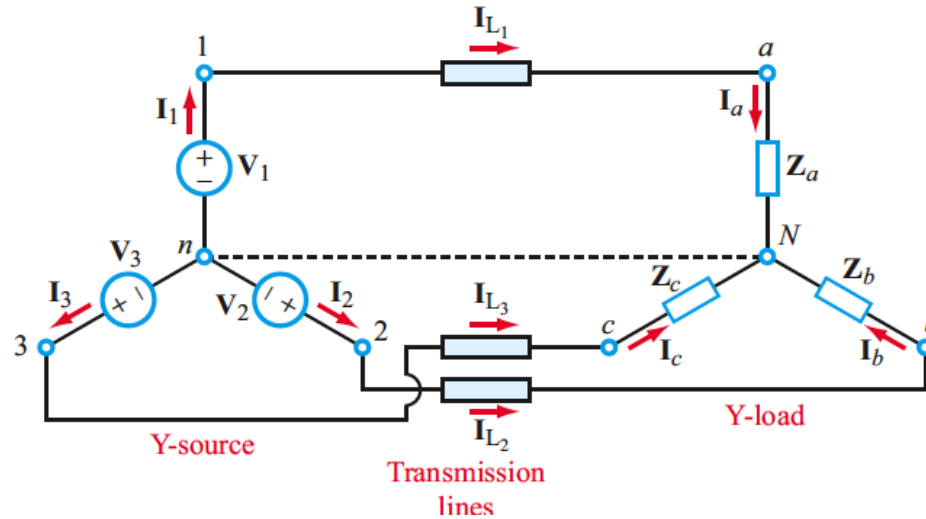


Load Phase Currents

I_a, I_b, I_c
(same as line currents
 $I_{L1}, I_{L2}, \text{ and } I_{L3}$)

Load Phase Voltages

V_{aN}, V_{bN}, V_{cN}

Y-Delta

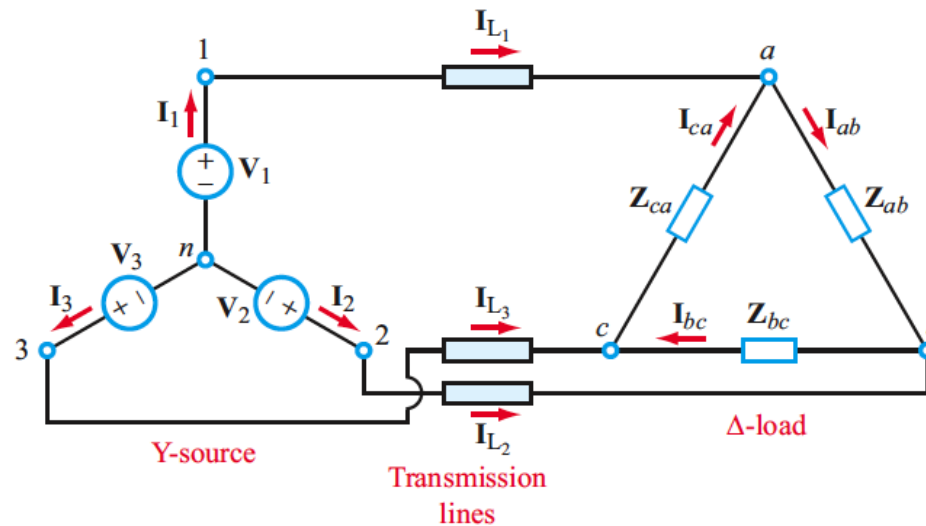

Load Phase Currents

I_{ab}, I_{bc}, I_{ca}


Load Phase Voltages

V_{ab}, V_{bc}, V_{ca}



Source-Load Configurations

Delta-Y

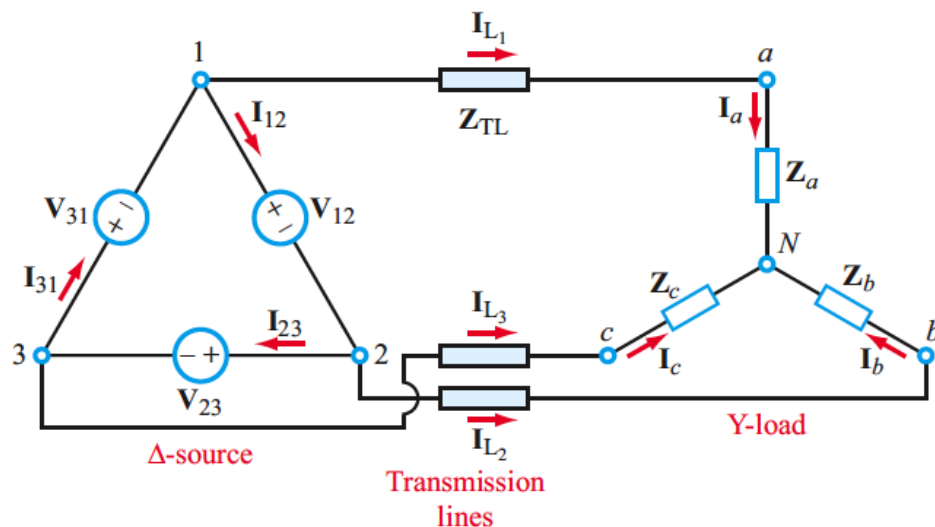


Load Phase Currents

I_a, I_b, I_c
(same as line currents
 $I_{L1}, I_{L2},$ and I_{L3})

Load Phase Voltages

V_{aN}, V_{bN}, V_{cN}

Delta-Delta

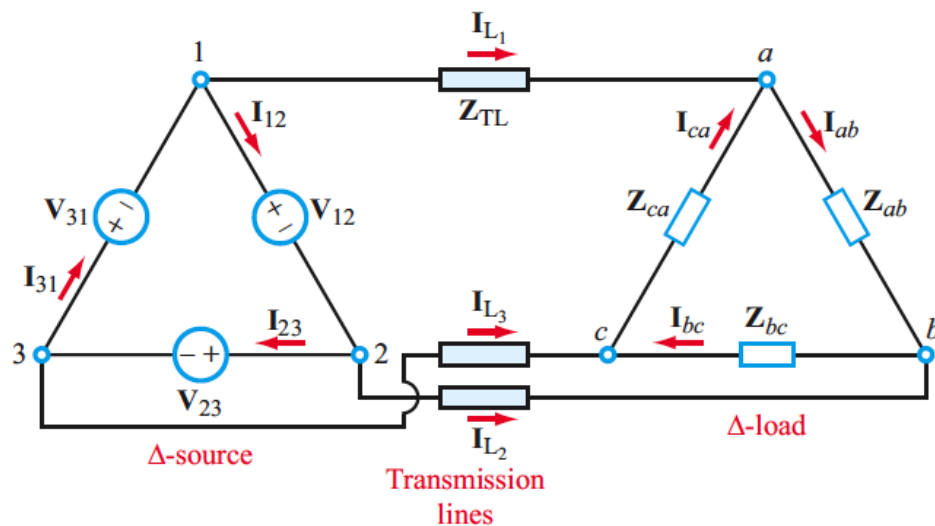

Load Phase Currents

I_{ab}, I_{bc}, I_{ca}

Load Phase Voltages


V_{ab}, V_{bc}, V_{ca}
(same as source voltages
if Z_{TL} is negligible)

Balanced Y-Y connection


- The load impedance Z_Y will be assumed to be balanced.
 - This can be the source Z_S , line Z_l and load Z_L together.

$$Z_Y = Z_S + Z_\ell + Z_L$$

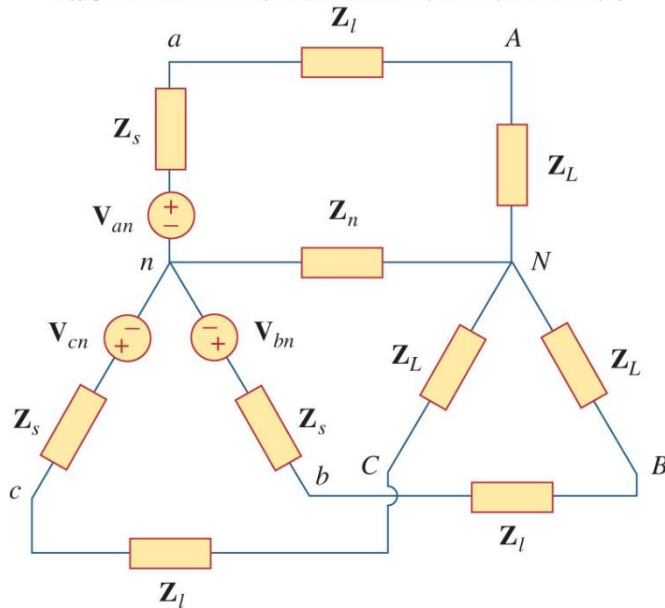Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



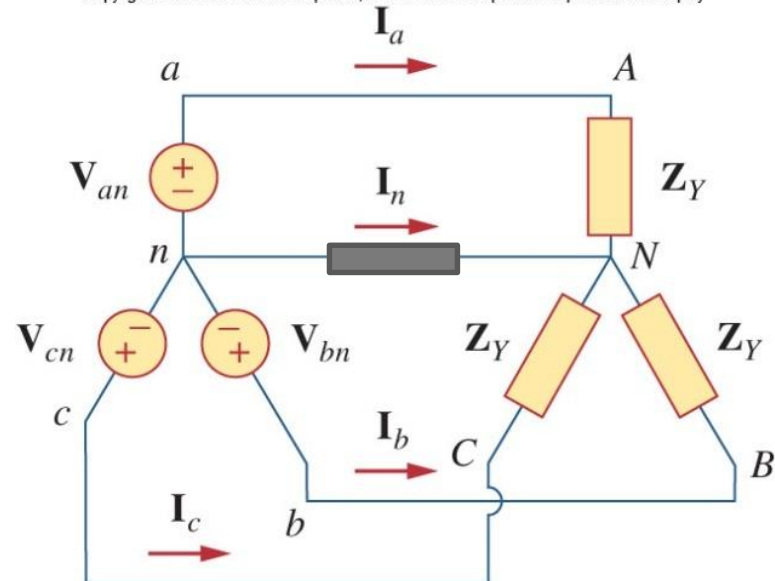Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display





Phase Voltage & Line-to-Line Voltage

- Use the positive sequence:

Phase Voltage

$$V_{an} = V_p \angle 0^\circ$$
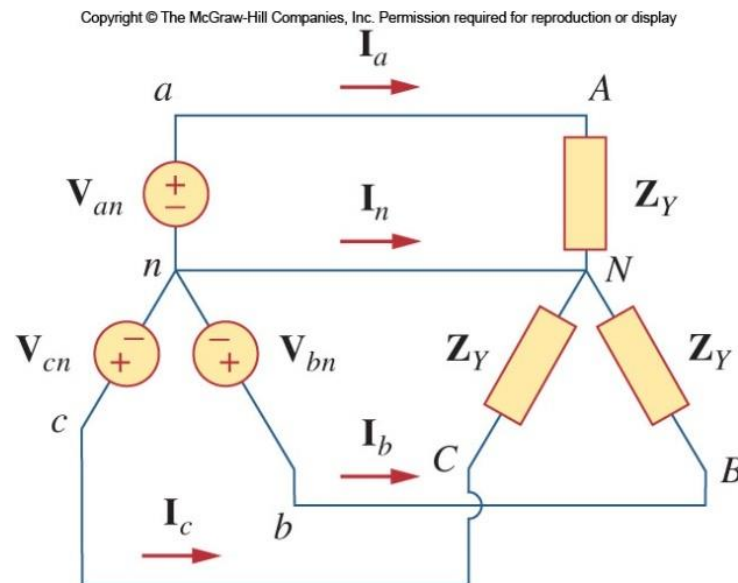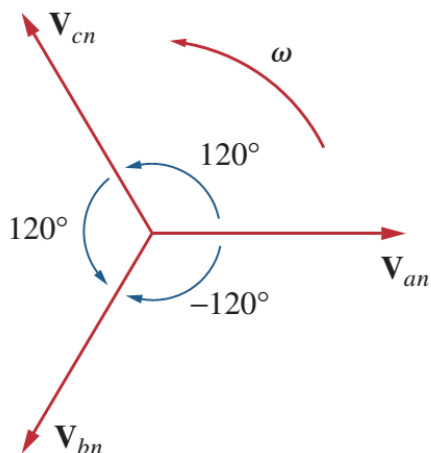
$$V_{bn} = V_p \angle -120^\circ \quad V_{cn} = V_p \angle +120^\circ$$




- The line to line voltages (or just line voltages in short):**



Line Currents

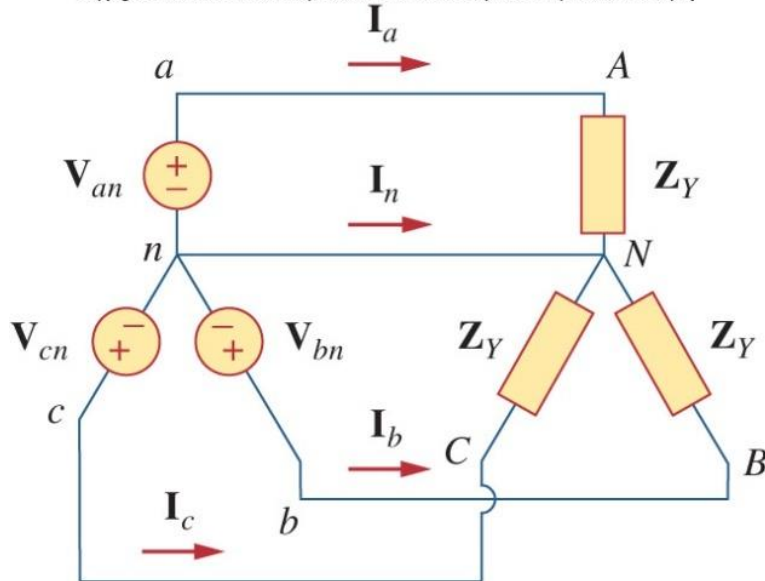
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display





Example


- Calculate the line currents.

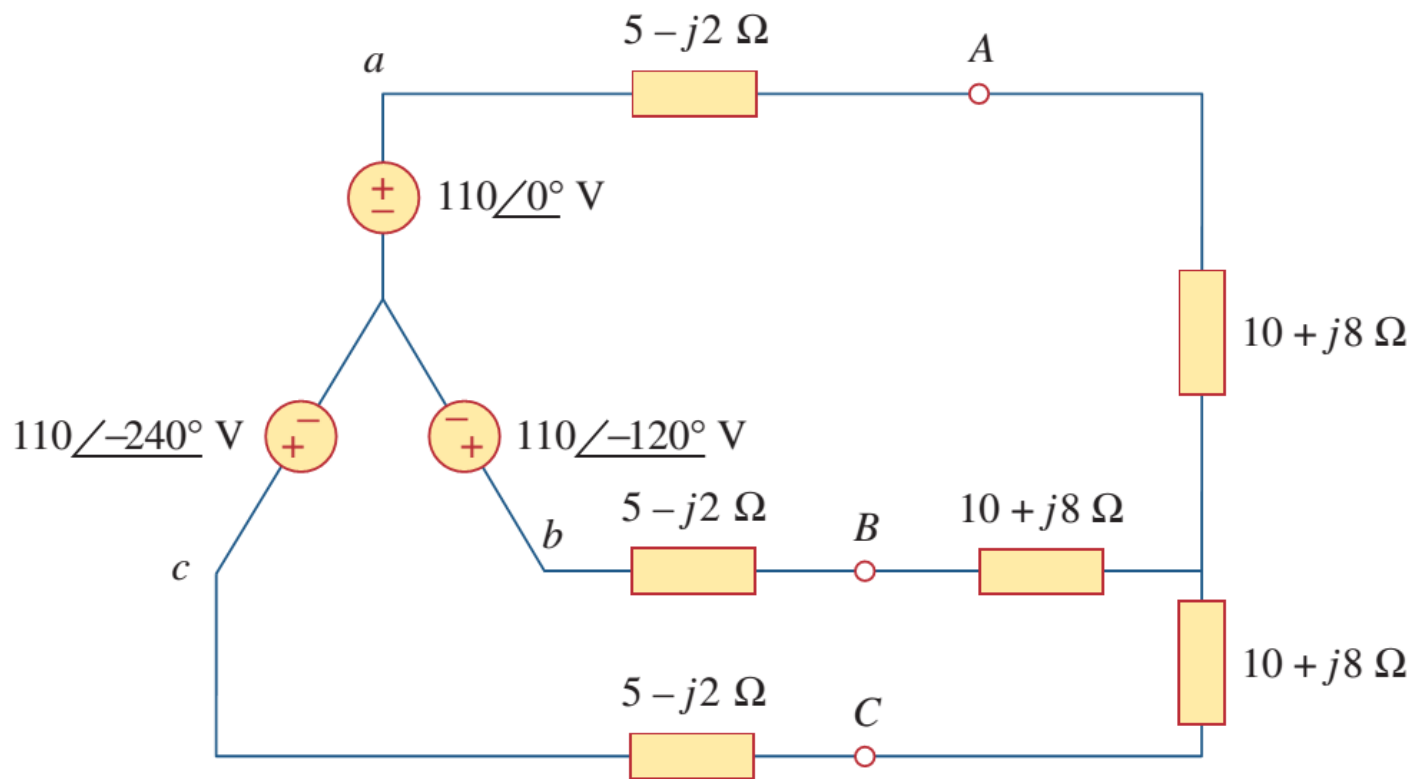



Wye- Δ


Y-Delta


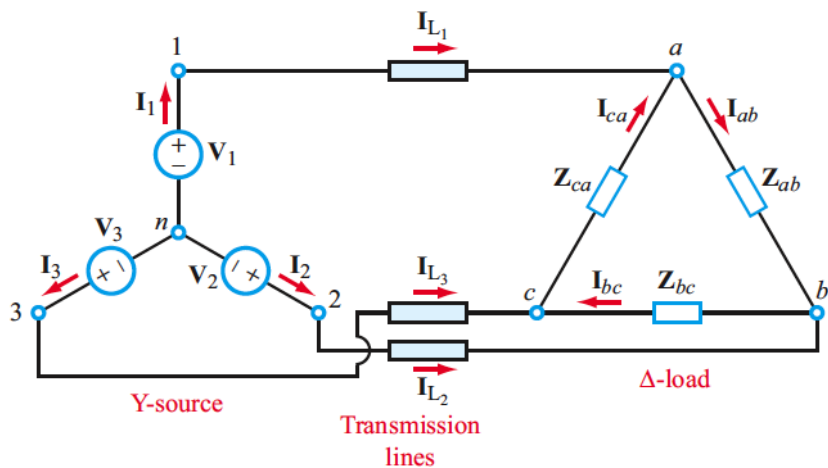


Load Phase Currents
 I_{ab}, I_{bc}, I_{ca}

Load Phase Voltages
 V_{ab}, V_{bc}, V_{ca}


Find complex power for each Z_L

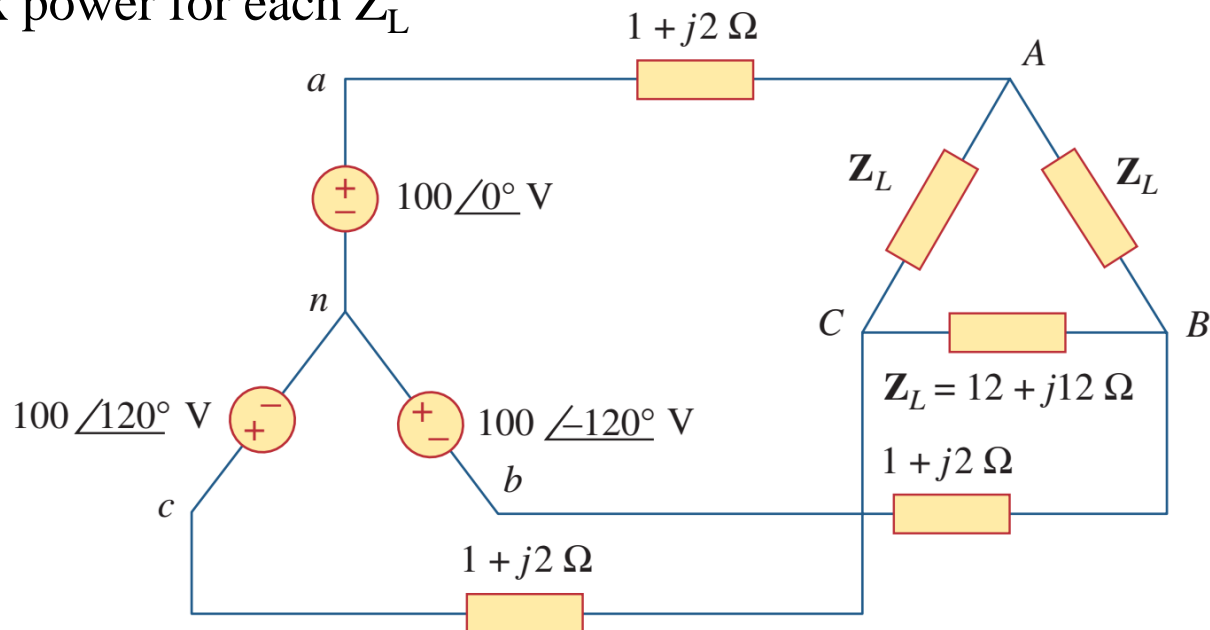

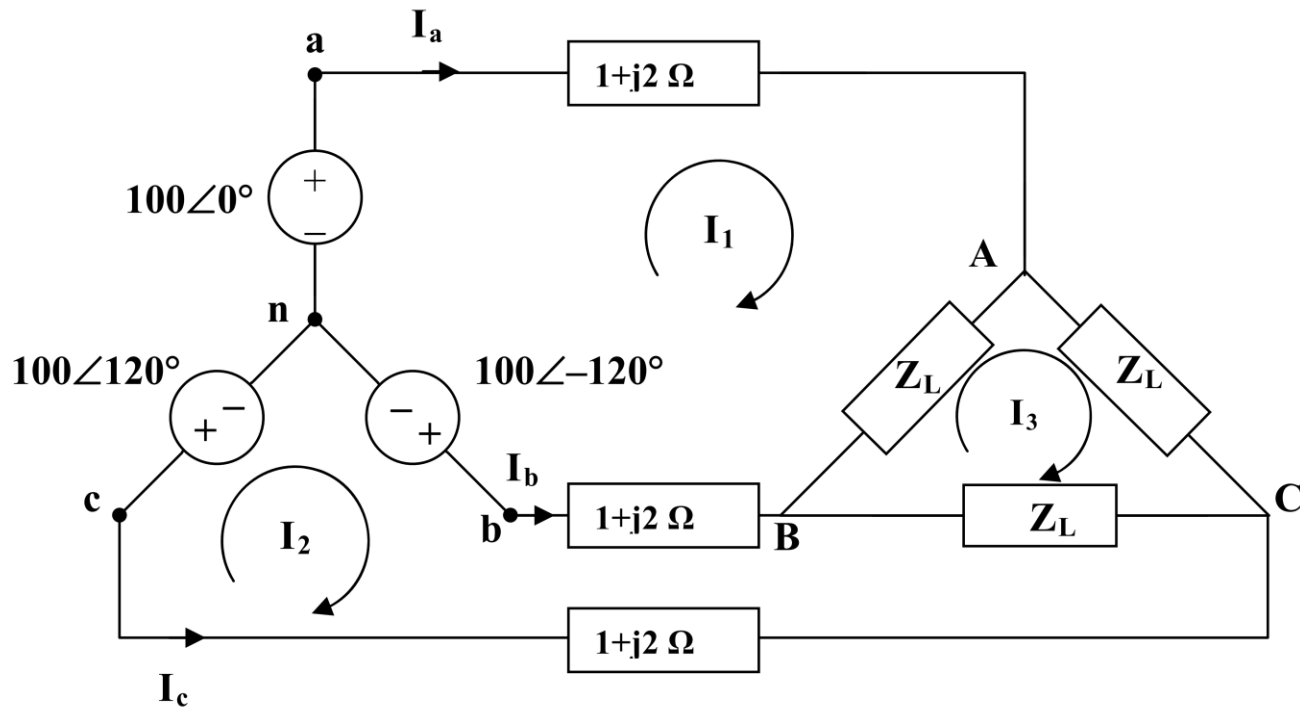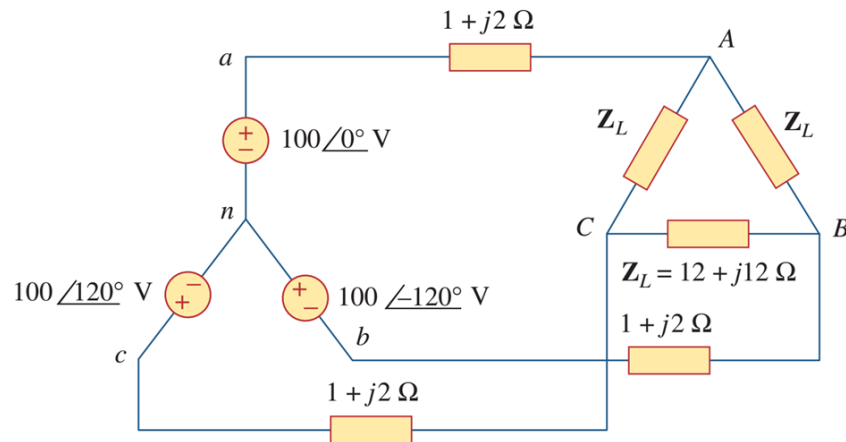



Wye- $\Delta \rightarrow$ Wye-Wye

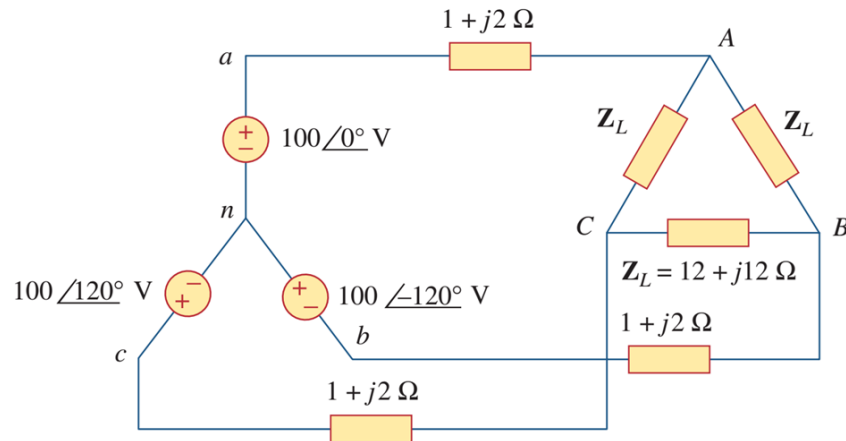






Wye- Δ


Find load phase current
and line current

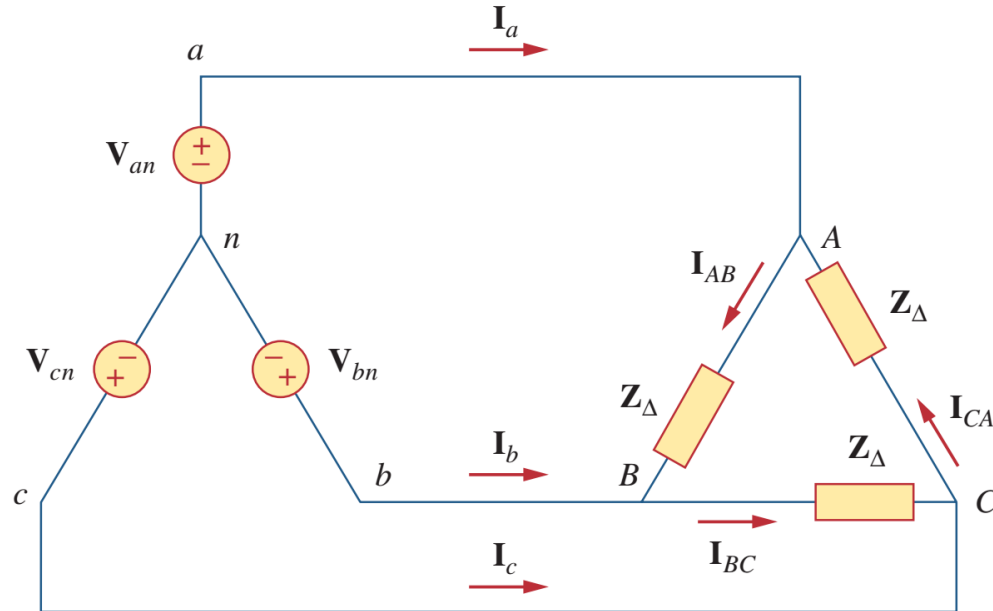



Wye- Δ

Find load phase current
and line current

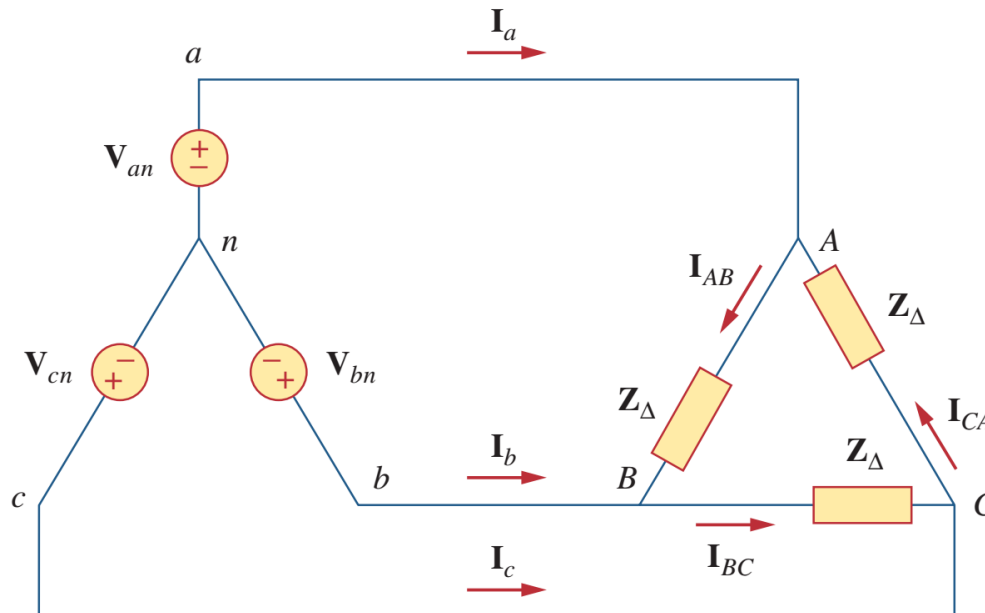


Assume positive
sequence:

$$\begin{aligned} \mathbf{V}_{an} &= V_p \angle 0^\circ \\ \mathbf{V}_{bn} &= V_p \angle -120^\circ, & \mathbf{V}_{cn} &= V_p \angle +120^\circ \end{aligned}$$

$$\begin{aligned} \mathbf{V}_{ab} &= \sqrt{3}V_p \angle 30^\circ = \mathbf{V}_{AB}, & \mathbf{V}_{bc} &= \sqrt{3}V_p \angle -90^\circ = \mathbf{V}_{BC} \\ \mathbf{V}_{ca} &= \sqrt{3}V_p \angle -150^\circ = \mathbf{V}_{CA} \end{aligned}$$

$$\mathbf{I}_{AB} = \frac{\mathbf{V}_{AB}}{\mathbf{Z}_{\Delta}}, \quad \mathbf{I}_{BC} = \frac{\mathbf{V}_{BC}}{\mathbf{Z}_{\Delta}}, \quad \mathbf{I}_{CA} = \frac{\mathbf{V}_{CA}}{\mathbf{Z}_{\Delta}}$$


Wye- Δ

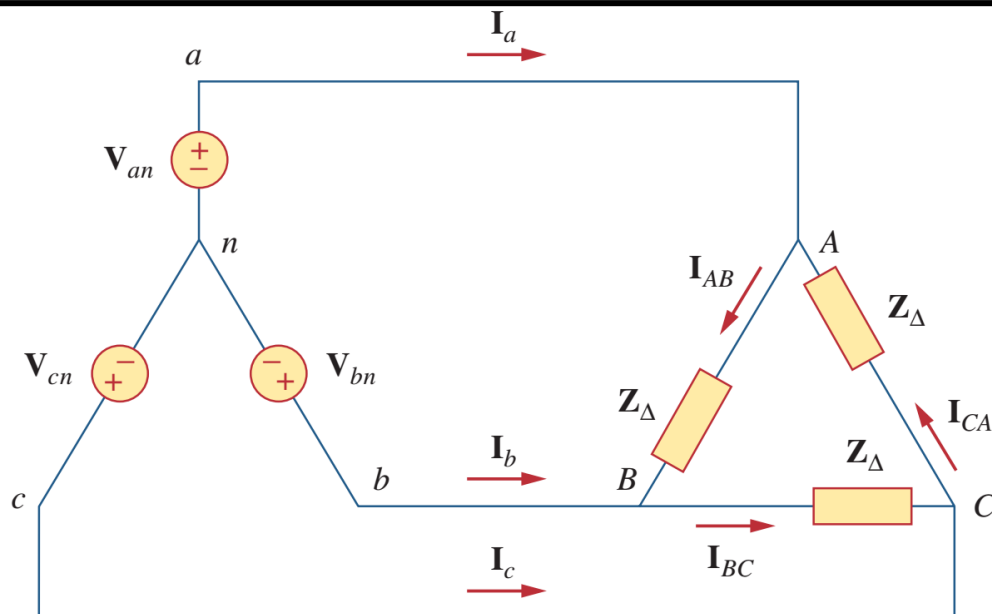

$$\mathbf{I}_a = \mathbf{I}_{AB} - \mathbf{I}_{CA}, \quad \mathbf{I}_b = \mathbf{I}_{BC} - \mathbf{I}_{AB}, \quad \mathbf{I}_c = \mathbf{I}_{CA} - \mathbf{I}_{BC}$$

Since $\mathbf{I}_{CA} = \mathbf{I}_{AB} \angle -240^\circ$,

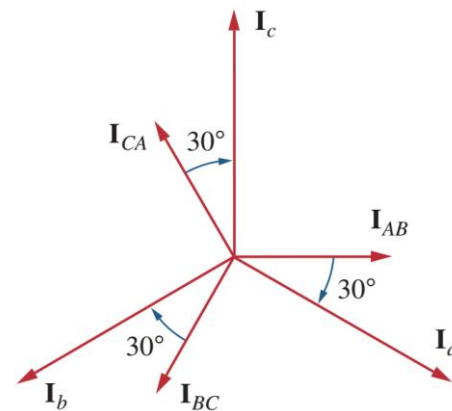
$$\begin{aligned} \mathbf{I}_a &= \mathbf{I}_{AB} - \mathbf{I}_{CA} = \mathbf{I}_{AB}(1 - 1 \angle -240^\circ) \\ &= \mathbf{I}_{AB}(1 + 0.5 - j0.866) = \mathbf{I}_{AB}\sqrt{3} \angle -30^\circ \end{aligned}$$





Source-Load Configurations


Delta-Y

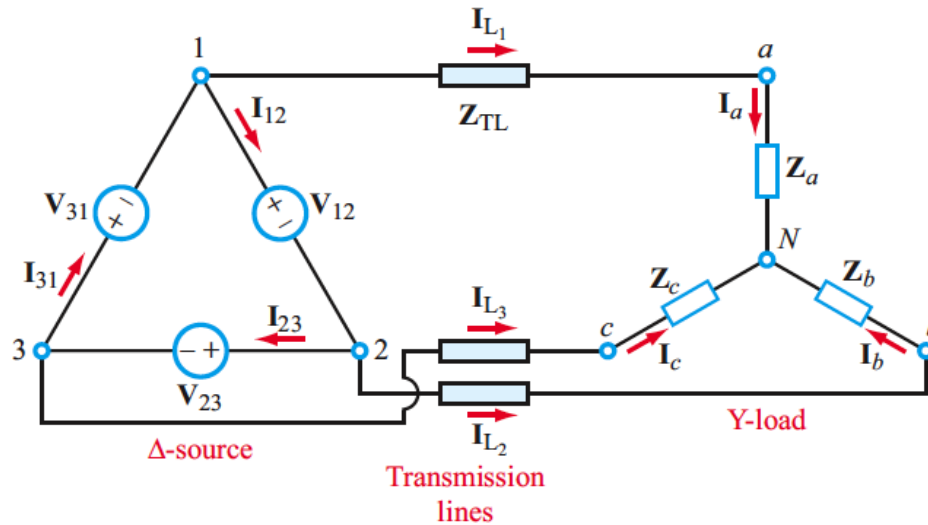

Load Phase Currents
 I_a, I_b, I_c
(same as line currents
 $I_{L1}, I_{L2}, \text{ and } I_{L3}$)

Load Phase Voltages
 V_{aN}, V_{bN}, V_{cN}

Delta-Delta

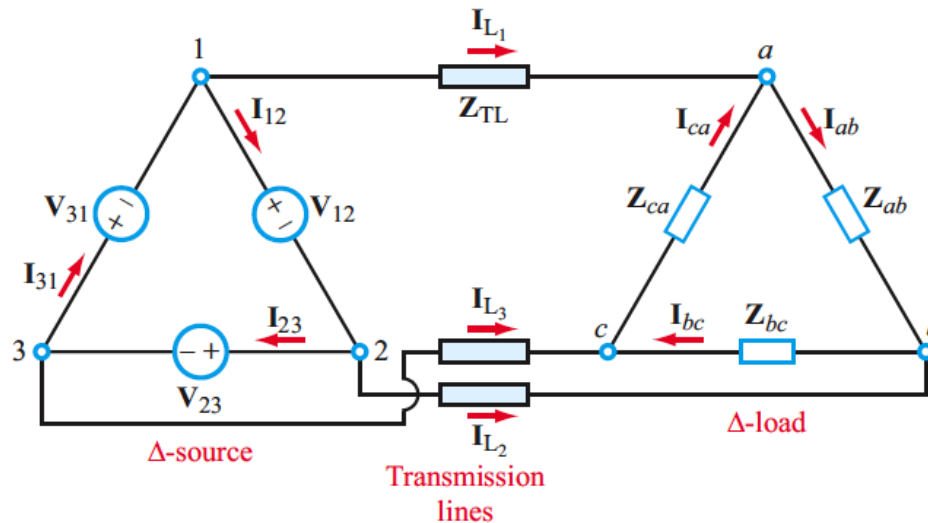


Load Phase Currents
 I_{ab}, I_{bc}, I_{ca}

Load Phase Voltages
 V_{ab}, V_{bc}, V_{ca}
(same as source voltages
if Z_{TL} is negligible)



Δ -Wye

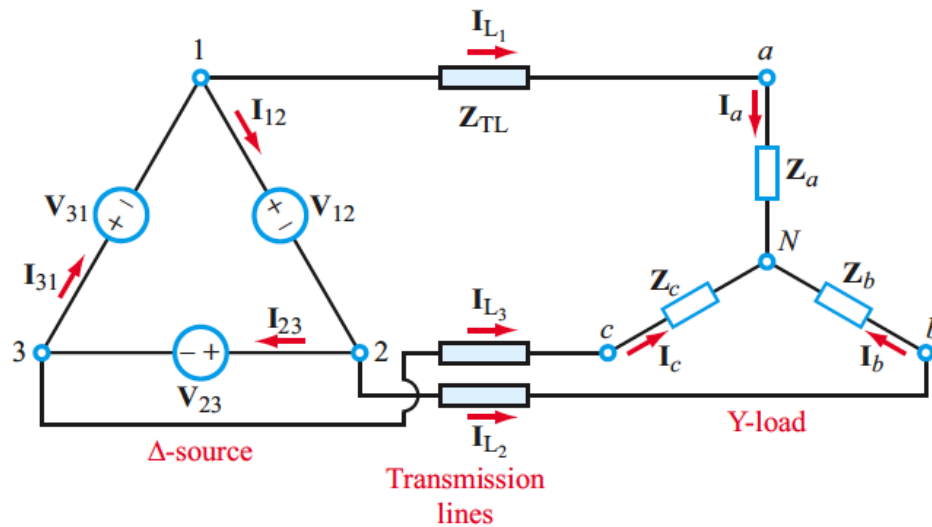


Load Phase Currents

I_a, I_b, I_c
(same as line currents
 $I_{L1}, I_{L2},$ and I_{L3})


Load Phase Voltages

V_{aN}, V_{bN}, V_{cN}

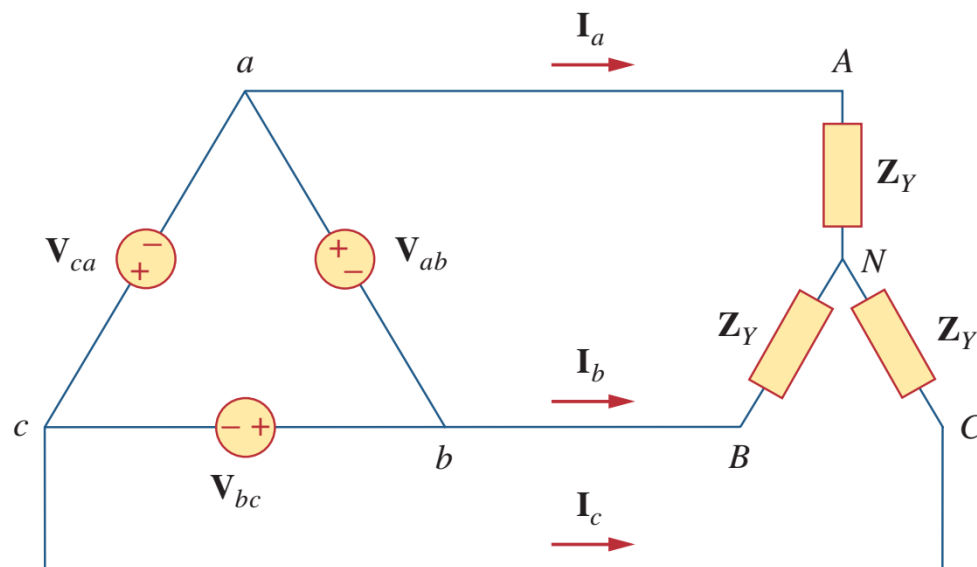




Delta-Y

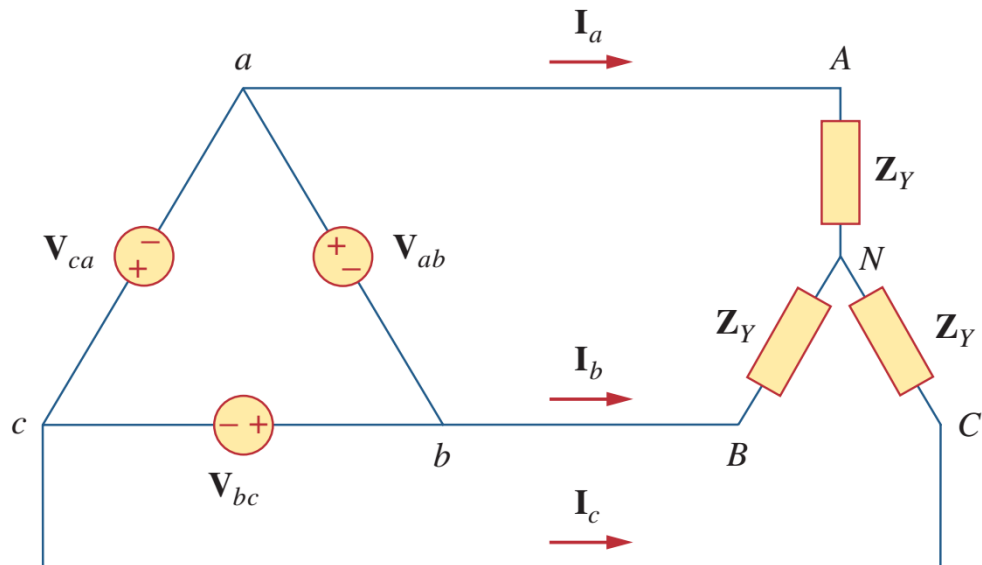



Delta-Delta

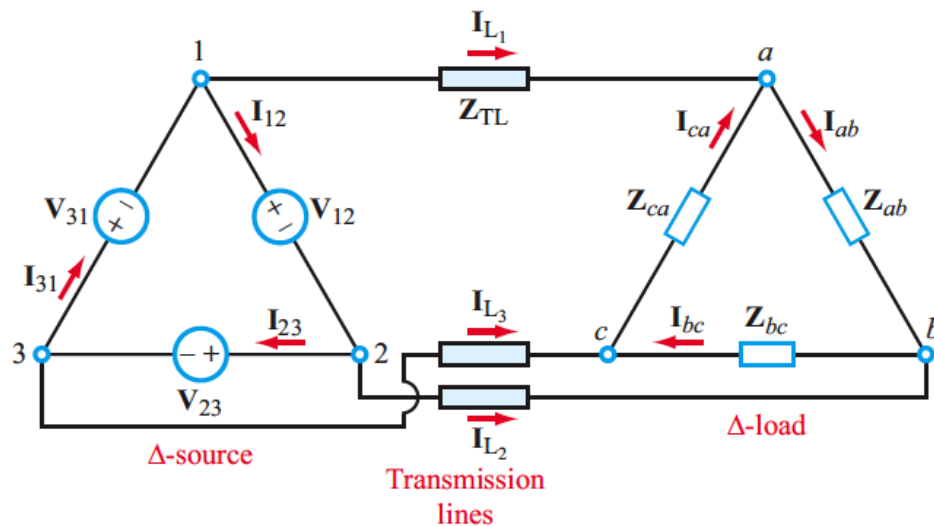

Load Phase Currents


I_{ab}, I_{bc}, I_{ca}


Load Phase Voltages

V_{ab}, V_{bc}, V_{ca}

(same as source voltages
if Z_{TL} is negligible)

• Δ - Δ

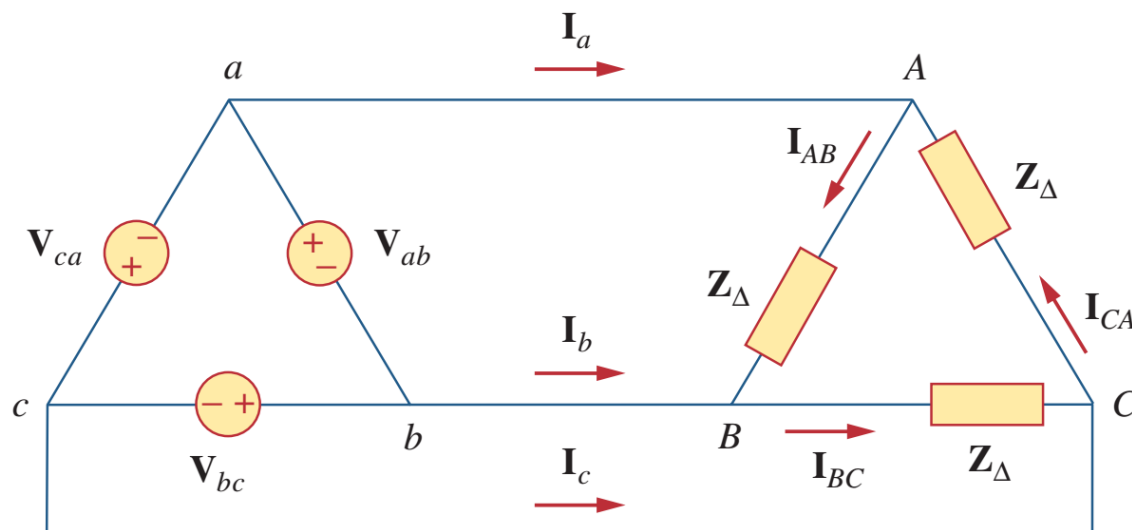

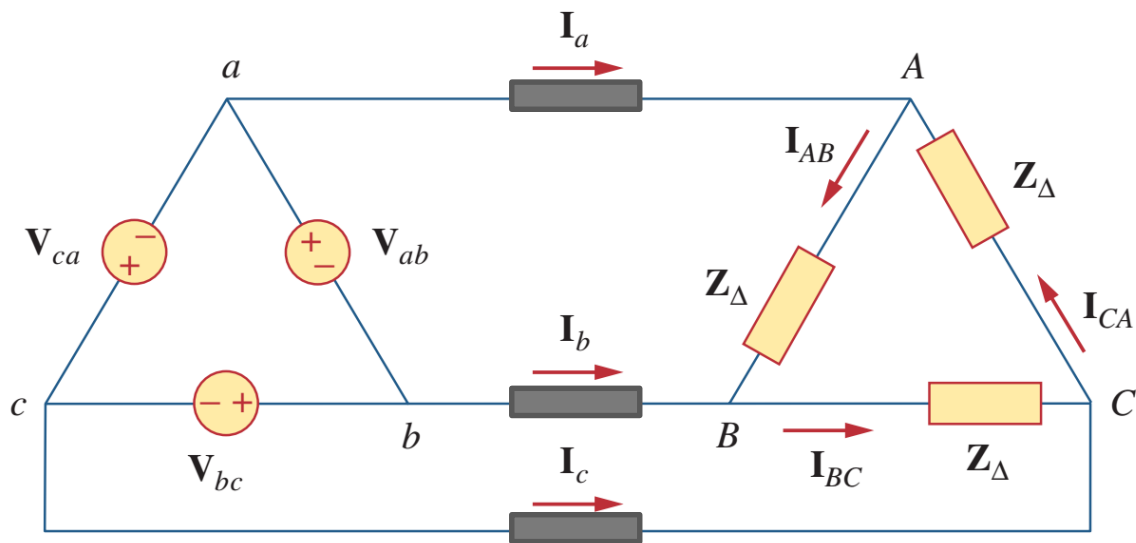

2. (16 points). Given the circuit in Fig.2 is in steady state, use phasor domain method to find $i_o(t)$; and $i_I(t)$.

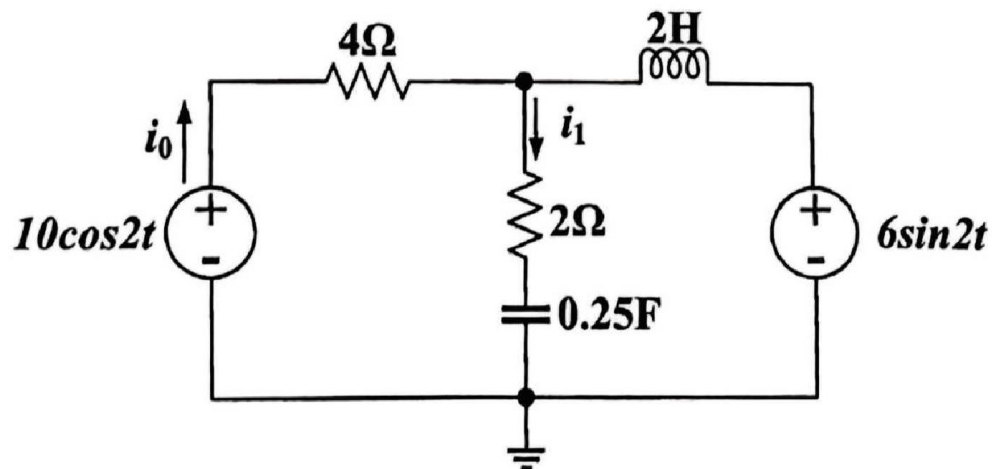


Fig.2

3. (16 points). As shown in Fig.3, the balanced three-phase circuit holds positive $a \rightarrow b \rightarrow c$ sequence. Calculate I_a , I_b , I_c and the total complex power delivered to the whole load.

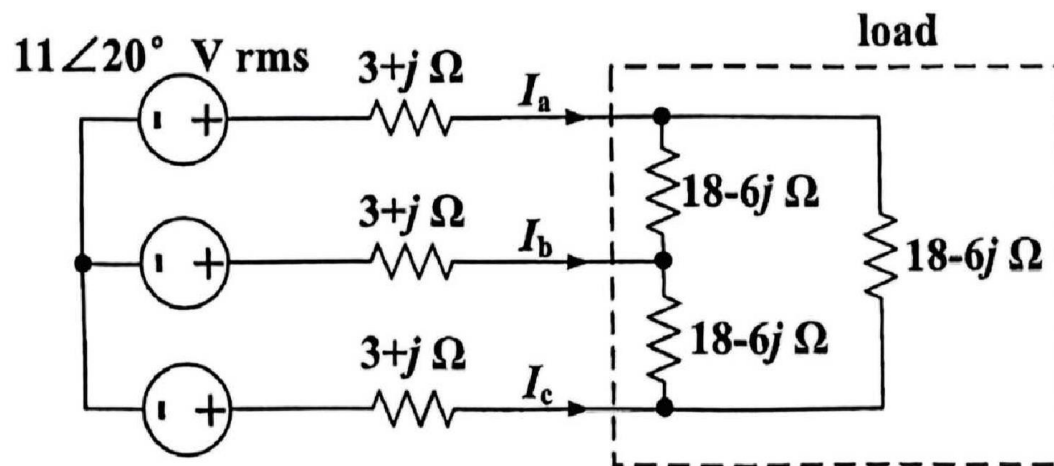


Fig.3