

## **Homework 6**

Due date: Dec. 14<sup>th</sup>, 2023

Turn in your hard-copy hand-writing homework in class

Rules:

- Work on your own. Discussion is permissible, but extremely similar submissions will be judged as plagiarism.
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.

1. Given that the voltage and current of two-terminal elements adopt the passive sign convention, the instantaneous values are expressed as:

(1)  $v(t) = 15\cos(400t + 30^\circ)$  V,  $i(t) = 3\sin(400t + 30^\circ)$  A;

(2)  $v(t) = 8\sin(500t + 50^\circ)$  V,  $i(t) = 2\sin(500t + 140^\circ)$  A;

(3)  $v(t) = 8\cos(250t + 60^\circ)$  V,  $i(t) = 5\sin(250t + 150^\circ)$  A;

(a) Transform the three voltage & current pairs into phasors.

(b) Try to determine whether the element is a resistor, inductor or capacitor, and determine its value ( $R=?$ ,  $C=?$ ,  $L=?$ ) for (1), (2), and (3), respectively.

1.

(1) 1)  $\dot{V} = 15\angle 30^\circ$ ,  $\dot{I} = 3\angle -60^\circ$ , at  $\omega = 400 \text{ rad/s}$  2'

2)  $\dot{V} = 8\angle -40^\circ$ ,  $\dot{I} = 2\angle 50^\circ$ , at  $\omega = 500 \text{ rad/s}$  2'

3)  $\dot{V} = 8\angle 60^\circ$ ,  $\dot{I} = 5\angle 60^\circ$ , at  $\omega = 250 \text{ rad/s}$  2'

(b) ①  $Z_{(1)} = \frac{\dot{V}}{\dot{I}} = 5\angle 90^\circ$  (inductor) 3'



$j\omega L = 5j \Rightarrow L = \frac{5}{400} \text{ H} = 0.0125 \text{ H}$

②  $Z_{(2)} = \frac{\dot{V}}{\dot{I}} = \frac{8\angle -40^\circ}{2\angle 50^\circ} = 4\angle -90^\circ$  (capacitor) 3'

$\frac{-j}{\omega C} = -4j \Rightarrow C = \frac{1}{4 \times 500} \text{ F} = 0.5 \mu\text{F}$

③  $Z_{(3)} = \frac{\dot{V}}{\dot{I}} = \frac{8\angle 60^\circ}{5\angle 60^\circ} = 1.6 \Omega$  (resistor) 3'

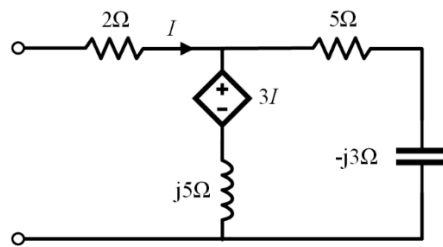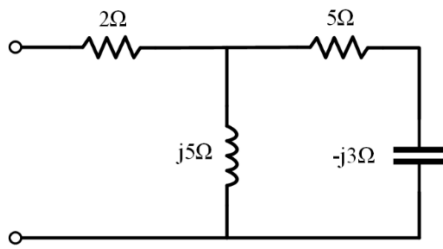
2. Finding the equivalent impedance and admittance of these **two** circuits.




$$\begin{aligned}
 2. \quad ① \quad R_{eq} &= 2 + j5 \parallel (5 - j3) \\
 &= 2 + \frac{j25 + 15}{5 + j2} \\
 &= 2 + \frac{j125 + 75 + 50 - j30}{29} \\
 &= \frac{125}{29} + 2 + j\frac{95}{29} = 6.31 + j3.28 = 7.11 \angle 27.43^\circ \Omega \quad 5
 \end{aligned}$$

$$\begin{aligned}
 ② \quad \begin{cases} \frac{v(5 - j3) - 3I}{j5} + v = I \\ v = 2I + v(5 - j3) \end{cases} &\Rightarrow R_{eq} = \frac{V}{I} = 8.28 + j0.69 = 8.31 \angle 4.76^\circ \Omega \quad 10
 \end{aligned}$$

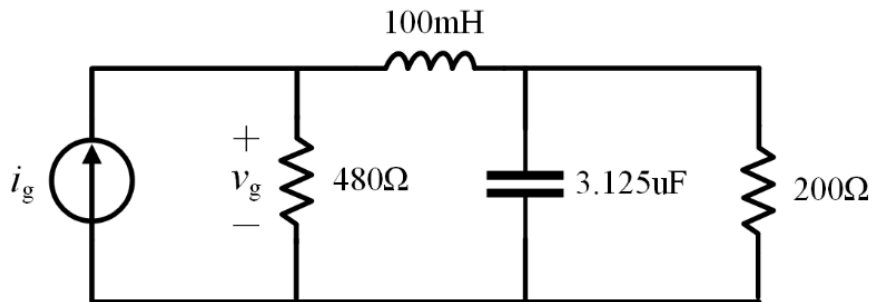3.  $i_g = 60\cos(\omega t)$  mA, if  $i_g$  is in phase with  $v_g$ , calculate the frequency of the current source and find the expression for  $v_g$



3.

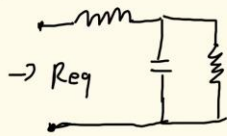

$$R_{eq} = j0.1\omega + 200 \parallel j\frac{1}{\omega} \cdot 32 \times 10^4 \quad 2$$

$$= j0.1\omega + \frac{-j\frac{1}{\omega} \cdot 64 \times 10^6}{200 - j\frac{1}{\omega} 32 \times 10^4}$$

$$= j0.1\omega + \frac{-j\frac{1}{\omega} 32 \times 10^4 + \frac{1}{\omega^2} 512 \times 10^6}{1 + \frac{1}{\omega^2} 16^2 \times 10^4}$$


$$= j(0.1\omega - \frac{\frac{1}{\omega} 32 \times 10^4}{1 + \frac{1}{\omega^2} 16^2 \times 10^4}) + \frac{512 \times 10^6}{\omega^2 + 256 \times 10^4} \quad 4$$

$$\therefore j0.1\omega = \frac{\frac{1}{\omega} 32 \times 10^4}{1 + \frac{1}{\omega^2} 16^2 \times 10^4} \Rightarrow \omega = 800 \quad 4$$


$$R_{eq} = 160 \Omega \quad 2$$

$$v_g = i_g \times (480 \parallel 160) = 7.2 \cos(800t) \text{ V} \quad 3$$

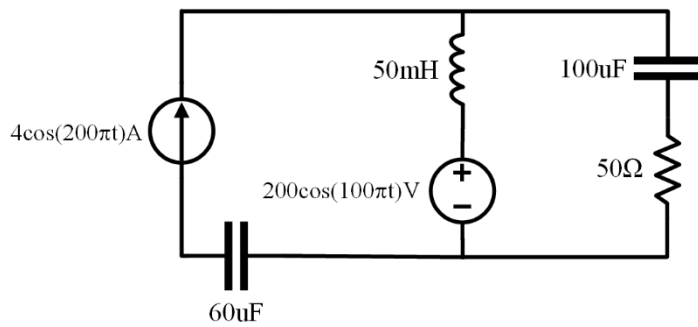4. Finding the Time Domain Voltage Expression for Resistance.



4.

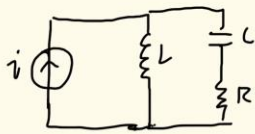


$$\dot{v}_R = \dot{v} \cdot \frac{j\omega L}{j\omega L - j\frac{1}{\omega C} + R} \quad 2, \quad \omega = 200\pi, \quad I = 4 \angle 0 \quad 2$$

$$V_R = \dot{v}_R \cdot R = \dot{v} \cdot \frac{j\omega L R}{j\omega L - j\frac{1}{\omega C} + R} \quad 2$$

$$= 4 \cdot \frac{j500\pi}{j10\pi - j\frac{50}{\pi} + 50} = 120.03 \angle 72.78^\circ \quad 2$$
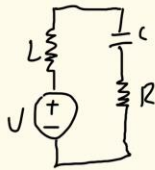
$$\therefore V_R = 120.03 \cos(200\pi t + 72.78) \quad 2$$




$$V_R' = V \cdot \frac{R}{j\omega L - j\frac{1}{\omega C} + R} \quad 4, \quad \omega = 100\pi, \quad V = 200 \angle 0 \quad 2$$

$$\therefore V_R' = \frac{200 \times 50}{j5\pi - j\frac{100}{\pi} + 50} = 190.35 \angle 17.87^\circ \quad 2$$


$$\therefore V_{R\text{total}} = V_R + V_R' = 120.03 \cos(200\pi t + 72.78) \quad 2$$

$$+ 190.35 \cos(100\pi t + 17.87)$$

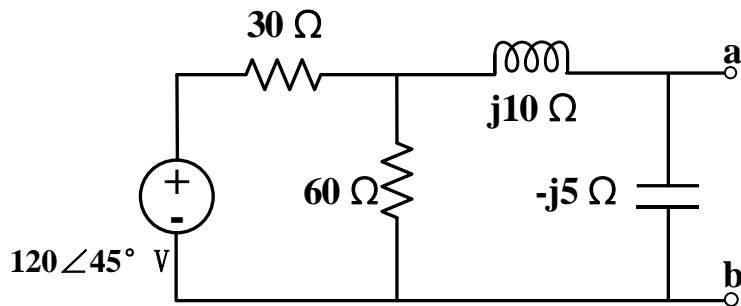5. For the circuit below, please find the Thevenin equivalent circuit with respect to node **a** and node **b**.


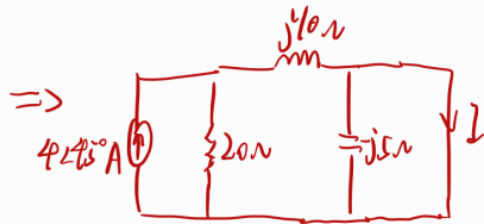
$$5. \quad Z_{TH} = -j5 \Omega \parallel (j10 \Omega + 30 \Omega \parallel 60 \Omega) = 5.42 \angle -77.47^\circ \Omega \quad 4'$$




$$I = \frac{20}{20 + j10} (4 \angle 45^\circ) = 3.578 \angle 18.43^\circ \text{ A} \quad 4'$$

$$V_{th} = Z_{th} I = 19.4 \angle -59^\circ \text{ V} \quad 4'$$



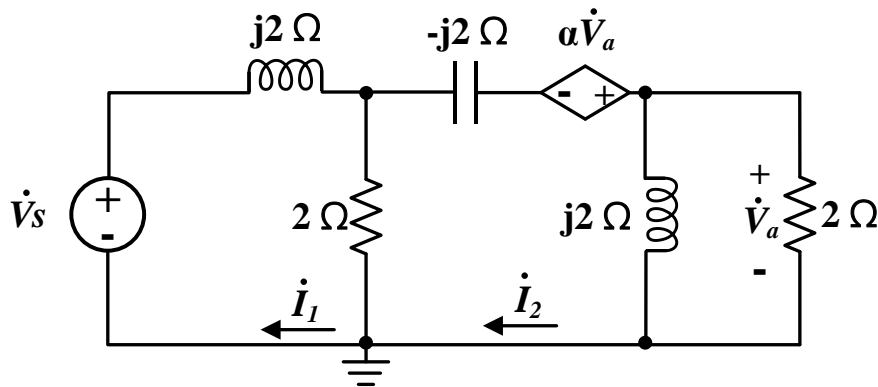6. Use **nodal AND mesh** analyze method to find  $\dot{V}_a$ ,  $\dot{I}_1$  and  $\dot{I}_2$  for the circuit below, assuming that  $\dot{V}_S = 10 \angle 0^\circ \text{ V}$ ,  $\alpha = 0.5$ .



6.

Mesh:

$$\begin{cases} j2 \cdot \dot{I}_1 + (\dot{I}_1 - \dot{I}_2) \cdot 2 = \dot{V}_S \\ (\dot{I}_2 - \dot{I}_1) \cdot 2 - j2 \cdot \dot{I}_2 - \alpha \dot{V}_a + j2(\dot{I}_2 - \dot{I}_3) = 0 \\ j2(\dot{I}_3 - \dot{I}_2) + \dot{I}_3 \cdot 2 = 0 \\ \dot{V}_a = 2 \cdot \dot{I}_3 \end{cases} \quad 12'$$

$$\Rightarrow \begin{cases} \dot{I}_1 = 6.75 \angle -57.53^\circ \text{ A} \\ \dot{I}_2 = 4.47 \angle -66.57^\circ \text{ A} \\ \dot{I}_3 = 3.16 \angle 18.43^\circ \text{ A} \end{cases} \quad 6'$$

$$\dot{V}_a = 2 \dot{I}_3 = 6.32 \angle 18.43^\circ \text{ V} \quad 7'$$

Nodal:

$$\begin{cases} \frac{\dot{V}_S - \dot{V}_1}{j2} + \frac{0 - \dot{V}_1}{2} + \frac{\dot{V}_2 - \alpha \dot{V}_a - \dot{V}_1}{-j2} = 0 \\ \frac{\dot{V}_2 - \alpha \dot{V}_a - \dot{V}_1}{-j2} + \frac{\dot{V}_2}{j2} + \frac{\dot{V}_2}{2} = 0 \\ \dot{V}_2 = \dot{V}_a \end{cases} \quad 11'$$