



# Lecture 14


## -- Laplace Transform in Circuit Analysis

## Example 2


Find (1) the voltage across the capacitor ✓

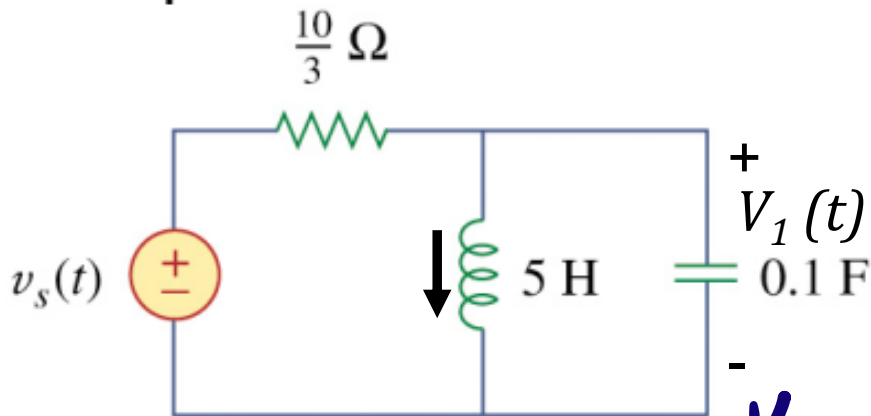(2) current through the inductor

assuming that  $v_s(t) = 10u(t)$  V, and assume that at  $t = 0$ ,  $-1$  A flows through the inductor and  $+5$  V is across the capacitor.


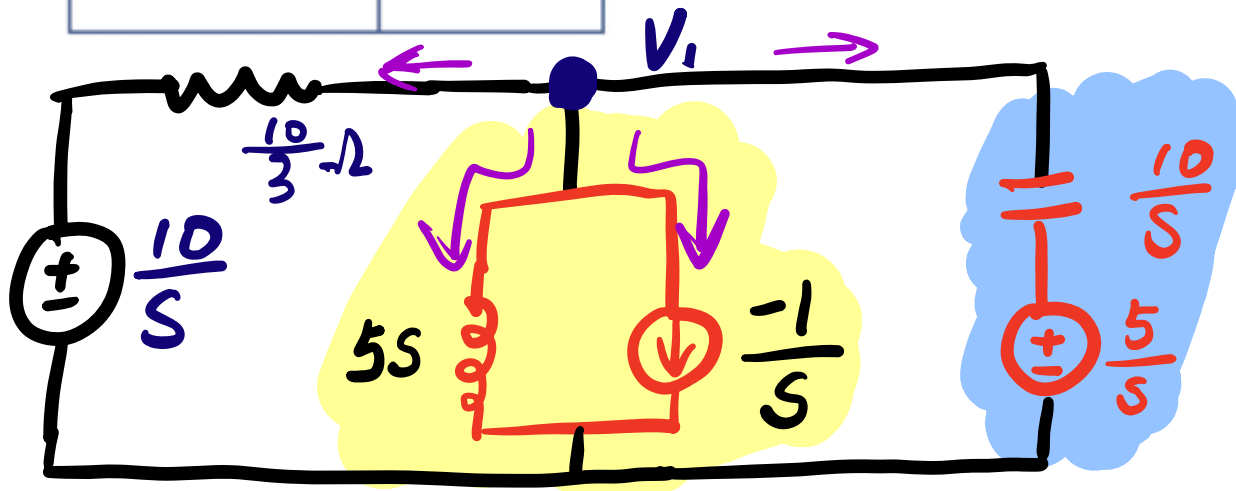
$$-1\text{A} \cdot u(t) \rightarrow \frac{-1}{s}$$



$$\frac{V_1 - \frac{10}{s}}{\frac{10}{3}} + \frac{V_1 - 0}{5s} + \frac{-1}{s} + \frac{V_1 - \frac{5}{s}}{\frac{10}{s}} = 0$$

$$\Rightarrow \boxed{V_1^{(s)} = \frac{40 + 5s}{(s+1)(s+2)} = \frac{k_1}{s+1} + \frac{k_2}{s+2}}$$

For  $k_1$ :

$$\frac{(40 + 5s)(\cancel{s+1})}{(\cancel{s+1})(s+2)} = \frac{k_1(\cancel{s+1})}{\cancel{s+1}} + \frac{k_2(s+1)}{s+2}$$

Set  $s = -1 \Rightarrow$

$$k_1 = \frac{40 - 5}{-1 + 2} = 35$$

$$k_2 = -30.$$

$$\Rightarrow V_1 = \frac{35}{s+1} - \frac{30}{s+2}$$


$$\hookrightarrow \mathcal{L}^{-1} f(t): \underline{v_1(t) = (35 \cdot e^{-t} - 30 \cdot e^{-2t}) u(t)} \quad \checkmark$$

S-domain

$$\begin{aligned} I_L(s) &= \frac{V_1^{(s)} - 0}{5s} + \frac{-1}{s} = \frac{40 + 5s}{(s+1)(s+2) \cdot 5s} + \frac{-1}{s} \\ &= \frac{-s^2 - 2s + 6}{s(s+1)(s+2)} = \frac{k_3}{s} + \frac{k_4}{s+1} + \frac{k_5}{s+2} \end{aligned}$$

$\hookrightarrow \mathcal{F}^{-1}$
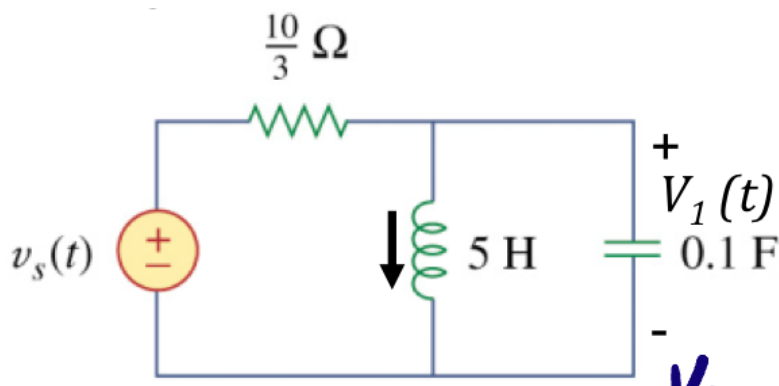
$$i_L(t) = (3 - 7e^{-t} + 3e^{-2t}) u(t) \text{ A}$$





$$i_L(t) = i_0 + \frac{1}{L} \int_0^t V_1(t) dt$$
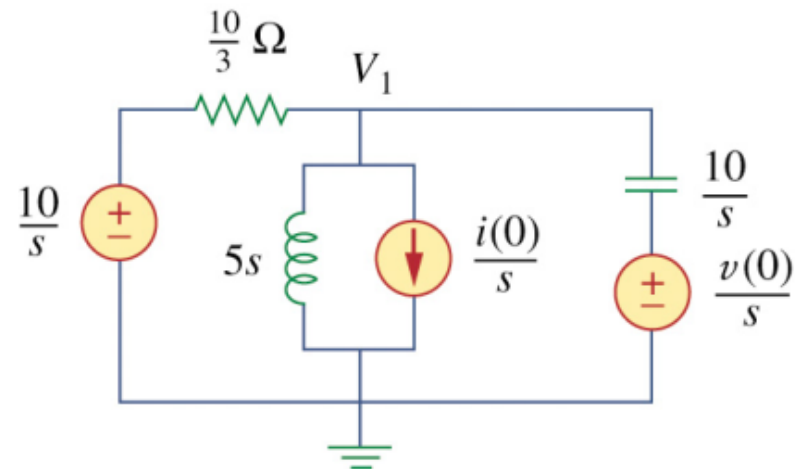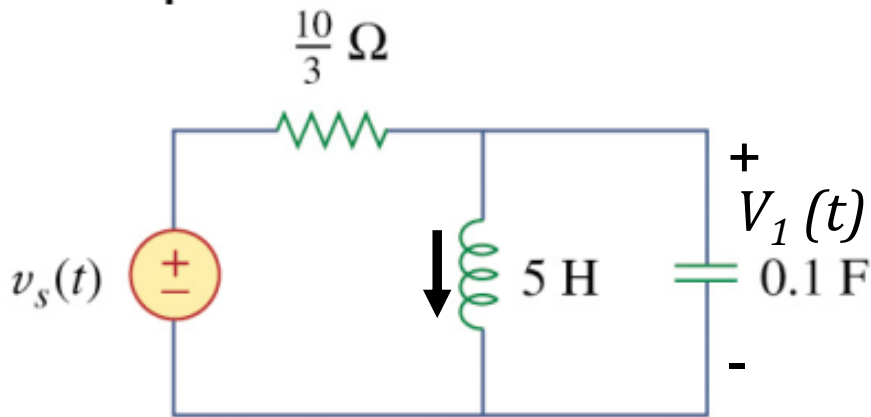
## Example 2



Find (1) the voltage across the capacitor  
(2) current through the inductor

assuming that  $v_s(t) = 10u(t)$  V, and assume that at  $t = 0$ ,  $-1$  A flows through the inductor and  $+5$  V is across the capacitor.


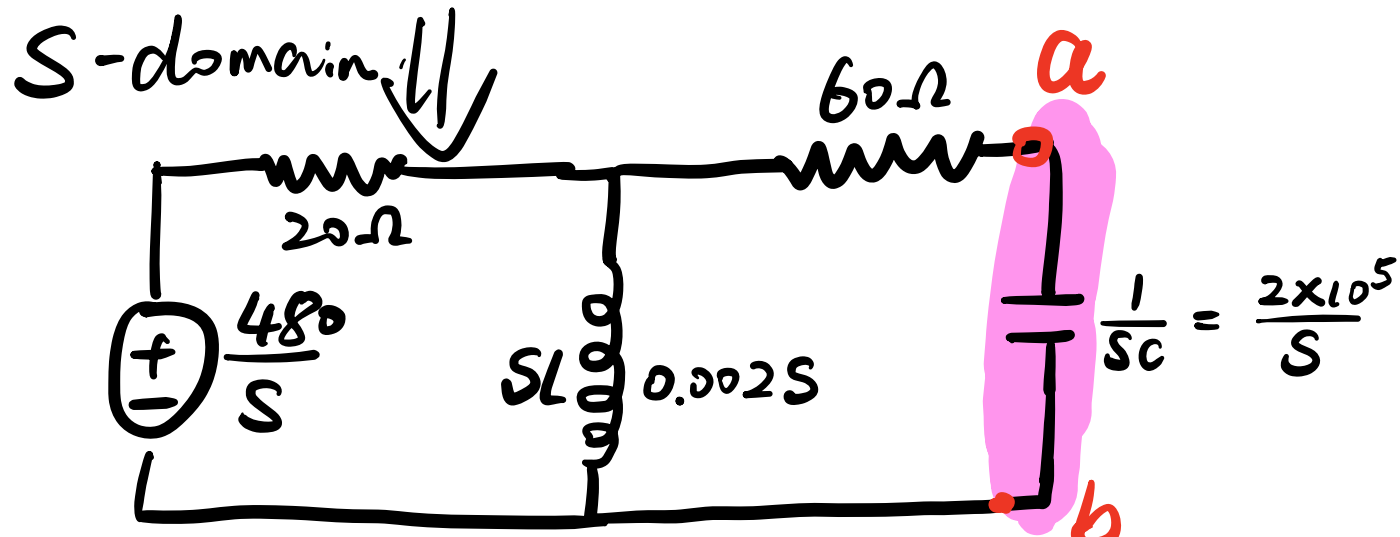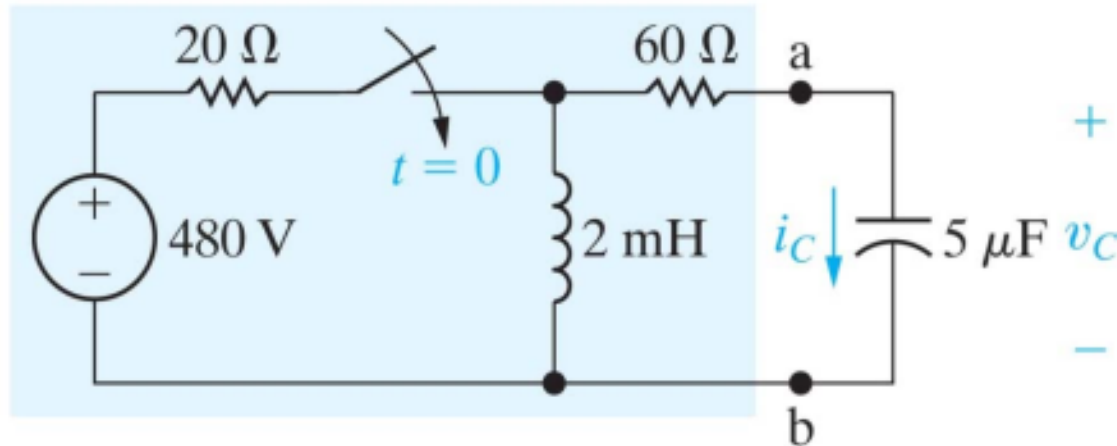
## Example 3


- Use Thevenin's equivalent circuit w.r.t. terminals  $a$ - $b$  to find current  $i_C(t)$  for  $t > 0$ .


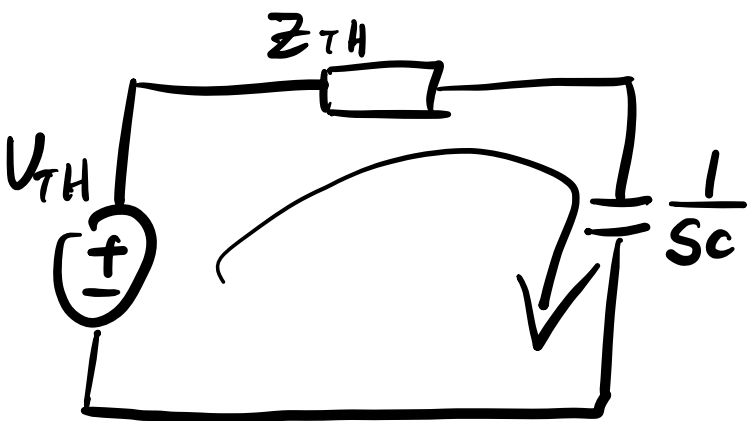
## Thevenin Equivalent Circuit:

$$V_{TH} = \frac{0.002S}{20 + 0.002S} \cdot \frac{480}{S} = \frac{480}{S + 10^4}$$

$$Z_{TH} = 60 + \frac{0.002S \cdot 20}{0.002S + 20} = \frac{80(S + 7500)}{S + 10^4}$$



$$I_C(s) = \frac{V_{TH}}{Z_{TH} + \frac{1}{s_C}}$$

$$= \frac{6S}{(S + 5000)^2} = \frac{A}{(S + 5000)^2} + \frac{B}{S + 5000}$$

$$\text{For A: } \frac{6S \cancel{(S + 5000)^2}}{\cancel{(S + 5000)^2}} = \frac{A \cancel{(S + 5000)^2}}{\cancel{(S + 5000)^2}} + \frac{B \cancel{(S + 5000)^2}}{\cancel{(S + 5000)^2}}$$

$$A|_{S = -5000} = 6S|_{S = -5000} = -30000$$

$$\text{For } B: \left[ \frac{6S \cancel{(S+5000)^2}}{\cancel{(S+5000)^2}} = \frac{A \cancel{(S+5000)^2}}{\cancel{(S+5000)^2}} + \frac{B \cancel{(S+5000)^2}}{\cancel{(S+5000)^2}} \right]$$

$$(6S)' = [A + B(S+5000)]'$$

$$B = (6S)' = 6$$

$$I_c(s) = \frac{-30000}{(S+5000)^2} + \frac{6}{S+5000}$$

$$\downarrow \mathcal{L}^{-1}$$


$$i_c(t) = [-30000 t \cdot e^{-5000t} + 6 \cdot e^{-5000t}] u(t) \text{ A.}$$




---



## Example 4

- Find  $v_o(t)$  for  $t > 0$

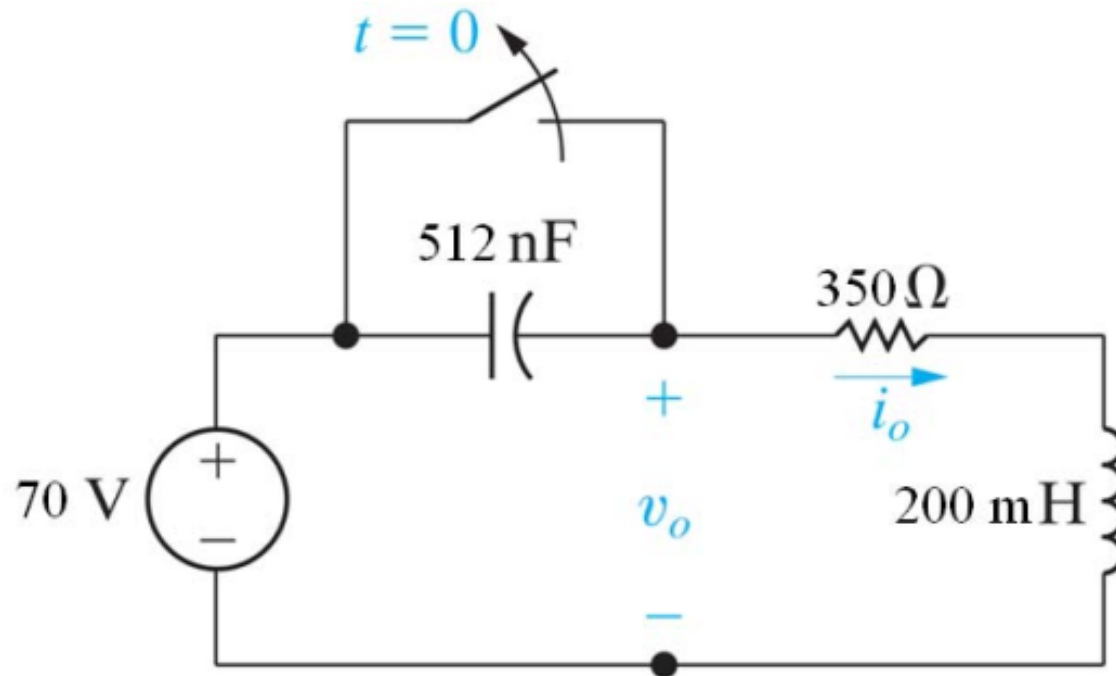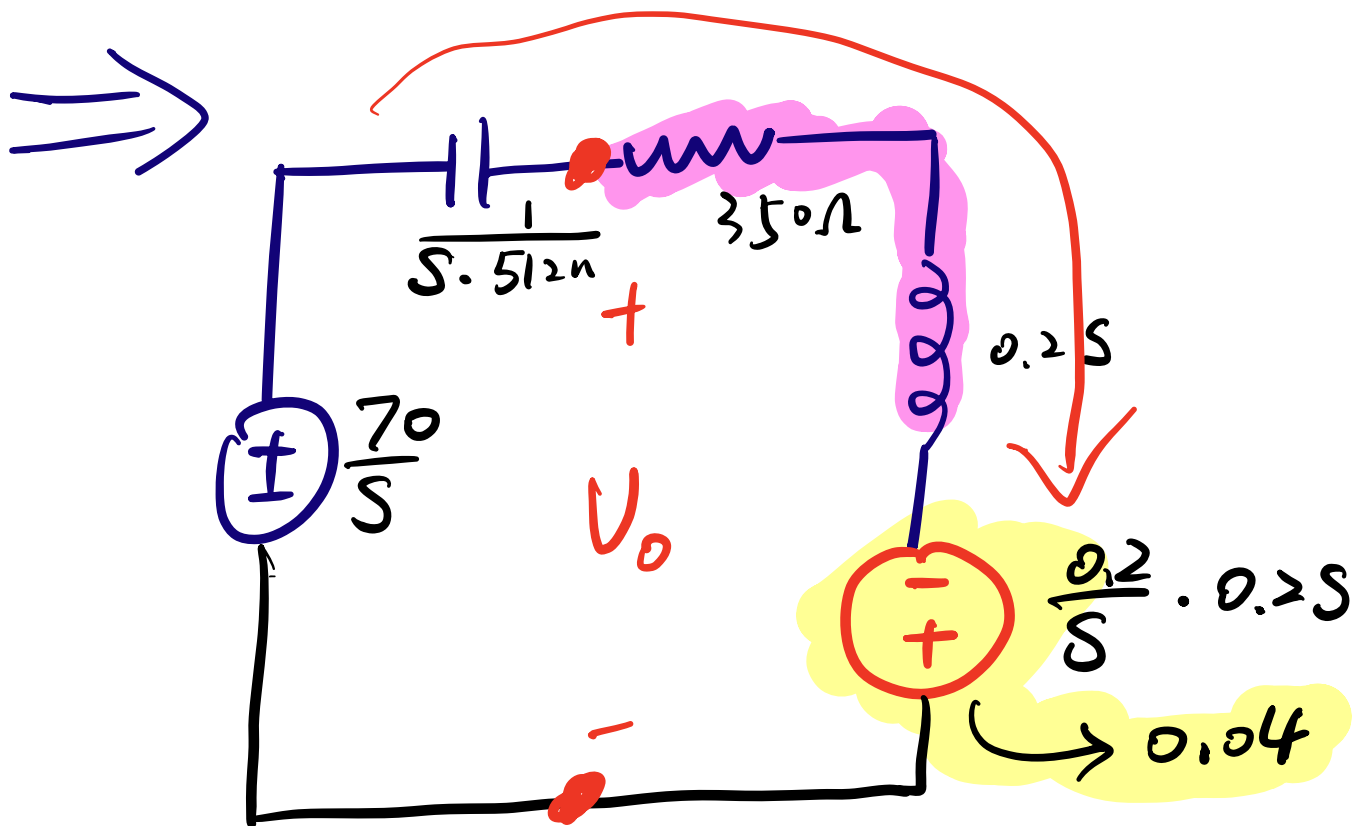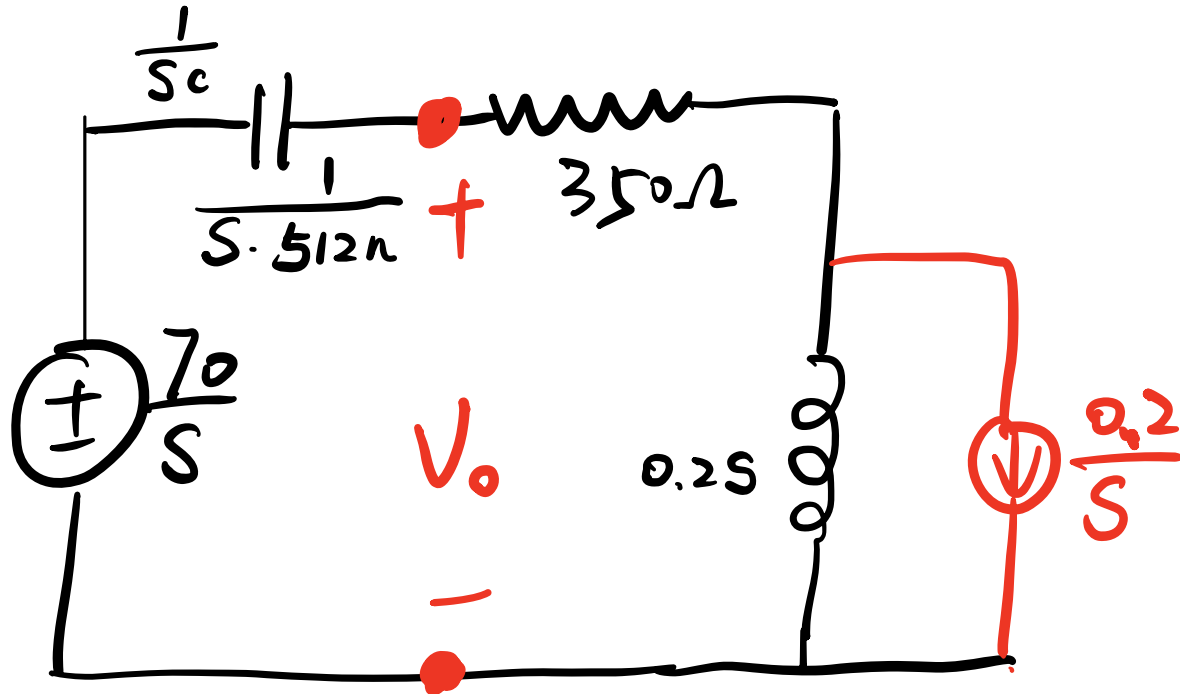



$$I(s) = \frac{\frac{70}{S} + 0.04}{\frac{1}{S \cdot 512n} + 350 + 0.2S}$$

$$V_o(s) = I(s) \cdot (350 + 0.2S) - 0.04$$



$$s^2 + 1750s + \dots = 0 \quad \alpha = -875 \quad \omega = 3000j$$

$$s_1, s_2 = -875 \pm 3000j$$

$$= \frac{K_1}{s - (-875 + 3000j)} + \frac{K_2}{s - (-875 - 3000j)}$$

$$V_0(s) = \frac{70s - 268,125}{s^2 + 1750s + 9,765,625} = \frac{K_1}{(s + 875 - j3000)} + \frac{K_2}{(s + 875 + j3000)}$$

$$K_1 = \left. \frac{70s - 268,125}{(s + 875 + j3000)} \right|_{s=-875-j3000} = \frac{70(-875 + j3000) - 268,125}{[(-875 + j3000) + 875 + j3000]} = \frac{65.1 \angle 57.48^\circ}{1 \angle 1} \quad \underline{\underline{\phi_k}}$$

$$K_2 = \left. \frac{70s - 268,125}{(s + 875 - j3000)} \right|_{s=-875+j3000} = \frac{70(-875 - j3000) - 268,125}{[(-875 - j3000) + 875 - j3000]} = \frac{65.1 \angle -57.48^\circ}{1 \angle -1} \quad \underline{\underline{\phi_k}}$$

$$V_0(s) = \frac{65.1 \angle 57.48^\circ}{(s + 875 - j3000)} + \frac{65.1 \angle -57.48^\circ}{(s + 875 + j3000)}$$

$$v_0(t) = 2(65.1)e^{-875t} \cos(3000t + 57.48^\circ) = 130.2e^{-875t} \cos(3000t + 57.48^\circ)u(t) \text{ V}$$

$\downarrow \quad \downarrow \quad \downarrow \quad \downarrow$   
 $|K| \quad \alpha \quad \omega \quad \phi_k$


$$\alpha = -875$$


## Example 5


- Example---Find  $i_x$  (S.S.) assuming no initial energy stored

Using (1) phasor method

(2) Laplace transform method

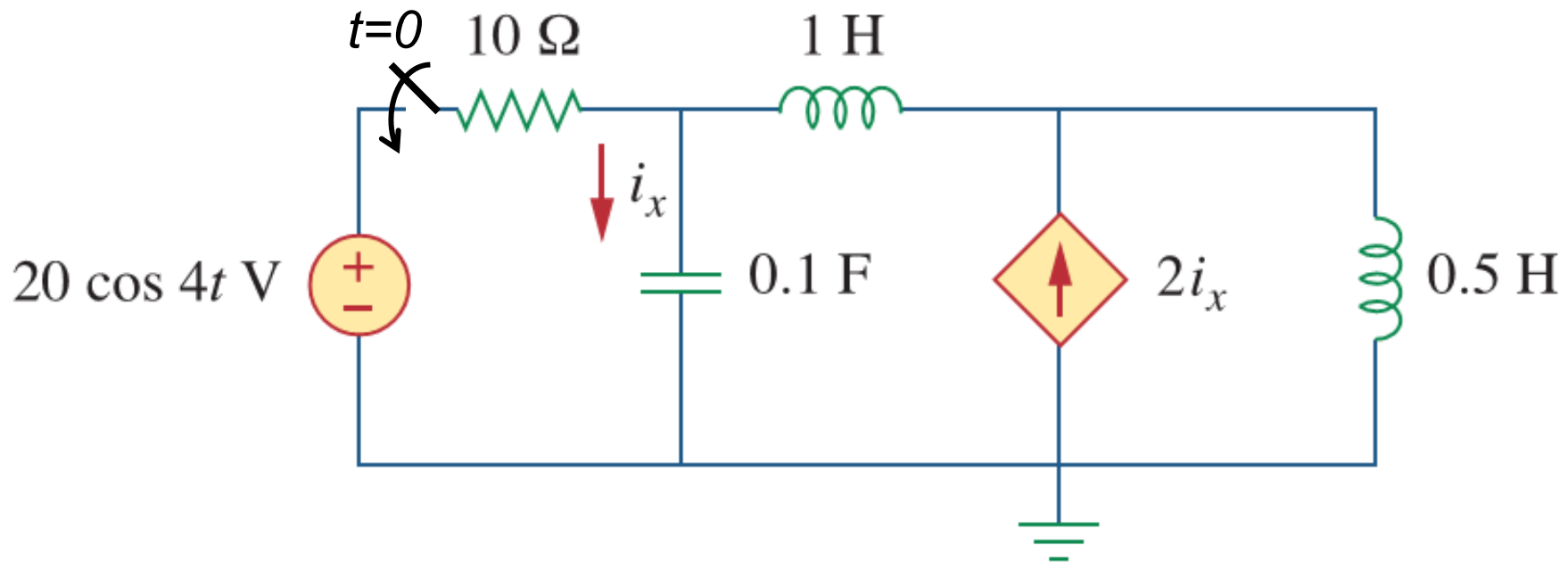

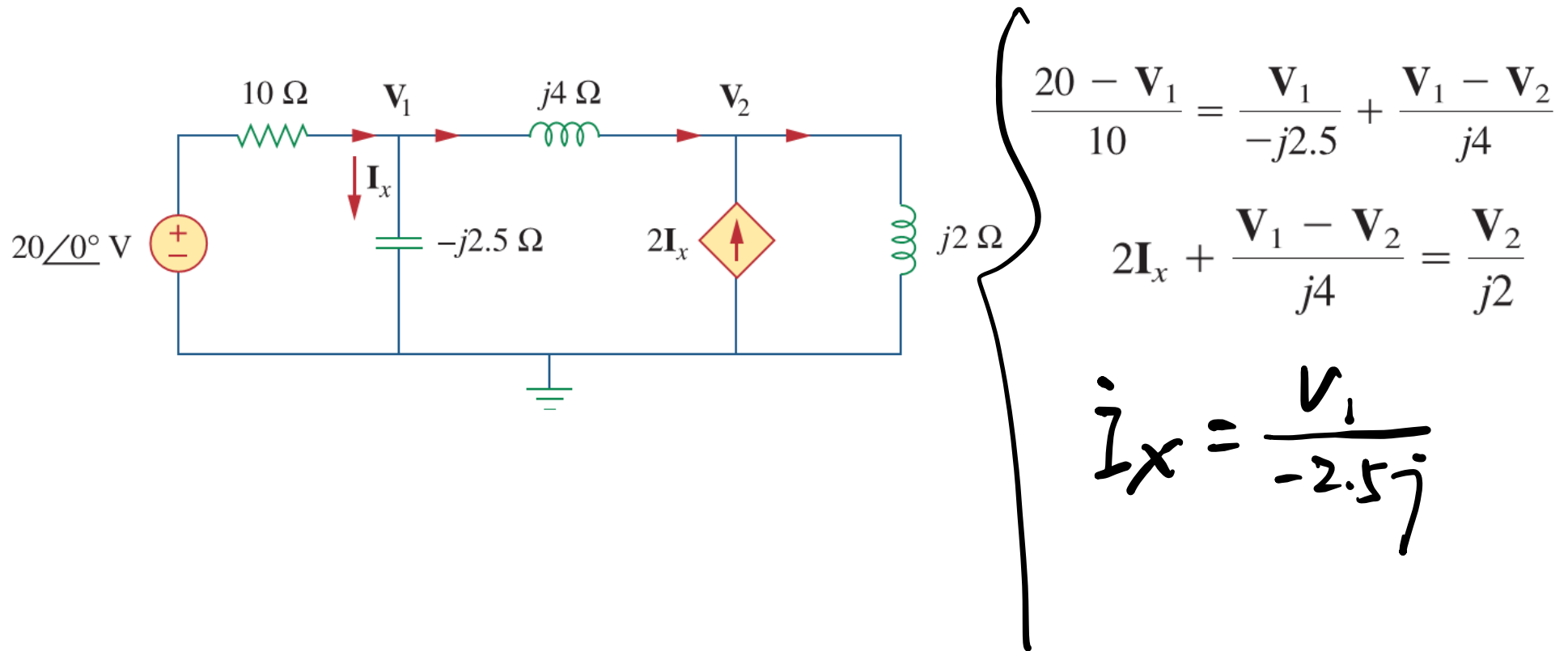


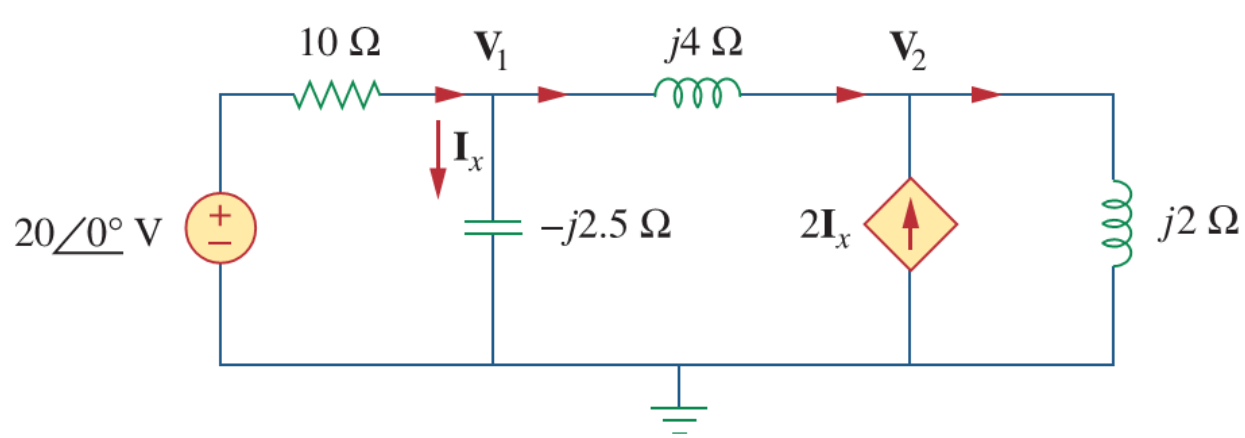


$$\frac{20 - V_1}{10} = \frac{V_1}{-j2.5} + \frac{V_1 - V_2}{j4}$$

$$2I_x + \frac{V_1 - V_2}{j4} = \frac{V_2}{j2}$$
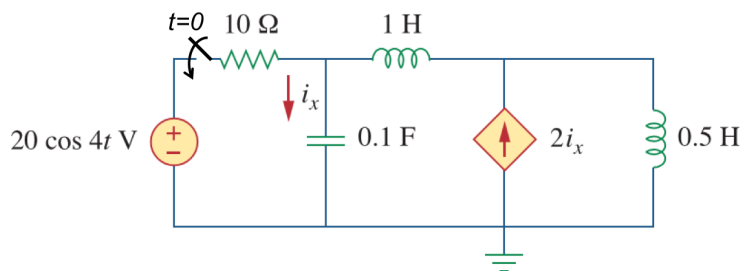
$$i_x = 7.59 \cos(4t + 108.4^\circ) \text{ A}$$



S-domain:  $\Downarrow$

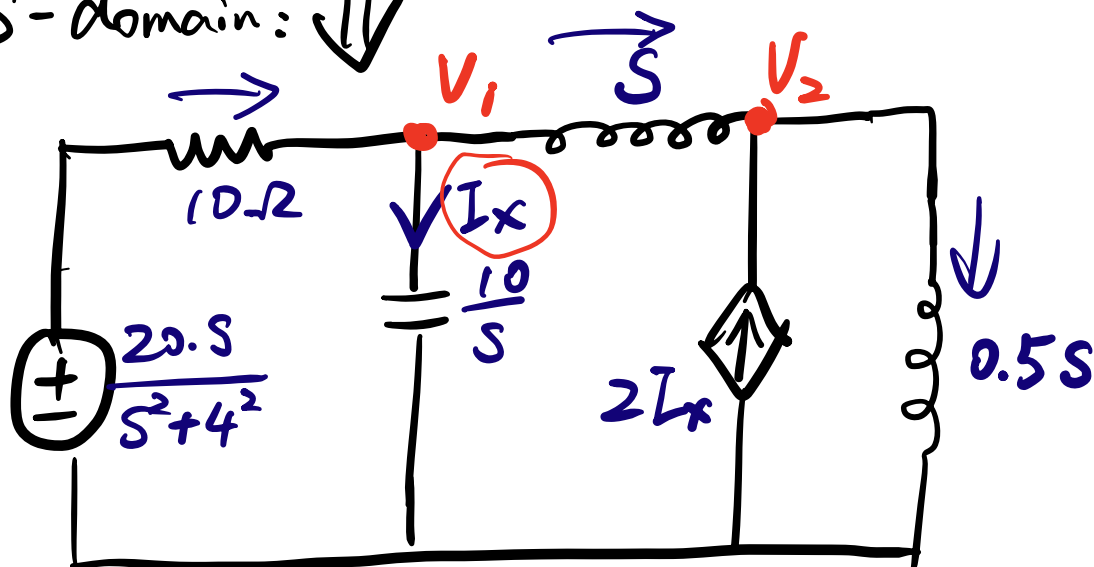

$$\frac{\frac{20.s}{s^2+4^2} - V_1}{10} = \frac{V_1}{\frac{10}{s}} + \frac{V_1 - V_2}{s}$$

$$\frac{V_1 - V_2}{s} + 2I_x = \frac{V_2}{0.5s}$$

$$I_x = \frac{V_1}{\frac{10}{s}} = \frac{V_1 \cdot s}{10}$$

$$I_x = \frac{6s^3}{(s^2+4^2)(s^2+3s+20)}$$

$$= \frac{k_1}{(s-(4j))} + \frac{k_1^*}{(s-(-4j))}$$

$$\alpha = 0$$

$$\omega = 4$$

$$+ \frac{k_2}{s-(-1.5+4.2j)} + \frac{k_2^*}{s-(-1.5-4.2j)}$$

$$\alpha = -1.5$$

$$\omega = 4.2j$$

$e^{\alpha t}$

$$\alpha = 0 \rightarrow$$

S.S.

$$\alpha < 0 \rightarrow$$

t.s.

$$\rightarrow e^{\alpha t} \cos(\omega t + \phi)$$



$$k_1 = 3.79 \angle 108.43^\circ$$

$$k_2 = 5.0 \angle -146.2^\circ$$

$$= \frac{k_1}{(s - (4j))} + \frac{k_1^*}{(s - (-4j))} + \frac{k_2}{s - (-1.5 + 4.2j)} + \frac{k_2^*}{s - (-1.5 - 4.2j)}$$

$\alpha_1 = 0$   
 $\omega_1 = 4$

$\alpha_2 = -1.5$   
 $\omega_2 = 4.2j$

↓

φ-1

$$v(t) = 2|k_1| \cdot e^{\alpha_1 t} \cos(\omega_1 t + \varphi_{k_1})$$

$$+ 2|k_2| e^{\alpha_2 t} \cos(\omega_2 t + \varphi_{k_2})$$



## Example 6

- There is no initial energy stored in this circuit. Find  $i(t)$  if
- $v(t) = e^{-0.6t} \sin 0.8t$  V.