





Outline

- Capacitors and inductors
- Natural response of RC/RL circuits
- Step response of RC/RL circuits
- Others

RC and RL Circuits

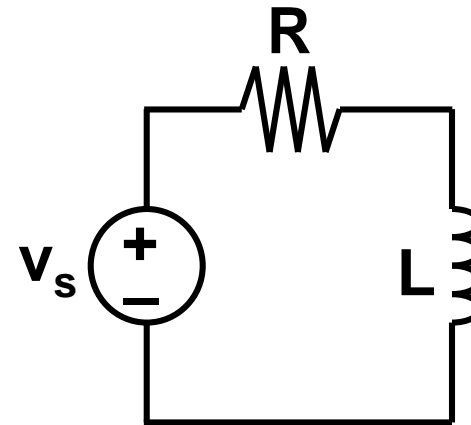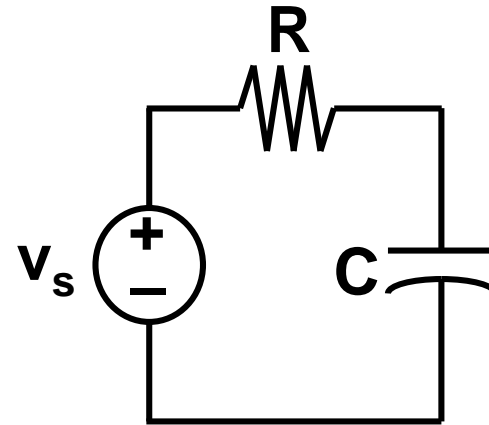
- A circuit that contains only source(s), resistor(s) and a capacitor is called an **RC circuit**.
- A circuit that contains only source(s), resistor(s) and an inductor is called an **RL circuit**.




Natural Response

Behavior (*i.e.*, current and voltage) when stored energy in the inductor or capacitor is released to the resistive part of the network (containing no independent sources).


Natural Response of a Charged Capacitor

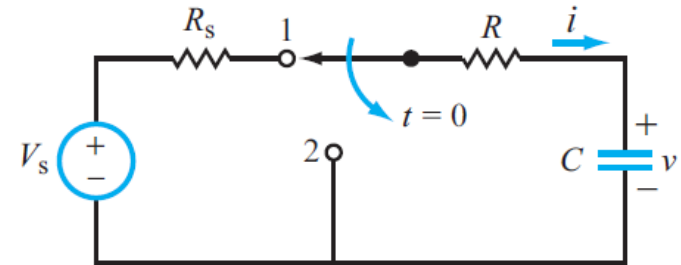

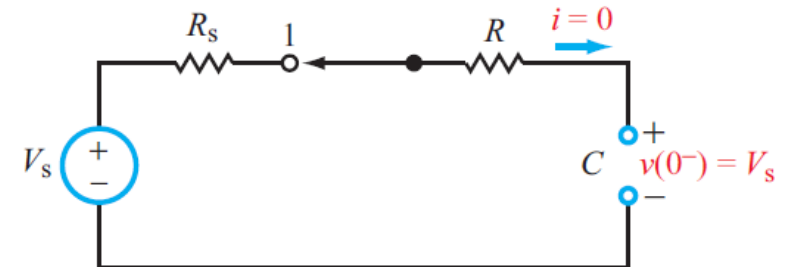(a) $t = 0^-$ is the instant just before the switch is moved from terminal 1 to terminal 2;




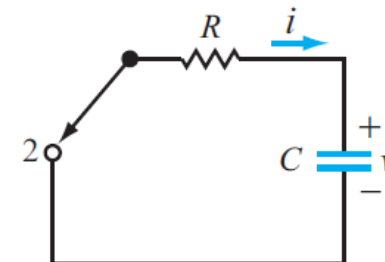(b) $t = 0$ is the instant just after it was moved, $t = 0$ is synonymous with $t = 0^+$.








Natural Response of a Charged Capacitor

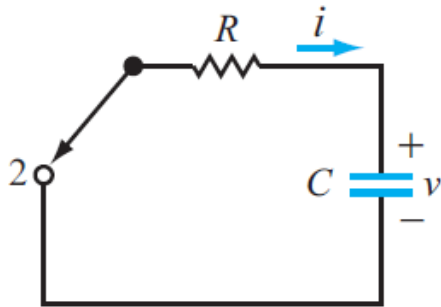



Natural Response of RC Circuit

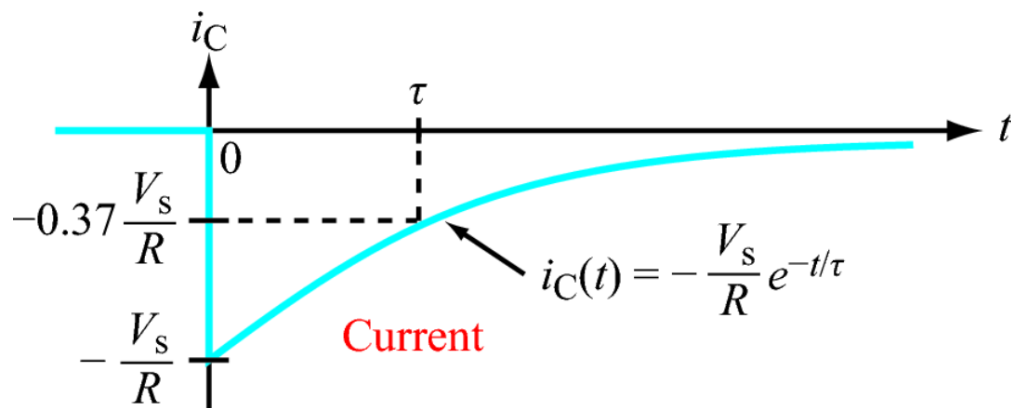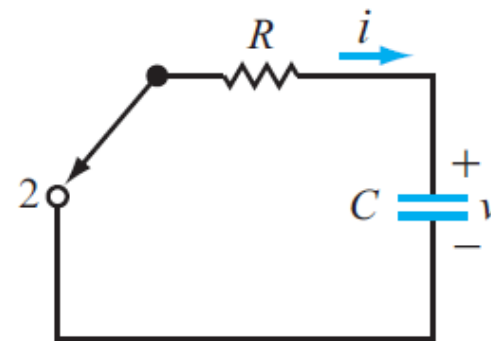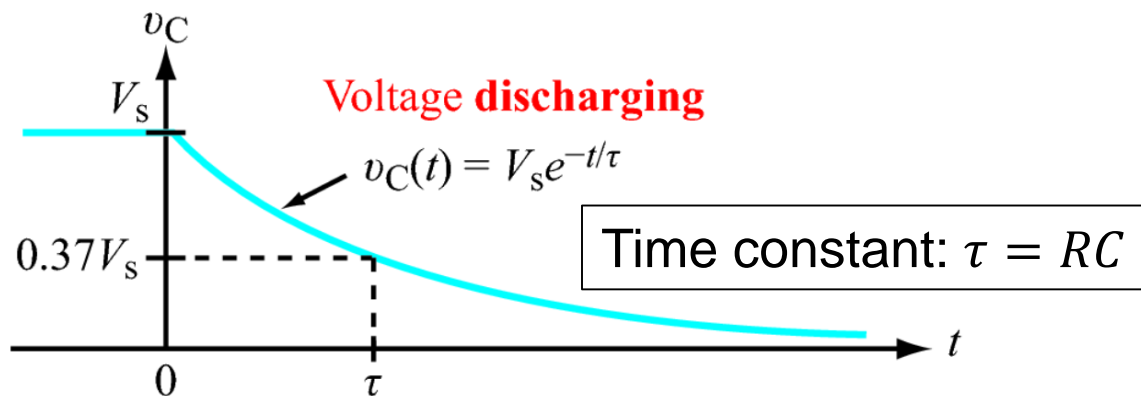

Time Constant $\tau (= RC)$




- A circuit with a small time constant has a fast response and vice versa.

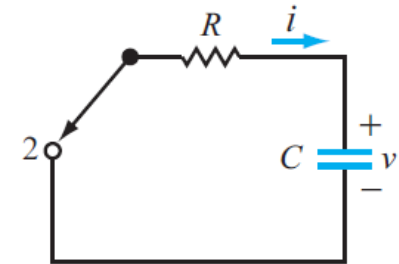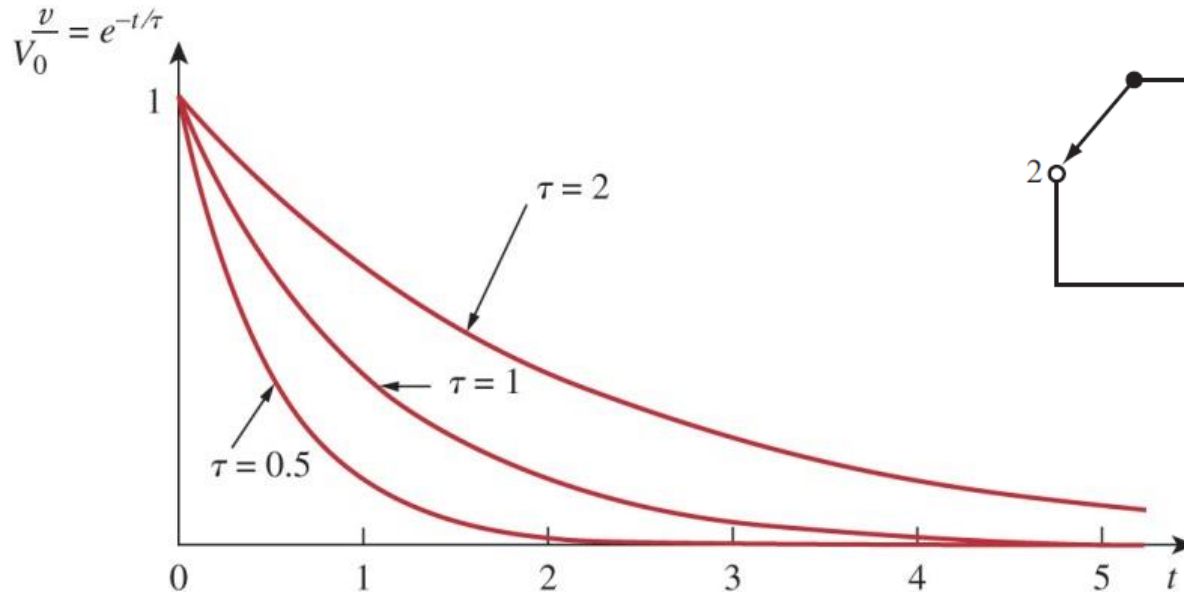Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display






Natural Response of the RL Circuit

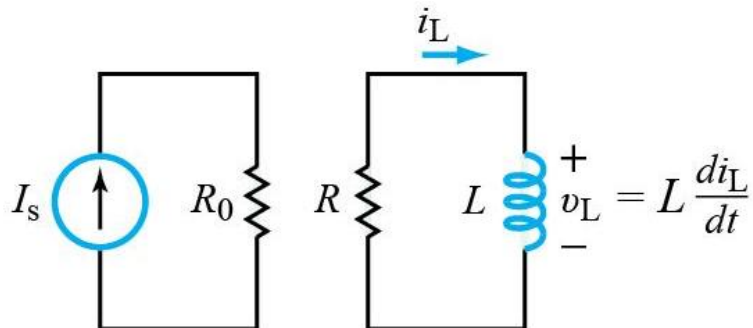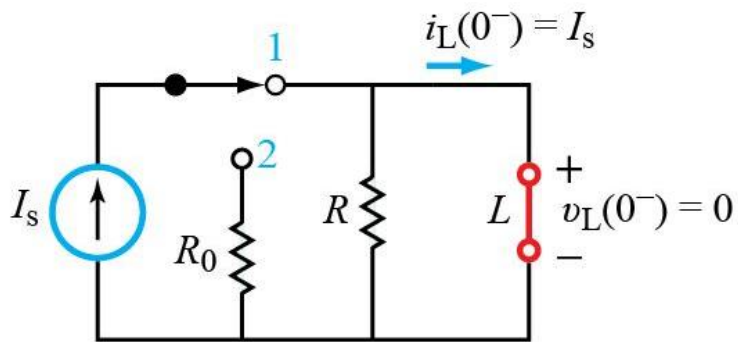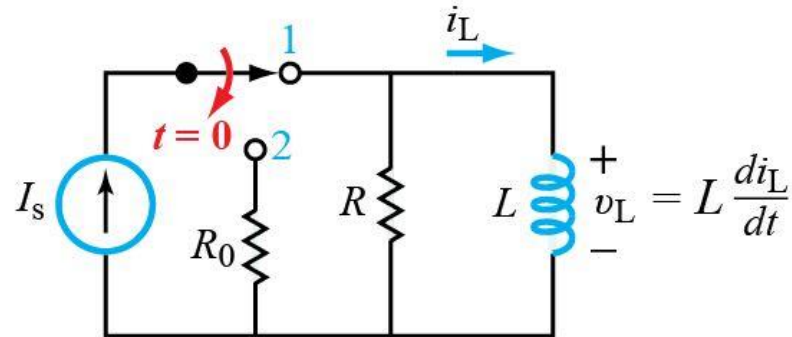




Natural Response of the RL Circuit

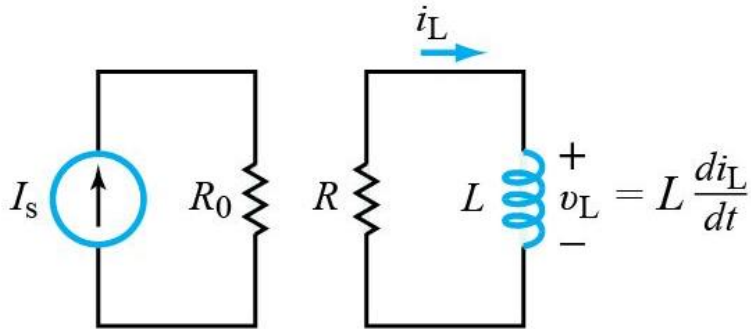




Natural Response of the RL Circuit

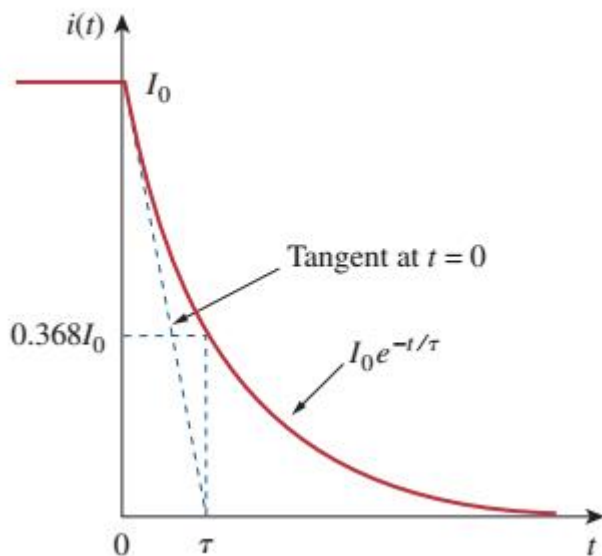

Natural Response Summary

RC Circuit

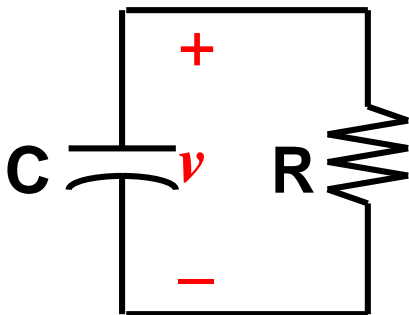


- **Capacitor voltage** cannot change instantaneously

$$v(0^-) = v(0^+)$$

$$v(t) = v(0)e^{-t/\tau}$$

- time constant $\tau = RC$

RL Circuit

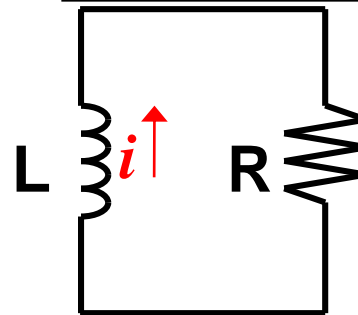

- **Inductor current** cannot change instantaneously

$$i(0^-) = i(0^+)$$

$$i(t) = i(0)e^{-t/\tau}$$


- time constant $\tau = \frac{L}{R}$



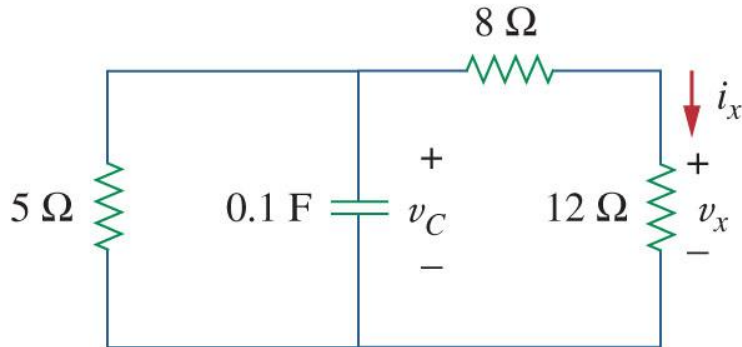Example

- In the circuit below, let $v_C(t = 0) = 15\text{V}$. Find v_C , v_x , and i_x for $t > 0$.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display






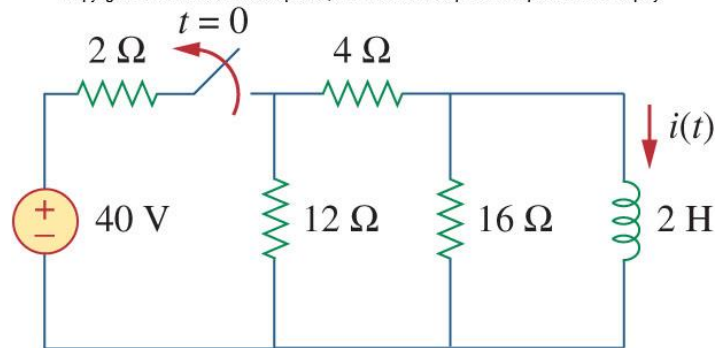
Example

- The switch in the circuit below has been closed for a long time. At $t = 0$, the switch is opened. Calculate $i(t)$ for $t > 0$.


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



When $t < 0$

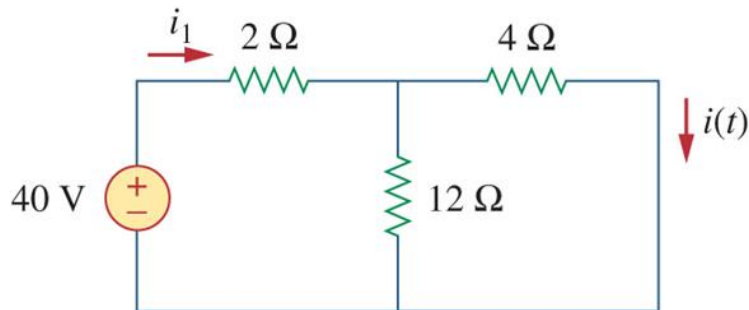

When $t > 0$

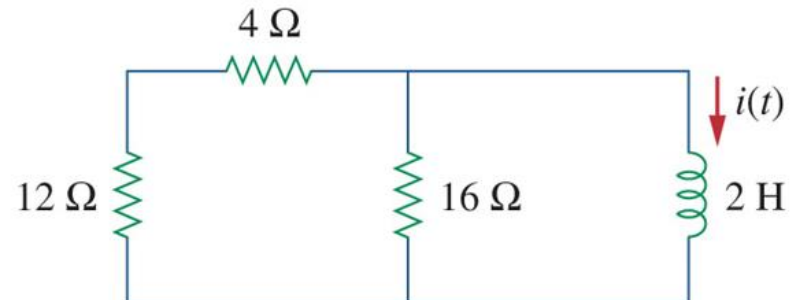




Outline

- Capacitors and inductors
- Natural response of RC/RL circuits
- Step response of RC/RL circuits
- Others

Step Response of RC Circuit

- When a **DC source** is suddenly applied to a RC circuit, the circuit response is known as the step response.

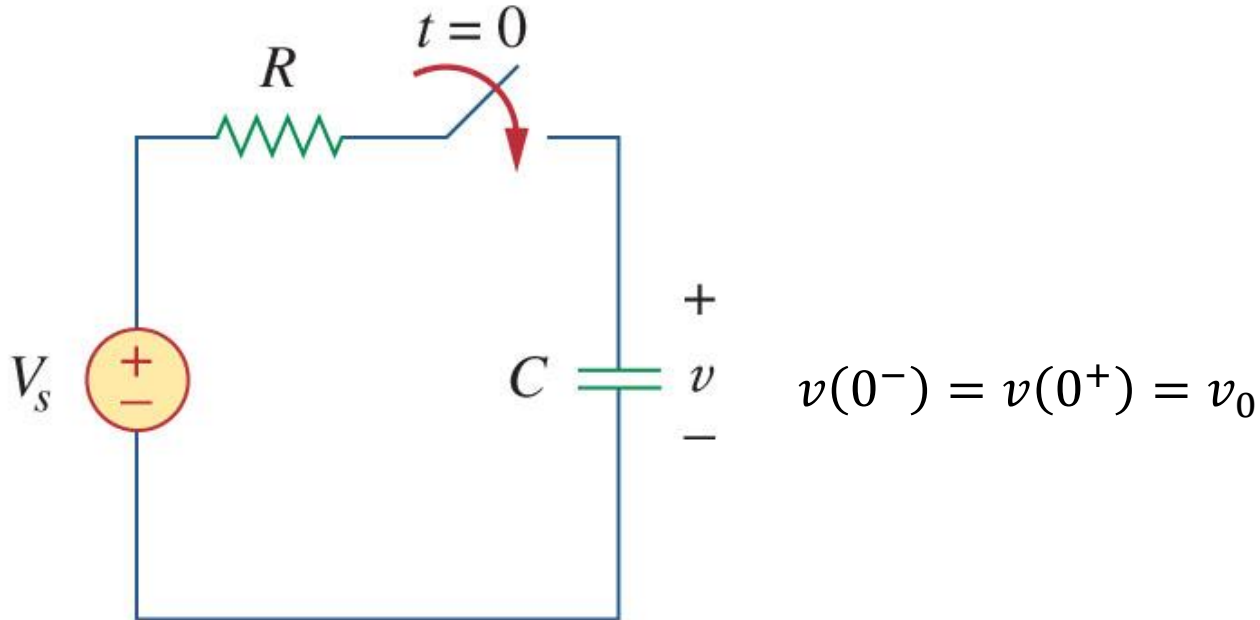
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



The unit step function $u(t)$


- A step function is one that maintains a constant value before a certain time and then changes to another constant afterwards.

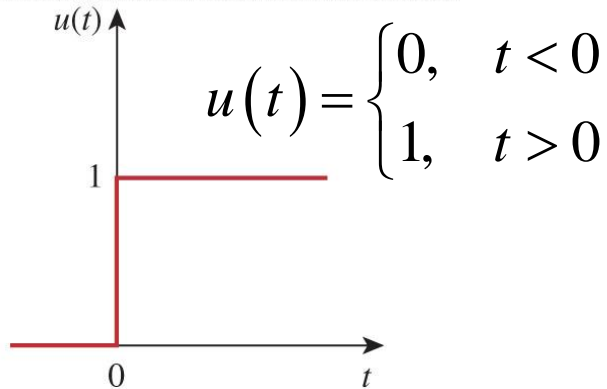Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display




switching time may be shifted to $t = t_0$ by
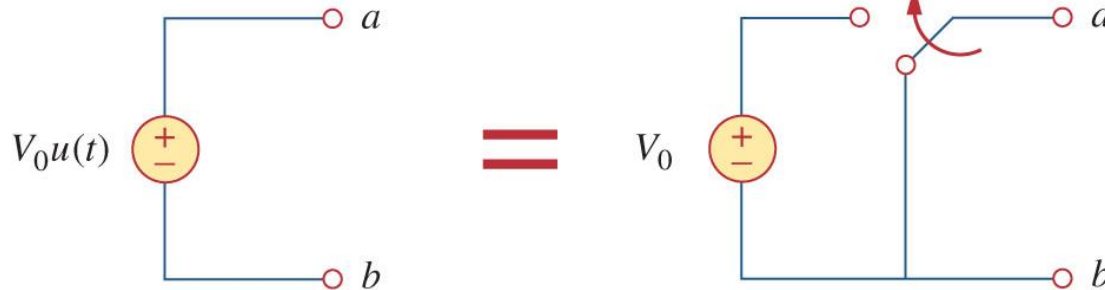
$$u(t - t_0) = \begin{cases} 0, & t < t_0 \\ 1, & t > t_0 \end{cases}$$




Equivalent Circuit of Unit Step

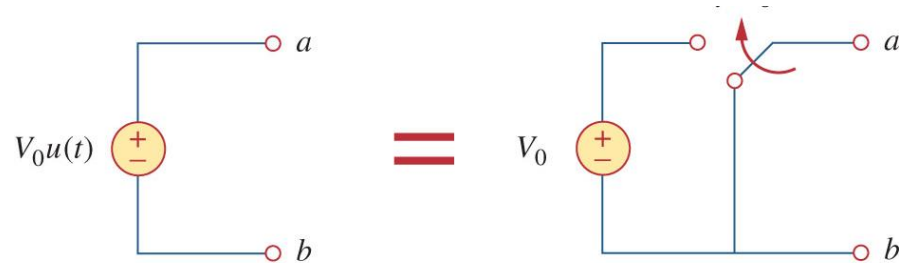- The unit step function has an equivalent circuit to represent when it is used **to switch on** a source.




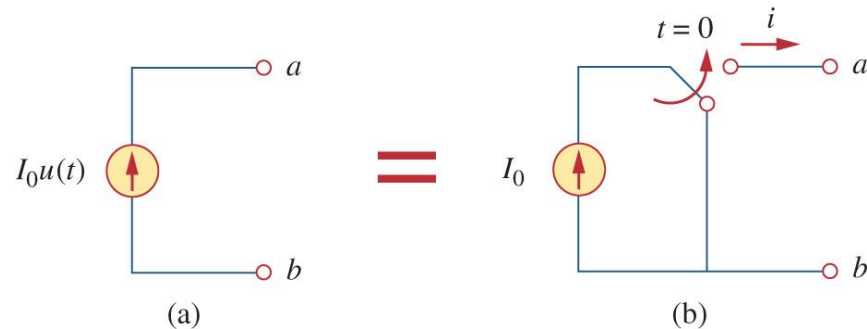Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display





Step Response of the RC Circuit

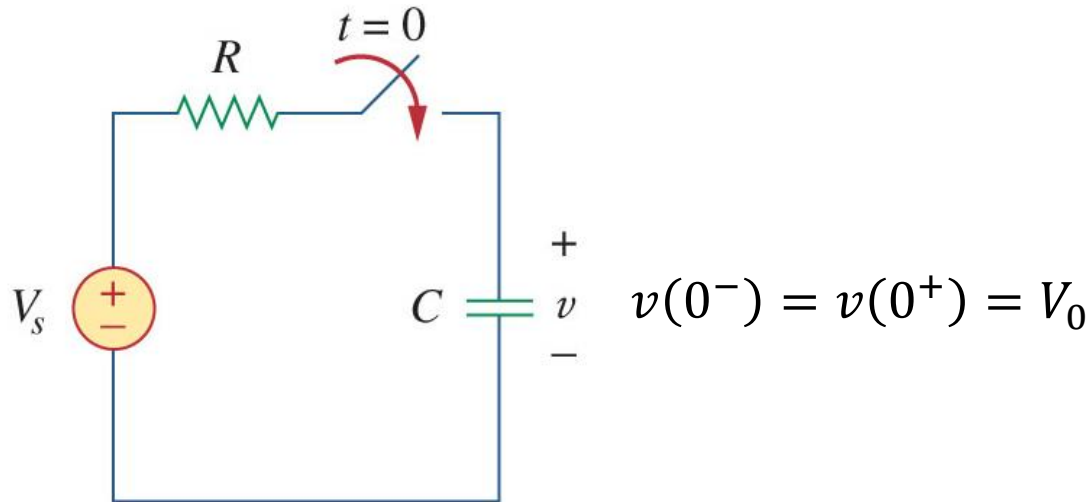






Step Response of the RC Circuit

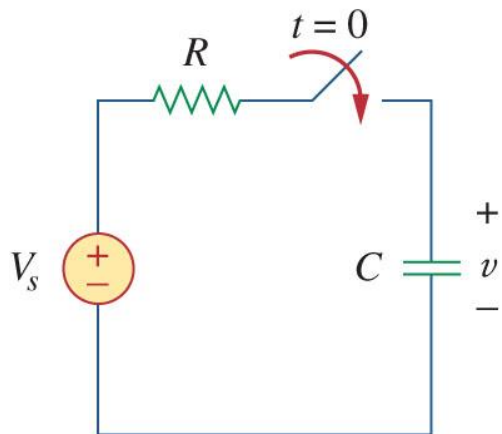
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



$$v(0^-) = v(0^+) = V_0$$

$$v(t) = \begin{cases} V_0, & t < 0 \\ V_s + (V_0 - V_s)e^{-t/\tau} & t > 0 \end{cases}$$

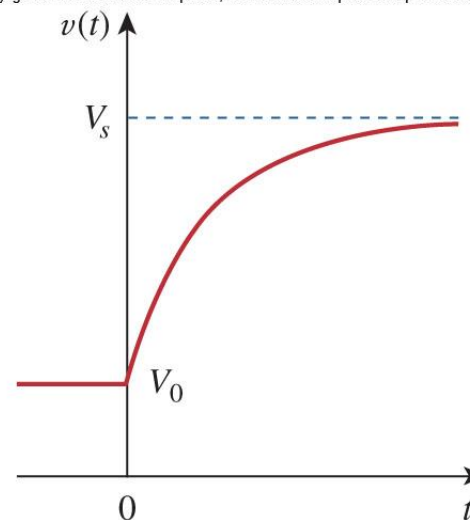Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display




- This is known as the complete response, or total response.



Complete response

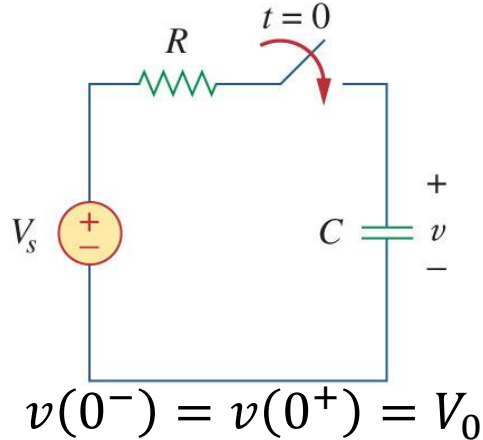Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display




- The complete response

$$v(t) = \begin{cases} V_0, & t < 0 \\ V_s + (V_0 - V_s)e^{-t/\tau} & t > 0 \end{cases}$$

can be written as:

$$v = v_n + v_f$$

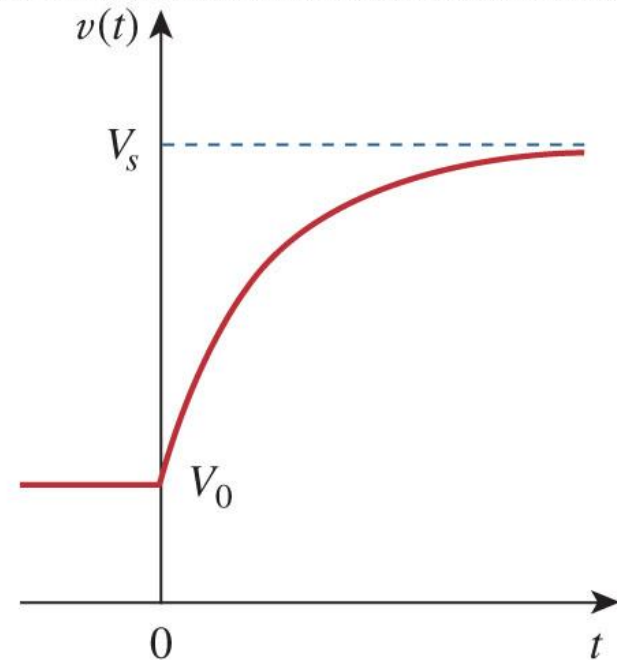Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display





$$\text{Complete response} = \underset{\text{stored energy}}{\text{natural response}} + \underset{\text{independent source}}{\text{forced response}}$$

or

$$v = v_n + v_f$$

where


$$v_n = V_o e^{-t/\tau}$$

and

$$v_f = V_s(1 - e^{-t/\tau})$$

Another Perspective
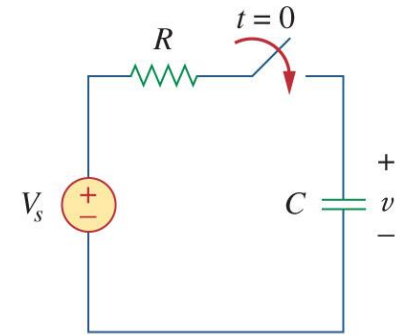
$$v(t) = \begin{cases} V_0, & t < 0 \\ V_s + (V_0 - V_s)e^{-t/\tau} & t > 0 \end{cases}$$



- Another way to look at the response is to break it up into the transient response and the steady state response:

$$v(t) = \underbrace{v(\infty)}_{\text{steady } v_{ss}} + \underbrace{[v(0) - v(\infty)]e^{-t/\tau}}_{\text{transient } v_t}$$



Step Response of the RL Circuit

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display

