




Steps in Applying the Laplace transform

- Transform the circuit from the time domain to the Laplace (s) domain, including initial conditions.
--The elegance of using the Laplace transform in circuit analysis lies in (1) transforming the differential equation into an *algebraic* equation; and (2) automatic inclusion of initial conditions in the transformation process, thus providing a complete (**transient and steady-state**) solution.
- Solve the circuit using nodal analysis, mesh analysis, source transformation, superposition, or any other analysis technique with which we are familiar.
- Take the inverse transform of the solution and thus obtain the solution in the time domain.

Example 1

Assuming no initial energy storage, find $i_1(t)$ and $i_2(t)$ for $t > 0$.

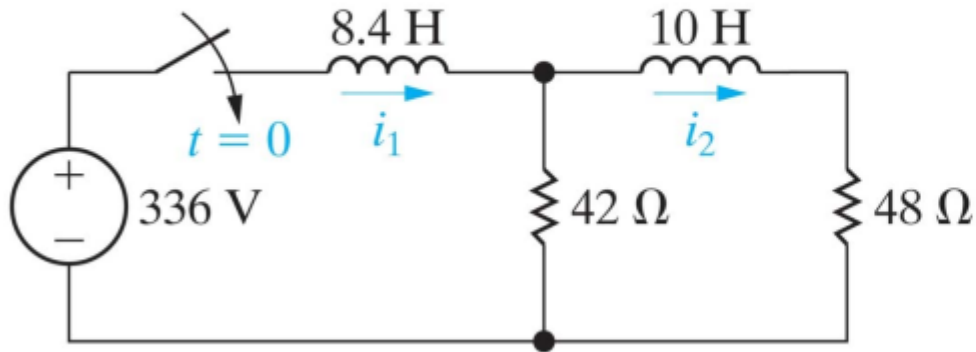






Example 2


Determine $v_o(t)$ for $t > 0$ assuming zero initial conditions:

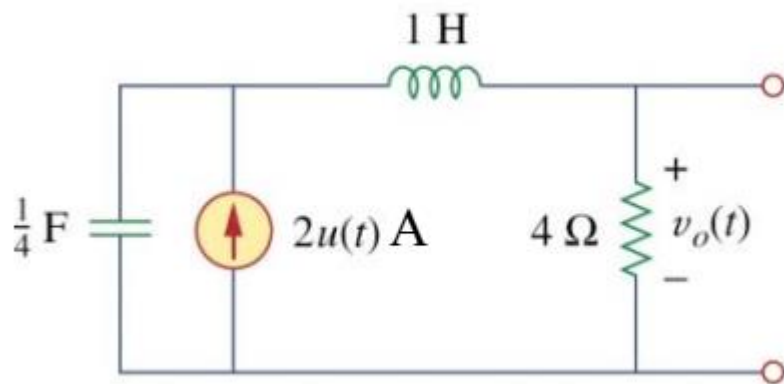



Example 3


- The switch has been in position *b* for a long time. It is moved to position *a* at $t = 0$. Determine $v(t)$ for $t > 0$.

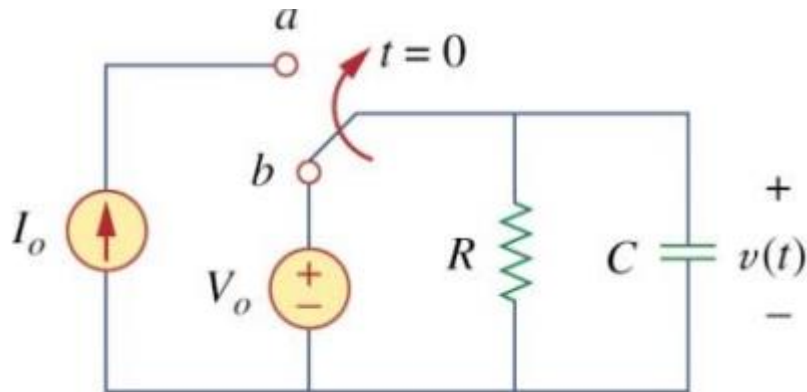

Example 4

- Find (1) the voltage across the capacitor
(2) current through the inductor



assuming that $v_s(t) = 10u(t)$ V, and assume that at $t = 0$, -1 A flows through the inductor and $+5$ V is across the capacitor.

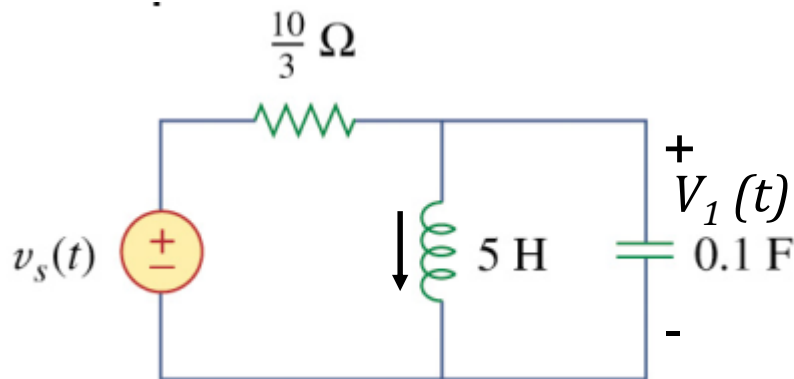

Example 4

- Find (1) the voltage across the capacitor
(2) current through the inductor


assuming that $v_s(t) = 10u(t)$ V, and assume that at $t = 0$, -1 A flows through the inductor and $+5$ V is across the capacitor.

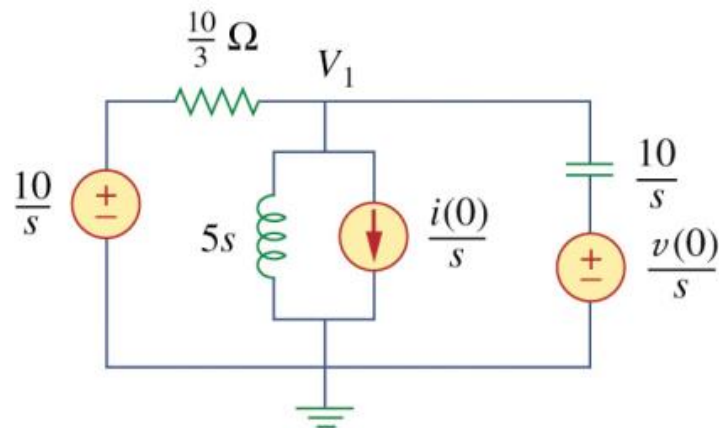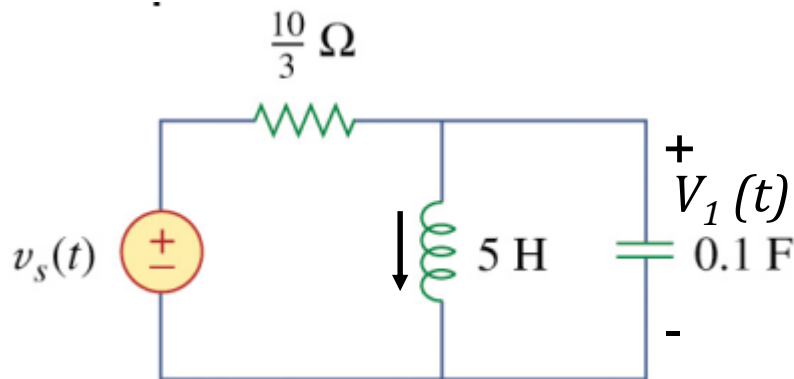



Example 5


- Use Thevenin's equivalent circuit w.r.t. terminals a - b to find current $i_C(t)$ for $t > 0$.

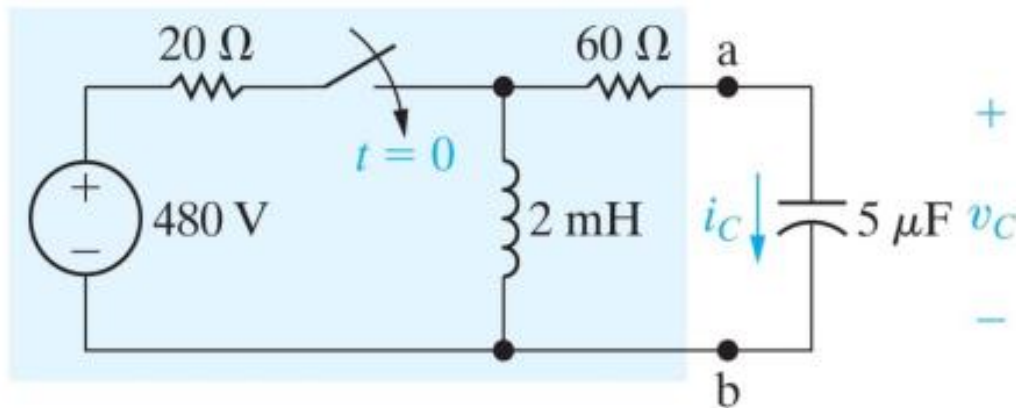



Example 6

- Find $v_o(t)$ for $t > 0$

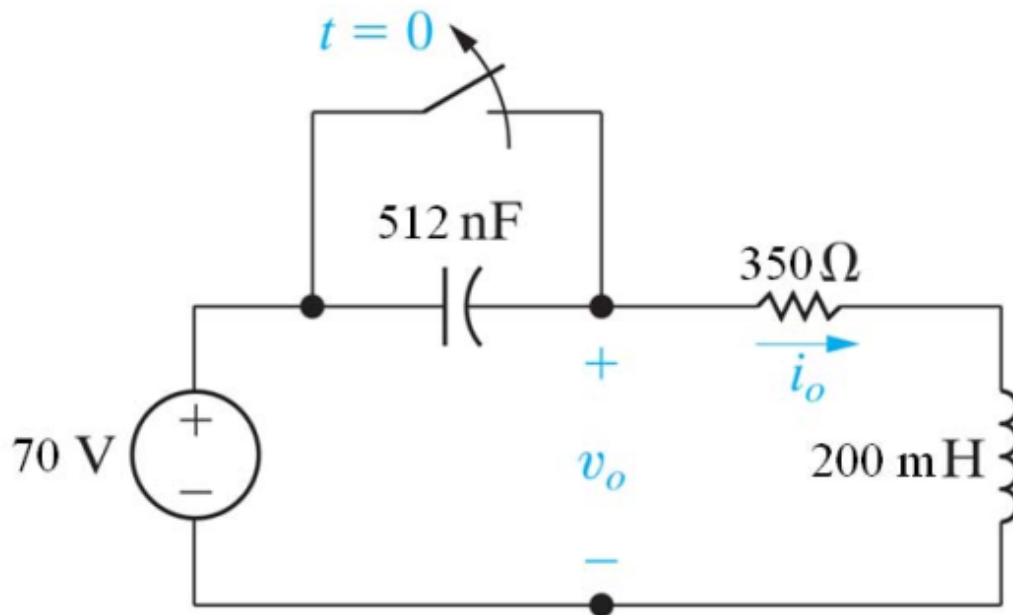





$$V_0(s) = \frac{70s - 268,125}{s^2 + 1750s + 9,765,625} = \frac{K_1}{(s + 875 - j3000)} + \frac{K_2}{(s + 875 + j3000)}$$

$$K_1 = \left. \frac{70s - 268,125}{(s + 875 + j3000)} \right|_{s=-875+j3000} = \frac{70(-875 + j3000) - 268,125}{[(-875 + j3000) + 875 + j3000]} = 65.1 \angle 57.48^\circ$$


$$K_2 = \left. \frac{70s - 268,125}{(s + 875 - j3000)} \right|_{s=-875-j3000} = \frac{70(-875 - j3000) - 268,125}{[(-875 - j3000) + 875 - j3000]} = 65.1 \angle -57.48^\circ$$


$$V_0(s) = \frac{65.1 \angle 57.48^\circ}{(s + 875 - j3000)} + \frac{65.1 \angle -57.48^\circ}{(s + 875 + j3000)}$$

$$v_0(t) = 2(65.1)e^{-875t} \cos(3000t + 57.48^\circ) = 130.2e^{-875t} \cos(3000t + 57.48^\circ)u(t) \text{ V}$$


Example 7

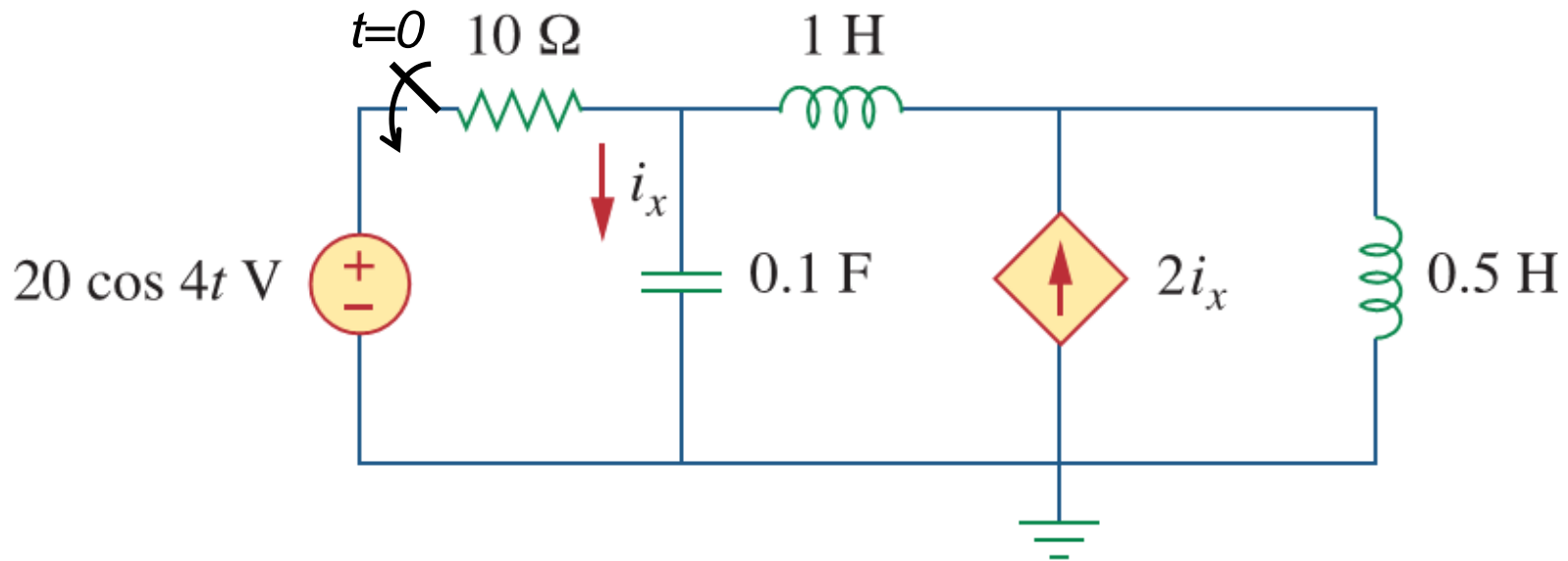- Example---Find i_x (s.s.) assuming no initial energy stored
Using phasor method and Laplace transform method



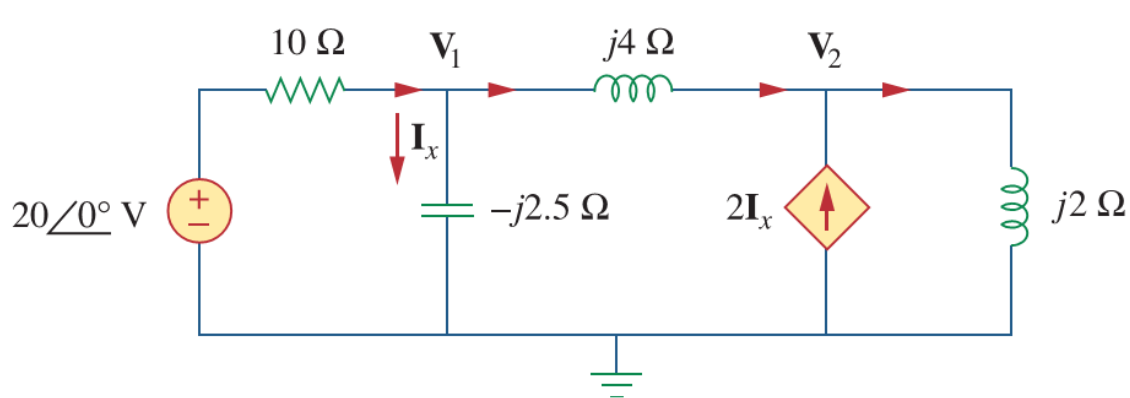
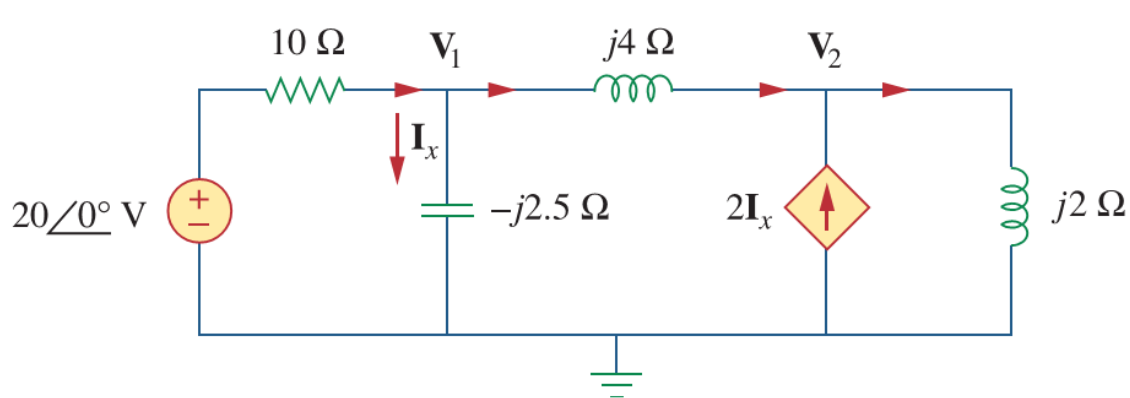
$$\frac{20 - \mathbf{V}_1}{10} = \frac{\mathbf{V}_1}{-j2.5} + \frac{\mathbf{V}_1 - \mathbf{V}_2}{j4}$$
$$2\mathbf{I}_x + \frac{\mathbf{V}_1 - \mathbf{V}_2}{j4} = \frac{\mathbf{V}_2}{j2}$$



$$\frac{20 - \mathbf{V}_1}{10} = \frac{\mathbf{V}_1}{-j2.5} + \frac{\mathbf{V}_1 - \mathbf{V}_2}{j4}$$
$$2\mathbf{I}_x + \frac{\mathbf{V}_1 - \mathbf{V}_2}{j4} = \frac{\mathbf{V}_2}{j2}$$

$$i_x = 7.59 \cos(4t + 108.4^\circ) \text{ A}$$



